

香港中文大學
The Chinese University of Hong Kong

CENG 4480

L10 Memory 2

Bei Yu


Reference:

- Chapter 11 Memories
- CMOS VLSI Design—A Circuits and Systems Perspective
- by H.E.Weste and D.M.Harris

CENG4480 v.s. CENG3420


- CENG3420:
 - ◆ architecture perspective
 - ◆ memory coherent
 - ◆ data address
- CENG4480: more details on how data is stored

Memory Arrays

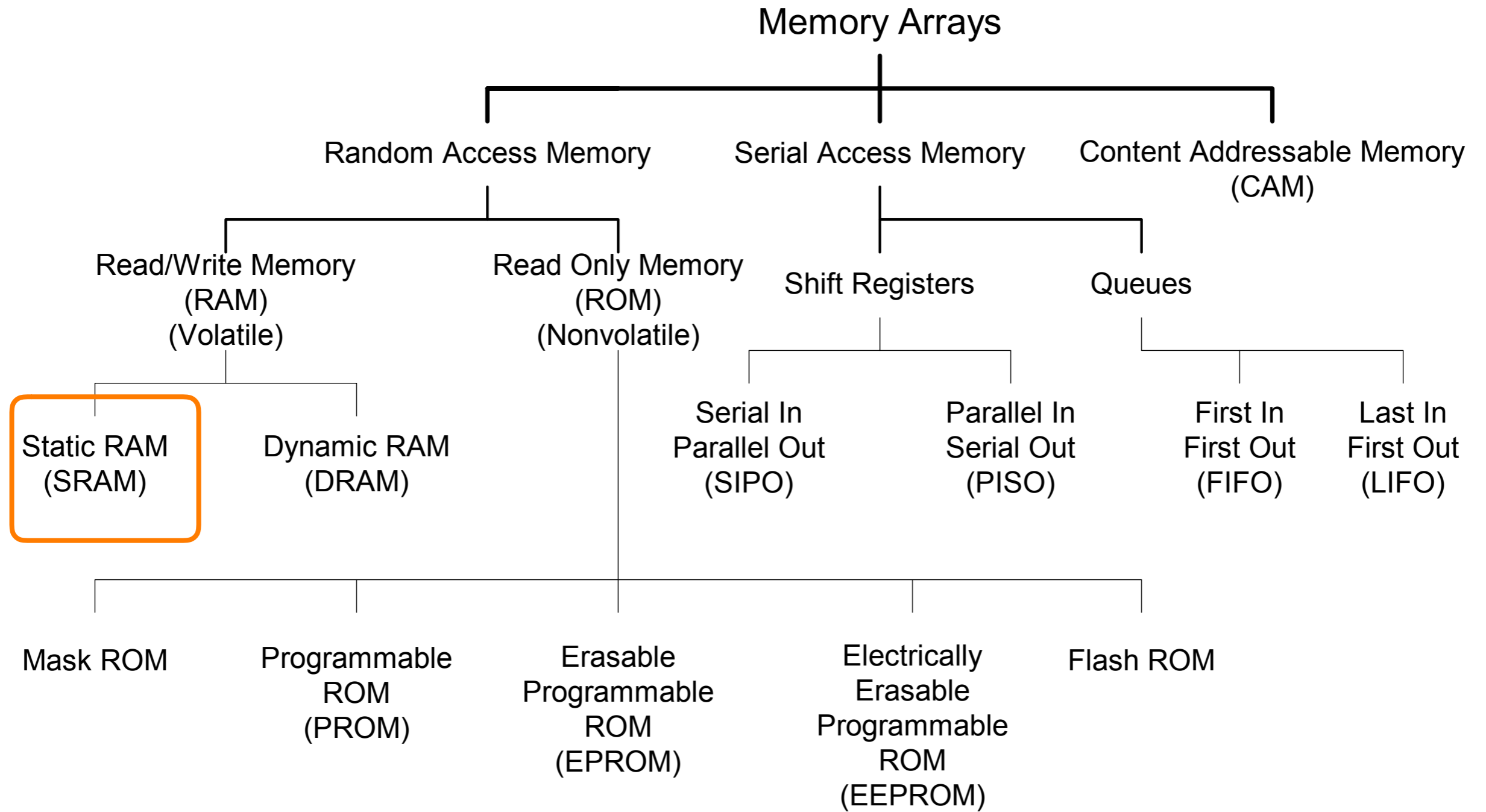


Storage based on Feedback

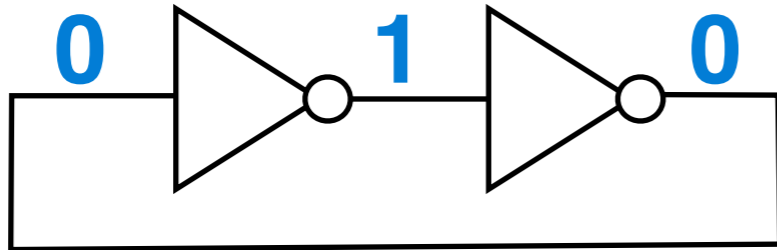- What if we add feedback to a pair of inverters?




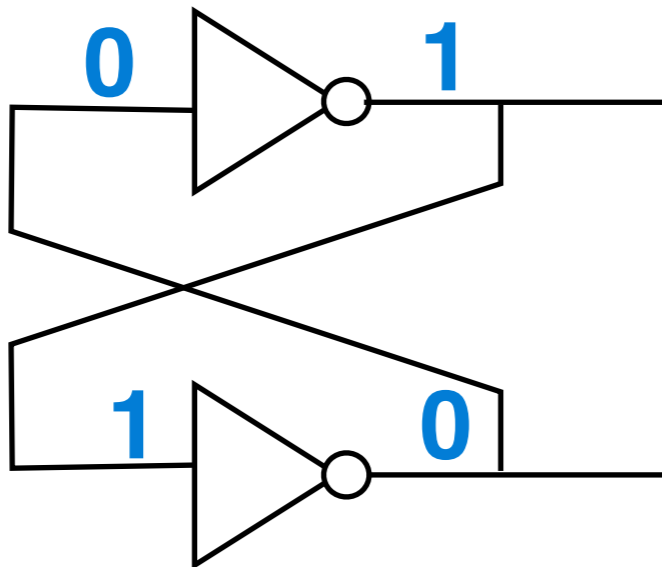
- Usually drawn as a ring of **cross-coupled** inverters
- Stable way to store one bit of information (w. power)



How to change the value stored?



- Replace inverter with NAND gate
- RS Latch

| A | B | A nand B |
|---|---|----------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

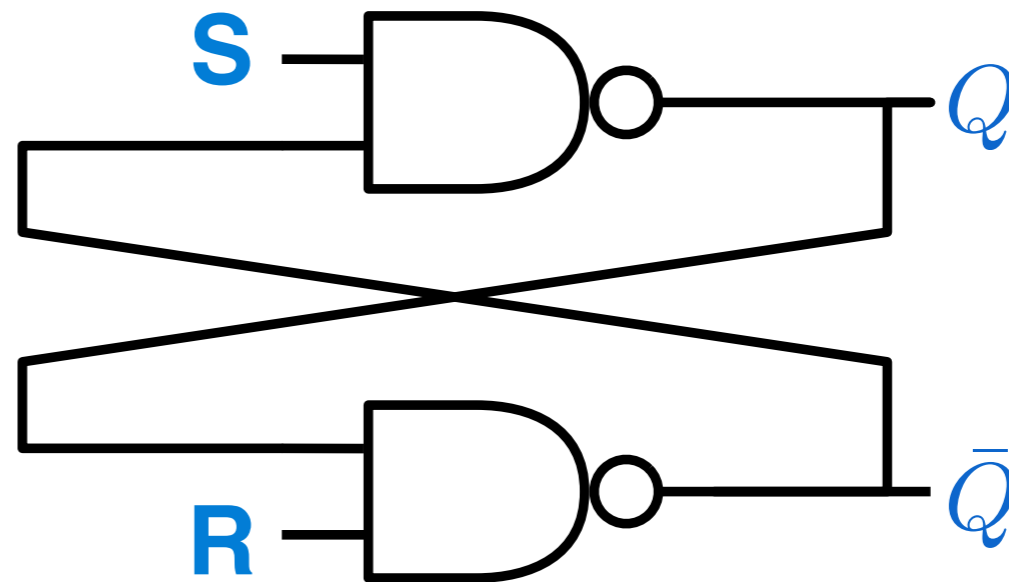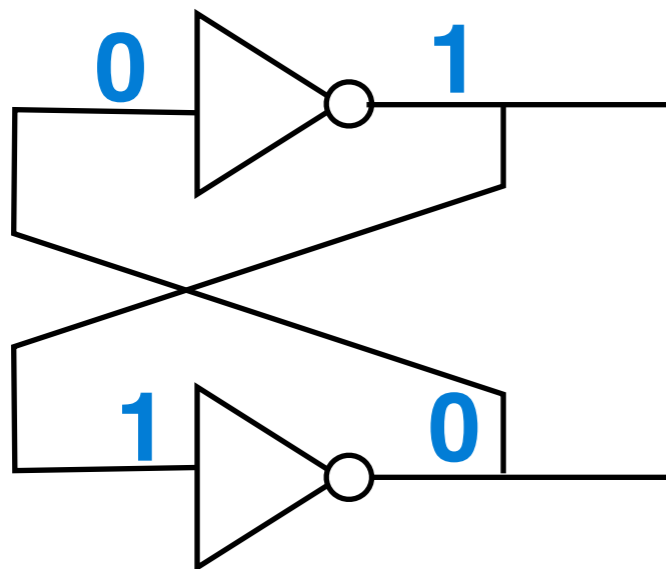

12T SRAM Cell

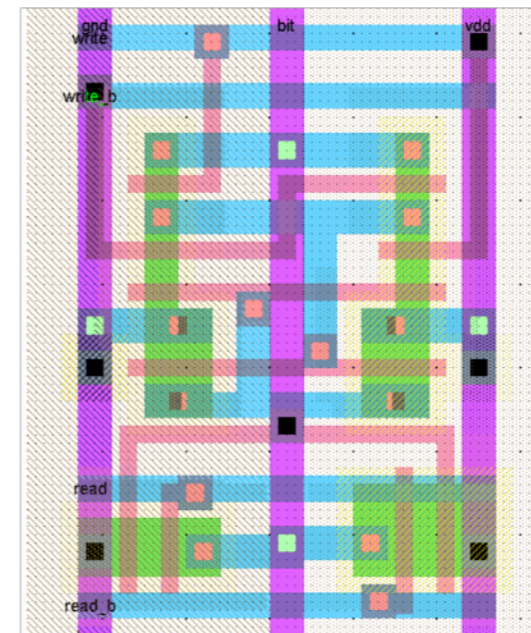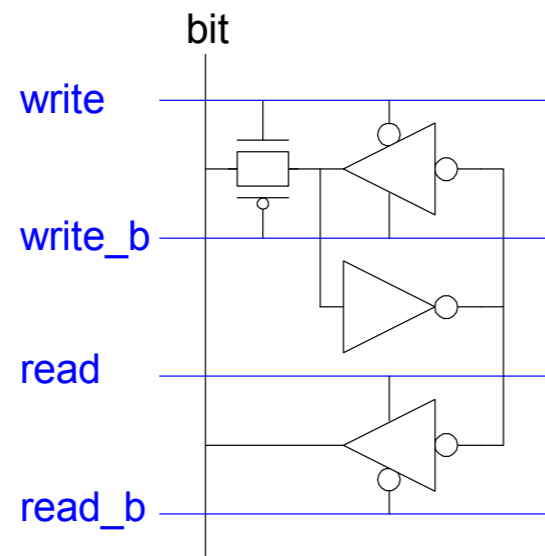- Basic building block: SRAM Cell
 - ◆ Holds one bit of information, **like a latch**
 - ◆ Must be read and written
- 12-transistor (**12T**) SRAM cell
 - ◆ Use a simple latch connected to bitline
 - ◆ 46 x 75 λ unit cell



nMOS, pMOS, Inverter

- nMOS:



- ◆ Gate = 1, transistor is ON
- ◆ Then electric current path

- pMOS:

- ◆ Gate = 0, transistor is ON
- ◆ Then electric current path



- Inverter:

- ◆ $Q = \text{NOT}(A)$

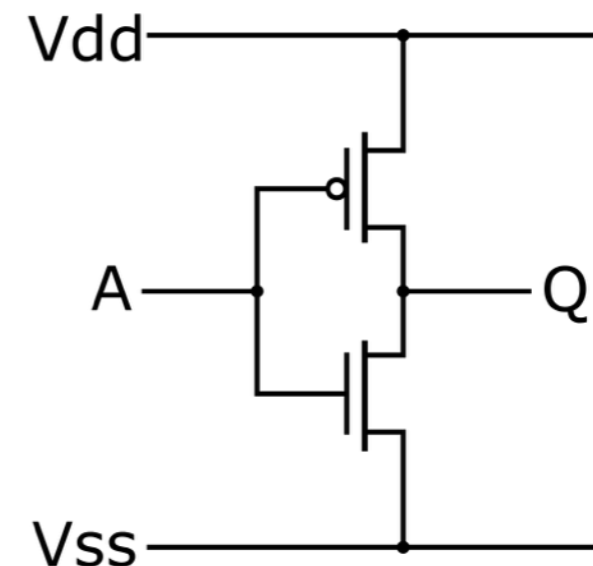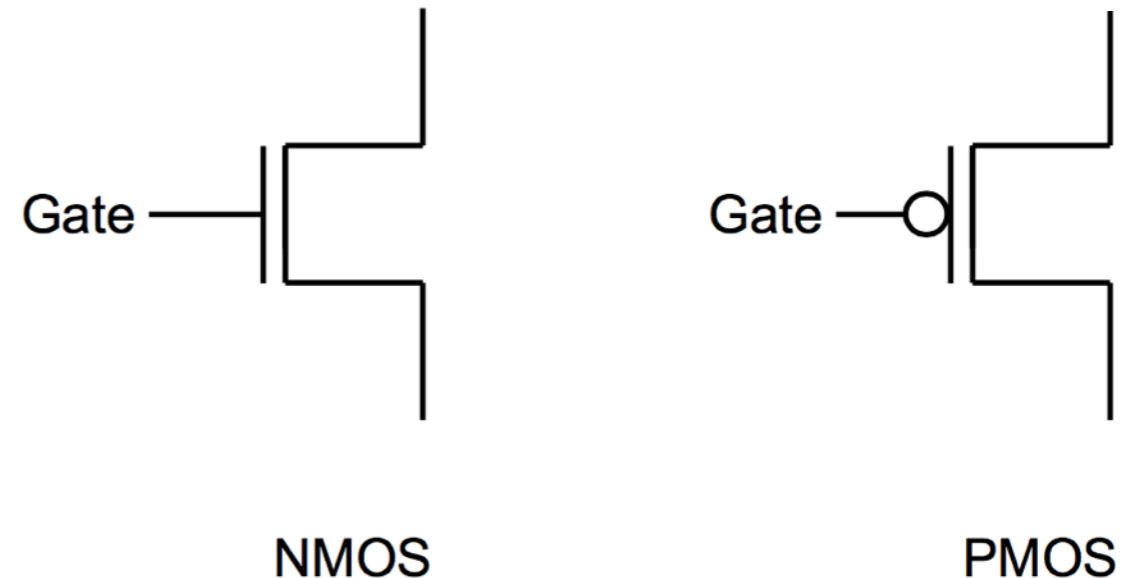



6T SRAM Read

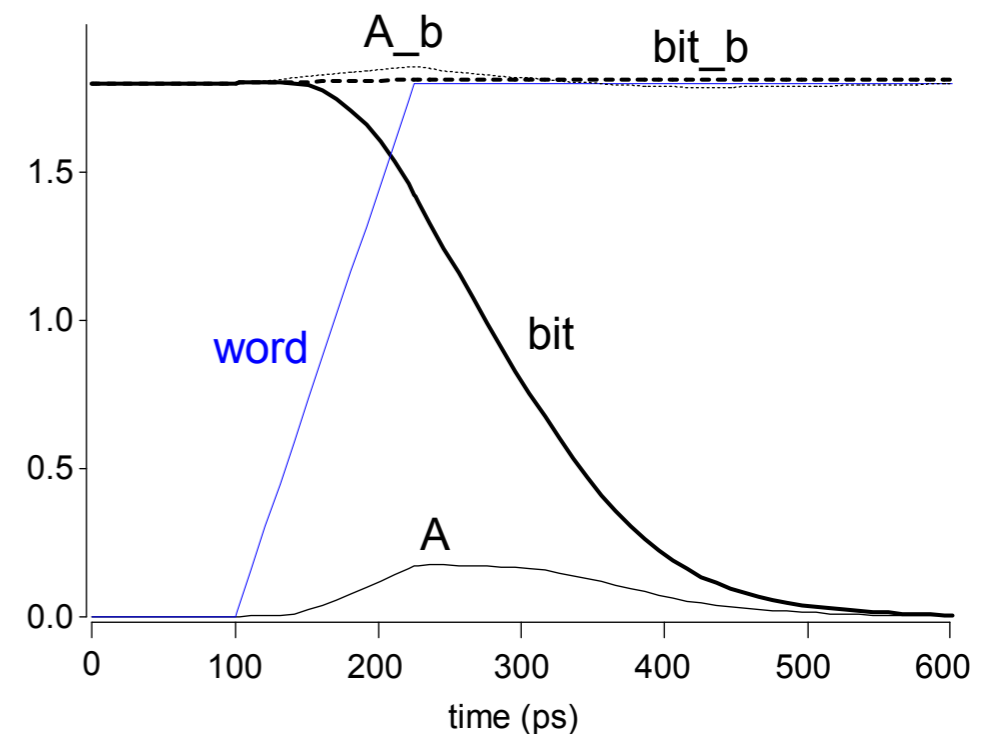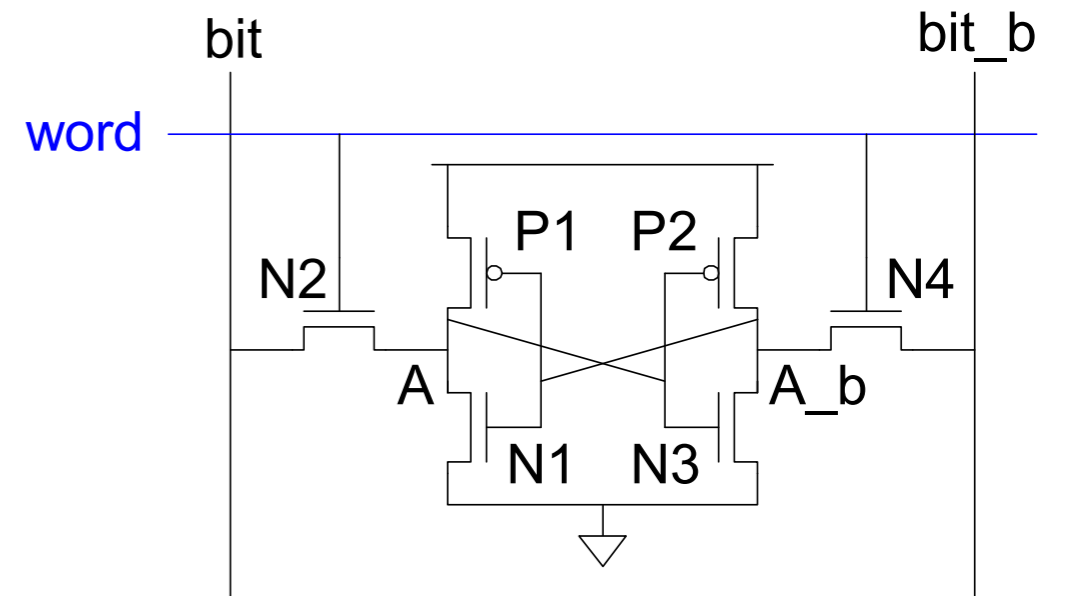- Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- **Read stability**
 - A must not flip
 - $N1 \gg N2$



6T SRAM Write

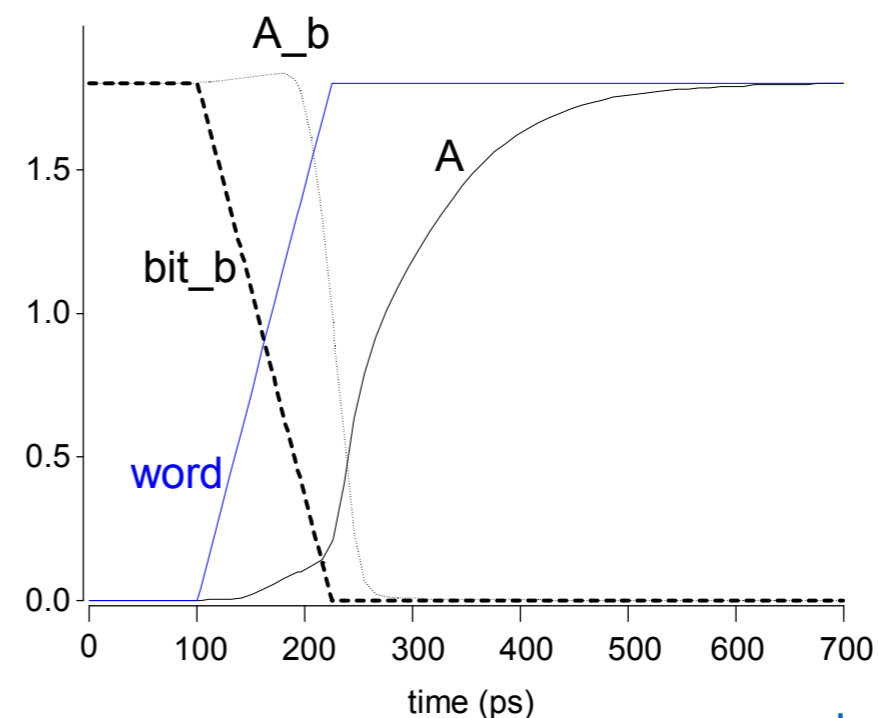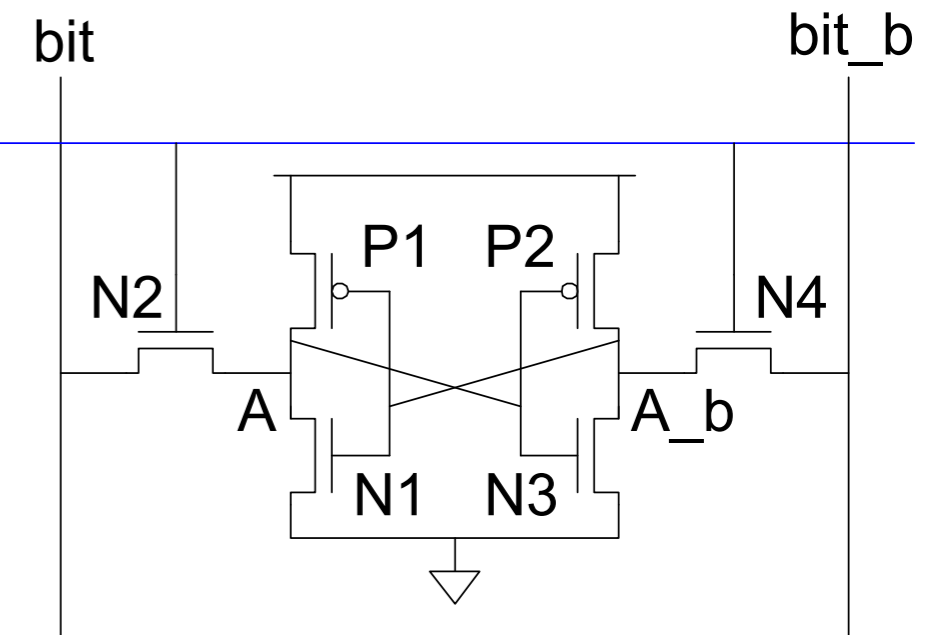
- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- **Writability**
 - Must overpower feedback inverter
 - $N4 \gg P2$
 - $N2 \gg P1$ (symmetry)




EX: 6T SRAM Write

- **Question 1:** $A = 0$, $A_b = 1$, discuss the behavior:

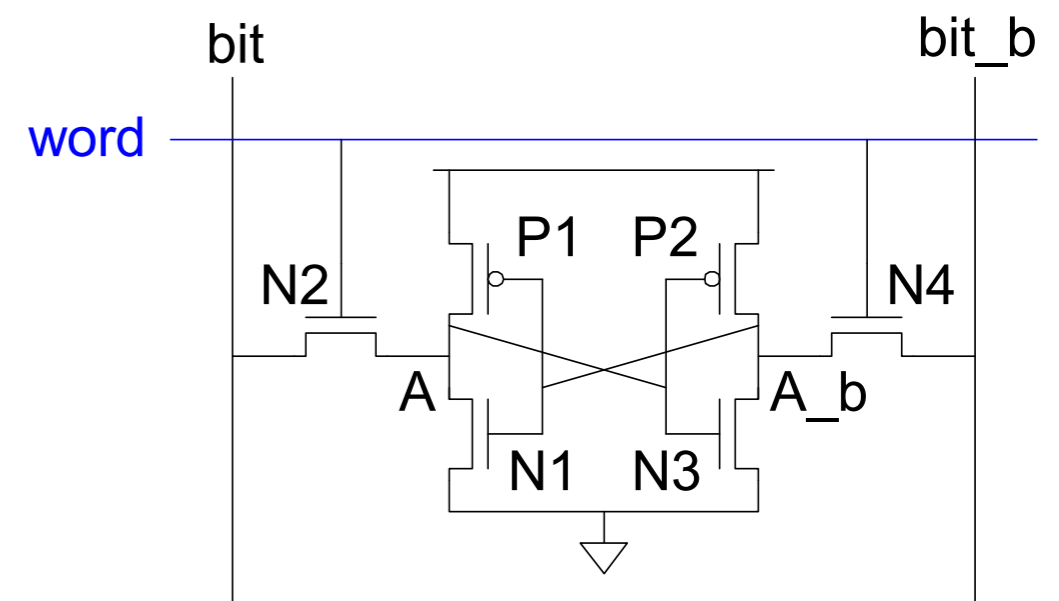- **Question 2:** At least how many bit lines to finish write?



Memory Arrays

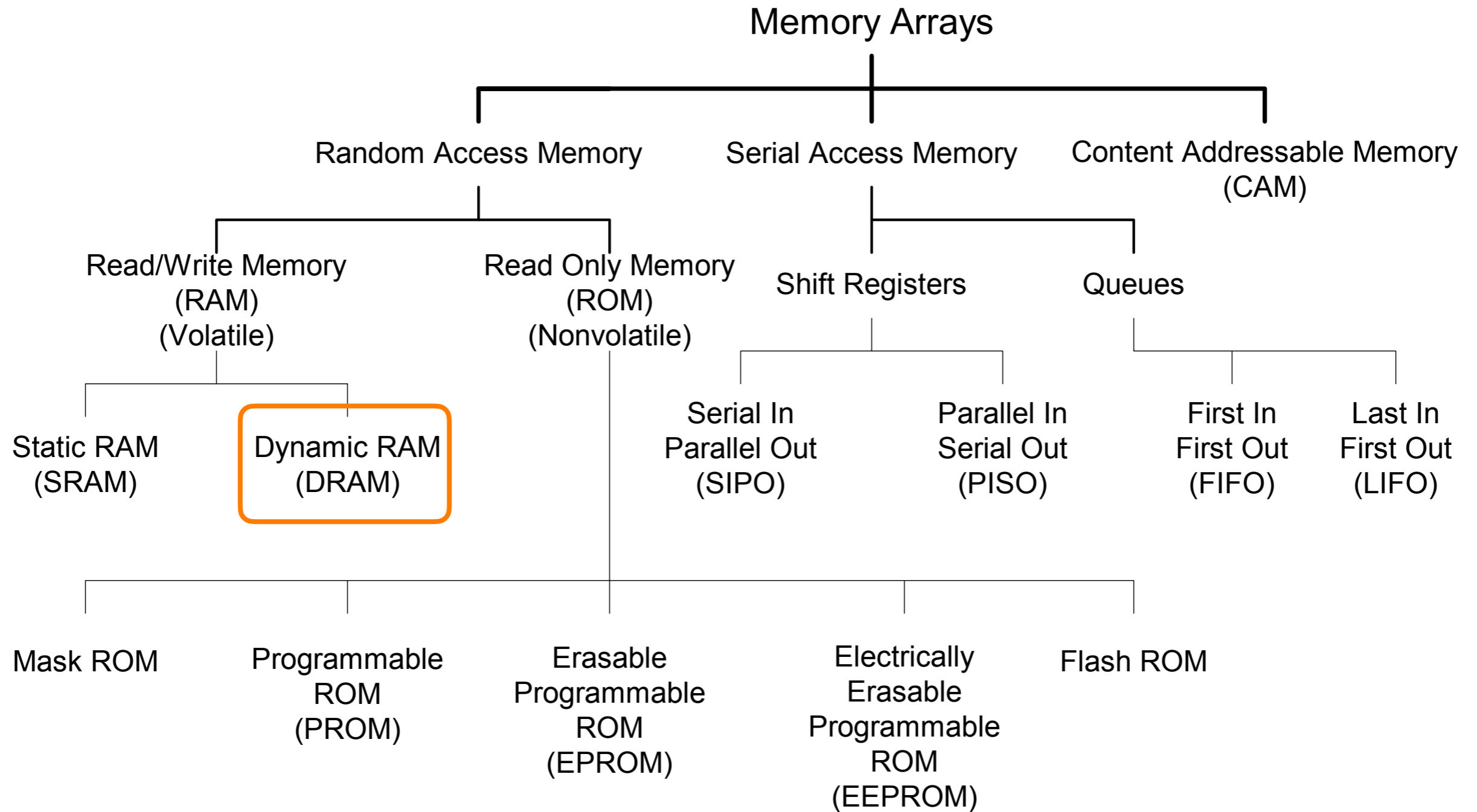


Dynamic RAM (DRAM)

- Basic Principle: Storage of information on **capacitors**
- **Charge & discharge** of capacitor to change stored value
- Use of transistor as “switch” to:
 - ♦ Store charge
 - ♦ Charge or discharge

4T DRAM Cell


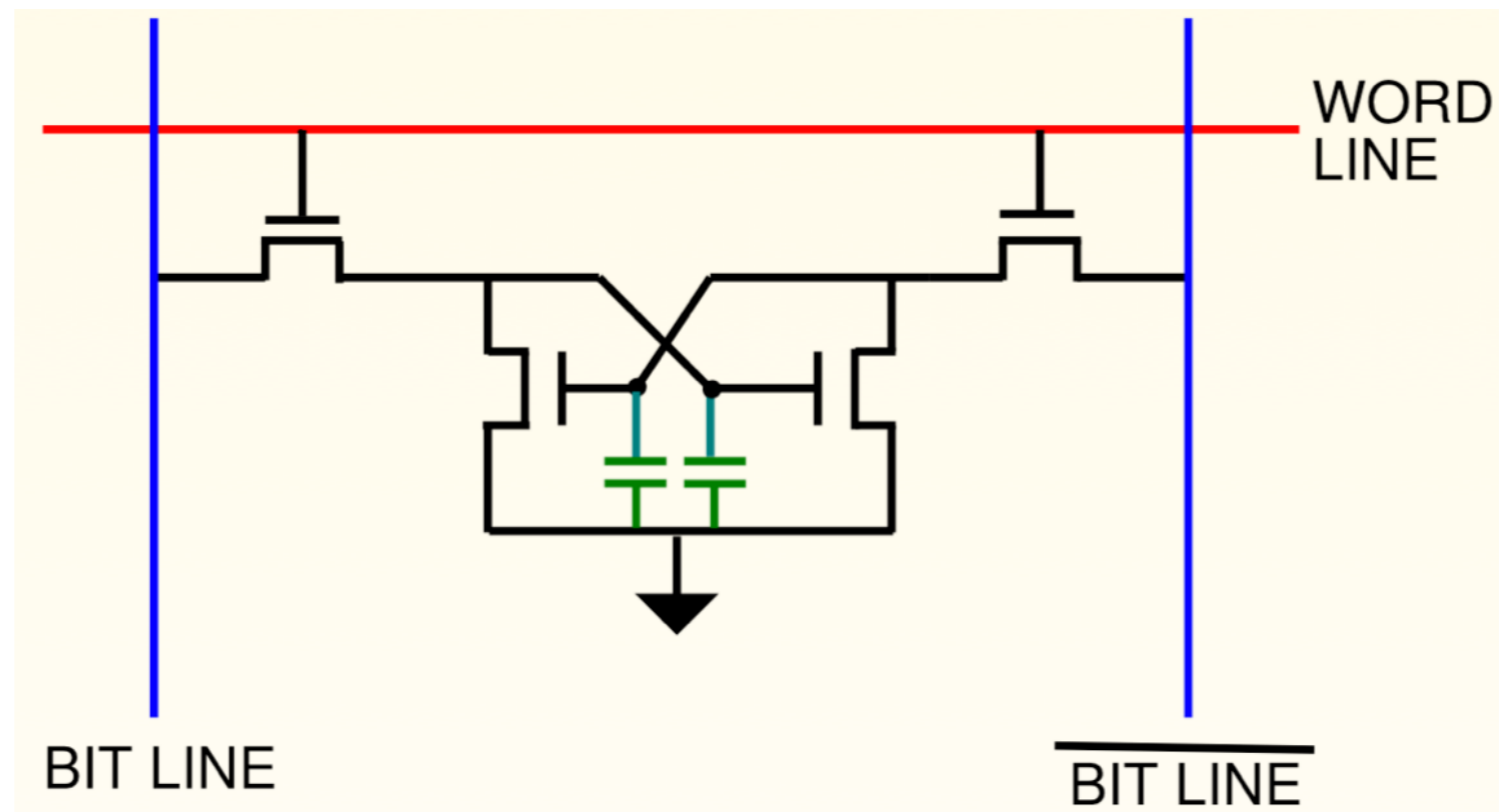
Remove the two p-MOS transistors from static RAM cell, to get a four-transistor dynamic RAM cell.





- Data must be refreshed regularly
- Dynamic cells must be designed very carefully
- Data stored as charge on gate capacitors (complementary nodes)

3T DRAM Cell

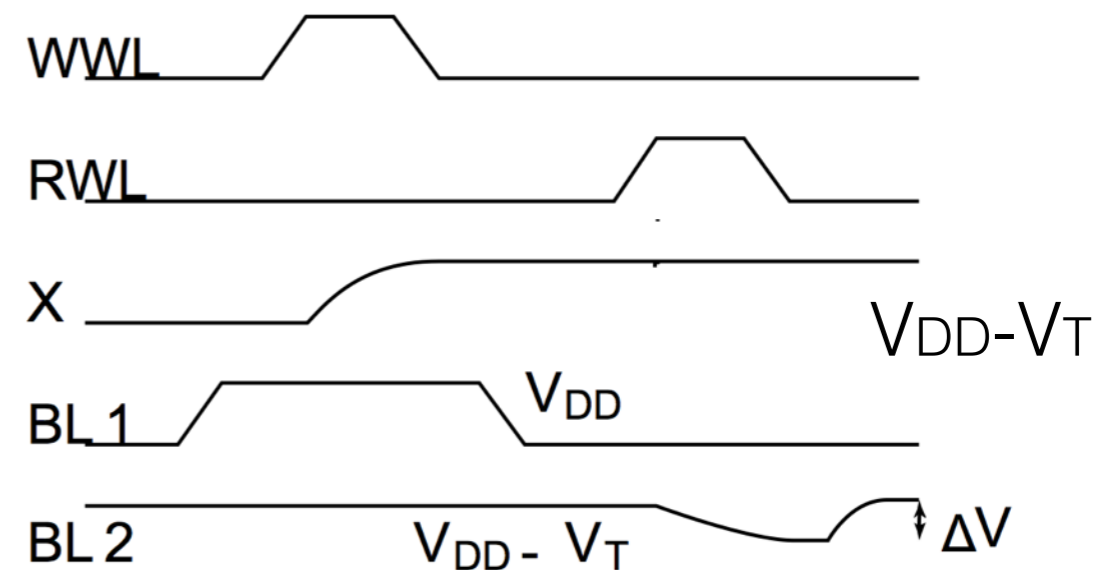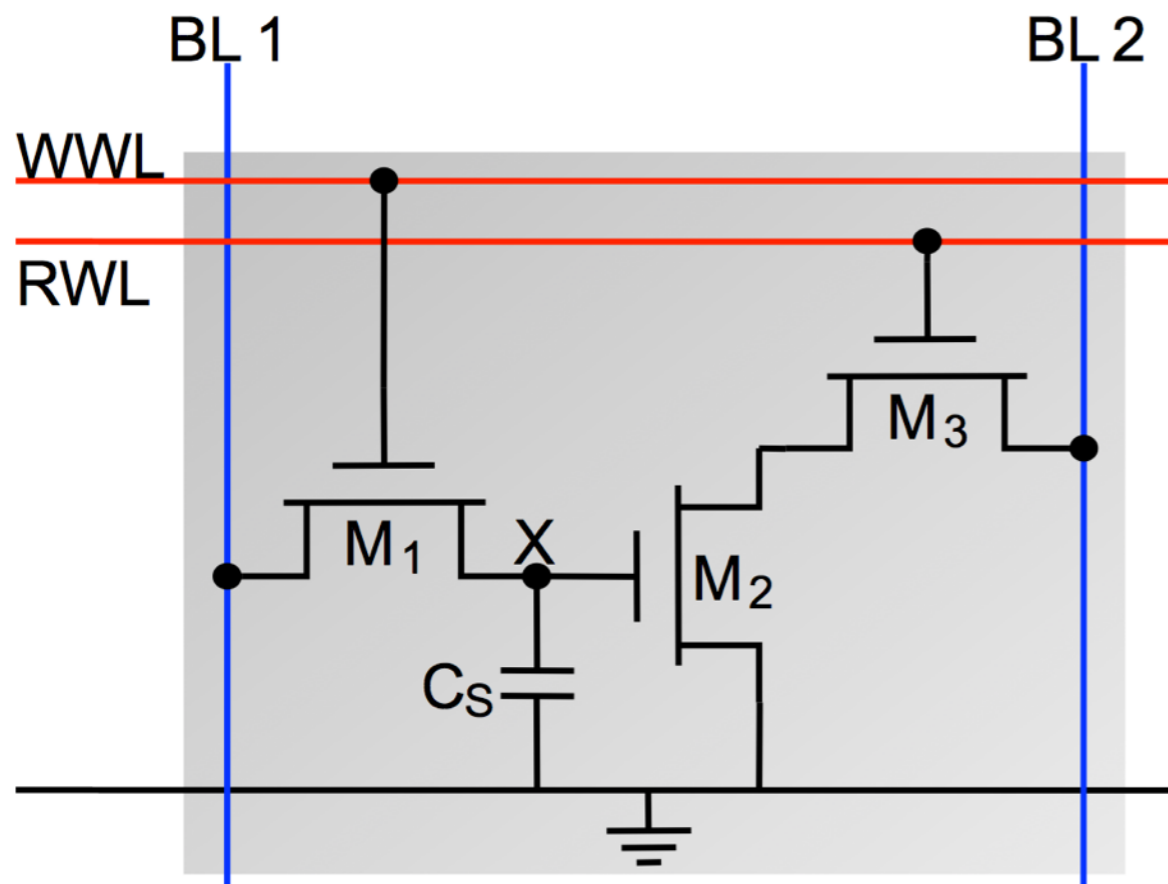- No constraints on device ratios
- Reads are non-destructive
- Value stored at node X when writing a “1” = $V_{DD} - V_T$




3T DRAM Layout

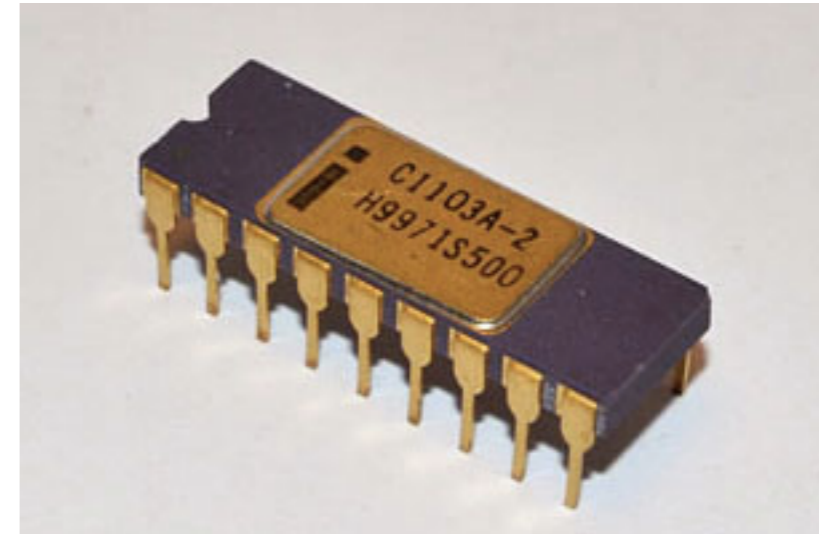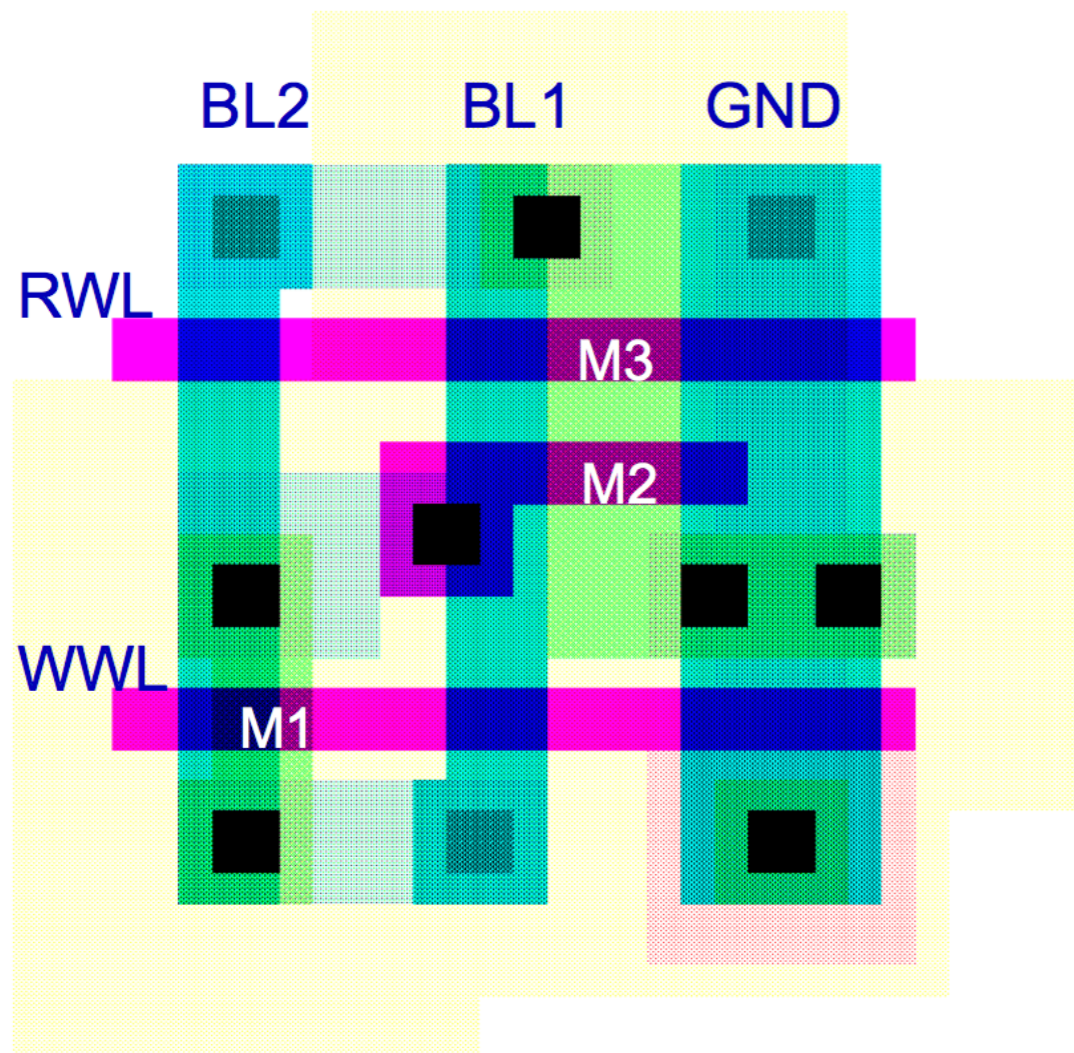


[1970: Intel 1003]

- 576 λ 3T DRAM v.s. 1092 λ 6T SRAM
- Further simplified


1T DRAM Cell

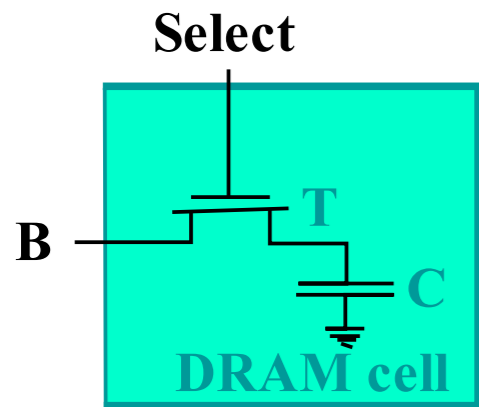


(a)

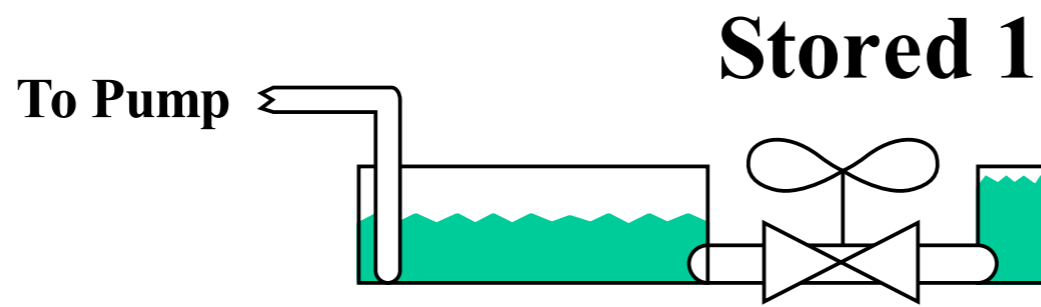


(b)

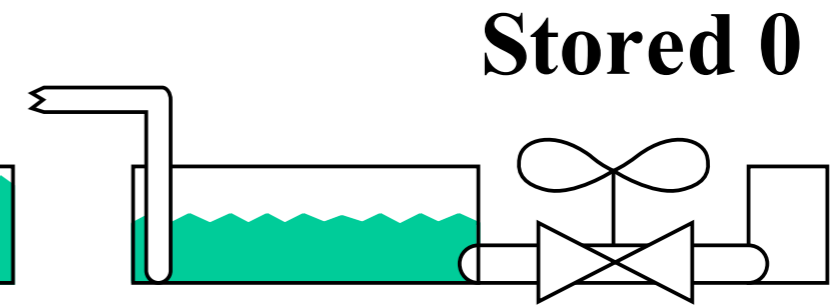


(c)

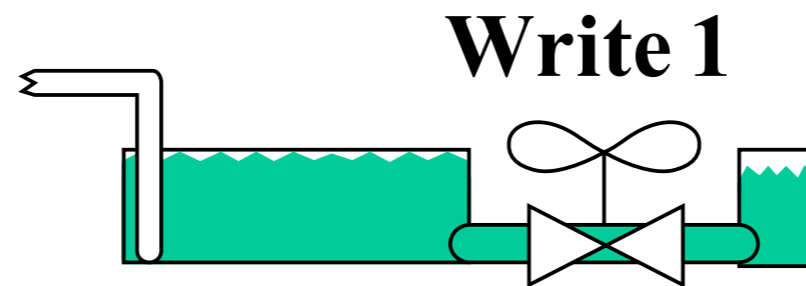


(d)

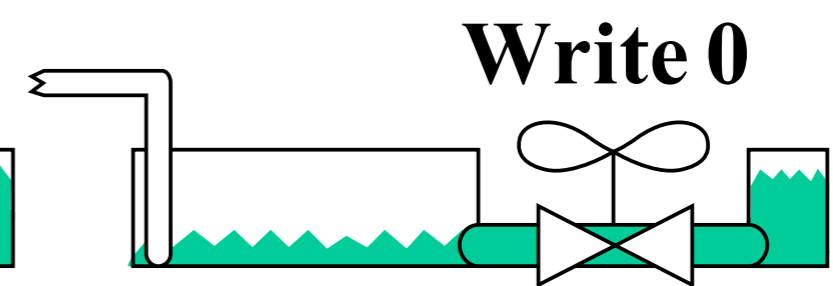

(e)

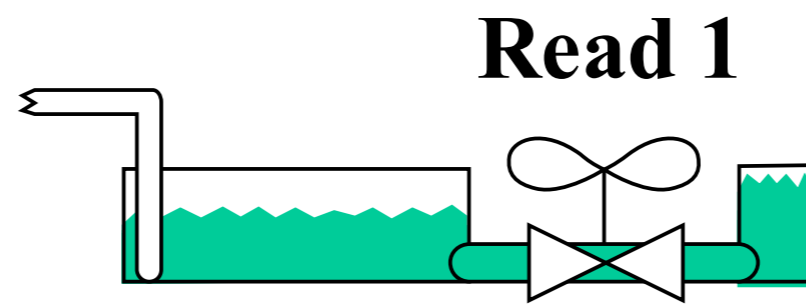


(f)

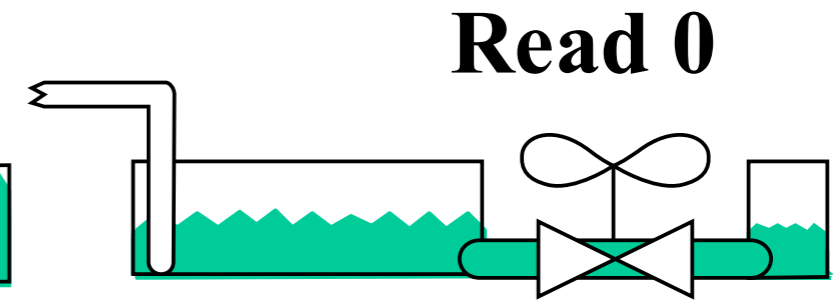

(g)



- Need sense amp helping reading

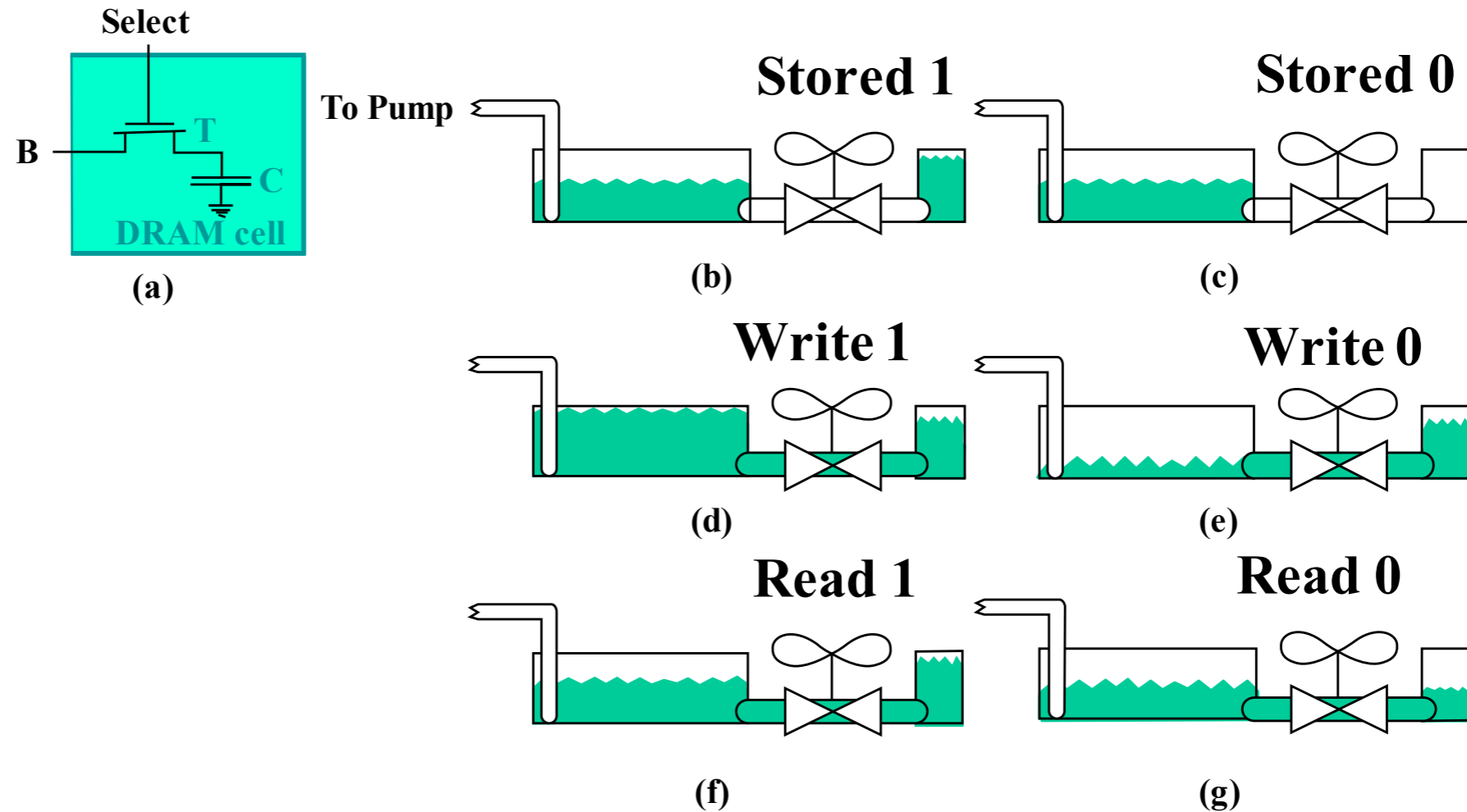

- Read:
 - ◆ Pre-charge large tank to $V_{DD}/2$
 - ◆ If $T_s = 0$, for large tank : $V_{DD}/2 - V_1$
 - ◆ If $T_s = 1$, for large tank: $V_{DD}/2 + V_1$
 - ◆ V_1 is very insignificant
 - ◆ Need sense amp

1T1R DRAM Cell

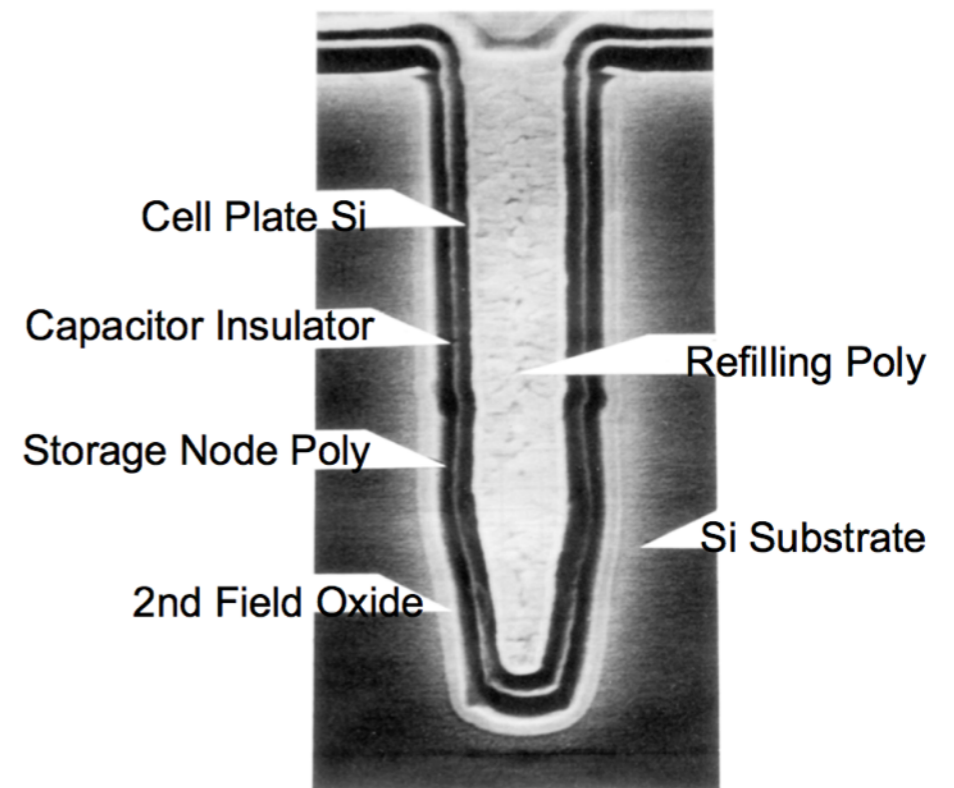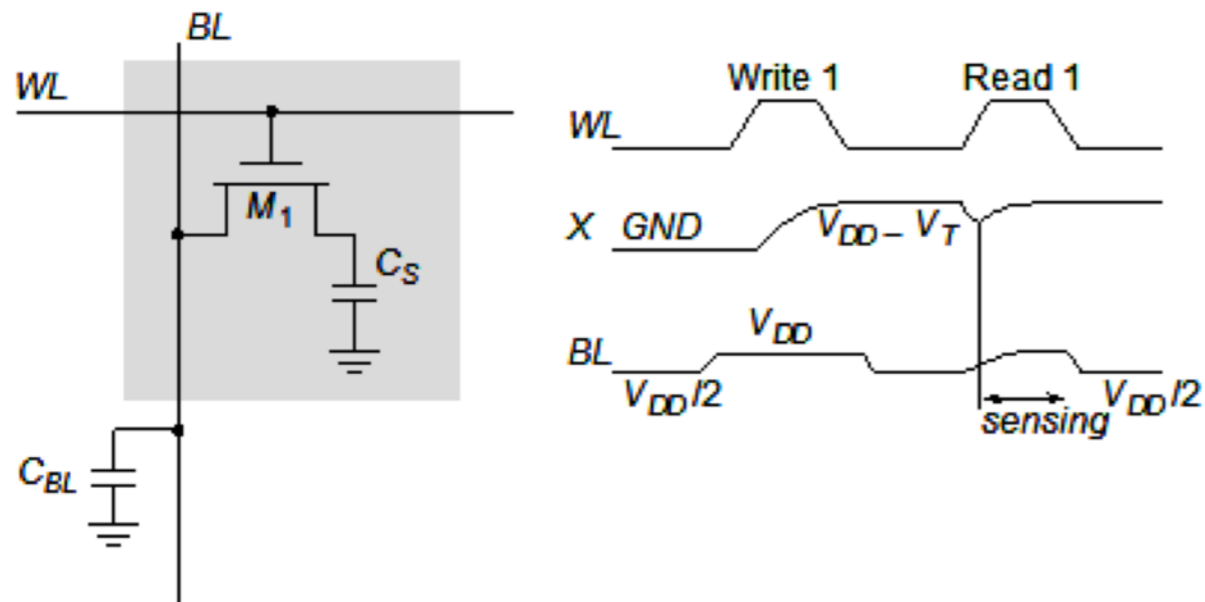- **Write:** C_s is charged or discharged by asserting WL and BL
- **Read:** Charge redistribution takes place between bit line and storage capacitance
- Voltage swing is small; typically around 250 mV



Trench-capacitor cell [Mano87]

EX. 1T DRAM Cell

- **Question:** $V_{DD}=4V$, $C_S=100pF$, $C_{BL}=1000pF$. What's the voltage swing value?
- **Note:**
$$\Delta V = \frac{V_{DD}}{2} \cdot \frac{C_S}{C_S + C_{BL}}$$

SRAM v.s. DRAM

Static (SRAM)


- Data stored as long as supply is applied
- Large (6 transistors/cell)
- Fast
- Compatible with current CMOS manufacturing

Dynamic (DRAM)

- Periodic refresh required
- Small (1-3 transistors/cell)
- Slower
- Require additional process for trench capacitance


Array Architecture

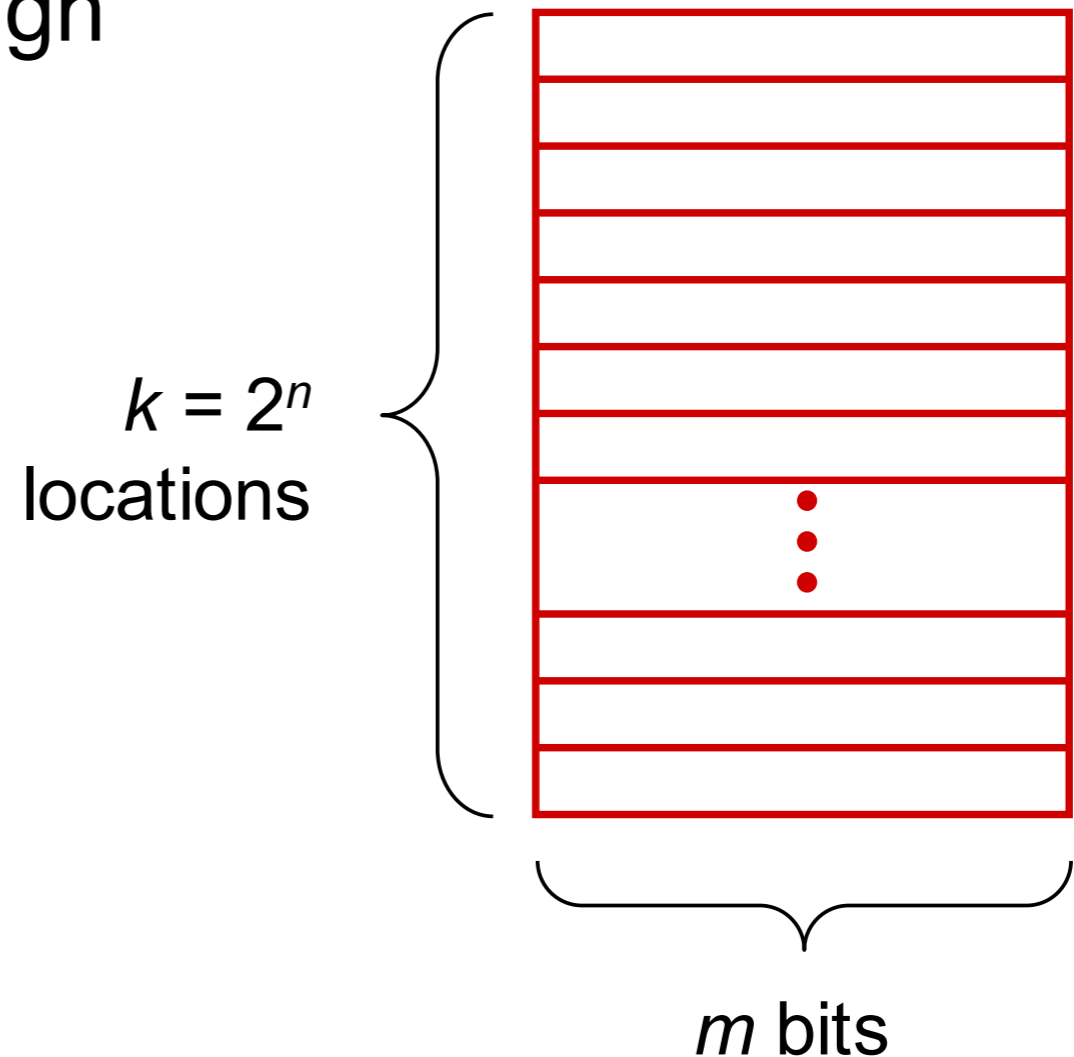- 2^n words of 2^m bits each
- Good regularity – easy to design




SRAM Memory Structure

- Latch based memory

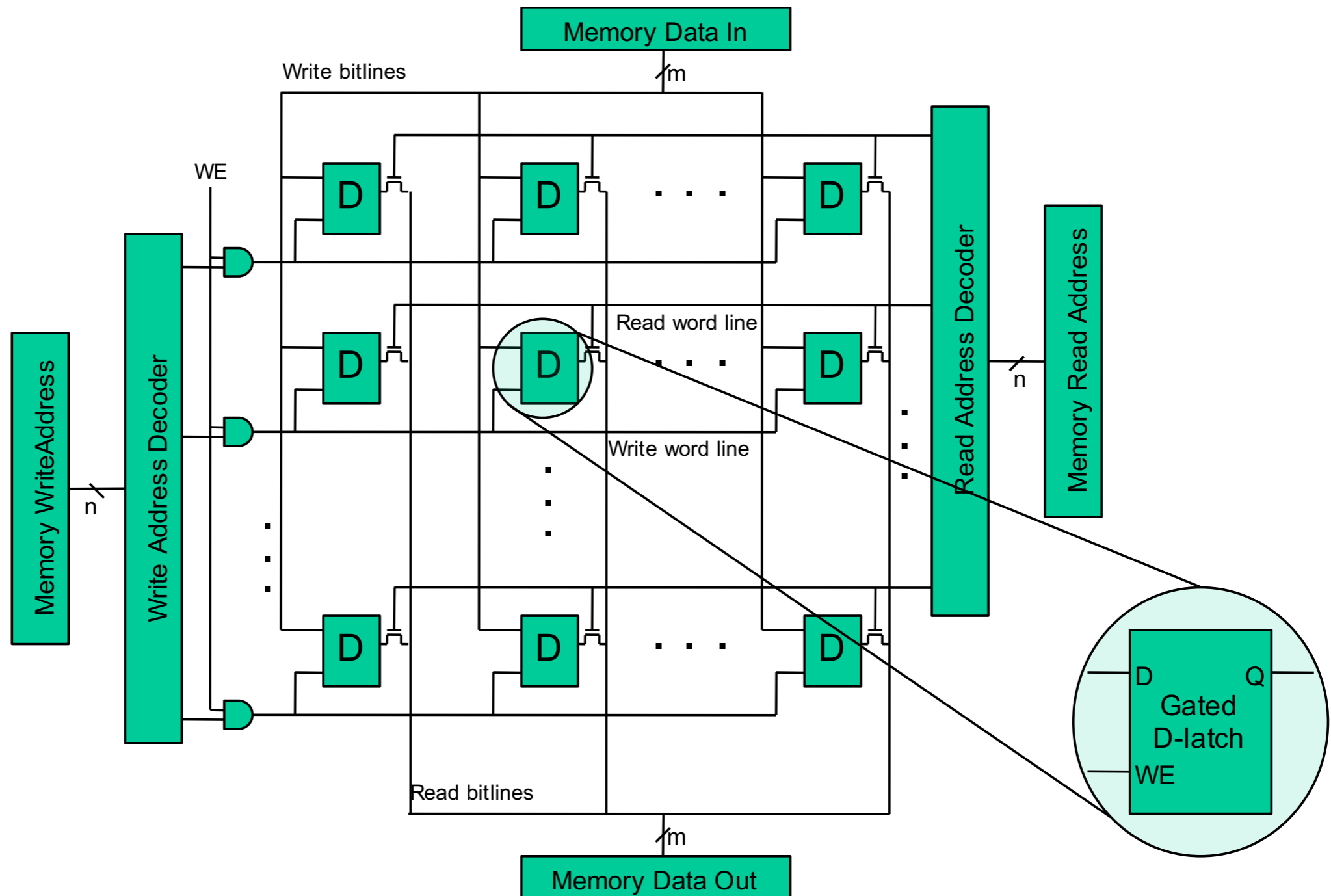

Array Architecture

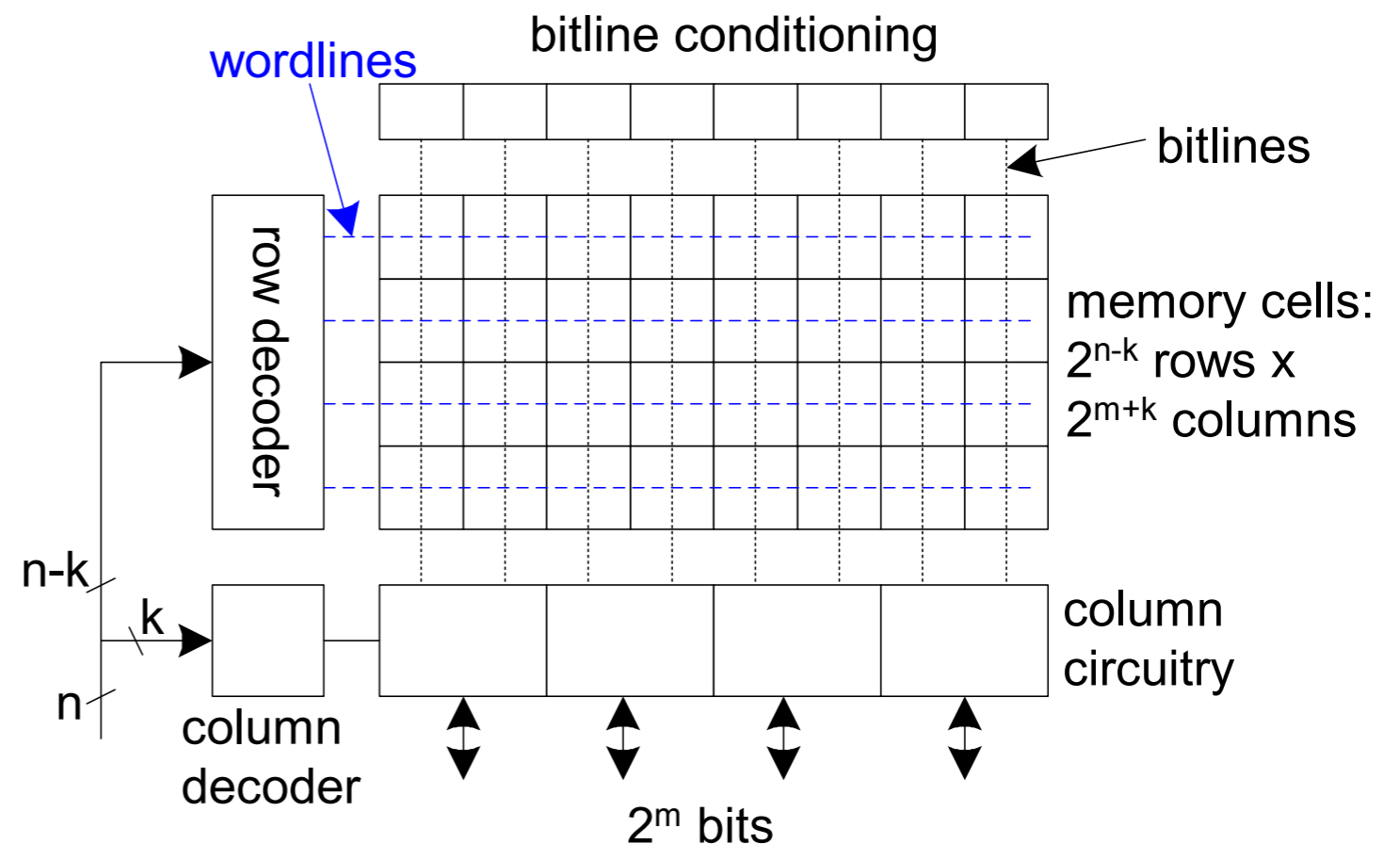
- 2^n words of 2^m bits each
- How to design if $n \gg m$?
- Fold by 2^k into fewer rows of more columns





Decoders

- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND with **NAND** or **NOR** gates

Static CMOS

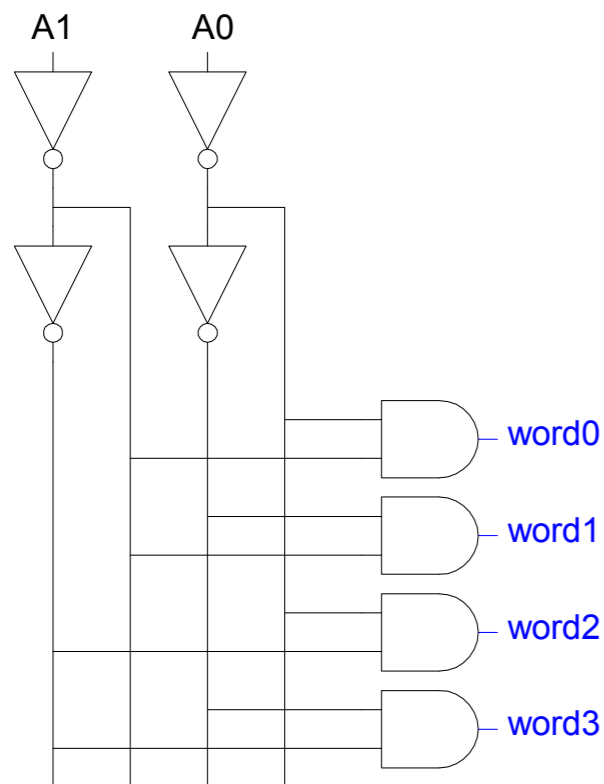


Using **NOR** gates

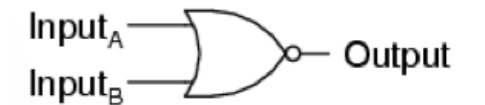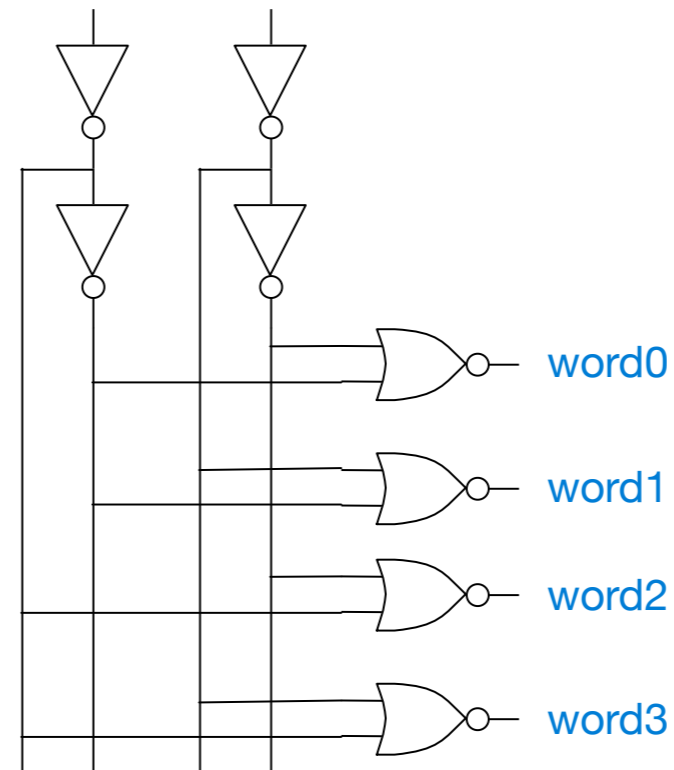

| A | B | Output |
|---|---|--------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


EX. Decoder

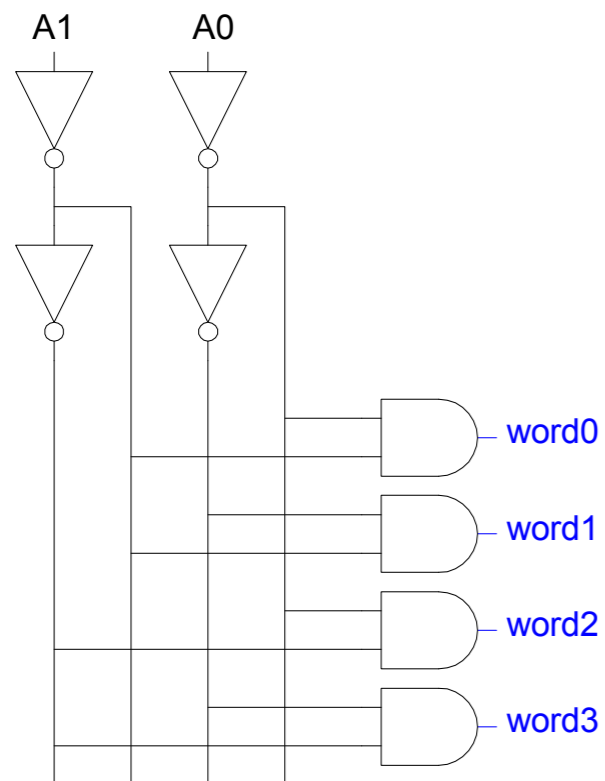- **Question:** AND gates \Rightarrow NAND gate structure




Large Decoders

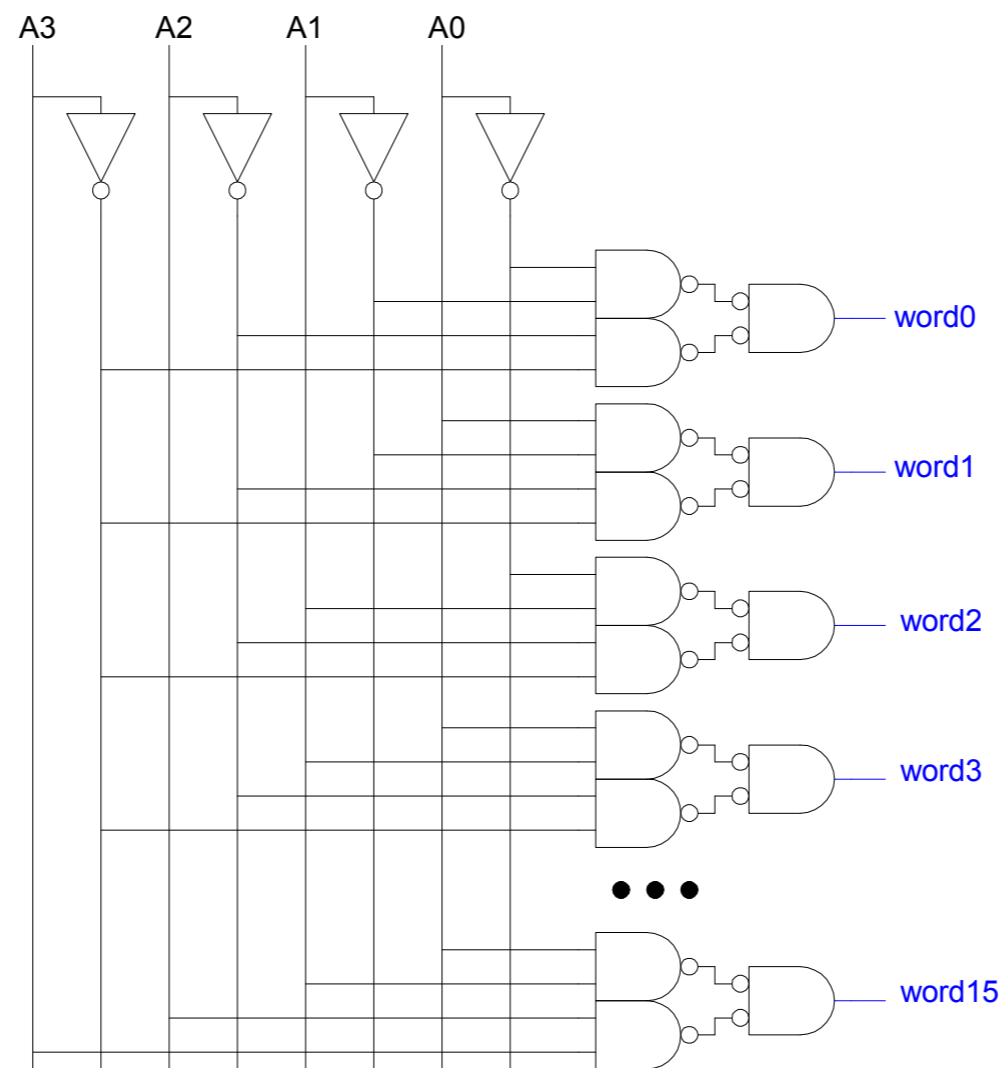- For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates



Predecoding

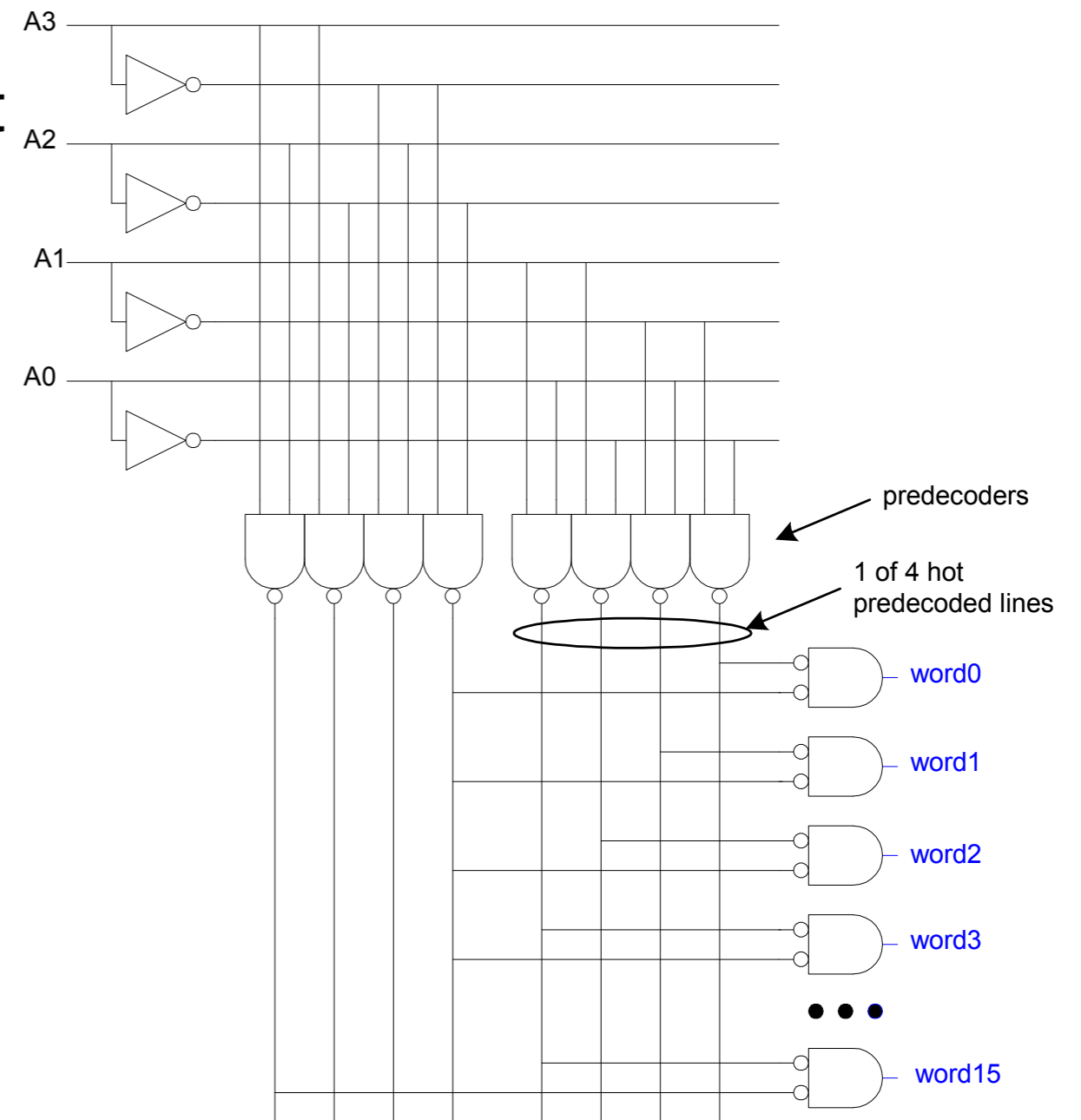
- Many of these gates are redundant
 - Factor out common gates
 - => Predecoder
 - Saves area
 - Same path effort



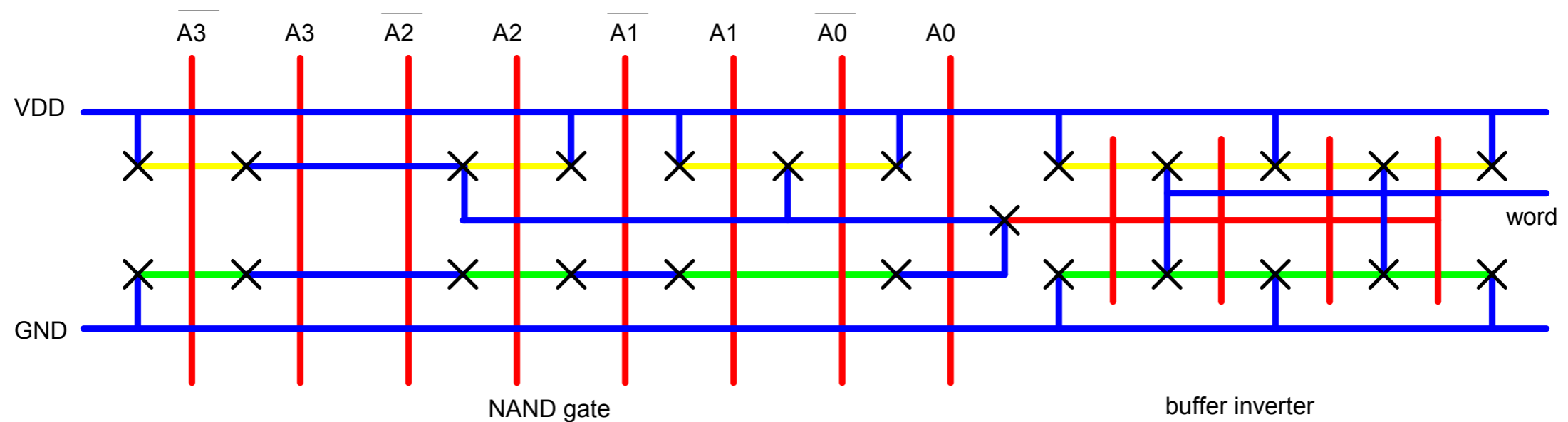- **Question:** How many NANDs can be saved?


*Decoder Layout

- Decoders must be pitch-matched to SRAM cell
 - Requires very skinny gates




*Column Circuitry

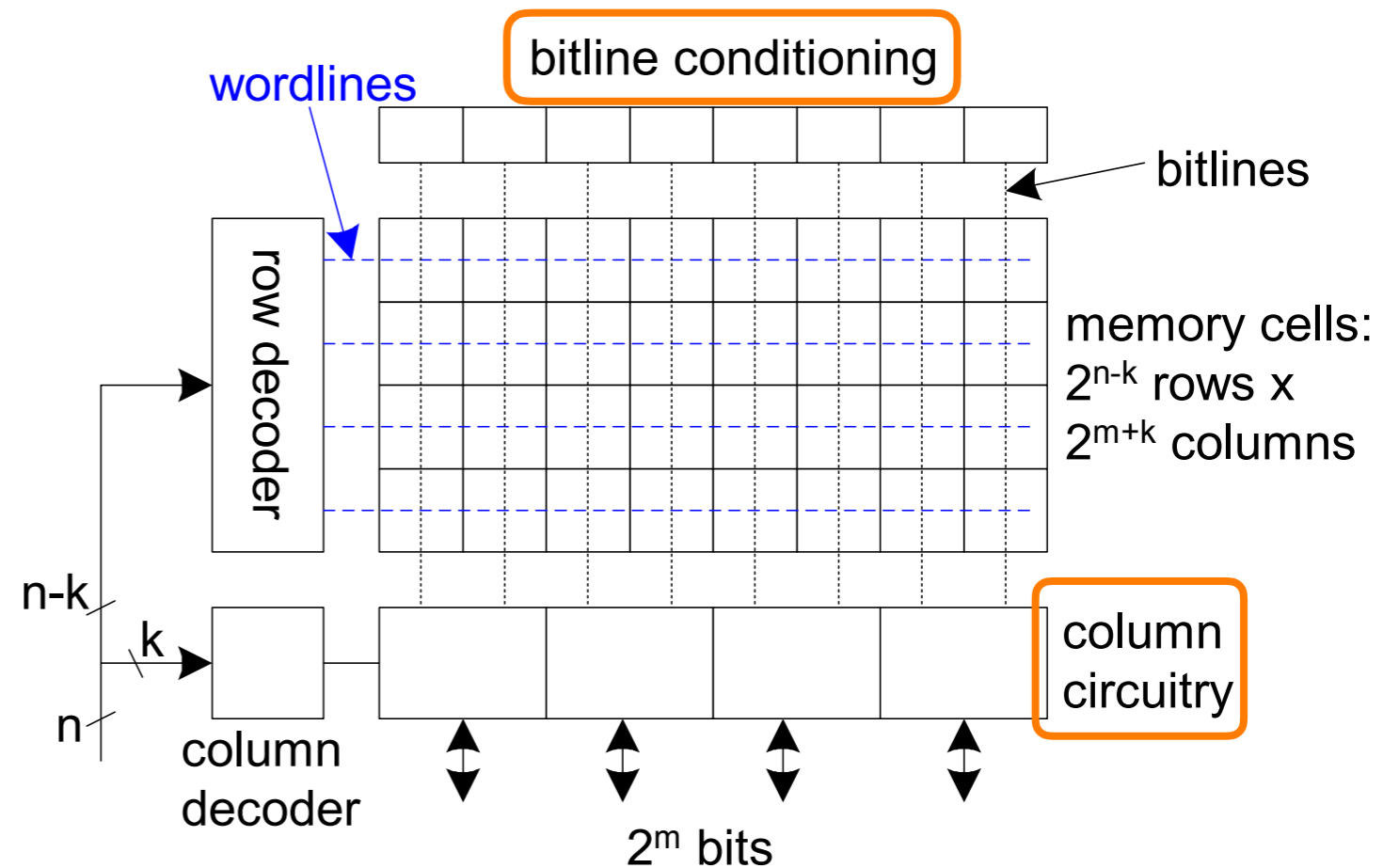- Some circuitry is required for each column
 - Bitline conditioning
 - Column multiplexing
 - *Sense amplifiers (DRAM)




*Bitline Conditioning

- Precharge bitlines high before reads

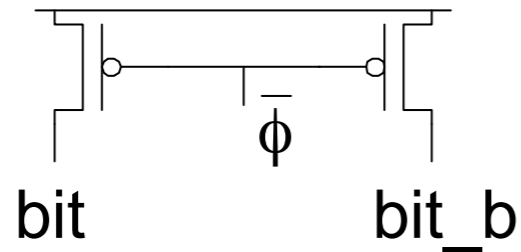


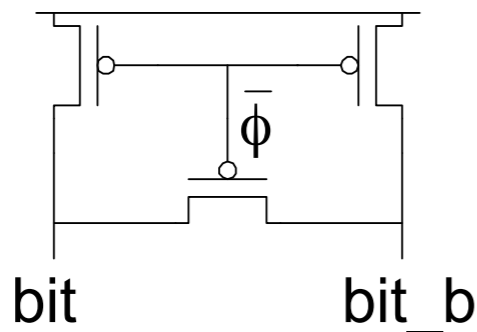- Equalize bitlines to minimize voltage difference when using sense amplifiers





*Twisted Bitlines

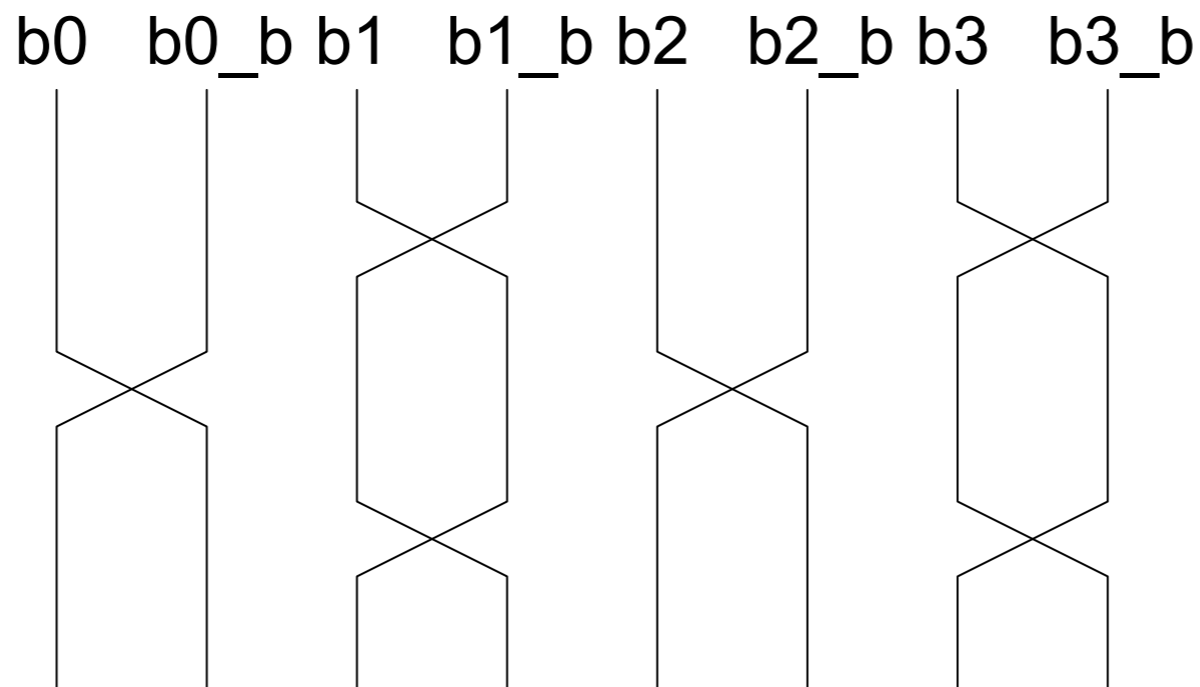- Sense amplifiers also amplify noise
 - Coupling noise is severe in modern processes
 - Try to couple equally onto bit and bit_b
 - Done by *twisting* bitlines




*SRAM Column Example

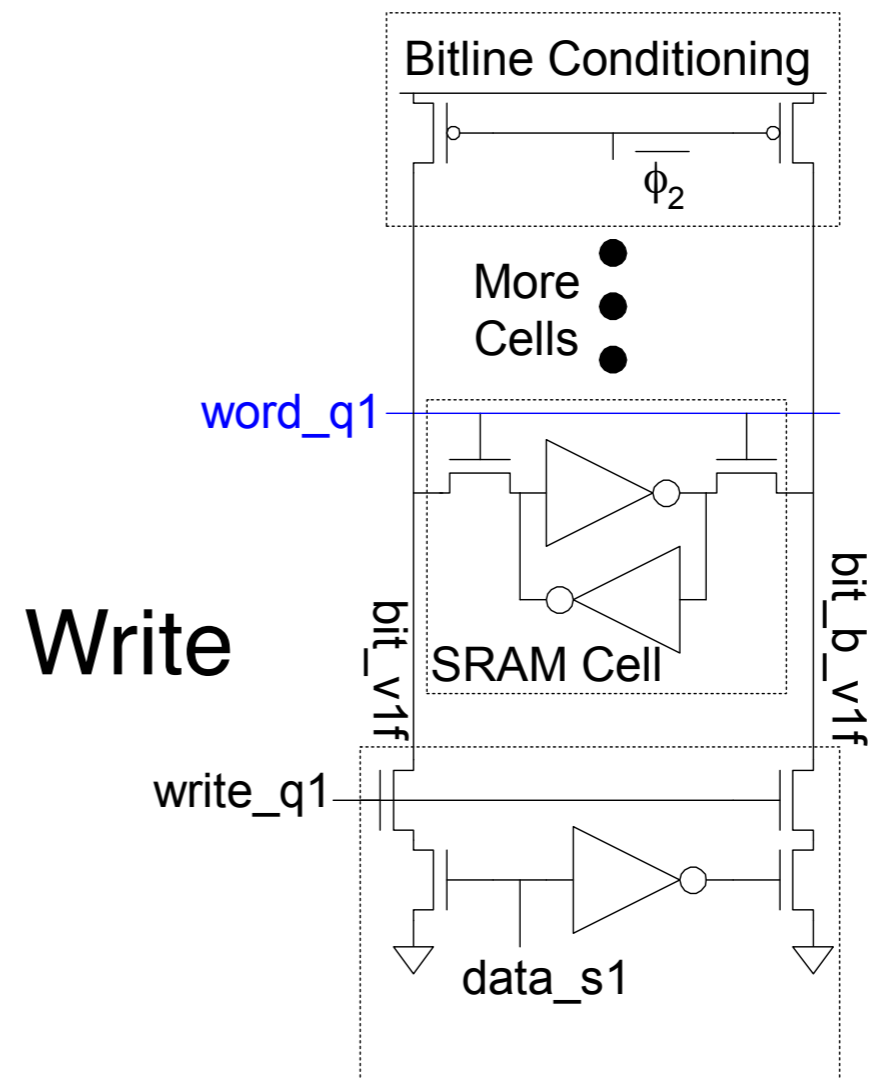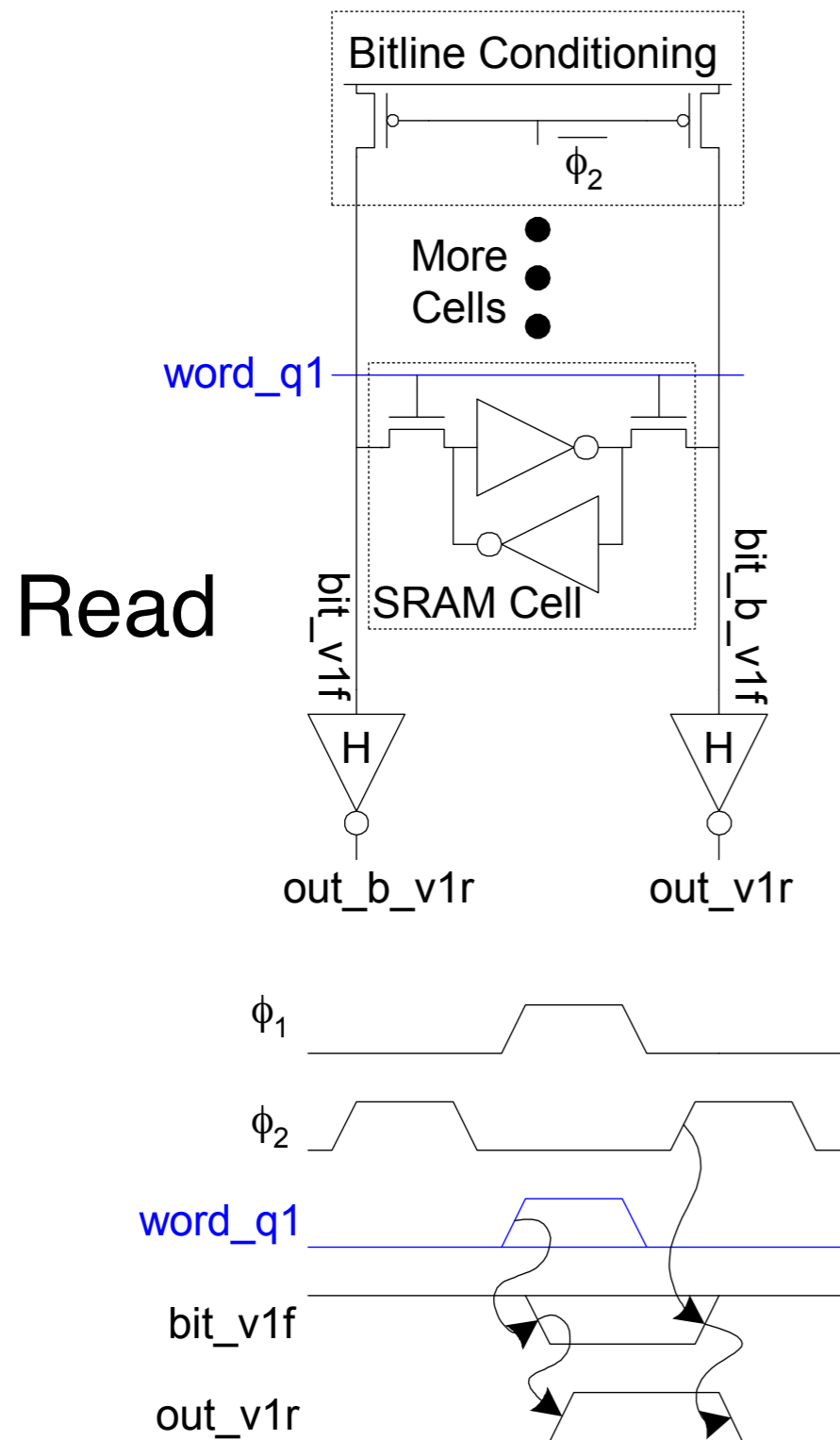

*Column Multiplexing


- Recall that array may be folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
 - Must select 16 output bits from the 128 columns
 - Requires 16 8:1 column multiplexers

*Ex: 2-way Muxed SRAM

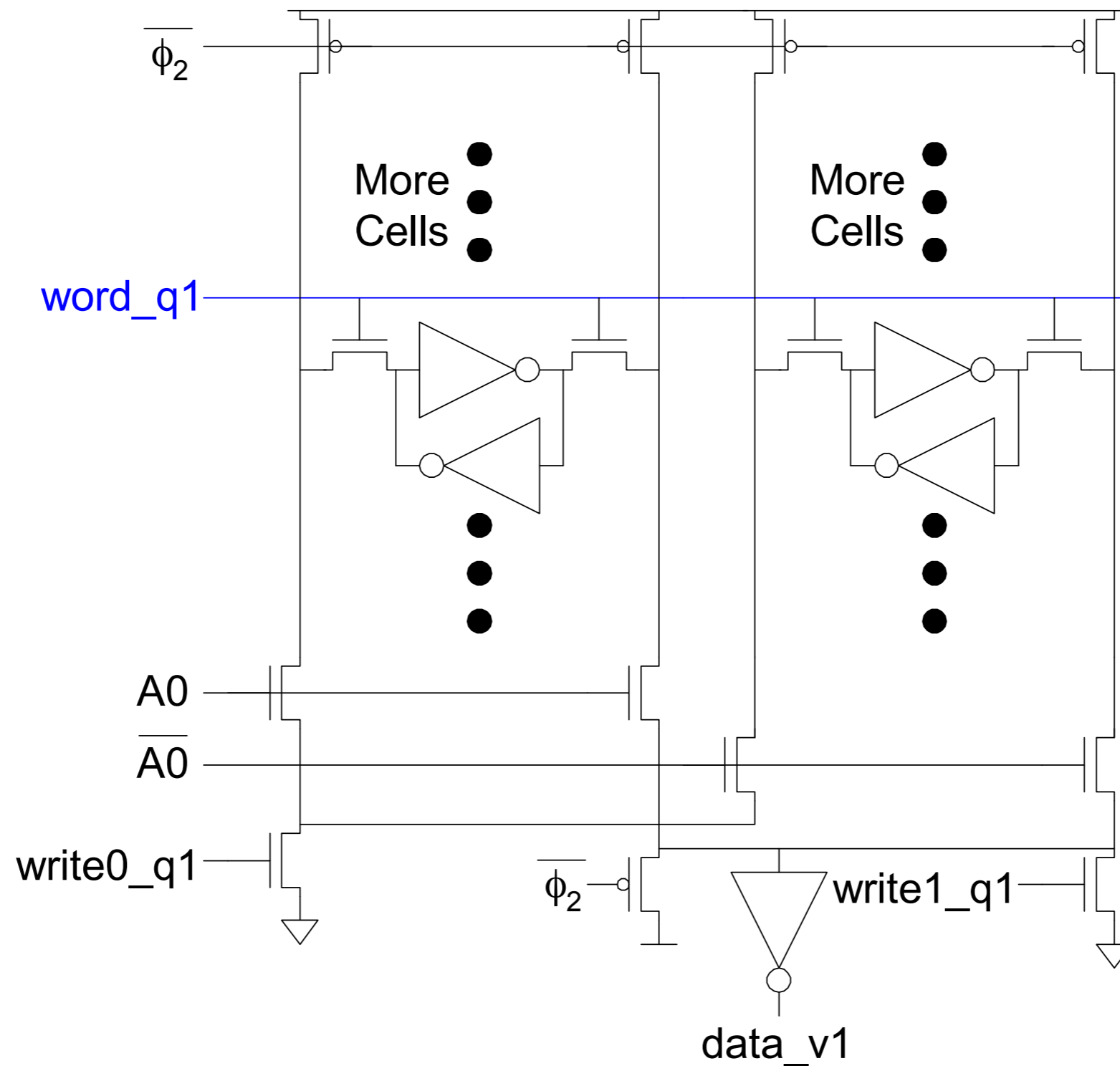


*Tree Decoder Mux

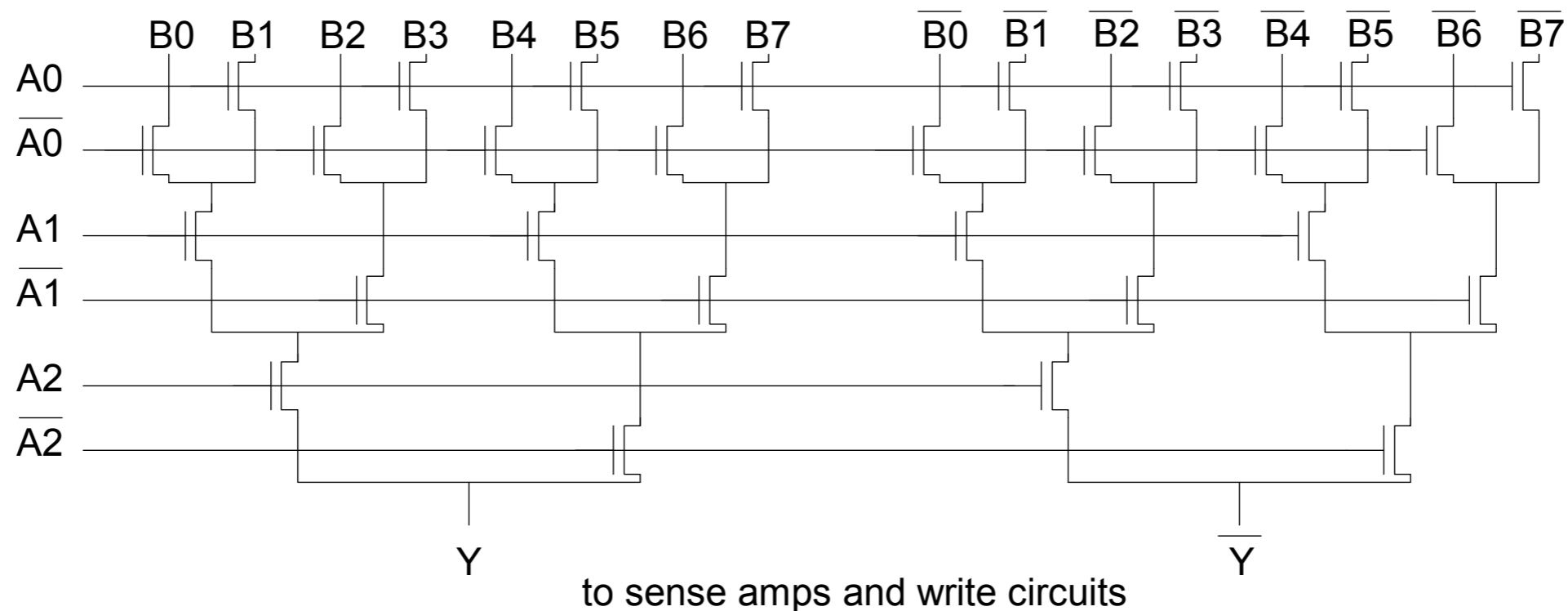
- Column mux can use pass transistors
 - Use nMOS only, precharge outputs
- One design is to use k series transistors for $2^k:1$ mux
 - No external decoder logic needed



*SRAM from ARM

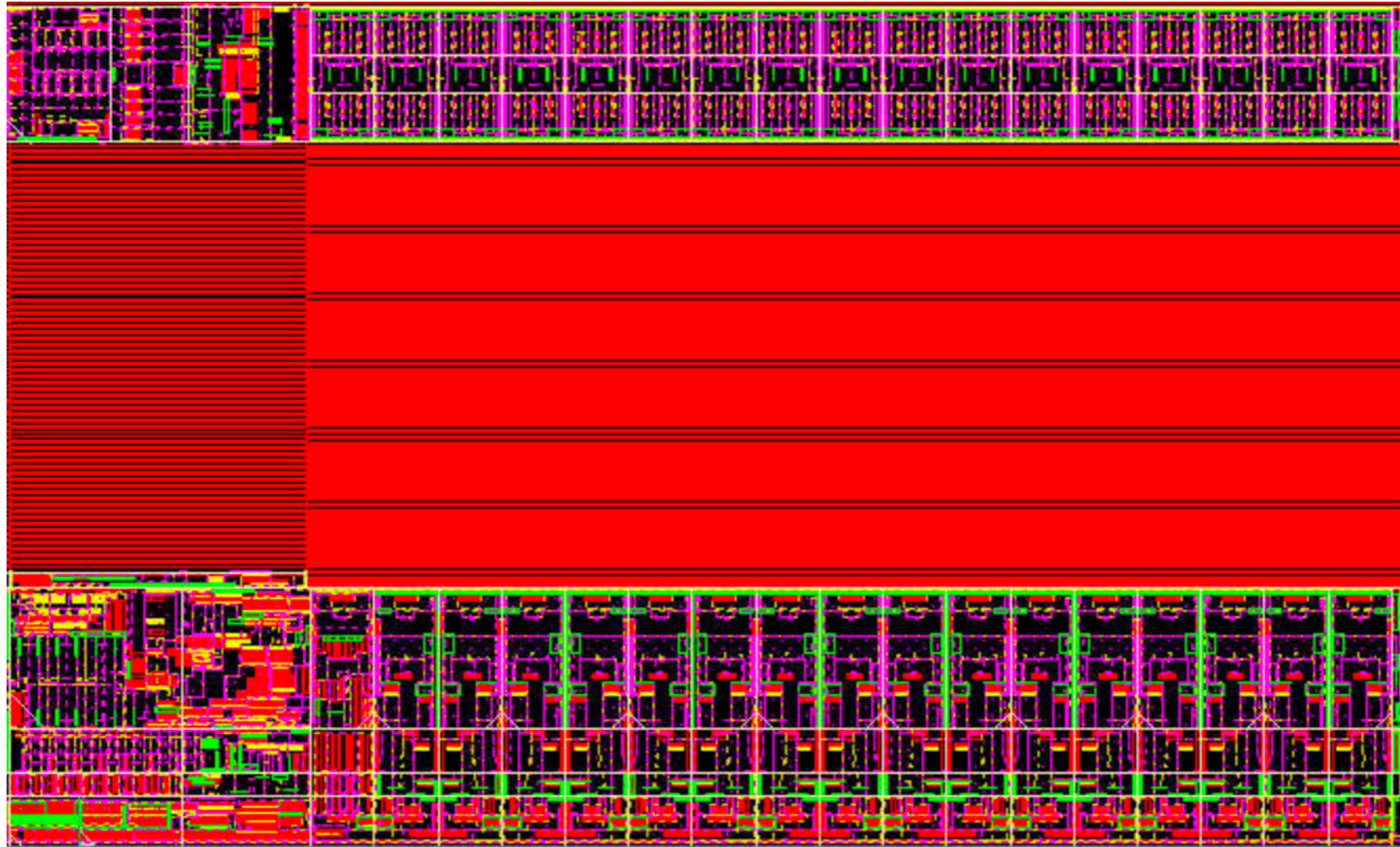

*Sense Amp Operation for 1T DRAM

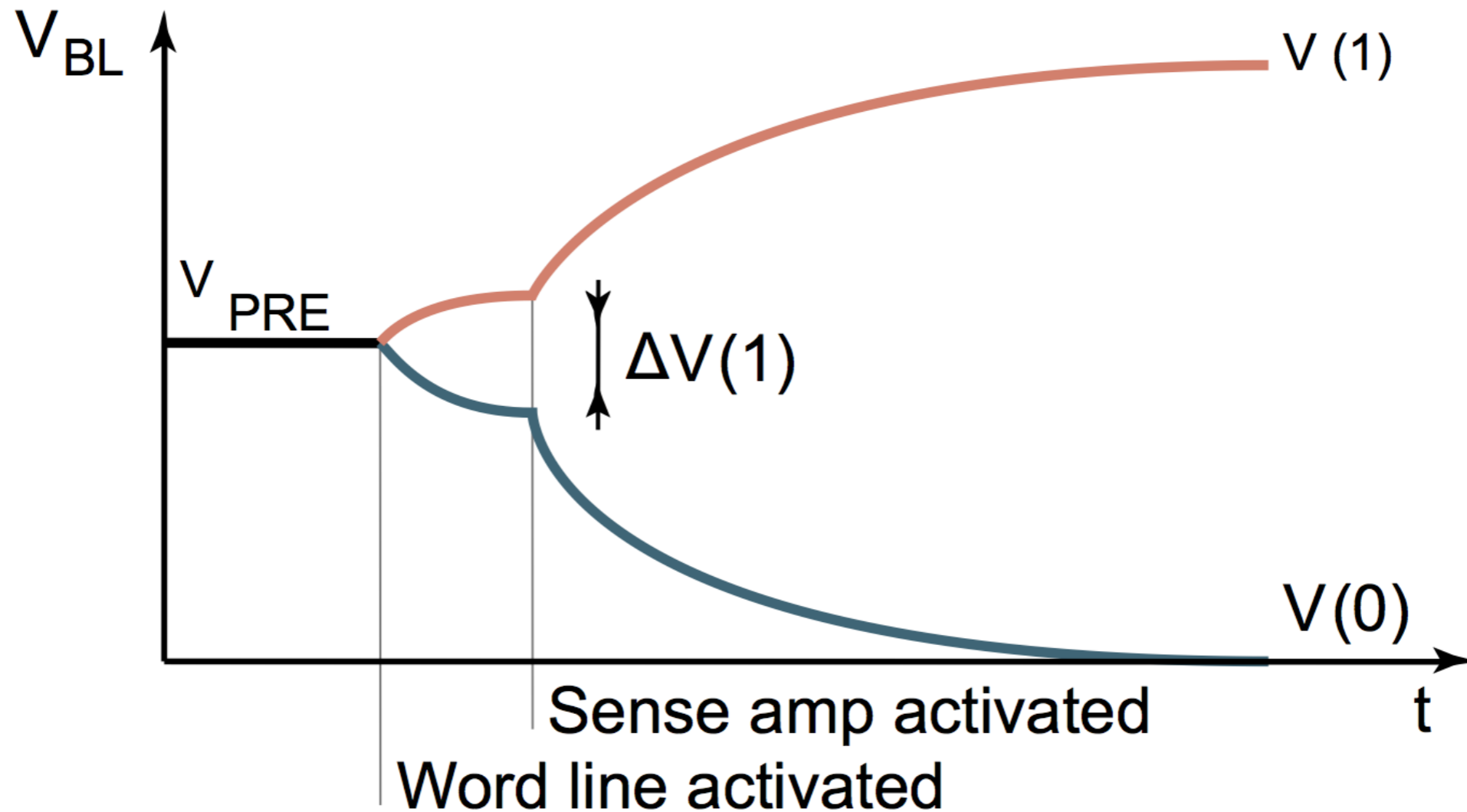


- 1T DRAM read is destructive
- Read and refresh for 1T DRAM

*Sense Amplifiers (DRAM)

- Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 256 rows x 128 cols
 - 256 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- Sense amplifiers are triggered on small voltage swing (reduce ΔV)


*Differential Pair Amp

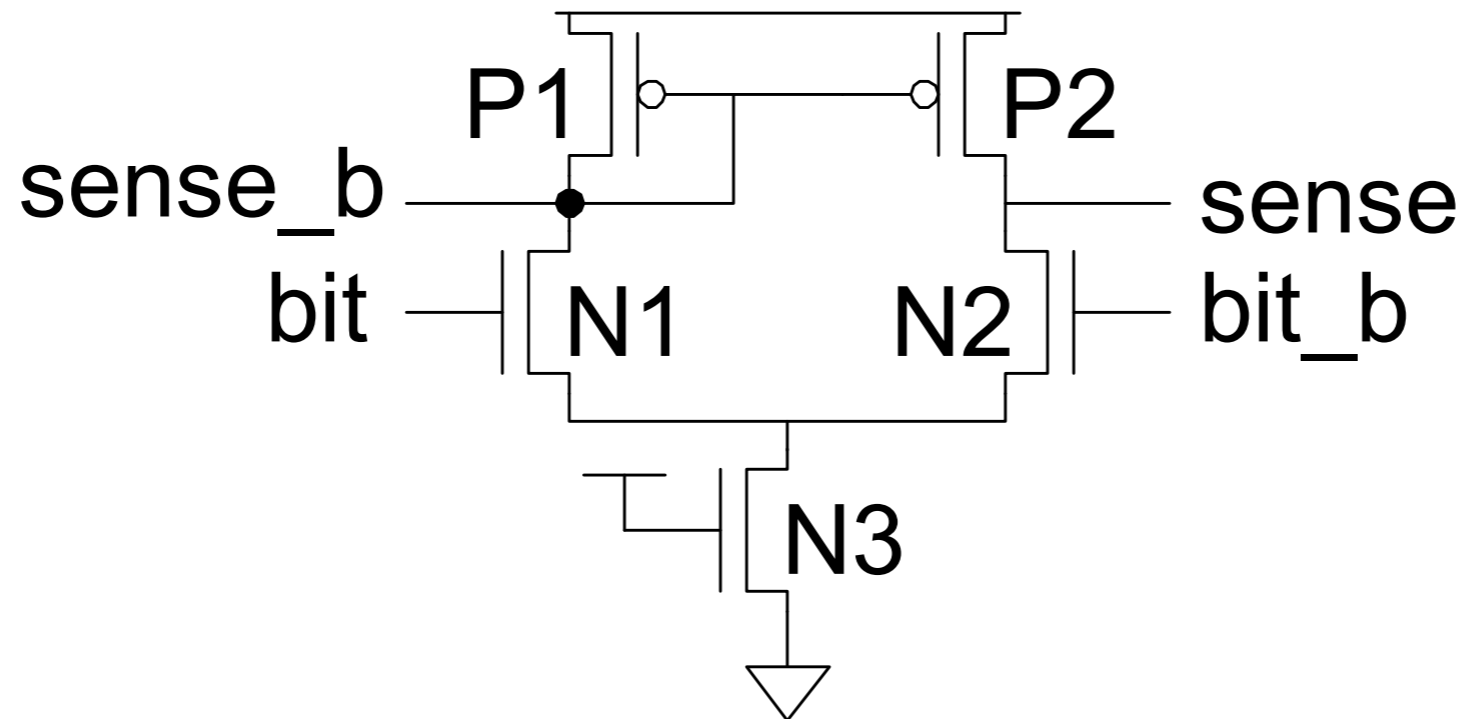- Differential pair requires no clock
- But always dissipates static power



*Clocked Sense Amp

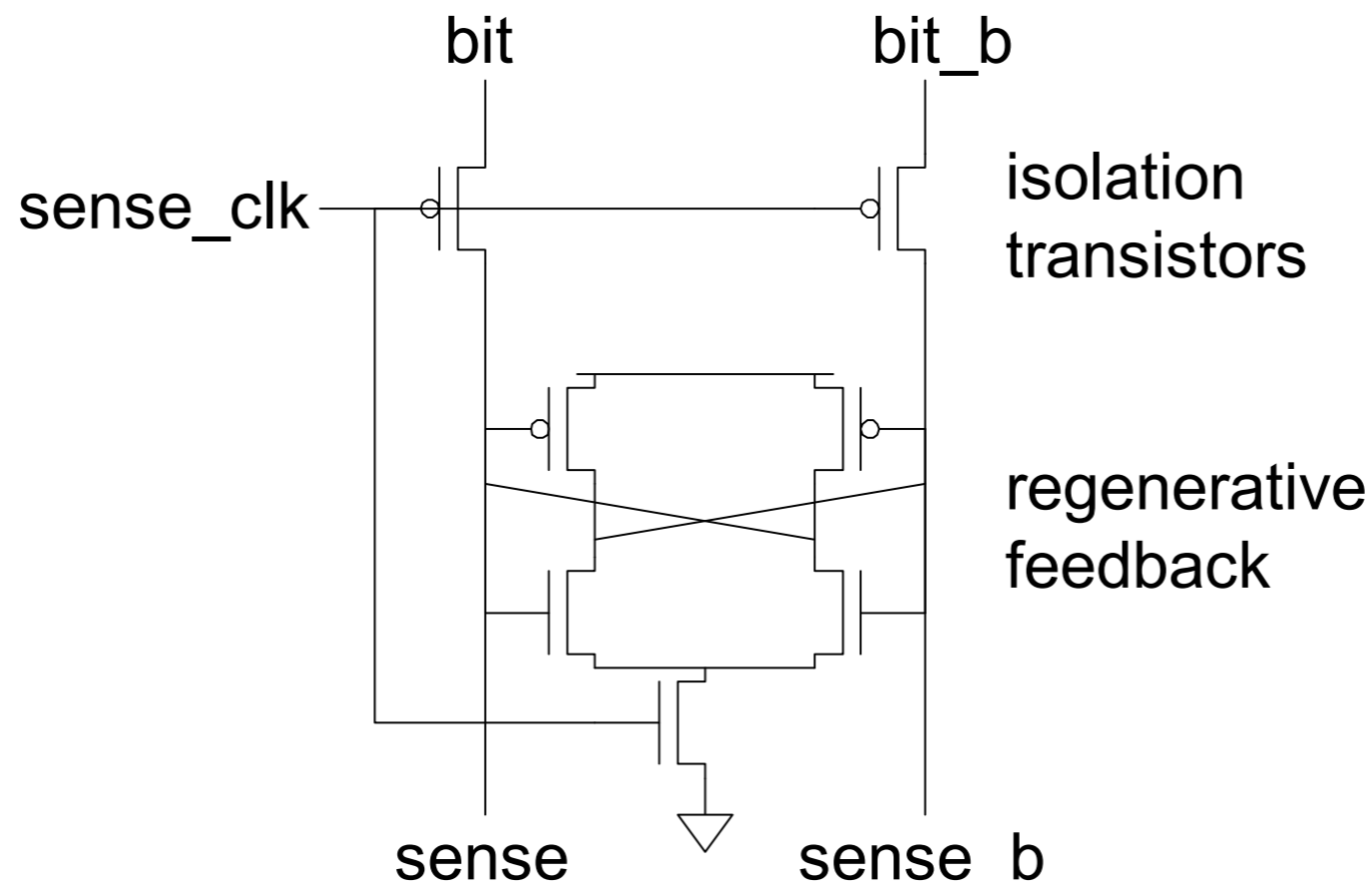- Clocked sense amp saves power
- Requires sense_clk after enough bitline swing
- Isolation transistors cut off large bitline capacitance



Thank You :-)