



香港中文大學

The Chinese University of Hong Kong

CENG3430 Rapid Prototyping of Digital Systems

Lecture 10:

VHDL versus Verilog


Ming-Chang YANG

mcyang@cse.cuhk.edu.hk



- **VHDL vs. Verilog**
 - Background
 - Syntax and Popularity
 - Operators
 - Overall Structure
 - External I/O Declaration
 - Concurrent Statements
 - Sequential Statements
 - Edge Detection
 - Wire vs. Reg
 - Structural Design
 - Design Constructions
 - Case Study: Flip-flop

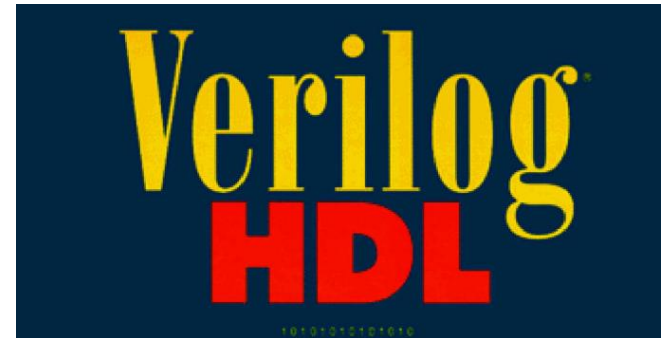
VHDL
Very High Speed Integrated Circuit
Hardware Description Language



What are VHDL and Verilog?



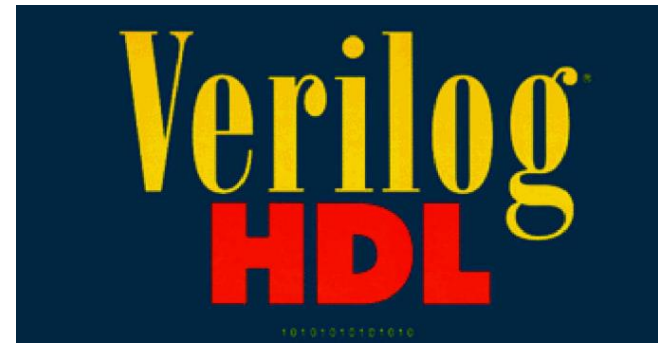VHDL
Very High Speed Integrated Circuit
Hardware Description Language



- They are both **hardware description languages** for **modeling hardware**.
- They are each a **notation** to describe the **behavioral** and **structural** aspects of an electronic digital circuit.

VHDL: Background




- **V**HSIC **H**ardware **D**escription **L**anguage
 - VHSIC: Very High Speed Integrated Circuit.
- Developed by **Department of Defense** (1981)
 - In 1986 rights were given to **IEEE**.
 - Became a standard and published in 1987.
 - Revised standard we know now published in 1993 (VHDL 1076-1993) regulated by VHDL international (VI).

VHDL
Very High Speed Integrated Circuit
Hardware Description Language

VHDL: Design Concept



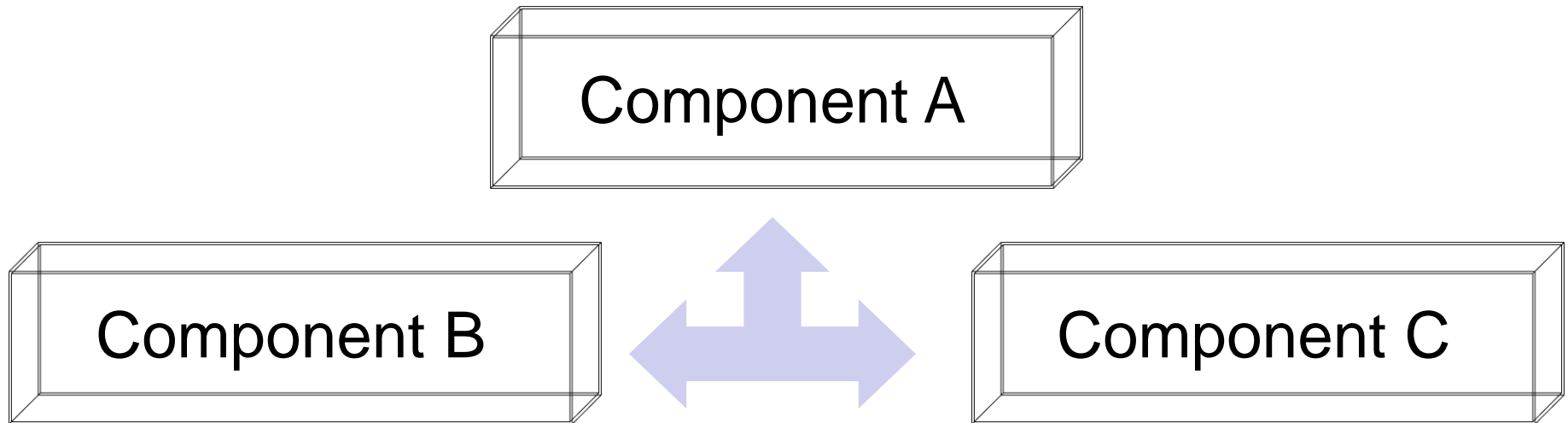- VHDL uses **top-down approach** to partition a design into small building blocks (i.e., **components**).
 - **Entity**: Describe interface signals and basic building blocks.
 - **Architecture**: Describe behavior, each entity can have multiple Architectures.



Connected by **port map** in architecture body

Verilog: Background




- Developed by **Gateway Design Automation** (1980)
 - Later acquired by **Cadence Design** (1989) who made it public in 1990.
 - Became a standardized in 1995 by **IEEE** (Std 1364) regulated by Open Verilog International (OVI).



Verilog: Design Concept



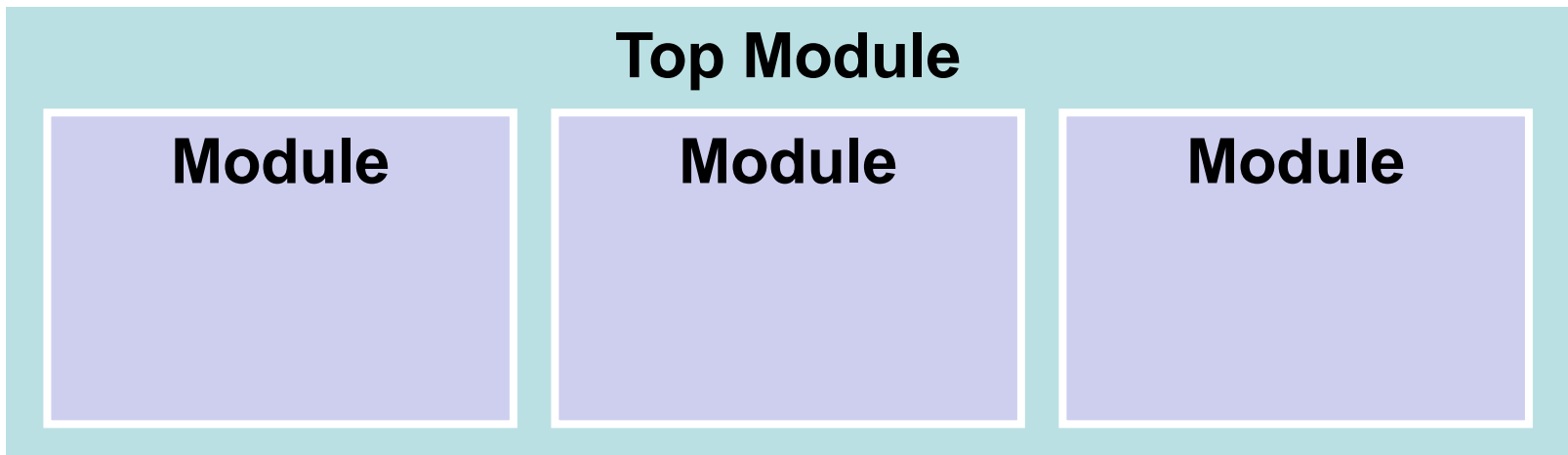- The building block in Verilog is called **module**.
 - There is only one module per file (.v) usually.
 - Modules connect through their **ports** (similarly as in VHDL).
 - A **top level module** invokes instances of other modules.



Connected by relating **I/O** and **internal** wires

Syntax and Popularity



VHDL

Very High Speed Integrated Circuit
Hardware Description Language



Popularity

VHDL is more popular with **European** companies.

Verilog is more popular with **US** companies.

Programming Style (Syntax)

VHDL is similar to **Ada** programming language.

Verilog is similar to **C/Pascal** programming language.

VHDL is **NOT** case-sensitive. **Verilog** is **case-sensitive**.

VHDL is more “**verbose**” than **Verilog**.


Operators



	VHDL	Verilog		VHDL	Verilog
Add	<code>+</code>	<code>+</code>	Bitwise Negation	<code>not</code>	<code>~</code>
Subtract	<code>-</code>	<code>-</code>	Bitwise NAND	<code>nand</code>	<code>~&</code>
Multiplication	<code>*</code>	<code>*</code>	Bitwise NOR	<code>nor</code>	<code>~ </code>
Division	<code>/</code>	<code>/</code>	Bitwise XNOR	<code>xnor</code>	<code>~^</code>
Modulo	<code>mod</code>	<code>%</code>	Greater (or Equal)	<code>>, >=</code>	<code>>, >=</code>
Absolute	<code>abs</code>	N/A	Less (or Equal)	<code><, <=</code>	<code><, <=</code>
Exponentiation	<code>**</code>	<code>**</code>	Logical Equality	<code>=</code>	<code>==</code>
Concatenation	<code>&</code>	<code>{ , }</code>	Logical Inequality	<code>/=</code>	<code>!=</code>
Left Shift	<code>sll</code>	<code><<</code>	Logical AND	<code>and</code>	<code>&&</code>
Right Shift	<code>srl</code>	<code>>></code>	Logical OR	<code>or</code>	<code> </code>
Bitwise AND	<code>and</code>	<code>&</code>	Logical Negation	<code>not</code>	<code>!</code>
Bitwise OR	<code>or</code>	<code> </code>	Case Equality	N/A	<code>===</code>
Bitwise XOR	<code>xor</code>	<code>^</code>	Case Inequality	N/A	<code>!==</code>

- **VHDL vs. Verilog**
 - Background
 - Syntax and Popularity
 - Operators
 - Overall Structure
 - External I/O Declaration
 - Concurrent Statements
 - Sequential Statements
 - Edge Detection
 - Wire vs. Reg
 - Structural Design
 - Design Constructions
 - Case Study: Flip-flop

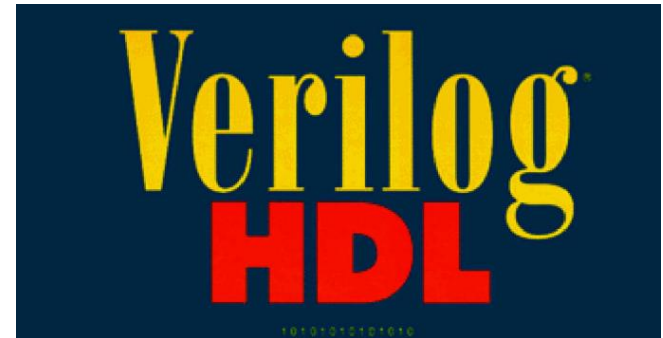VHDL
Very High Speed Integrated Circuit
Hardware Description Language



Overall Structure



VHDL (.vhd)

-- Library Declaration

```
library IEEE;
```

...

-- Entity Declaration

```
entity ex is
```

...

```
end ex
```

-- Architecture Body

```
architecture arch of ex is
```

```
begin
```

...

```
end arch;
```

Verilog (.v)

// One Module

```
module ex ( ... );
```

...

```
endmodule
```

External I/O Declaration



VHDL

-- Entity Declaration

```
entity ex is
```

```
port(a, b: in std_logic;  
c: in std_logic_vector(3  
down to 0),  
y: out std_logic);
```

```
end ex
```

-- Architecture Body

```
architecture arch of mux is
```

```
begin
```

```
...
```

```
end ex;
```

Verilog

// One Module

```
module ex ( a, b, s, y );  
input a, b;  
input[3:0] c;  
output y;
```

or

```
module ex(input a, input b,  
input[3:0] c, output y);
```

```
...
```

```
endmodule
```

Concurrent & Sequential Statements



VHDL

-- Entity Declaration

```
entity ex is
```

```
...
```

```
end ex
```

```
architecture arch of ex is
```

```
Begin
```

```
-- concurrent statements
```

```
process ( sensitivity list )  
begin
```

```
    -- sequential statements
```

```
end process;
```

```
end arch;
```

Verilog

// One Module

```
module ex ( ... );
```

```
-- concurrent statements
```

```
always @( sensitivity list )  
begin
```

```
    -- sequential statements
```

```
end
```

```
endmodule
```

1) Concurrent Statement



VHDL: inside architecture body, outside the process

```
signal a, b: std_logic_vector(7 downto 0); -- array
```

```
signal c, d, e: std_logic;
```

```
a(3 downto 0) <= b(7 downto 4);
```

```
b(7 downto 4) <= "0000";
```

```
c <= d and e; -- bitwise AND
```

LHS <= RHS;

- LHS must be **signal**.
- The LHS will be updated whenever RHS changes.

Verilog: outside the `always@block`

```
wire [7:0] a, b; // array
```

```
wire c, d, e;
```

```
assign a[3:0] = b[7:4];
```

```
assign b[7:4] = 'b0000; // binary
```

```
assign c = d & e; // bitwise AND
```

assign LHS = RHS;

- LHS must be **wire**.
- The LHS will be updated whenever RHS changes.


Class Exercise 10.1

Student ID: _____ Date: _____

Name: _____

- Translate the following VHDL program to Verilog:
 
```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity abc is
    port (a,b,c: in std_logic;
          y: out std_logic);
end abc;
architecture abc_arch of
abc is
signal x : std_logic;
begin
    x <= a nor b;
    y <= x and c;
end abc_arch;
```



2) Sequential Statement



VHDL

```
architecture arch of ex is
begin
process ( sensitivity list )
variable a, b, c;
begin
    -- LHS could be signals
    (suggested) or variables
    -- variable assignment (:=)
    -- signal assignment (<=)
end;
end arch;
```

Verilog

```
module ex (...);
    reg a, b, c;
    always @ ( sensitivity list )
    begin
        // LHS must be reg (not wire)
        // blocking assignment (=)
        // non-blocking assignment
        (<=)
    end
endmodule
```


2) Sequential Statements: Blocking



- **Blocking assignments (=)** in a sequential block (i.e., `always@`) are executed before the execution of the statements that follow it.
 - All blocking assignments are executed in a **sequential** way.
- **Usage:** Use blocking assignments in `always@` blocks to synthesize combinational logic (i.e. **no clock!**).

```
reg r1, r2, r3;
```

```
...
```

```
always @ (a or b)
```


```
begin
```

```
    r1 = a & b;
```

```
    r2 = a | b;
```

```
    r3 = r1 | r2;
```

```
end
```

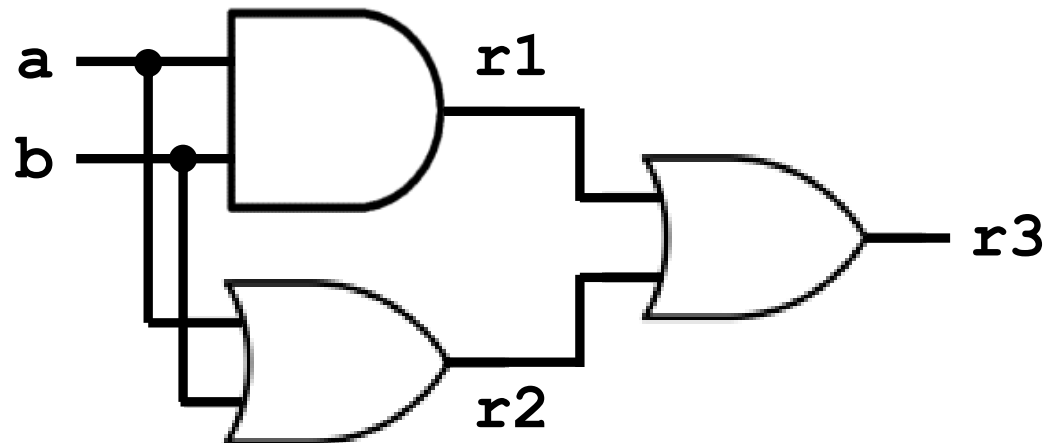


Class Exercise 10.2

Student ID: _____ Date: _____

Name: _____

- Translate the following Verilog program to VHDL:

```
reg r1, r2, r3;  
...  
always @ (a or b)  
begin  
    r1 = a & b;  
    r2 = a | b;  
    r3 = r1 | r2;  
end
```

 

2) Sequential Statements: Non-Blocking

- **Non-blocking assignments** (`<=`) in a sequential block (i.e., `always@`) are executed within the same time step regardless of the order.
 - All non-blocking assignments will take effect at the next clock edge (concurrently, **not sequentially!**).
- **Usage:** Use non-blocking assignments in `always@` blocks to synthesize sequential logic (i.e. **has clock!**).

```
reg r1, r2;
```

```
...
```


```
always @ (posedge clk)
```

```
begin
```


```
→ r1 <= a;
```

```
→ r2 <= r1;
```

```
end
```

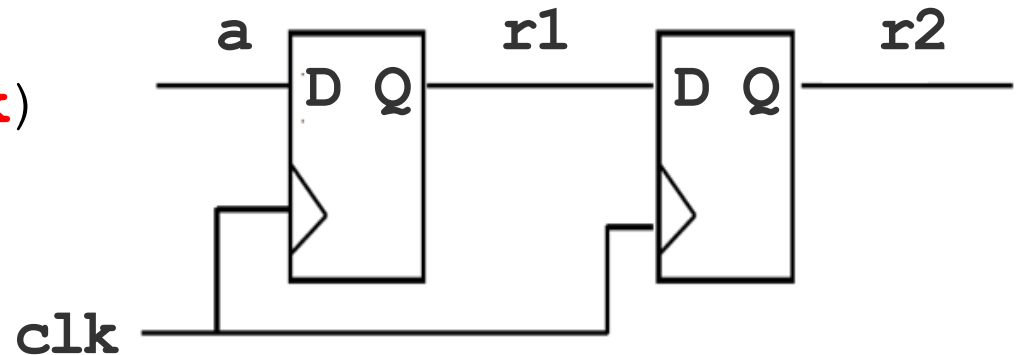

Edge Detection

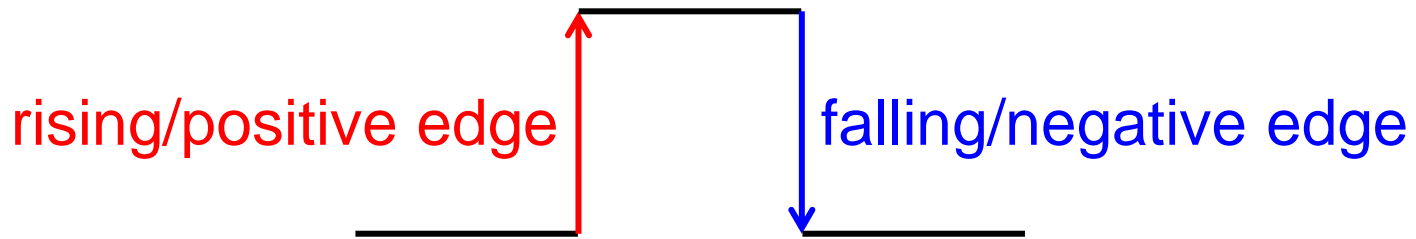

VHDL

```
process (clk)
begin
    ...
    if rising_edge (CLK)
        or
    if falling_edge (CLK)
        ...
end
```

Verilog

```
always @ (posedge clk)
    or
always @ (negedge clk)
begin
    ...
end
```


Class Exercise 10.3

Student ID: _____ Date: _____

Name: _____

- Translate the following Verilog program to VHDL:
 
```
reg r1, r2;  
...  
always @ (posedge clk)  
begin  
    r1 <= a;  
    r2 <= r1;  
end
```



“wire” vs. “reg” in Verilog



- **Wire:** Has no memory
 - It must be **physical wire** in the circuit.
 - It does not hold the value.
 - **Usage:** Cannot use “**wire**” in the left-hand-side of assignments inside **always@** blocks!
- **Reg:** Has memory
 - It could be a **flip-flop** or a **physical wire**.
 - It holds the value until a new value is assigned.
 - **Usage:** Cannot use “**reg**” in the left-hand side of assignments outside **always@** blocks (i.e., concurrent assignment)!

- **VHDL vs. Verilog**
 - Background
 - Syntax and Popularity
 - Operators
 - Overall Structure
 - External I/O Declaration
 - Concurrent Statements
 - Sequential Statements
 - Edge Detection
 - Wire vs. Reg
 - Structural Design
 - Design Constructions
 - Case Study: Flip-flop


VHDL
Very High Speed Integrated Circuit
Hardware Description Language



Structural Design in VHDL (1/2)



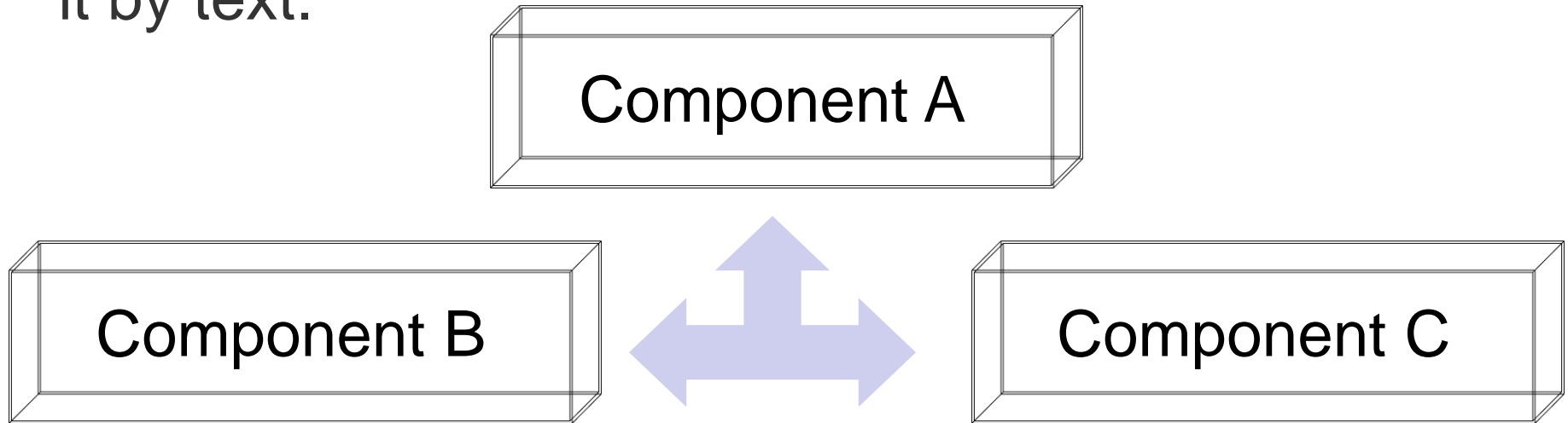- **Structural Design in VHDL:** Like a circuit but describe it by text.



Connected by **port map** in architecture body

- **Design Steps:**
 - Step 1: Create **entities**
 - Step 2: Create **components** from **entities**
 - Step 3: Use “**port map**” to relate the components

Structural Design in VHDL (2/2)



```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity and2 is Step 1
4 port (a,b: in STD_LOGIC;
5       c: out STD_LOGIC );
6 end and2;
7 architecture and2_arch of and2 is
8 begin
9     c <= a and b;
10 end and2_arch;
```

```
11 -----
12 library IEEE;
13 use IEEE.STD_LOGIC_1164.ALL;
14 entity or2 is Step 1
15 port (a,b: in STD_LOGIC;
16       c: out STD_LOGIC );
17 end or2;
18 architecture or2_arch of or2 is
19 begin
20     c <= a or b;
21 end or2_arch;
```


```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 -----
4 entity test is
5 port ( in1: in STD_LOGIC; in2: in STD_LOGIC;
6       in3: in STD_LOGIC;
7       out1: out STD_LOGIC );
8 end test;
9 architecture test_arch of test is
10 component and2 --create component Step 2
11   port (a,b: in std_logic; c: out std_logic);
12 end component ;
13 component or2 --create component
14   port (a,b: in std_logic; c: out std_logic);
15 end component ;
16 signal inter_sig: std_logic;
17 begin Step 3
18     label1: and2 port map (in1, in2, inter_sig);
19     label2: or2 port map (inter_sig, in3, out1);
20 end test_arch;
```



Structural Design in Verilog (1/2)



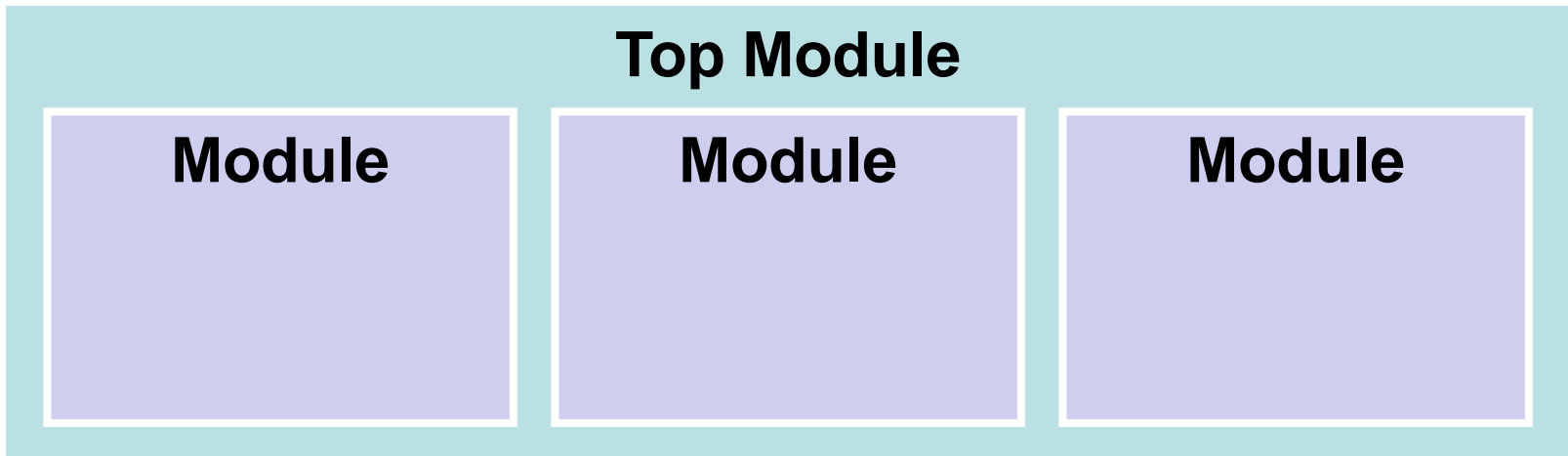- **Structural Design in Verilog:** One top module, several (sub) modules.



Connected by relating **I/O** and **internal** wires

- **Design Steps:**

Step 1: Create (sub) **module(s)** (usually in separate **.v** files)

Step 2: Define a **top-module** to interconnect **module(s)**

Structural Design in Verilog (2/2)



and2.v

```
module and2 ( Step 1
    input a,
    input b,
    output c
);
    assign c = a & b;
endmodule
```

or2.v

```
module or2 ( Step 1
    input a,
    input b,
    output c
);
    assign c = a | b;
endmodule
```

top_module.v

```
module top_module( Step 2
    input in1, input in2, input in3,
    output out1 );
    wire inter_sig;
    and2 and2_ins(
        .a(in1),
        .b(in2),
        .c(inter_sig)
    );
    or2 or2_ins(
        .a(inter_sig),
        .b(in3),
        .c(out1)
    );
endmodule
```




Class Exercise 10.4

Student ID: _____ Date: _____

Name: _____

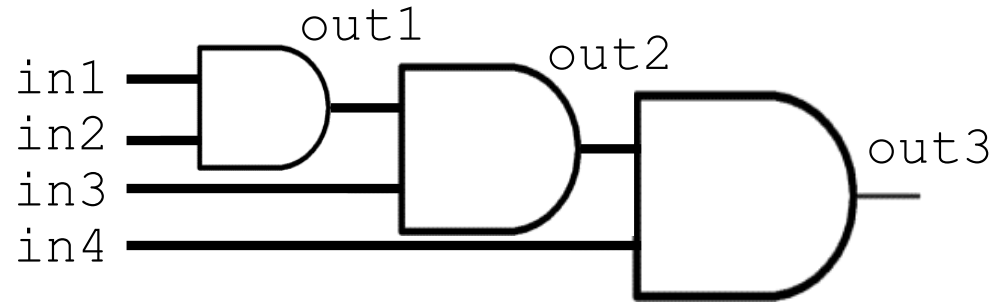- Implement the following circuit in Verilog:



Design Constructions (1/4)



VHDL: when-else (*concurrent, outside process*)

```
architecture arch of ex is
```

```
begin
```

```
    out1 <= '1' when in1 = '1' and in2 = '1' else '0';
```

```
end arch ex_arch;
```

Verilog: assign ? : (*concurrent, outside always@ block*)

```
module ex (...);
```

```
    assign out1 = (in1=='b1 && in2=='b1) ? 'b1 : 'b0;
```

```
    // 'b: binary; 'o: octal; 'd: decimal; 'h: hexadecimal
```

```
endmodule
```

Design Constructions (2/4)



VHDL: **if-then-else**

(*sequential, inside process*)

```
process(in1, in2)
begin
  if in1='1' and in2='1'
  then
    out1 <= '1';
  else
    out1 <= '0';
  end if;
end process;
```

Verilog: **if-else**

(*sequential, inside always@*)

```
always @(in1, in2)
begin
  if (in1=='b1 && in2=='b1)
  begin
    out1 = 'b1;
  end
  else
  begin
    out1 = 'b0;
  end
end
```

Design Constructions (3/4)



VHDL: **case-when**

(*sequential, inside process*)

```
process (b)
```

```
begin
```

```
  case b is
```

```
    when "00"|"11" =>
```

```
      out1 <= '0';
```

```
      out2 <= '1';
```

```
    when others      =>
```

```
      out1 <= '1';
```

```
      out2 <= '0';
```

```
  end case;
```

```
end process;
```

Verilog: **case**

(*sequential, inside always@*)

```
always @ (b)
```

```
begin
```

```
  case (b)
```

```
    'b00 || 'b11:
```

```
      out1 = 'b0;
```

```
      out2 = 'b1;
```

```
  default:
```


```
    out1 = 'b1;
```

```
    out2 = 'b0;
```

```
  endcase
```

```
end
```

Design Constructions (4/4)

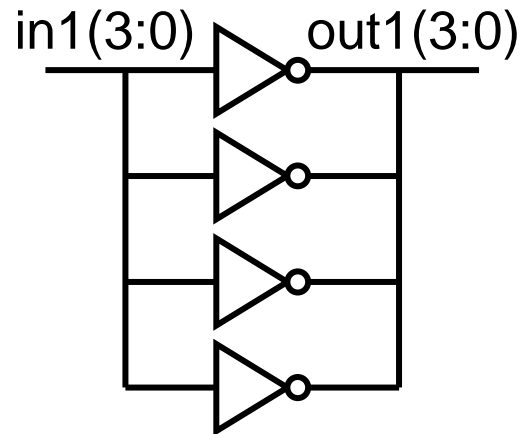

VHDL: for-in-to-loop
(*sequential, inside process*)


```
process (in1)
begin
    for i in 0 to 3 loop
        out1(i) <= not in1(i);
    end loop;
end process;
```

Verilog: for-loop
(*sequential, inside always@*)

```
always @(in1)
begin
    for (idx=0; idx<4; idx+=1)
        begin
            out1[idx] = ~in1[idx];
        end
end
```


- **VHDL vs. Verilog**
 - Background
 - Syntax and Popularity
 - Operators
 - Overall Structure
 - External I/O Declaration
 - Concurrent Statements
 - Sequential Statements
 - Edge Detection
 - Wire vs. Reg
 - Structural Design
 - Design Constructions
 - **Case Study: Flip-flop**

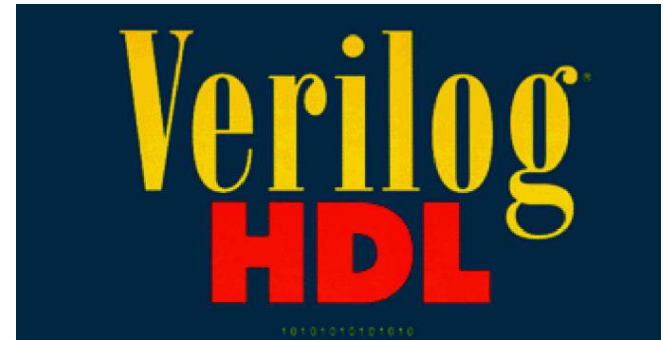VHDL
Very High Speed Integrated Circuit
Hardware Description Language



Posedge Flip-flop with Sync Reset (1/2)

VHDL

```
entity dff is
port (D,CLK,RESET:
      in std_logic;
      Q: out std_logic);
end dff;
architecture dff_arch of
dff is begin
  process(CLK) begin
    if rising_edge(CLK) then
      if (RESET = '1') then
        Q <= '0';
      else
        Q <= D;
      end if;
    end if;
  end process;
end dff_arch;
```

Verilog

```
module dff(
  input D,
  input CLK,
  input RESET,
  output reg Q);
always @(posedge CLK)
begin
  if (RESET) begin
    Q <= 1'b0;
  end
  else begin
    Q <= D;
  end
end
endmodule
```

Posedge Flip-flop with **Sync** Reset (2/2)

Verilog

```
module dff(  
    input D,  
    input CLK,  
    input RESET,  
    output reg Q);  
always @(posedge CLK)  
begin  
  
    if (RESET) begin  
        Q <= 1'b0;  
    end  
    else begin  
        Q <= D;  
    end  
  
end  
endmodule
```

- **Input** must be **wire**.
- **Output** could be either **wire** or **reg**.
 - The default option is **wire**.
 - But you can specify an **output** as **wire** or **reg** depending on how you will assign it a value.

Posedge Flip-flop with Async Reset (1/2)

VHDL

```
entity dff is
port (D,CLK,RESET:
      in std_logic;
      Q: out std_logic);
end dff;
architecture dff_arch of
dff is begin
  process(CLK,RESET) begin
    if (RESET = '1')
    then
      Q <= '0';
    elsif rising_edge(CLK)
    then
      Q <= D;
    end if;
  end process;
end dff_arch;
```

Verilog

```
module dff(
  input D,
  input CLK,
  input RESET,
  output reg Q);
  always @(posedge CLK or
         posedge RESET)
  begin
    if (RESET) begin
      Q <= 1'b0;
    end
    else begin
      Q <= D;
    end
  end
end
endmodule
```


Posedge Flip-flop with Async Reset (2/2)

Verilog

```
module dff(  
    input D,  
    input CLK,  
    input RESET,  
    output reg Q);  
always @(posedge CLK or  
    posedge RESET)  
begin  
    if (RESET) begin  
        Q <= 1'b0;  
    end  
    else begin  
        Q <= D;  
    end  
end  
endmodule
```

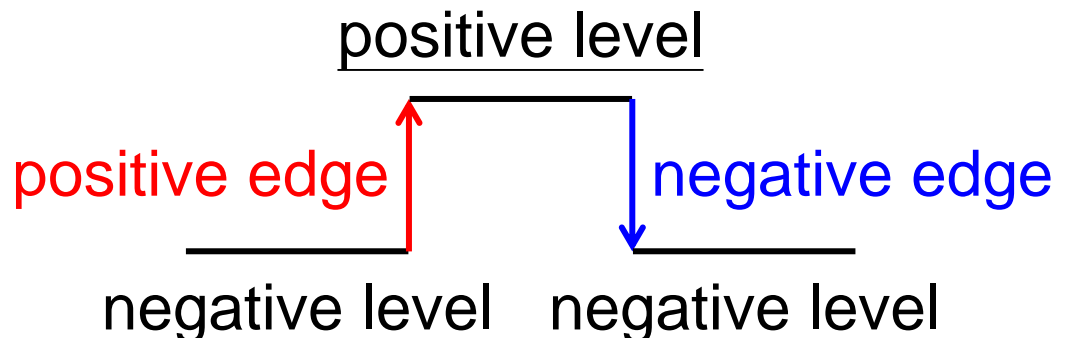Question: What if we do not specify “posedge” for the RESET signal?

! [Synth 8-434] mixed level sensitive and edge triggered event controls are **not supported** for synthesis!



- **VHDL vs. Verilog**
 - Background
 - Syntax and Popularity
 - Operators
 - Overall Structure
 - External I/O Declaration
 - Concurrent Statements
 - Sequential Statements
 - Edge Detection
 - Wire vs. Reg
 - Structural Design
 - Design Constructions
 - Case Study: Flip-flop

VHDL
Very High Speed Integrated Circuit
Hardware Description Language

