



香港中文大學

The Chinese University of Hong Kong

*CENG3430 Rapid Prototyping of Digital Systems*

**Lecture 04:**

# **Combinational Circuit and Sequential Circuit**

**Ming-Chang YANG**

[mcyang@cse.cuhk.edu.hk](mailto:mcyang@cse.cuhk.edu.hk)



# Recall: Concurrent vs. Sequential



- **Concurrent Statement**

- ① Statements inside the architecture body can be executed **concurrently**, except statements enclosed by a **process**.
- ② Every statement will be executed once whenever any signal in the statement changes.

- **Sequential Statement**

- ① Statements within a process are executed **sequentially**, and the result is obtained when the process is complete.
- ② **process (sensitivity list)**: When one or more signals in the sensitivity list change state, the process executes once.
- ③ A **process** can be treated as one **concurrent statement** in the architecture body.

# Recall: Concurrent vs. Sequential



## Concurrent Statement

### when-else

```
b <= "1000" when a = "00" else  
"0100" when a = "01" else  
"0010" when a = "10" else  
"0001" when a = "11";
```

### with-select-when

```
with a select  
b <= "1000" when "00",  
"0100" when "01",  
"0010" when "10",  
"0001" when "11";
```

## Sequential Statement

### if-then-else

```
if a = "00" then b <= "1000"  
elsif a = "01" then b <= "0100"  
elsif a = "10" then b <= "0010"  
else b <= "0001"  
end if;
```

### case-when

```
case a is  
when "00" => b <= "1000";  
when "01" => b <= "0100";  
when "10" => b <= "0010";  
when others => b <= "0001";  
end case;
```




- Combinational Circuit and Sequential Circuit
- Building Blocks of a Processor
  - Combinational Circuit: No Memory
    - Decoder
    - Multiplexer
    - Bi-directional Bus
  - Sequential Circuit: Has Memory
    - Latch
    - Flip-flop with Asynchronous Reset
    - Flip-flop with Synchronous Reset
 
# Combinational Circuit



- **Combinational Circuit: no memory**
  - Outputs are a function of the *present* inputs only.
    - As soon as inputs change, the values of previous outputs are **lost**.
    - It has **no** internal state (i.e., has **no memory**).
    - Common Examples: Full/Half Adders (*Lab01*), Encoders/Decoders (*Lab02*), Multiplexers (*Lab03*), Bi-directional Bus (*Lec04*), etc.
  - **Rule:** You can build a combinational circuit using either concurrent or sequential (i.e., `process`) statements.



# Combinational Logic as a Process



- Consider a simple combinational logic:

`c <= a and b;`

- This logic can be also modeled as a **process**:

- All signals **referenced** in process must be in **sensitivity list**.

```
entity And_Good is
```

```
  port (a, b: in std_logic; c: out std_logic);
```

```
end And_Good;
```

```
architecture Synthesis_Good of And_Good is
```

```
begin
```

```
  process (a, b) -- sensitive to signals a and/or b
```

```
  begin
```

```
    c <= a and b; -- c updated
```


```
  end process;
```

```
end;
```
 
# Sequential Circuit




- **Sequential Circuit: has memory**
  - Outputs are a function of the present inputs and the previous outputs (i.e., the **internal state**).
    - It changes outputs based on inputs; but the outputs also depend upon previous outputs (i.e., the **internal state**) (i.e., has **memory**).
    - Example: Latch (*Lec04*), Flip-Flops (*Lec04*), Counters (*Lec05*), etc.
  - **Rule:** You **must** build a sequential circuit with **only** sequential (i.e., `process`) statements.


 
# Combinational vs. Sequential Circuit



- **Combinational Circuit: no memory**
  - ① Outputs are a function of the *present* inputs only.
  - ② **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
  - ① Outputs are a function of the *present* inputs and the *previous* outputs (i.e., the **internal state**).
  - ② **Rule: Must use sequential** (i.e., `process`) statements.








- Combinational Circuit and Sequential Circuit
- Building Blocks of a Processor
  - Combinational Circuit: No Memory
    - Decoder
    - Multiplexer
    - Bi-directional Bus
  - Sequential Circuit: Has Memory
    - Latch
    - Flip-flop with Asynchronous Reset
    - Flip-flop with Synchronous Reset


# Typical Processor Organization

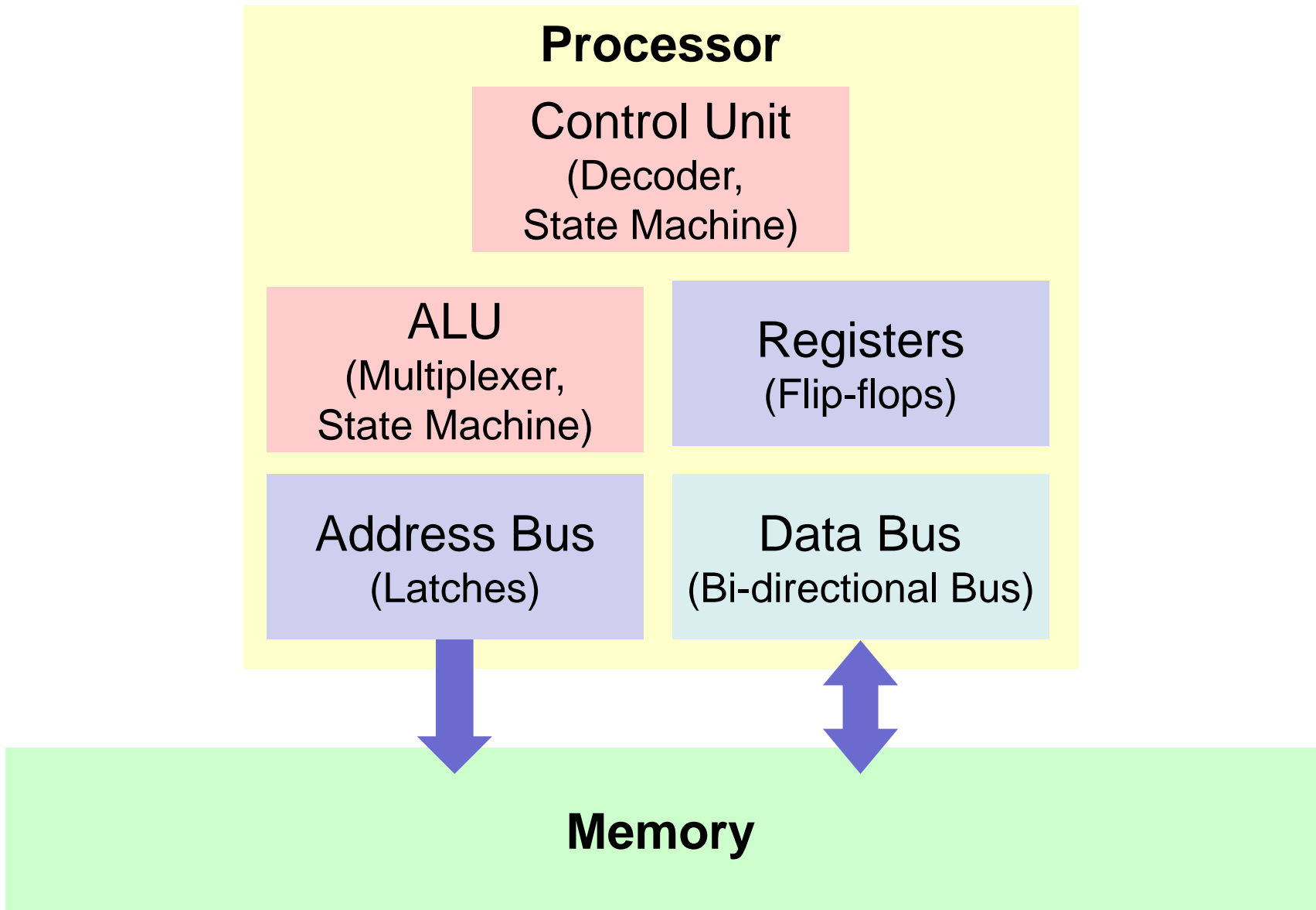



- Combinational Circuit and Sequential Circuit
- Building Blocks of a Processor
  - Combinational Circuit: No Memory
    - Decoder
    - Multiplexer
    - Bi-directional Bus
  - Sequential Circuit: Has Memory
    - Latch
    - Flip-flop with Asynchronous Reset
    - Flip-flop with Synchronous Reset

# Building Blocks: Decoder

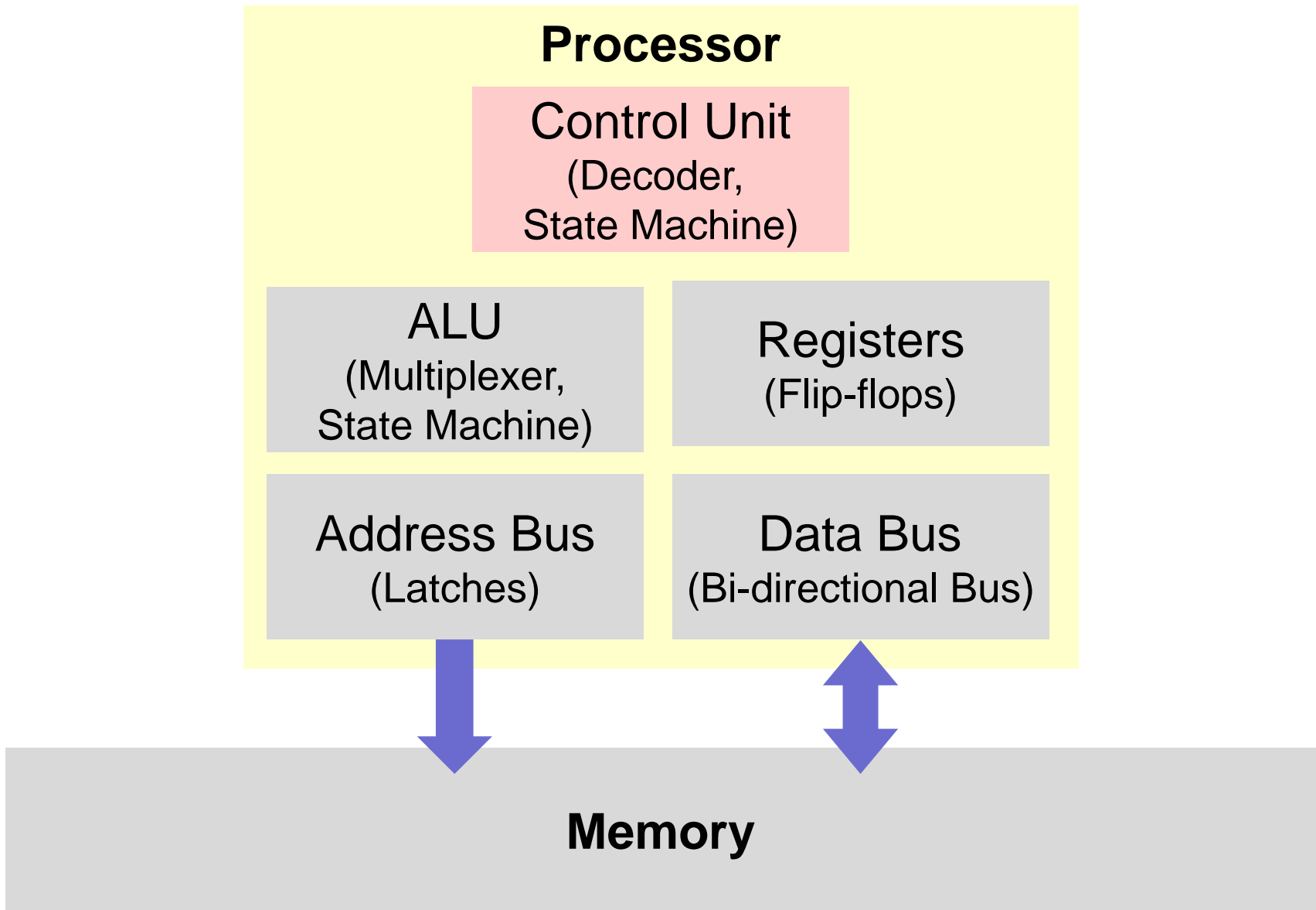

# Combinational Circuit: Decoder (1/2)



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity decoder_ex is
port (in0,in1: in std_logic;
      out00,out01,out10,out11: out std_logic);
end decoder_ex;
architecture decoder_ex_arch of decoder_ex is
begin
  process (in0, in1)
  begin
```

```
    if in0 = '0' and in1 = '0' then
      out00 <= '1';
    else
      out00 <= '0';
    end if;
```

**out00**

```
    if in0 = '0' and in1 = '1' then
      out01 <= '1';
    else
      out01 <= '0';
    end if;
```

**out01**

in	in	out	out	out	out
0	1	00	01	10	11
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

# Combinational Circuit: Decoder (2/2)




...

```
if in0 = '1' and in1 = '0' then
  out10 <= '1';
else
  out10 <= '0';
end if;
if in0 = '1' and in1 = '1' then
  out11 <= '1';
else
  out11 <= '0';
end if;
```

```
end process;
end decoder_ex_arch;
```

in	in	out	out	out	out
0	1	00	01	10	11
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

<https://www.allaboutcircuits.com/textbook/digital/chpt-9/decoder/>

# Class Exercise 4.1

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

- Implement the **Encoder** based on the given table:

```
port (

```

```
...
architecture encoder_ex_arch of encoder_ex is
begin
  process (
    )
  begin

```

```
end process;
end encoder_ex_arch;
```


in	in	in	in	out	out
00	01	10	11	0	1
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1



- Combinational Circuit and Sequential Circuit
- Building Blocks of a Processor
  - Combinational Circuit: No Memory
    - Decoder
    - Multiplexer
    - Bi-directional Bus
  - Sequential Circuit: Has Memory
    - Latch
    - Flip-flop with Asynchronous Reset
    - Flip-flop with Synchronous Reset




# Building Blocks: Multiplexer

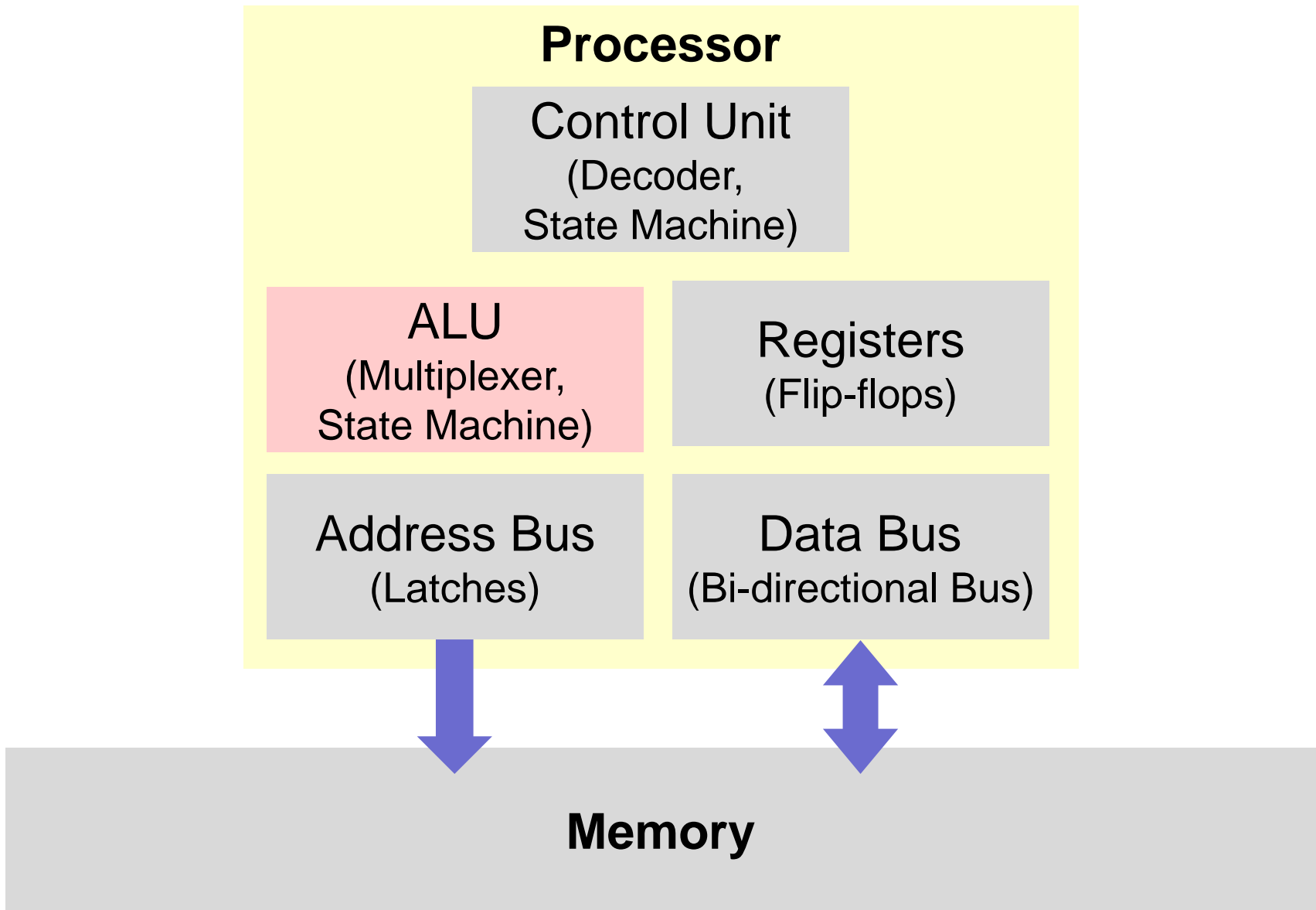

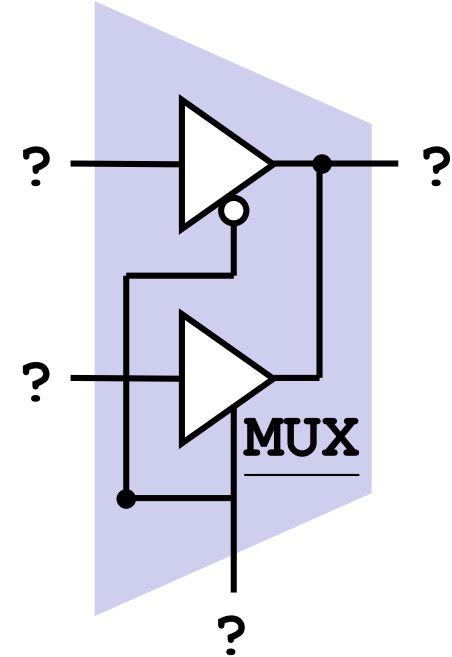
# Combinational Circuit: Multiplexer



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity mux_ex is
port (in1,in2,sel: in std_logic;
      out1: out std_logic);
end mux_ex;
architecture mux_ex_arch of mux_ex is
begin
  process (in1, in2, sel)
  begin
    if sel = '0' then
      out1 <= in1; -- select in1
    else
      out1 <= in2; -- select in2
    end if;
  end process;
end mux_ex_arch;
```



# Recall: Tri-state Buffer

 

in1	enable	out1
0	0	Z
1	0	Z
0	1	0
1	1	1


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity tri_ex is
port (in1, enable: in std_logic;
      out1: out std_logic);
end tri_ex;
architecture tri_ex_arch of tri_ex is
begin
    out1 <= in1 when enable = '1' else 'Z';
end tri_ex_arch;
```

# Class Exercise 4.2

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_  
Name: \_\_\_\_\_

- Specify the I/O signals in the circuit:

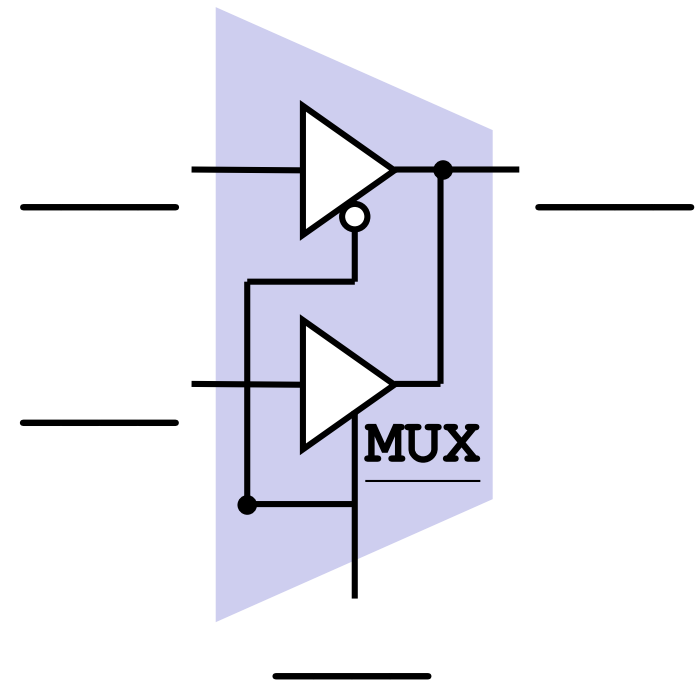
```
entity mux_ex is
port (in1,in2,sel: in std_logic;
      out1: out std_logic);
end mux_ex;
architecture mux_ex_arch of mux_ex is
begin
  process (in1, in2, sel)
  begin
    if sel = '0' then
      out1 <= in1;
    else
      out1 <= in2;
    end if;
  end process;
end mux_ex_arch;
```






- Combinational Circuit and Sequential Circuit
- Building Blocks of a Processor
  - Combinational Circuit: No Memory
    - Decoder
    - Multiplexer
    - Bi-directional Bus
  - Sequential Circuit: Has Memory
    - Latch
    - Flip-flop with Asynchronous Reset
    - Flip-flop with Synchronous Reset

# Building Blocks: Bi-directional Bus

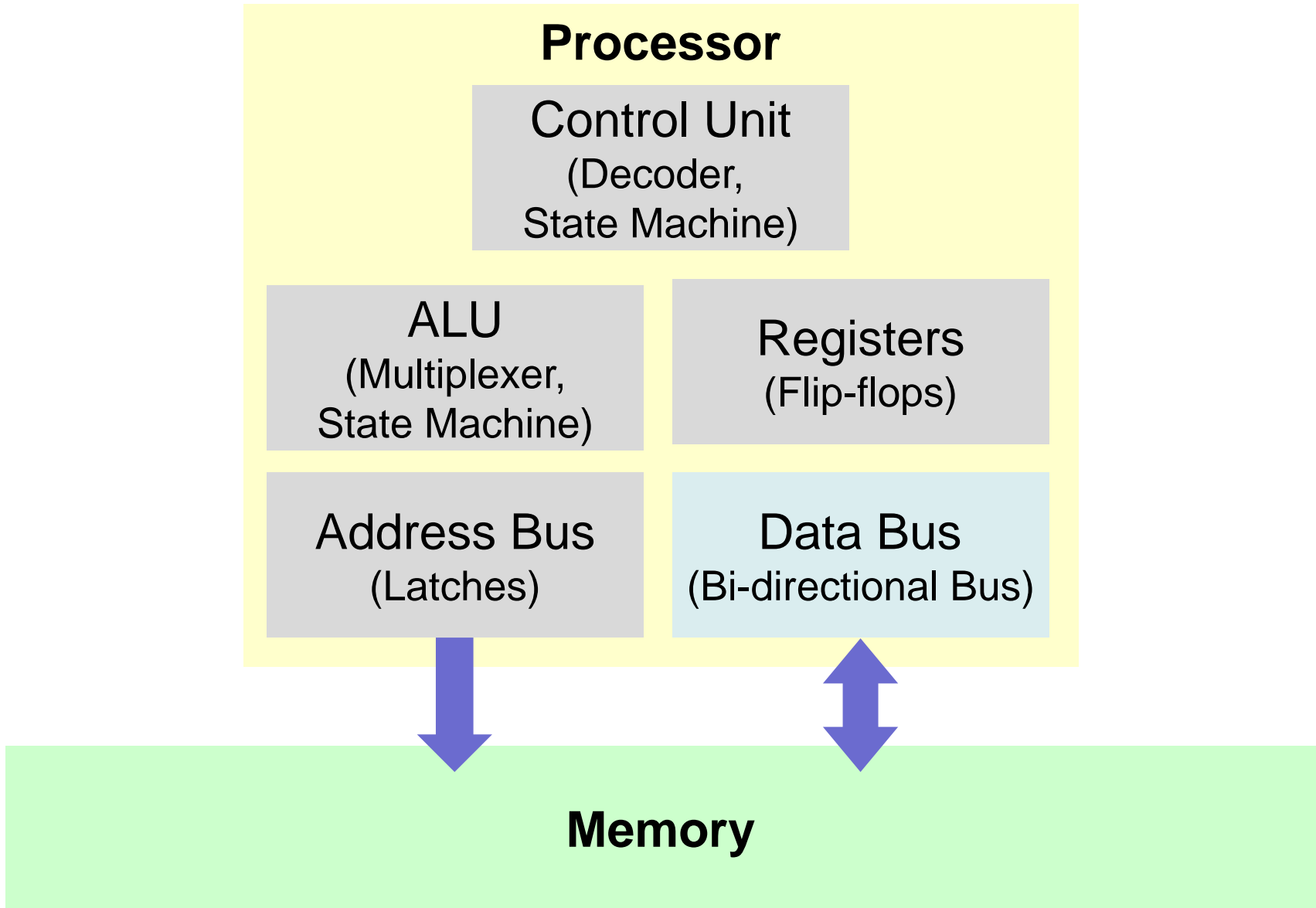
 
# Combinational Circuit: Bi-directional Bus

```
entity inout_ex is
port (io1, io2: inout std_logic;
      ctrl: in std_logic);
end inout_ex;
architecture inout_ex_arch of inout_ex is
begin
  process (io1, io2, ctrl) is begin
    if (ctrl = '1') then io1 <= io2;
    else io1 <= 'Z';
    end if;
  end process;
  process (io1, io2, ctrl) is begin
    if (ctrl = '0') then io2 <= io1;
    else io2 <= 'Z';
    end if;
  end process;
end inout_ex_arch;
```



io1 follows "io2.in"



io2 follows "io1.in"

# Class Exercise 4.3

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_  
Name: \_\_\_\_\_

```
entity inout_ex is
port (io1, io2: inout std_logic;
      ctrl: in std_logic);
end inout_ex;
architecture inout_ex_arch of inout_ex is
begin
  process (io1, io2, ctrl) is begin
    if (ctrl = '1') then io1 <= io2;
    else io1 <= 'Z';
    end if;
  end process;
  process (io1, io2, ctrl) is begin
    if (ctrl = '0') then io2 <= io1;
    else io2 <= 'Z';
    end if;
  end process;
end inout_ex_arch;
```

- Specify I/O signals:

  





- Combinational Circuit and Sequential Circuit
- Building Blocks of a Processor
  - Combinational Circuit: No Memory
    - Decoder
    - Multiplexer
    - Bi-directional Bus
  - Sequential Circuit: Has Memory
    - Latch
    - Flip-flop with Asynchronous Reset
    - Flip-flop with Synchronous Reset

# Latches and Flip Flops




- Latches and Flip-flops (FF) are the basic elements used to store information.
  - Each latch and flip flop can keep one bit of data.
- The main difference between latch and flip-flop:
  - A latch continuously checks input and changes the output whenever there is a change in input.
    - A latch has **no clock signal**.
  - A flip-flop continuously checks input and changes the output only at times determined by the clock signal.
    - A flip flop has a **clock signal**.



- Combinational Circuit and Sequential Circuit
- Building Blocks of a Processor
  - Combinational Circuit: No Memory
    - Decoder
    - Multiplexer
    - Bi-directional Bus
  - Sequential Circuit: Has Memory
    - Latch
    - Flip-flop with Asynchronous Reset
    - Flip-flop with Synchronous Reset


# Building Blocks: Latch

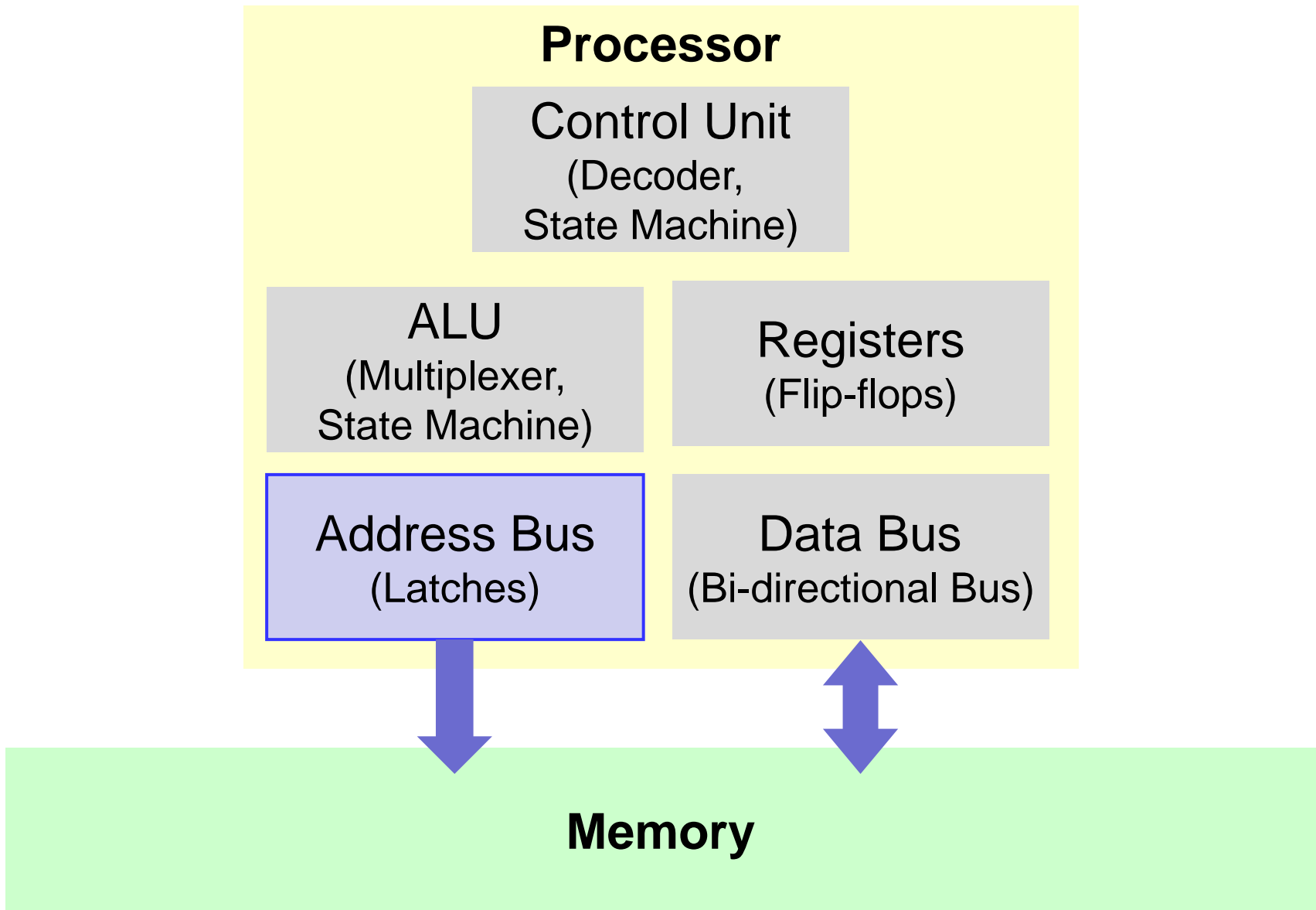
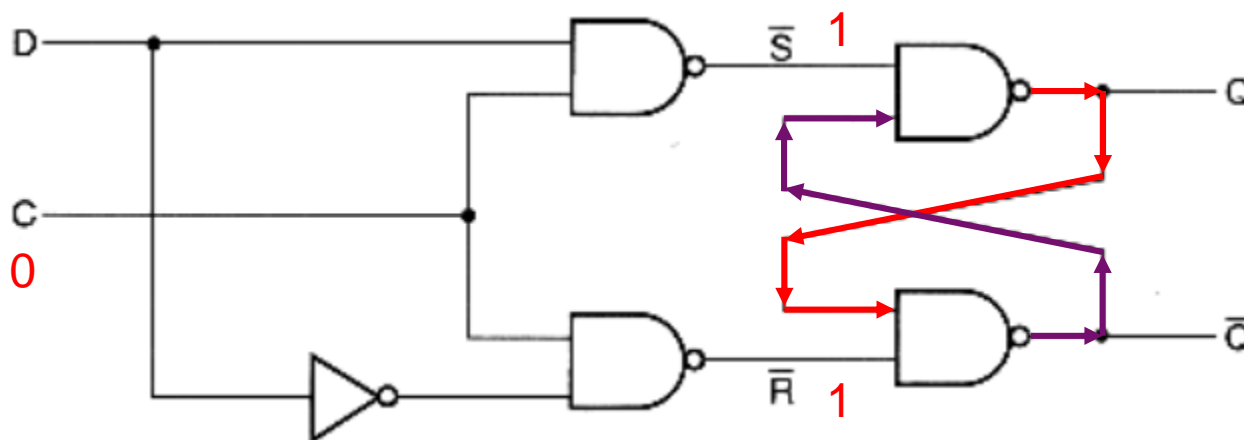
# Sequential Circuit: Latch (1/2)



- Latches are **asynchronous** (no CLOCK signal).
  - It changes output **only in response to input**.
- Case Study: D Latch**
  - When enable line C is high, the output Q follows input D.
  - That is why D latch is also called as **transparent latch**.
    - When enable line C is asserted, the latch is said to be transparent.
  - When C falls, the last state of D input is trapped and held.
  - That is why the latch **has memory!**



Data need to be held.


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

<https://www.edgefx.in/digital-electronics-latches-and-flip-flops/>
 
# Sequential Circuit: Latch (2/2)



```
1 library IEEE;--(ok vivado 2014.4)
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity latch_ex is
4 port (C, D: in std_logic;
5       Q: out std_logic);
6 end latch_ex;
7 architecture latch_ex_arch of latch_ex is
8 begin
9     process(C, D) -- sensitivity list
10    begin
11        if (C = '1') then
12            Q <= D;
13        end if;
14        -- no change (memory)
15    end process;
16 end latch_ex_arch;
```



C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

# Class Exercise 4.4


Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

- Given a D latch, draw Q in the following figure:



Q

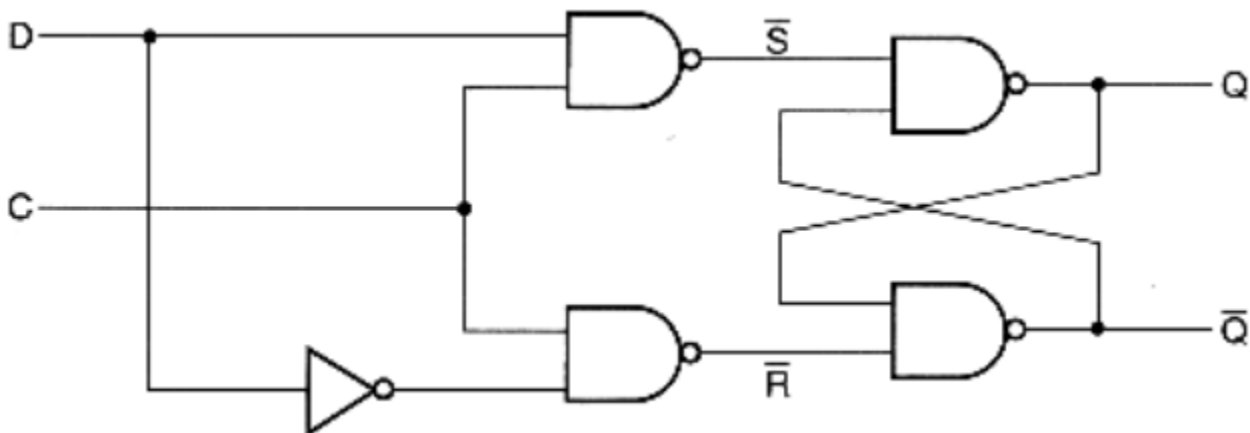


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state



- Combinational Circuit and Sequential Circuit
- Building Blocks of a Processor
  - Combinational Circuit: No Memory
    - Decoder
    - Multiplexer
    - Bi-directional Bus
  - Sequential Circuit: Has Memory
    - Latch
    - Flip-flop with Asynchronous Reset
    - Flip-flop with Synchronous Reset




# Building Blocks: Flip-flops

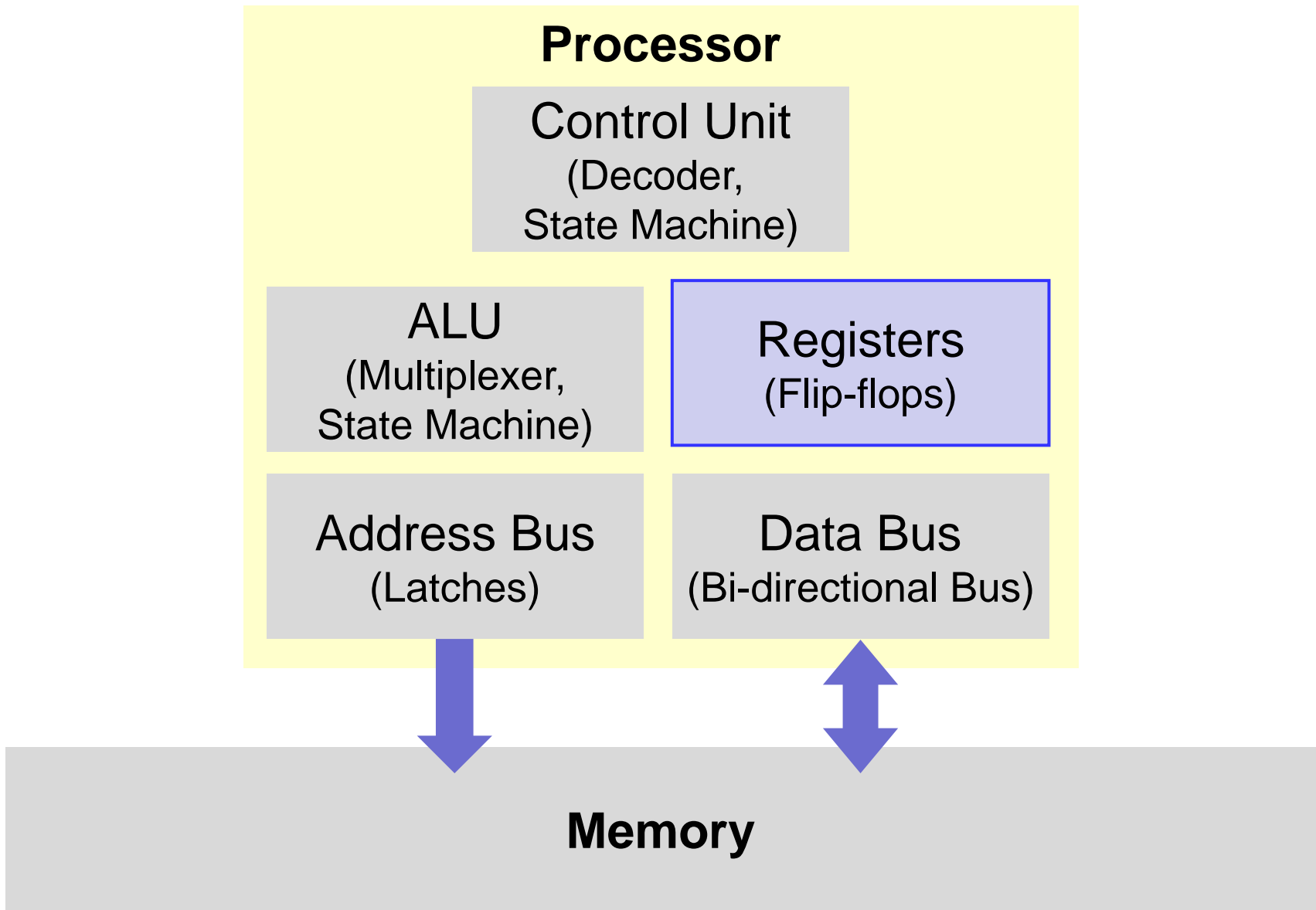
 
# Sequential Circuit: Flip-flop




- A **Latch** is a non-clock-controlled memory device.
  - ① It has **no** CLOCK signal.
  - ② It changes output only in response to data input. (i.e., the value is set **asynchronously**).
- A **Flip-flop (FF)** is a **clock-controlled** memory device.
  - ① Different from a Latch, it **has** a CLOCK signal as input.
  - ② It stores the input value (i.e., low or high) and **outputs** the stored value **only in response to** the CLOCK signal.
    - **Positive-Edge-Triggered**: At every **low to high** of CLOCK.
    - **Negative-Edge-Triggered**: At every **high to low** of CLOCK.
  - ③ The value can be **reset** **asynchronously** or **synchronously**.
    - **Async. Reset**: Reset the value **anytime**.
    - **Sync. Reset**: Reset the value on **positive** or **negative** clock edges.


 
# Positive-Edge-Triggered FF with Async. Reset

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity dff_async is
4 port (D, CLK, RESET: in std_logic;
5       Q: out std_logic);
6 end dff_async;
7 architecture dff_async_arch of dff_async is
8 begin
9     process (CLK, RESET) -- sensitivity list
10    begin
11        if (RESET = '1') then
12            Q <= '0'; -- Reset Q immediately
13        elsif CLK = '1' and CLK'event then
14            Q <= D; -- Q follows input D
15        end if;
16        -- no change (so has memory)
17    end process;
18 end dff_async_arch;
```



Positive-  
edge-  
triggered

# Recall: Attributes (Lec01)



- Another important signal attribute is the '**event**'.
  - This attribute yields a Boolean value of TRUE if an event has just occurred on the signal.
  - It is used primarily to determine if a **clock** has transitioned.
- Example (*more in Lec04*):

```
...  
port (my_in, clock: in std_logic;  
      my_out: out std_logic);  
...  
if clock = '1' and clock'event then  
    my_out <= my_in;
```

# Class Exercise 4.5

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_  
Name: \_\_\_\_\_

- Consider the following VHDL implementation of a positive-edge-triggered FF with asynchronous reset:

```
...
9   process (CLK, RESET) -- sensitivity list
10  begin
11      if (RESET = '1') then
12          Q <= '0'; -- Reset Q
13      elsif CLK = '1' and CLK'event then
14          Q <= D; -- Q follows input D
15      end if;
16      -- no change (so has memory)
17  end process;
```

...

- When will line 9 be executed?

Answer: \_\_\_\_\_

- Which signal is more “powerful”? CLK or RESET?



Answer: \_\_\_\_\_

# Class Exercise 4.6

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_


Name: \_\_\_\_\_

  - Given a “50%” Positive-edge-triggered D Flip-flop with **async.** reset, draw the output Q.
  - “50%” means it changes state when clock is 50% between high and low.


 
# Positive-Edge-Triggered FF with Sync. Reset

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity dff_sync is
4 port (D,CLK,RESET: in std_logic;
5       Q: out std_logic);
6 end dff_sync;
```



```
7 architecture dff_sync_arch of dff_sync is begin
8 process (CLK) ← RESET can be removed (why?)
```

```
9   begin
10     if CLK = '1' and CLK'event then
11       if (RESET = '1') then
12         Q <= '0'; -- Reset Q
13       else
14         Q <= D; -- Q follows input D
15       end if;
16     end if;
```

Positive-  
edge-  
triggered



```
    -- no change (so has memory)
```

```
17   end process;
18 end dff_syn_arch;
```
  
# Class Exercise 4.7

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_  
Name: \_\_\_\_\_

- Given a “50%” Positive-edge-triggered D Flip-flop with **sync.** reset, draw the output Q.
  - “50%” means it changes state when clock is 50% between high and low.





# Async. Reset vs. Sync. Reset (1/2)



- The order of the statements inside the process determines **asynchronous reset** or **synchronous reset**.


- **Asynchronous Reset** (check **RESET** first!)

```
11     if (RESET = '1') then
12         Q <= '0'; -- Reset Q
13     elsif CLK = '1' and CLK'event then
14         Q <= D; -- Q follows input D
15     end if;
```

- **Synchronous Reset** (check **CLK** first!)

```
10     if CLK = '1' and CLK'event then
11         if (RESET = '1') then
12             Q <= '0'; -- Reset Q
13         else
14             Q <= D; -- Q follows input D
15         end if;
16     end if;
```

# Aysnc. Reset vs. Sync. Reset (2/2)

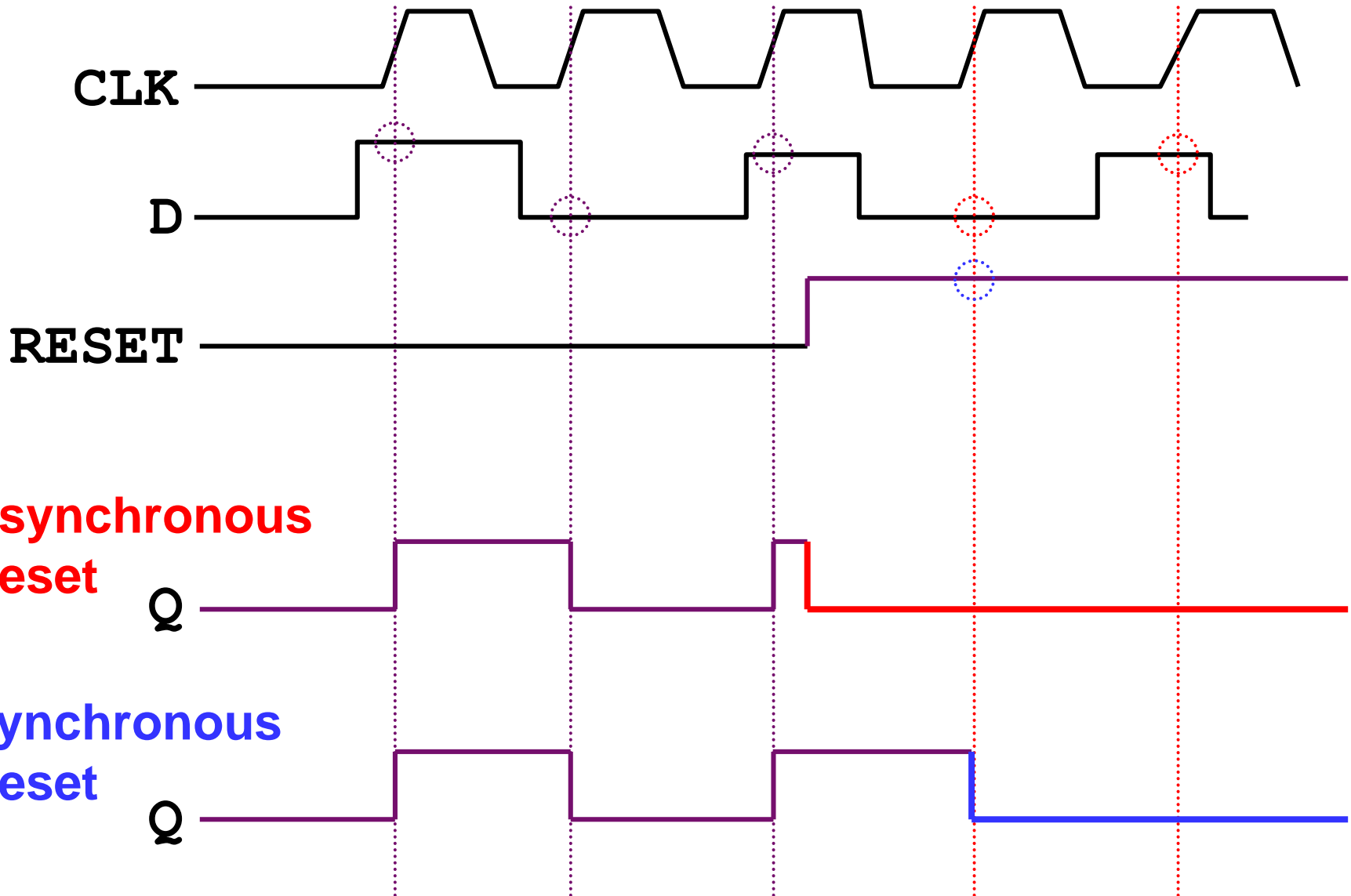



- Combinational Circuit and Sequential Circuit
- Building Blocks of a Processor
  - Combinational Circuit: **No Memory**
    - Decoder
    - Multiplexer
    - Bi-directional Bus
  - Sequential Circuit: **Has Memory**
    - Latch
    - Flip-flop with Asynchronous Reset
    - Flip-flop with Synchronous Reset

# What's the next? Finite State Machine!

