



香港中文大學

The Chinese University of Hong Kong

*CENG3430 Rapid Prototyping of Digital Systems*

**Lecture 12:**


**VHDL versus Verilog**

**Ming-Chang YANG**

[mcyang@cse.cuhk.edu.hk](mailto:mcyang@cse.cuhk.edu.hk)

- **VHDL vs. Verilog**
  - Background
  - Syntax and Popularity
  - Operators
  - Overall Structure
  - External I/O Declaration
  - Concurrent Statements
  - Sequential Statements
    - Edge Detection
  - Wire vs. Reg
  - Structural Design
  - Design Constructions
  - Case Study: Flip-flop

 
**VHDL**  
Very High Speed Integrated Circuit  
Hardware Description Language


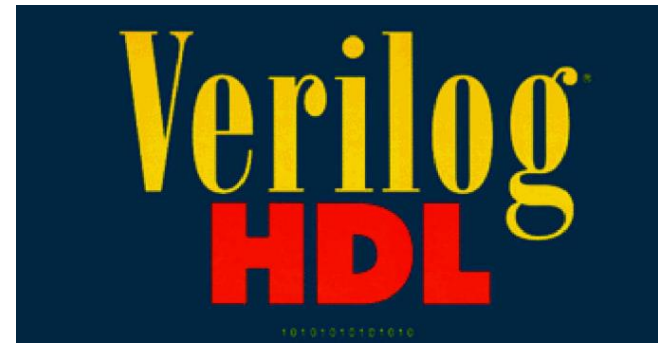
# What are VHDL and Verilog?



**VHDL**  
Very High Speed Integrated Circuit  
Hardware Description Language



- They are both **hardware description languages** for modeling hardware.
- They are each a **notation** to describe the **behavioral** and **structural** aspects of an electronic digital circuit.

# VHDL: Background




- **V**HSIC **H**ardware **D**escription **L**anguage
  - VHSIC: Very High Speed Integrated Circuit.
- Developed by **Department of Defense** (1981)
  - In 1986 rights were given to **IEEE**.
  - Became a standard and published in 1987.
  - Revised standard we know now published in 1993 (VHDL 1076-1993) regulated by VHDL international (VI).

**VHDL**  
Very High Speed Integrated Circuit  
Hardware Description Language
 
# VHDL: Design Concept



- VHDL uses **top-down approach** to partition a design into small building blocks (i.e., **components**).
  - **Entity**: Describe interface signals and basic building blocks.
  - **Architecture**: Describe behavior, each entity can have multiple Architectures.



Connected by **port map** in architecture body

# Verilog: Background




- Developed by **Gateway Design Automation** (1980)
  - Later acquired by **Cadence Design** (1989) who made it public in 1990
  - Became a standardized in 1995 by **IEEE** (Std 1364) regulated by Open Verilog International (OVI)


 
# Verilog: Design Concept



- The building block in Verilog is called **module**.
  - There is only one module per file (.v) usually.
  - Modules connect through their **ports** (similarly as in VHDL).
  - A **top level module** invokes instances of other modules.




Connected by relating **I/O** and **internal** wires

# Syntax and Popularity


 
# VHDL

Very High Speed Integrated Circuit  
Hardware Description Language



## Popularity

**VHDL** is more popular with **European** companies.

**Verilog** is more popular with **US** companies.

## Programming Style (Syntax)

**VHDL** is similar to **Ada** programming language.

**Verilog** is similar to **C/Pascal** programming language.

**VHDL** is **NOT** case-sensitive.

**Verilog** is **case-sensitive**.

**VHDL** is more “**verbose**” than **Verilog**.




# Operators



	VHDL	Verilog		VHDL	Verilog
Add	<code>+</code>	<code>+</code>	Bitwise Negation	<code>not</code>	<code>~</code>
Subtract	<code>-</code>	<code>-</code>	Bitwise NAND	<code>nand</code>	<code>~&amp;</code>
Multiplication	<code>*</code>	<code>*</code>	Bitwise NOR	<code>nor</code>	<code>~ </code>
Division	<code>/</code>	<code>/</code>	Bitwise XNOR	<code>xnor</code>	<code>~^</code>
Modulo	<code>mod</code>	<code>%</code>	Greater (or Equal)	<code>&gt;, &gt;=</code>	<code>&gt;, &gt;=</code>
Absolute	<code>abs</code>	N/A	Less (or Equal)	<code>&lt;, &lt;=</code>	<code>&lt;, &lt;=</code>
Exponentiation	<code>**</code>	<code>**</code>	Logical Equality	<code>=</code>	<code>==</code>
Concatenation	<code>&amp;</code>	<code>{ , }</code>	Logical Inequality	<code>/=</code>	<code>!=</code>
Left Shift	<code>sll</code>	<code>&lt;&lt;</code>	Logical AND	<code>and</code>	<code>&amp;&amp;</code>
Right Shift	<code>srl</code>	<code>&gt;&gt;</code>	Logical OR	<code>or</code>	<code>  </code>
Bitwise AND	<code>and</code>	<code>&amp;</code>	Logical Negation	<code>not</code>	<code>!</code>
Bitwise OR	<code>or</code>	<code> </code>	Case Equality	N/A	<code>===</code>
Bitwise XOR	<code>xor</code>	<code>^</code>	Case Inequality	N/A	<code>!==</code>

- **VHDL vs. Verilog**
  - Background
  - Syntax and Popularity
  - Operators
  - Overall Structure
  - External I/O Declaration
  - Concurrent Statements
  - Sequential Statements
    - Edge Detection
  - Wire vs. Reg
  - Structural Design
  - Design Constructions
  - Case Study: Flip-flop

 **VHDL**  
Very High Speed Integrated Circuit  
Hardware Description Language



# Overall Structure



## VHDL (.vhd)

*-- Library Declaration*

```
library IEEE;
```

...

*-- Entity Declaration*

```
entity mux is
```

...

```
end mux
```

*-- Architecture Body*

```
architecture arch of mux is
```

```
begin
```

...

```
end arch;
```

## Verilog (.v)

*// One Module*

```
module mux ( ... );
```

...

```
endmodule
```

# External I/O Declaration



## VHDL

*-- Library Declaration*

...

*-- Entity Declaration*

entity mux is

```
port (a,b,s: in std_logic;  
      y: out std_logic);
```

end mux

*-- Architecture Body*

architecture arch of mux is

begin

...

end arch;

## Verilog

*// One Module*

```
module mux (a, b, s, y);  
input a,b,s;  
output y;
```

...

endmodule

# Concurrent & Sequential Statements



## VHDL

### *-- Entity Declaration*

```
entity mux is
port(a,b,s: in std_logic;
      y: out std_logic);
end mux
```

```
architecture arch of mux is
begin
```

```
-- concurrent statements
```

```
process (...) begin
  -- sequential statements
end process;
```

```
end arch;
```

## Verilog

### *// One Module*

```
module mux (a, b, s, y);
input a,b,s;
output y;
```

```
-- concurrent statements
```

```
always @(...)
begin
  -- sequential statements
end process;
```

```
endmodule
```

# 1) Concurrent Statement



**VHDL:** *inside architecture body, outside the process*

```
signal a, b: std_logic_vector(7 downto 0); -- array
```

```
signal c, d, e: std_logic;
```

```
a(3 downto 0) <= b(7 downto 4);
```

```
b(7 downto 4) <= "0000";
```

```
c <= d and e; -- bitwise AND
```

**LHS <= RHS;**

- LHS must be **signal**.
- The LHS will be updated whenever RHS changes.

**Verilog:** *outside the always@ block*

```
wire [7:0] a, b; // array
```

```
wire c, d, e;
```

```
assign a[3:0] = c[7:4];
```

```
assign b[7:4] = 'b0000; // binary
```

```
assign c = d & e; // bitwise AND
```

**assign LHS = RHS;**

- LHS must be **wire**.
- The LHS will be updated whenever RHS changes.


# Class Exercise 12.1

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

- Translate the following VHDL program to Verilog:
 
```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity abc is
    port (a,b,c: in std_logic;
          y: out std_logic);
end abc;
architecture abc_arch of
abc is
signal x : std_logic;
begin
    x <= a nor b;
    y <= x and c;
end abc_arch;
```



# 2) Sequential Statement



## VHDL

```
architecture arch of ex is
begin
process ( sensitivity list )
variable a, b, c;
begin
-- LHS could be signals
-- (suggested) or variables
-- signal assignment (<=)
-- for both combinational logic
-- and sequential logic
-- variable assignment (:=)
end;
end arch;
```

## Verilog

```
module ex (...);
reg a, b, c;
always @ ( conditions )
begin
// LHS must be reg (not wire)
// blocking assignment (=)
// for combinational logic
// non-blocking assignment
// (<=) for sequential logic
end
endmodule
```



## 2) Sequential Statements: Blocking



- **Blocking assignments (=)** in a sequential block (i.e., `always@`) are executed before the execution of the statements that follow it.
  - All blocking assignments are executed in a **sequentially** way.
- **Usage:** Use blocking assignments in `always@` blocks to synthesize combinational logic (i.e. **no clock!**).

```
reg r1, r2, r3;
```

```
...
```

```
always @ (a or b)
```


```
begin
```

```
    r1 = a & b;
```

```
    r2 = a | b;
```

```
    r3 = r1 | r2;
```

```
end
```

 


# Class Exercise 12.2

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

- Translate the following Verilog program to VHDL:

```
reg r1, r2, r3;  
...  
always @ (a or b)  
begin  
    r1 = a & b;  
    r2 = a | b;  
    r3 = r1 | r2;  
end
```

 

## 2) Sequential Statements: Non-Blocking

- **Non-blocking assignments** (`<=`) in a sequential block (i.e., `always@`) are executed within the same time step regardless of the order.
  - All non-blocking assignments will take effect at the next clock edge (concurrently, **not sequentially!**).
- **Usage:** Use non-blocking assignments in `always@` blocks to synthesize sequential logic (i.e. **has clock!**).

```
reg r1, r2;
```

```
...
```


```
always @ (posedge clk)
```

```
begin
```


```
→ r1 <= a;
```

```
→ r2 <= r1;
```

```
end
```

 

# Edge Detection

 

## VHDL

```
process (clk)
begin
...
if rising_edge (CLK)
    or
if falling_edge (CLK)
...
end
```

**sensitivity list**

**conditions**

## Verilog

```
always @ (posedge clk)
    or
always @ (negedge clk)
begin
...
end
```

**conditions**


# Class Exercise 12.3

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

- Translate the following Verilog program to VHDL:
 
```
reg r1, r2;  
...  
always @ (posedge clk)  
begin  
    r1 <= a;  
    r2 <= r1;  
end
```



# “wire” vs. “reg” in Verilog



- **Wire:** Has no memory
  - It must be **physical wire** in the circuit.
  - It does not hold the value.
  - **Usage:** Cannot use “**wire**” in the left-hand-side of assignments inside **always@** blocks!
- **Reg:** Has memory
  - It could be a **flip-flop** or a **physical wire**.
  - It holds the value until a new value is assigned.
  - **Usage:** Cannot use “**reg**” in the left-hand side of assignments outside **always@** blocks (i.e., concurrent assignment)!

- **VHDL vs. Verilog**
  - Background
  - Syntax and Popularity
  - Operators
  - Overall Structure
  - External I/O Declaration
  - Concurrent Statements
  - Sequential Statements
    - Edge Detection
  - Wire vs. Reg
  - Structural Design
  - Design Constructions
  - Case Study: Flip-flop


**VHDL**  
Very High Speed Integrated Circuit  
Hardware Description Language


 
# Structural Design in VHDL (1/2)



- **Structural Design in VHDL:** Like a circuit but describe it by text.



Connected by **port map** in architecture body

- **Design Steps:**
  - Step 1: Create **entities**
  - Step 2: Create **components** from **entities**
  - Step 3: Use “**port map**” to relate the components



# Structural Design in VHDL (2/2)



```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity and2 is Step 1
4 port (a,b: in STD_LOGIC;
5       c: out STD_LOGIC );
6 end and2;
7 architecture and2_arch of and2 is
8 begin
9     c <= a and b;
10 end and2_arch;
```

```
11 -----
12 library IEEE;
13 use IEEE.STD_LOGIC_1164.ALL;
14 entity or2 is Step 1
15 port (a,b: in STD_LOGIC;
16       c: out STD_LOGIC );
17 end or2;
18 architecture or2_arch of or2 is
19 begin
20     c <= a or b;
21 end or2_arch;
```


```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 -----
4 entity test is
5 port ( in1: in STD_LOGIC; in2: in STD_LOGIC;
6       in3: in STD_LOGIC;
7       out1: out STD_LOGIC );
8 end test;
9 architecture test_arch of test is
10 component and2 --create component Step 2
11   port (a,b: in std_logic; c: out std_logic);
12 end component ;
13 component or2 --create component
14   port (a,b: in std_logic; c: out std_logic);
15 end component ;
16 signal inter_sig: std_logic;
17 begin Step 3
18     label1: and2 port map (in1, in2, inter_sig);
19     label2: or2 port map (inter_sig, in3, out1);
20 end test_arch;
```


 
# Structural Design in Verilog (1/2)



- **Structural Design in Verilog:** One top module, several (sub) modules.



Connected by relating **I/O** and **internal** wires

- **Design Steps:**
  - Step 1:** Create (sub) **module(s)** (usually in separate **.v** files)
  - Step 2:** Define a **top-module** to interconnect **module(s)**

# Structural Design in Verilog (2/2)



## and2.v

```
module and2 ( Step 1
    input a,
    input b,
    output c
);
    assign c = a & b;
endmodule
```

## or2.v

```
module or2 ( Step 1
    input a,
    input b,
    output c
);
    assign c = a | b;
endmodule
```

## top\_module.v

```
module top_module( Step 2
    input in1, input in2, input in3,
    output out1 );
    wire inter_sig;
    and2 and2_ins(
        .a(in1),
        .b(in2),
        .c(inter_sig)
    );
    or2 or2_ins(
        .a(inter_sig),
        .b(in3),
        .c(out1)
    );
endmodule
```




# Class Exercise 12.4

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

 - Implement the following circuit in Verilog:



# Design Constructions (1/4)



**VHDL: when-else** (*concurrent, outside process*)

```
architecture arch of ex is
```

```
begin
```

```
    out1 <= '1' when in1 = '1' and in2 = '1' else '0';
```

```
end arch ex_arch;
```

**Verilog: assign ?** : (*concurrent, outside always@ block*)

```
module ex (...);
```

```
    assign out1 = (in1=='b1 && in2=='b1) ? 'b1 : 'b0;
```

```
    // 'b: binary; 'o: octal; 'd: decimal; 'h: hexadecimal
```

```
endmodule
```

# Design Constructions (2/4)



## VHDL: **if-then-else**

(*sequential, inside process*)

```
process (in1, in2)
begin
  if in1='1' and in2='1'
  then
    out1 <= '1';
  else
    out1 <= '0';
  end if;
end process;
```

## Verilog: **if-else**

(*sequential, inside always@*)

```
always @(in1, in2)
begin
  if (in1=='b1 && in2=='b1)
  begin
    out1 = 'b1;
  end
  else
  begin
    out1 = 'b0;
  end
end
```

# Design Constructions (3/4)



## VHDL: **case-when**

(*sequential, inside process*)

```
process (b)
```

```
begin
```

```
  case b is
```

```
    when "00"|"11" =>
```

```
      out1 <= '0';
```

```
      out2 <= '1';
```

```
    when others      =>
```

```
      out1 <= '1';
```

```
      out2 <= '0';
```

```
  end case;
```

```
end process;
```

## Verilog: **case**

(*sequential, inside always@*)

```
always @ (b)
```

```
begin
```

```
  case (b)
```

```
    'b00 || 'b11:
```

```
      out1 = 'b0;
```

```
      out2 = 'b1;
```

```
  default:
```


```
    out1 = 'b1;
```

```
    out2 = 'b0;
```

```
  endcase
```

```
end
```

# Design Constructions (4/4)

 

**VHDL: for-in-to-loop**  
(*sequential, inside process*)

```
process (in1)
begin
    for i in 0 to 3 loop
        out1(i) <= not in1(i);
    end loop;
end process;
```


**Verilog: for-loop**  
(*sequential, inside always@*)

```
always @(in1)
begin
    for (idx=0; idx<4; idx+=1)
        begin
            out1[idx] = ~in1[idx];
        end
end
```



- **VHDL vs. Verilog**
  - Background
  - Syntax and Popularity
  - Operators
  - Overall Structure
  - External I/O Declaration
  - Concurrent Statements
  - Sequential Statements
    - Edge Detection
  - Wire vs. Reg
  - Structural Design
  - Design Constructions
  - **Case Study: Flip-flop**

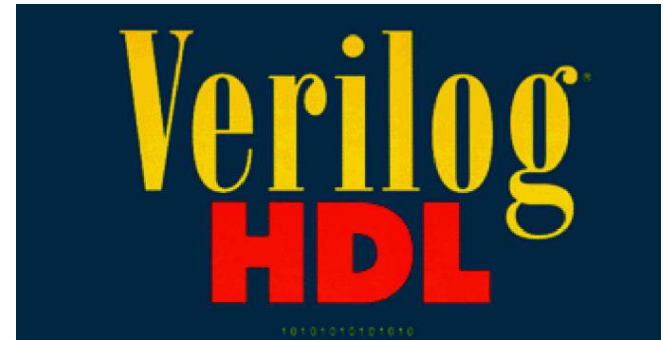**VHDL**  
Very High Speed Integrated Circuit  
Hardware Description Language



# Posedge Flip-flop with Sync Reset (1/2)

## VHDL

```
entity dff is
port (D,CLK,RESET:
      in std_logic;
      Q: out std_logic);
end dff;
architecture dff_arch of
dff is begin
  process(CLK) begin
    if rising_edge(CLK) then
      if (RESET = '1') then
        Q <= '0';
      else
        Q <= D;
      end if;
    end if;
  end process;
end dff_arch;
```

## Verilog

```
module dff(
  input D,
  input CLK,
  input RESET,
  output reg Q);
always @(posedge CLK)
begin
  if (RESET) begin
    Q <= 1'b0;
  end
  else begin
    Q <= D;
  end
end
endmodule
```

# Posedge Flip-flop with **Sync** Reset (2/2)

## Verilog

```
module dff(  
    input D,  
    input CLK,  
    input RESET,  
    output reg Q);  
always @(posedge CLK)  
begin  
  
    if (RESET) begin  
        Q <= 1'b0;  
    end  
    else begin  
        Q <= D;  
    end  
  
end  
endmodule
```

- **Input** must be **wire**.
- **Output** could be either **wire** or **reg**.
  - The default option is **wire**.
  - But you can specify an **output** as **wire** or **reg** depending on how you will assign it a value.

# Posedge Flip-flop with Async Reset (1/2)

## VHDL

```
entity dff is
port (D,CLK,RESET:
      in std_logic;
      Q: out std_logic);
end dff;
architecture dff_arch of
dff is begin
  process(CLK,RESET) begin
    if (RESET = '1')
    then
      Q <= '0';
    elsif rising_edge(CLK)
    then
      Q <= D;
    end if;
  end process;
end dff_arch;
```

## Verilog

```
module dff(
  input D,
  input CLK,
  input RESET,
  output reg Q);
  always @(posedge CLK or
         posedge RESET)
  begin
    if (RESET) begin
      Q <= 1'b0;
    end
    else begin
      Q <= D;
    end
  end
end
endmodule
```


# Posedge Flip-flop with Async Reset (2/2)

## Verilog

```
module dff(  
    input D,  
    input CLK,  
    input RESET,  
    output reg Q);  
always @(posedge CLK or  
    posedge RESET)  
begin  
    if (RESET) begin  
        Q <= 1'b0;  
    end  
    else begin  
        Q <= D;  
    end  
end  
end  
endmodule
```

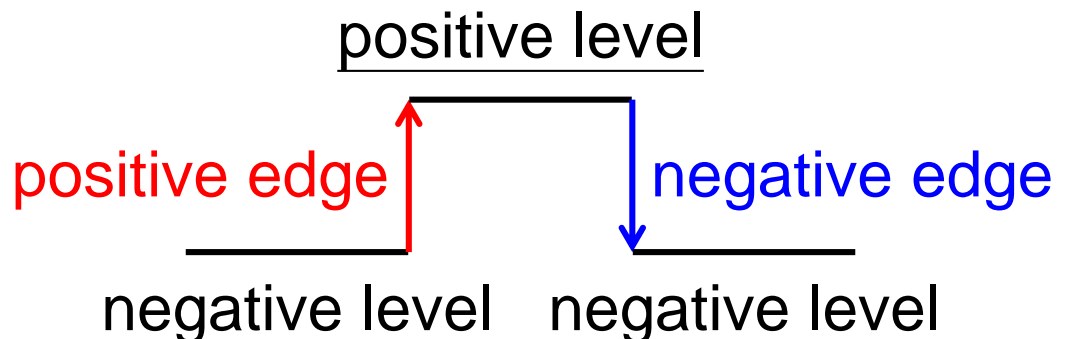**Question:** What if we do not specify “posedge” for the RESET signal?

**!** [Synth 8-434] mixed level sensitive and edge triggered event controls are **not supported** for synthesis!



- **VHDL vs. Verilog**
  - Background
  - Syntax and Popularity
  - Operators
  - Overall Structure
  - External I/O Declaration
  - Concurrent Statements
  - Sequential Statements
    - Edge Detection
  - Wire vs. Reg
  - Structural Design
  - Design Constructions
  - Case Study: Flip-flop

**VHDL**  
Very High Speed Integrated Circuit  
Hardware Description Language

