

CENG4480

Lab3 : Active Filters

Tutor: CHEN Tinghuan and GENG Hao

Outline

- 5 experiments
- Common mistakes
- Hint

5 experiments

- Low pass filter; Two-pole low pass filter; High pass filter; Band stop filter; Non-inverting Schmitt filter.
- Complicated circuits, complex procedures:
 - containing many components per experiment.
 - also need to measure V_{in} and V_{out} under many frequencies.
- We also got into trouble on pre-lab. Completing these 5 labs in 2 hours is like an impossible-mission.
- Take easy and do your best!

Common mistakes

- Power supply.
- The settings of waveform generator.
 - e.g. Amplitude, Offset, Waveform type
- Wrong connectivity.

Hint

- Cursors / Meas.

You will get familiar with these two tools in this lab. Remember to use them to measure voltage.

- Intersection

