

B3. Memory—1 Summary

Bei Yu



Reference:

- **Chapter 11 Memories**
- **CMOS VLSI Design—A Circuits and Systems Perspective**
- **by H.E.Weste and D.M.Harris**

How to change the value stored?

- Replace inverter with NAND gate
- RS Latch
- If S or R=1, NAND gate works as **inverter**


A	B	A nand B
0	0	1
0	1	1
1	0	1
1	1	0

  

EX. RS Latch Summary


- **Question:** What's the Q value based on different R, S input.
 - ♦ R=S=1: latch holds current value
 - ♦ S=0, R=1: set value to 1
 - ♦ S=1, R=0: set value to 0
 - ♦ R=S=0: not determined, not allowed

A	B	A nand B
0	0	1
0	1	1
1	0	1
1	1	0

 


Gated D-Latch

 - Two inputs: **D** (data) & **WE** (write enable)
- When $WE=1$, $S=NOT(D)$, $R=D$;
- When $WE=0$, $S=R=1$



EX. Gated D-Latch

 

- **Question 1:** will S & R be zero at the same time?

No. D and NOT(D) make sure S and R are never zero at the same time

- **Question 2:** out values when

- ♦ WE=1: $S=NOT(D)$, $R=D$. $out=D$


- ♦ WE=0: $S=R=1$, out holds current value

EX: 6T SRAM Read

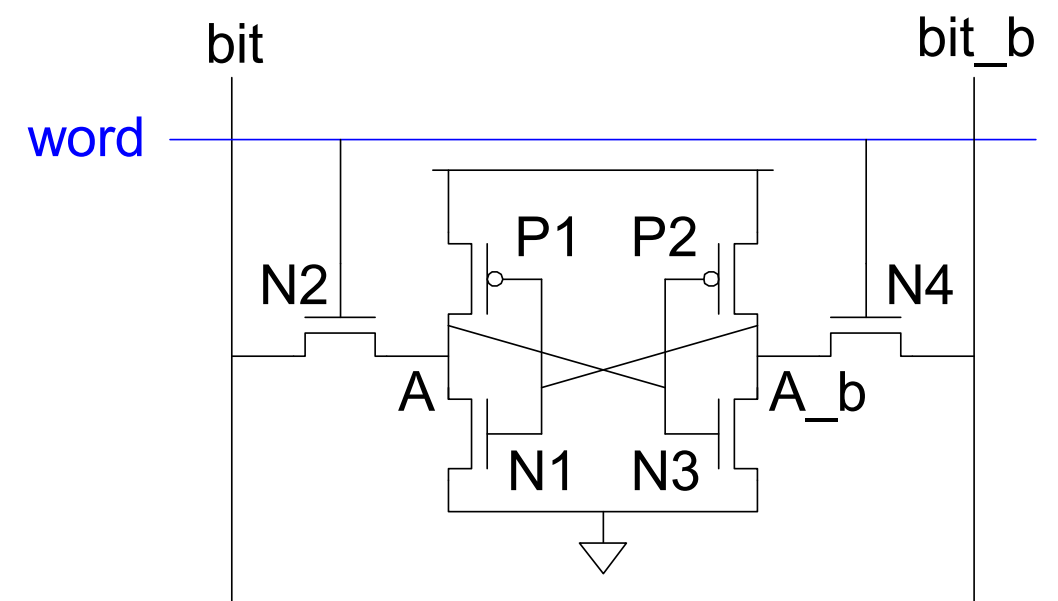- **Question 1:** $A = 0$, $A_b = 1$, discuss the behavior:
 1. bit & bit_b are pre-charged to high, then float
 2. word is set to high
 - 3.1 bit_b= A_b =1, thus right side remains the same
 - 3.2 bit line is pulled down through N2 and N1
- **Question 2:** At least how many bit lines to finish read?

One line.


For example, only bit is enough for reading.




EX: 6T SRAM Write

- **Question 1:** $A = 0$, $A_b = 1$, discuss the behavior:
 1. $bit = 1$ & $bit_b = 0$;
 2. word is set to high
 - 3 $A=0 \Rightarrow P2$ is open $\Rightarrow P2 \ll N4$
 $\Rightarrow A_b$ would be pulled down by bit_b (0)
- **Question 2:** At least how many bit lines to finish write?


We need two.

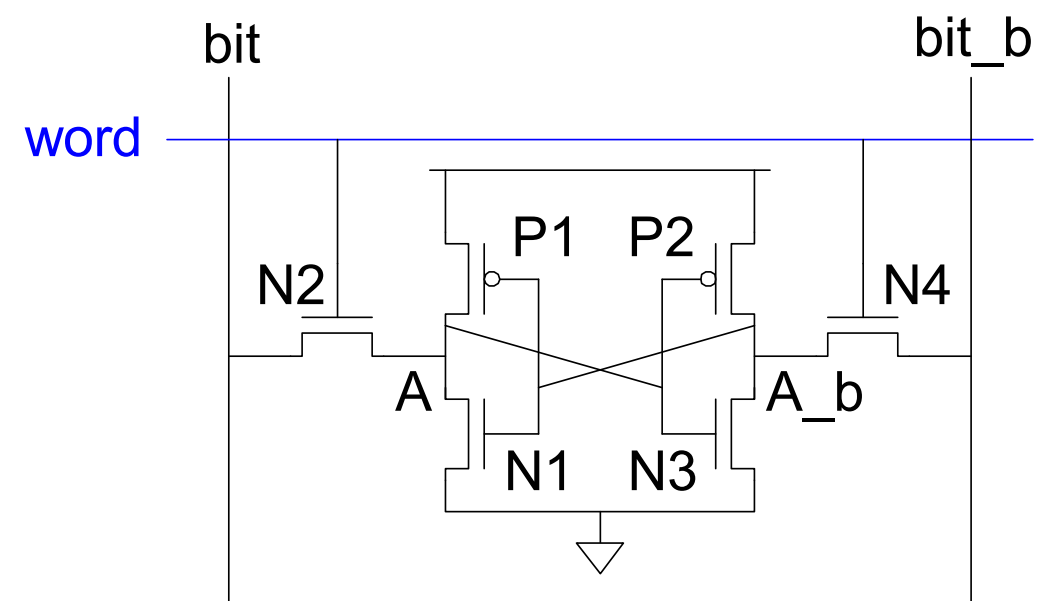


1T1R DRAM Cell

 


(a)

 


(b)

 


(c)

 


(d)

 

(e)

 

(f)

 

(g)

- Need sense amp helping reading

EX. 1T DRAM Cell

- **Question:** $V_{DD}=4V$, $C_S=100pF$, $C_{BL}=1000pF$. What's the voltage swing value?

- **Note:**
$$\Delta V = \frac{V_{DD}}{2} \cdot \frac{C_S}{C_S + C_{BL}}$$

$$\Delta V = 2 * 100 / (1000+100) = 0.045V = 45mV$$

SRAM v.s. DRAM

Static (SRAM)


- Data stored as long as supply is applied
- Large (6 transistors/cell)
- Fast
- Compatible with current CMOS manufacturing

Dynamic (DRAM)

- Periodic refresh required
- Small (1-3 transistors/cell)
- Slower
- Require additional process for trench capacitance


Array Architecture

 - 2^n words of 2^m bits each
- How to design if $n \gg m$?
- fold by 2^k into fewer rows of more columns




EX. Decoder using NOR gates

 - **Question:** AND gates \Rightarrow NOR gate structure





A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

- **Answer:**

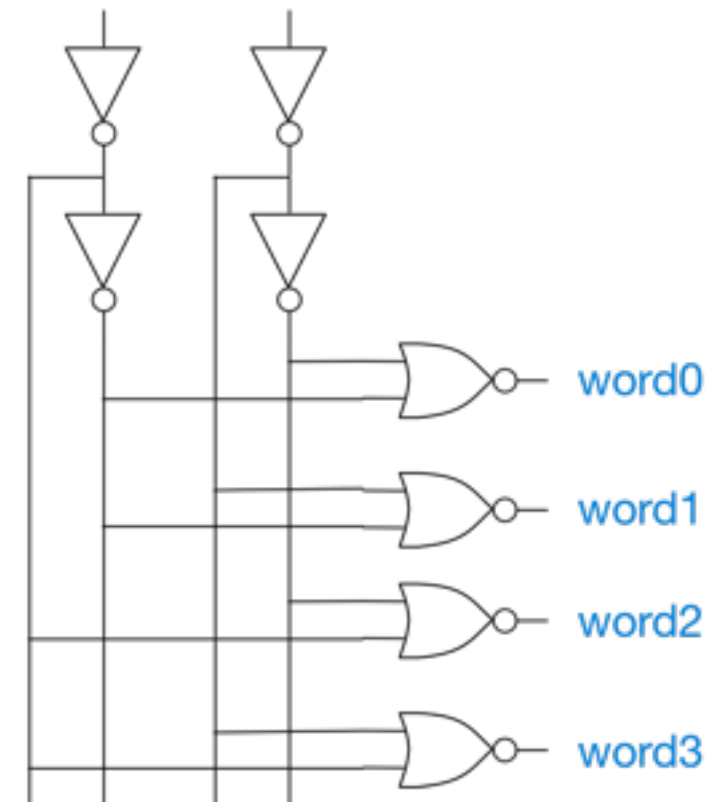

EX. Decoder using NAND gate

 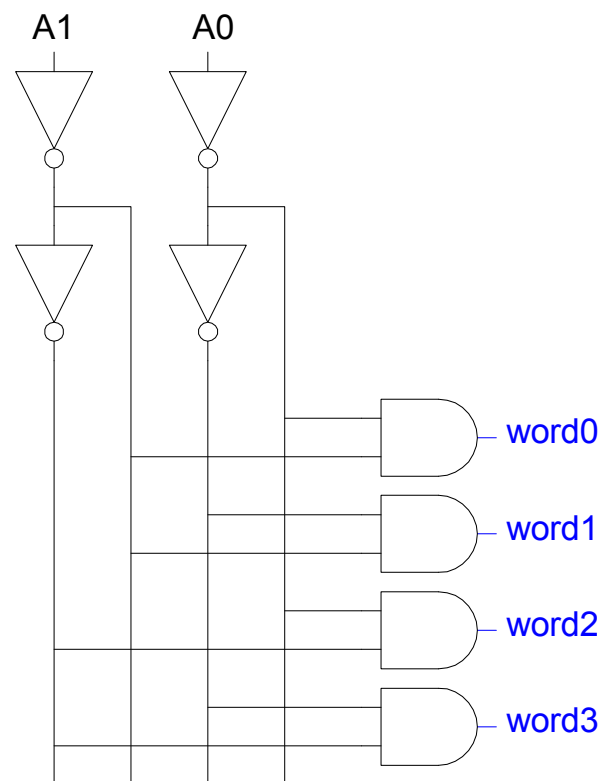- **Question:** AND gates \Rightarrow NAND gate structure



A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

- **Answer:** [replace AND gates with NAND gates, followed by inverters]

Thank You :-)