

B4. Memory—2 Summary

Bei Yu

Reference:

- **Chapter 11 Memories**
- **CMOS VLSI Design—A Circuits and Systems Perspective**
- **by H.E.Weste and D.M.Harris**

NOR ROM


- 4-word x 6-bit NOR-ROM
 - Selected word-line high
 - Represented with dot diagram

Word 0: **010101**


Word 1: **011001**

Word 2: **100101**

Word 3: **101010**

 

Looks like 6 4-input pseudo-nMOS NORs

 

EX: NOR ROM

- Draw 4-word 4-bit NOR-ROM structure and dot diagram


Word 0: **0100**

Word 1: **1001**

Word 2: **0101**


Word 3: **0000**

- **Answer:**

 


NAND ROM

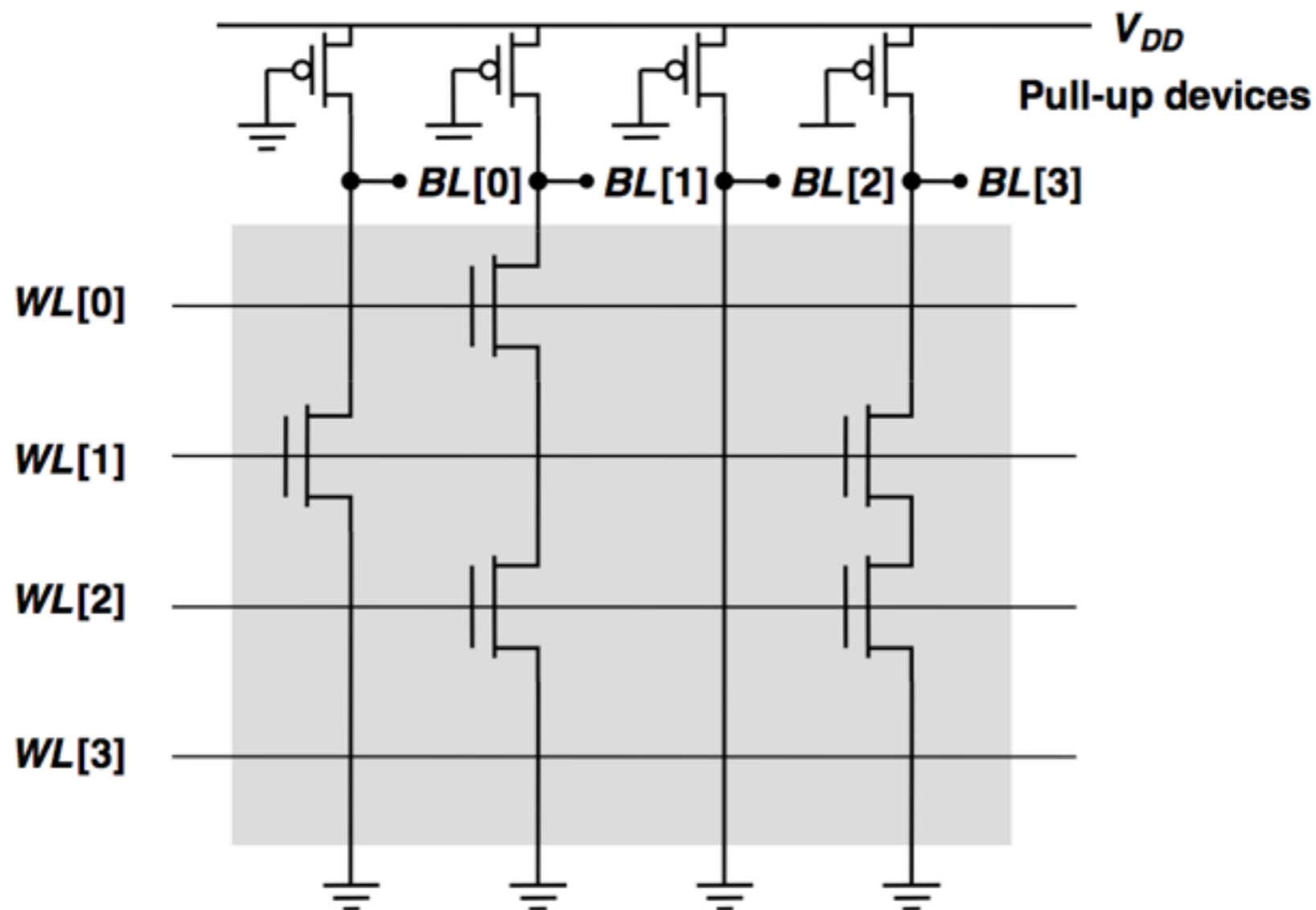- 4-word x 4-bit NAND-ROM
 - All word-lines high with exception of selected row



EX. NAND ROM

- **Question:** What's its function?

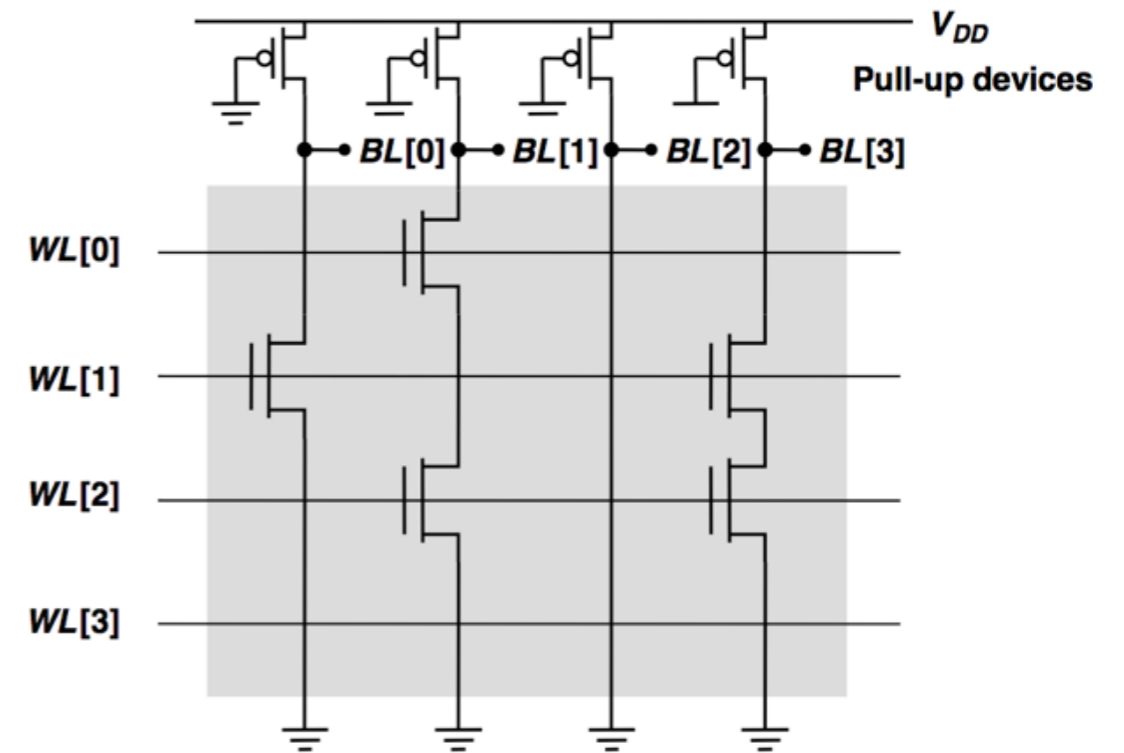


- **Answer:**

WL [0] = 0 : **0100**

WL [1] = 0 : **1001**

WL [2] = 0 : **0101**


WL [3] = 0 : **0000**

 

NOR ROM v.s. NAND ROM

- **NOR ROM:**

 
- (+) Faster
- (-) Larger Area (VDD lines)



- **NAND ROM:**



- (+) High density, small area
- (-) Slower

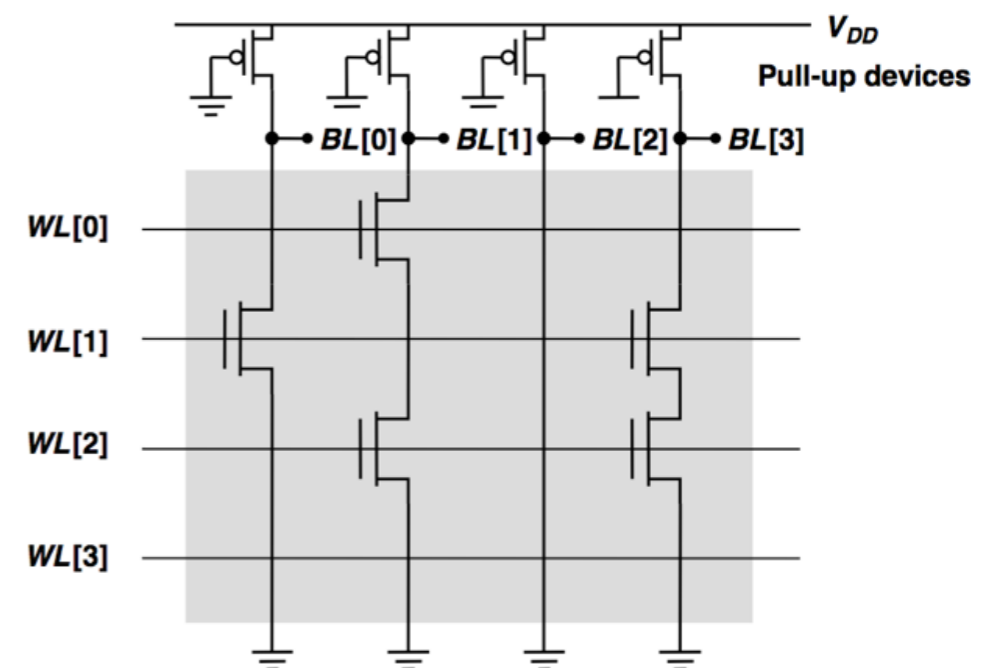delay grows quadratically with the number of series transistors discharging the bitline.



ROM Implementation

- 16-word x 5 bit ROM

  


PLAs

- A *Programmable Logic Array* performs any function in sum-of-products form.
- *Literals*: inputs & complements
- *Products / Minterms*: AND of literals
- *Outputs*: OR of Minterms
- Example: Full Adder


$$s = a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}c + abc$$

$$c_{out} = ab + bc + ac$$

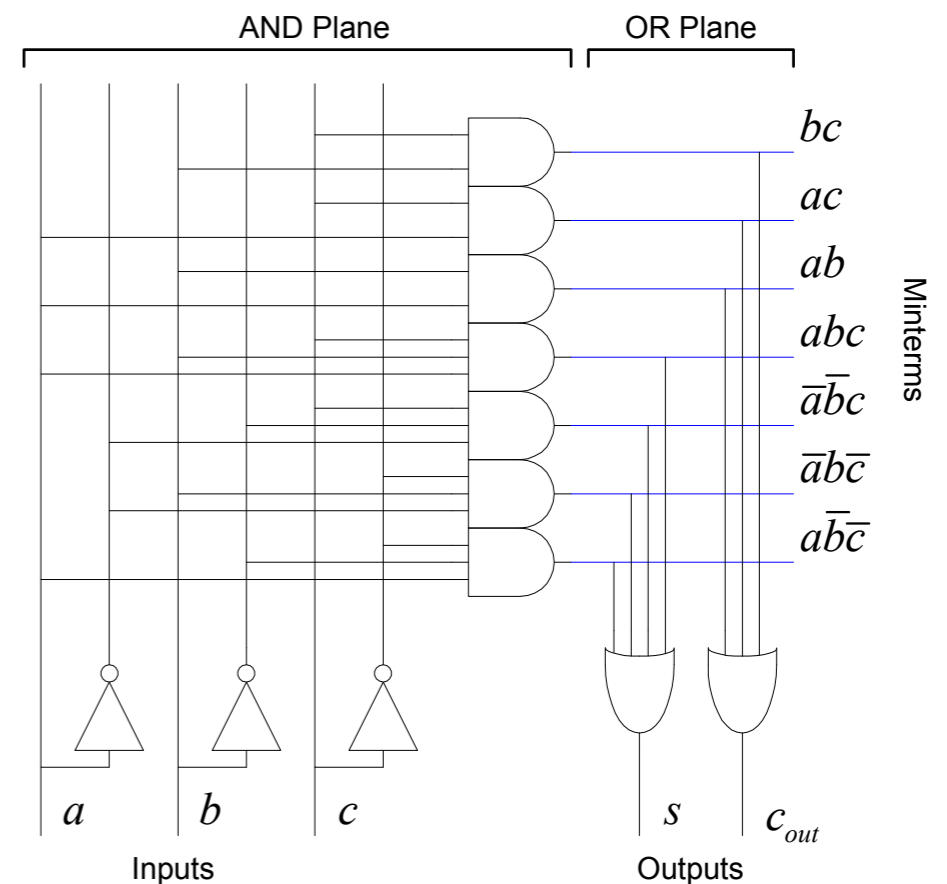


NOR-NOR PLAs

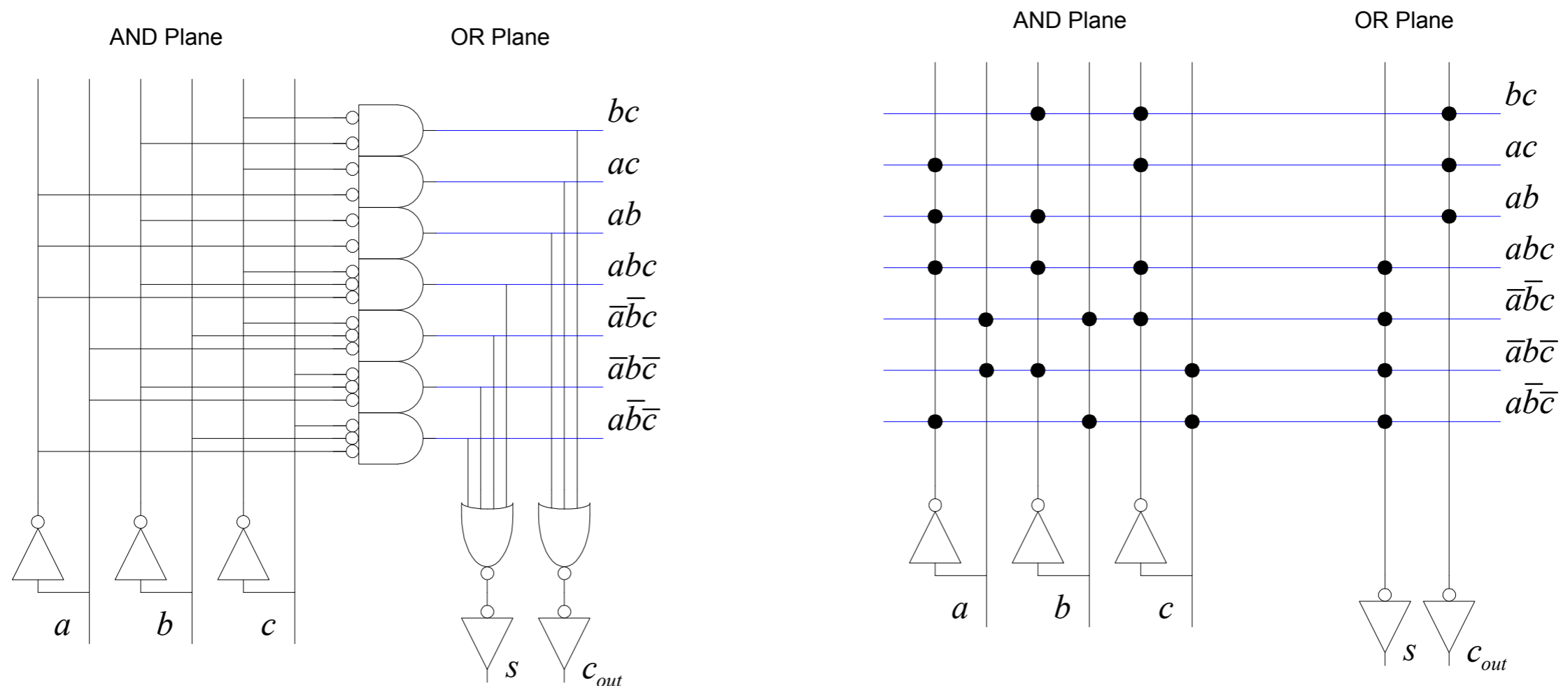- ANDs and ORs not very efficient in CMOS
- Dynamic or Pseudo-nMOS NORs very efficient
- Use **DeMorgan's Law** to convert to all NORs




PLA Question 1

 - Using PLA, design a comparator with function $a \neq b$
- **Answer:** $a'b + ab'$



PLA Question 2

 - Design PLA comparator with function $A_1A_0 > B_1B_0$
- **Answer:** $A_1B_1' + A_1B_1A_0B_0' + A_1'B_1'A_0B_0'$



RoboAnt PLA

- Convert state transition table to logic
- Karnaugh map

$S_{1:0}$	L	R	$Y_{1:0}$	TR	TL	F
00	0	0	00	0	0	1
00	1	X	01	0	0	1
00	0	1	01	0	0	1
01	1		01	0	1	0
01	0	1	01	0	1	0
01	0	0	10	0	1	0
10	X	0	10	1	0	1
10	X	1	11	1	0	1
11	1	X	01	0	1	1
11	0	0	10	0	1	1
11	0	1	11	0	1	1

$S1'$

	$S_1 S_0$			
	00	01	11	10
00	0	1	1	1
LR 01	0	0	1	1
11	0	0	0	1
10	0	0	0	1

$$Y1 = S_1 \overline{S_0} + \overline{L} S_1 + \overline{L} R S_0$$

$S0'$

	$S_1 S_0$			
	00	01	11	10
00	0	0	0	0
LR 01	1	1	1	1
11	1	1	1	1
10	1	1	1	0

$$Y0 = R + \overline{L} S_1 + L S_0$$

$$TR = S_1 \overline{S_0}$$

$$TL = S_0$$

$$F = S_1 + \overline{S_0}$$

EX. RoboAnt Dot Diagram


$$Y1 = S_1 \overline{S_0} + \overline{L} S_1 + \overline{L} R S_0$$

$$Y0 = R + L \overline{S_1} + L S_0$$

$$TR = S_1 \overline{S_0}$$

$$TL = S_0$$

$$F = S_1 + \overline{S_0}$$

 

PLAs vs. ROMs

- The OR plane of the PLA is like the ROM array
- The AND plane of the PLA is like the ROM decoder
- PLAs are more flexible than ROMs
 - No need to have 2^n rows for n inputs
 - Only generate the minterms that are needed
 - Take advantage of logic simplification