

CENG4480 Homework 1

- **Small-Signal Gain:** For given amp circuits, small changes of input ΔV_{in} will cause output change of ΔV_{out} . Small-signal gain is defined by $\frac{\Delta V_{out}}{\Delta V_{in}}$.

Solutions

- Q1** Given a non-inverting amplifier as shown in Fig. 1, calculate the exact finite gain. Assume $A_0 = 1000$, determine the gain difference if the circuit is expected to have an ideal gain of 5 under $A_0 = \infty$.

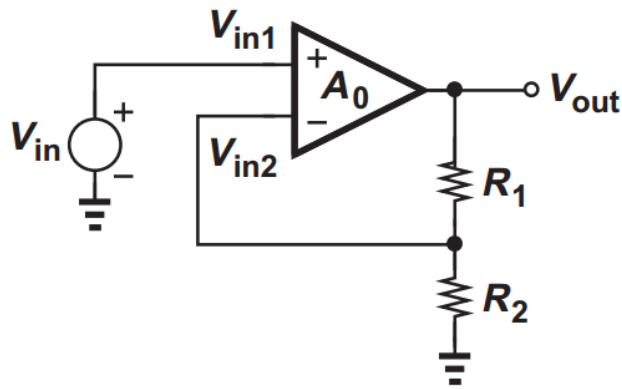


Figure 1: Non-inverting Amplifier

- A1** From the properties of Op Amplifier,

$$V_{out} = A_0(V_{in1} - V_{in2}) \quad (1)$$

Given that,

$$V_{in2} = \frac{R_2}{R_1 + R_2} V_{out} \quad (2)$$

Substituting into (1) we have,

$$g_{real} = \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0} \quad (3)$$

Besides,

$$g_{ideal} = \left(1 + \frac{R_1}{R_2}\right) \quad (4)$$

Substituting data into Eqs. (3) and (4),

$$g_{real} = 4.975, g_{ideal} = 5 \quad (5)$$

Thus, real circuit gain has a 0.5% difference from ideal gain.

Q2 An op amp exhibits the following nonlinear characteristic:

$$V_{out} = \alpha \tanh[\beta(V_{in1} - V_{in2})]. \quad (6)$$

Determine the small-signal gain of the op amp in the case $V_{in1} \approx V_{in2}$.

A2 Taylor expansion of \tanh has the following form:

$$\tanh(Z) = Z - \frac{1}{3}Z^3 + \frac{2}{15}Z^5 - \dots \quad (7)$$

When $V_{in1} \approx V_{in2}$,

$$V_{out} \approx \alpha\beta(V_{in1} - V_{in2}) \quad (8)$$

Thus, small-signal gain is,

$$\frac{dV_{out}}{d(V_{in1} - V_{in2})} = \alpha\beta \quad (9)$$

Q3 Assuming $A_0 = \infty$, compute the closed-loop gain of the inverting op amp shown in Fig. 2. Verify that the result reduces to ideal version when $R_1 \rightarrow 0$.

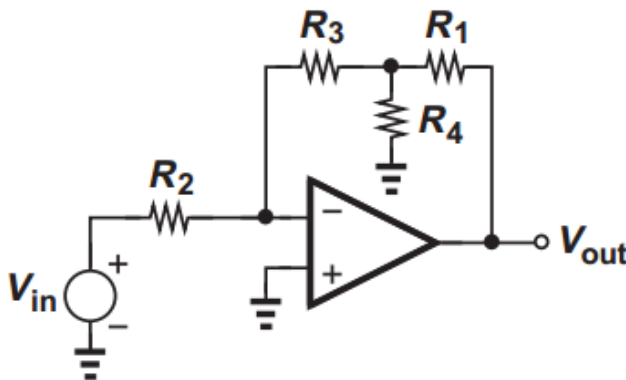


Figure 2: Inverting Op Amp

A3 Given infinite open-loop gain,

$$V_- = V_+ = 0 \quad (10)$$

Let V_x be the voltage of the point where R_1 , R_3 and R_4 crossed, then,

$$\frac{V_{in}}{R_2} = \frac{V_x}{R_3} \quad (11)$$

In addition,

$$\frac{V_x}{R_3 // R_4} = \frac{V_{out} - V_x}{R_1} \quad (12)$$

Combine (11) and (12),

$$\frac{V_{out}}{V_{in}} = -\frac{R_3}{R_2} \frac{R_1 + R_3 // R_4}{R_3 // R_4} \quad (13)$$

If $R_1 \rightarrow \infty$, (13) reduces to,

$$\frac{V_{out}}{V_{in}} = -\frac{R_3}{R_2}, \quad (14)$$

which is the typical case of inverting op amp.

Q4 Calculate the transfer function (in other word, gain) of the circuit shown in Fig. 3 if $A_0 = \infty$.

Would it be possible that $|\frac{V_{out}}{V_{in}}| = 1$ for all frequencies.

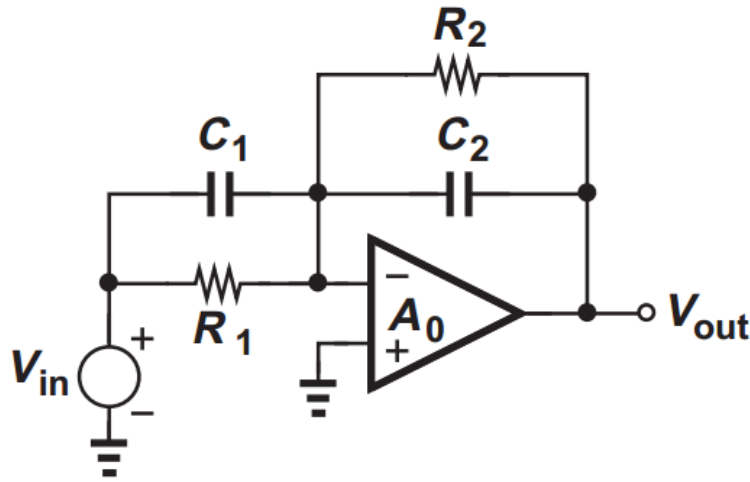


Figure 3: Sample Differentiator

A4 Since $A_0 = \infty$, $V_- = V_+$, applying KCL,

$$\frac{V_{in}}{R_1 // \frac{1}{C_1 s}} = -\frac{V_{out}}{R_2 // \frac{1}{C_2 s}} \quad (15)$$

$$A(s) = \frac{V_{out}}{V_{in}} = -\frac{R_2 // \frac{1}{C_2 s}}{R_1 // \frac{1}{C_1 s}} \quad (16)$$

To make sure $|A(s)|$ is unity for all frequencies, thus Eq (21) should contain no frequency components, $R_1 = R_2$ and $C_1 = C_2$ is a feasible solution.

Q5 Repeat Q4 when A_0 is finite.

A5 Applying KCL, we have,

$$\frac{V_{in} - V_-}{R_1 // \frac{1}{C_1 s}} = \frac{V_{out} - V_-}{R_2 // \frac{1}{C_2 s}} \quad (17)$$

In addition,

$$V_{out} = -A_0 V_- \quad (18)$$

Solve (17) and (18),

$$\frac{V_{out}}{V_{in}} = -\frac{R_2 // \frac{1}{C_2 s}}{R_1 // \frac{1}{C_1 s}} \frac{A_0}{A_0 + 1 + R_2 // \frac{1}{C_2 s}} \quad (19)$$

Let $|\frac{V_{out}}{V_{in}}| = 1$, we have,

$$\left| \frac{R_1 // \frac{1}{C_1 s}}{R_2 // \frac{1}{C_2 s}} \right| = \frac{A_0 + 1}{A_0 - 1} \quad (20)$$

Since A_0 is rational, we can still have the following result,

$$R_1 = \frac{A_0 + 1}{A_0 - 1} R_2 \quad (21)$$

and,

$$C_2 = \frac{A_0 + 1}{A_0 - 1} C_1 \quad (22)$$

Q6 Consider the voltage adder shown in Fig. 4, where $V_1 = V_0 \sin \omega t$ and $V_2 = V_0 \sin 3\omega t$. Assume $R_1 = R_2$ and $A_0 = \infty$. Plot V_{out} as a function of time.

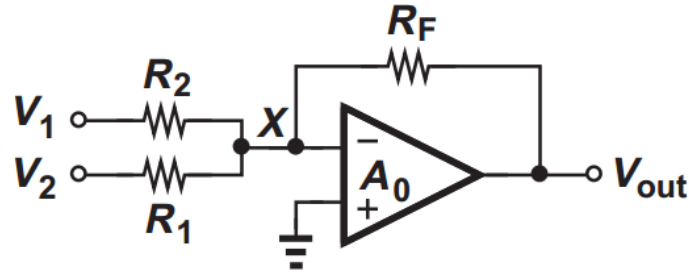


Figure 4: Voltage Adder

A6 Obviously,

$$V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \quad (23)$$

Since $R_1 = R_2$,

$$V_{out} = -\frac{R_F}{R_1} (V_1 + V_2) \quad (24)$$

V-t curve is shown in Fig. 5.

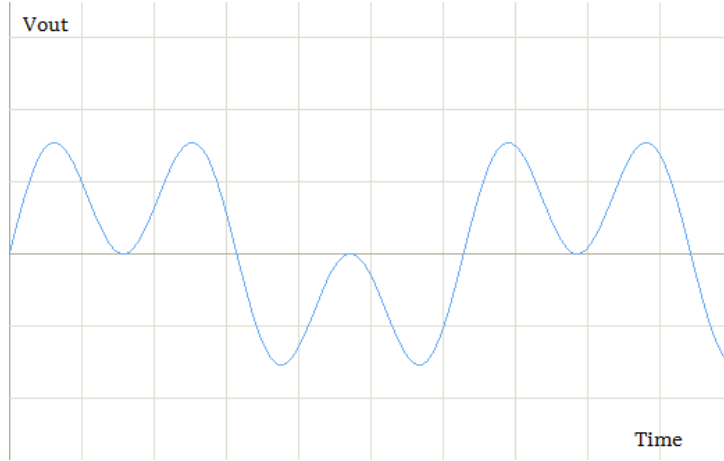


Figure 5: V_{out} vs. time

Q7 The input/output characteristic of an op amp can be approximated by the piecewise-linear behavior illustrated in Fig. 6, where the gain drops from A_0 to $0.8A_0$ and eventually to zero as $|V_{in1} - V_{in2}|$ increases. Suppose this op amp is used in a non-inverting amplifier (Fig. 1) with an ideal gain of 5. Plot the closed-loop input/output characteristic of the circuit.

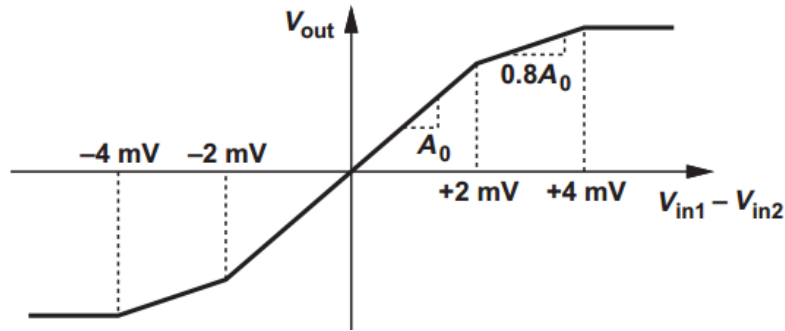


Figure 6: Open-loop Gain Variation

A7 From Eq. (3), we have closed-loop gain,

$$g_{closed} = \frac{V_{out}}{V_{in1}} = \frac{A_0}{1 + \frac{R_2}{R_1+R_2}A_0} \quad (25)$$

Combine (4) and (25),

$$g_{closed} = 5 - \frac{25}{5 + A_0} \approx 5 - \frac{25}{A_0} \quad (26)$$

Besides,

$$V_{out} = 5V_{in2} \quad (27)$$

Then,

$$V_{in2} = \left(1 - \frac{5}{A_0}\right)V_{in1}, V_{in1} - V_{in2} = \frac{5}{A_0}V_{in1} \quad (28)$$

When $V_{in1} - V_{in2}$ is $2mv$ and $4mv$, V_{in1} is $\frac{A_0}{5}(2mv)$ and $\frac{A_0}{5}(4mv)$ correspondingly. Accordingly, closed-loop input/output characteristic is presented in Fig. 7.

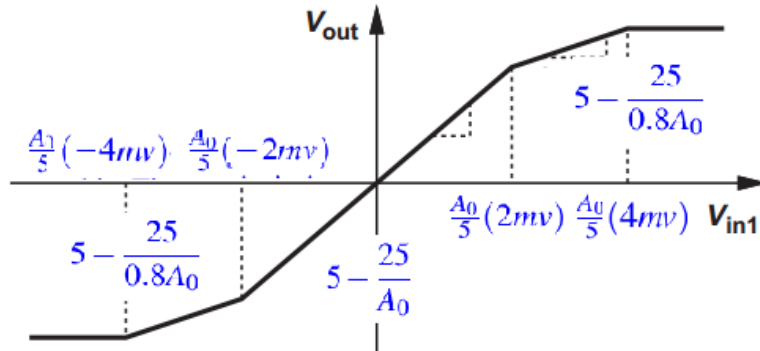


Figure 7: Closed-loop Gain Variation

Q8 Metal-Oxide-Semiconductor-Field-Effect-Transistor (MOSFET) is the core component of a variety of amplifiers. Fig. 8 shows a common source amplifier circuit with N-type MOS (M1). Typically, when M1 works as amplifier, drain current I_D has the following relationship with bias voltage V_{in} :

$$I_D = k(V_{in} - V_{th})^2, \quad (29)$$

where k is positive and related to material properties of MOSFET and V_{th} is threshold voltage to turn the device on. Calculate small-signal gain of common source amplifier and show that this amplifier is an inverting amplifier.

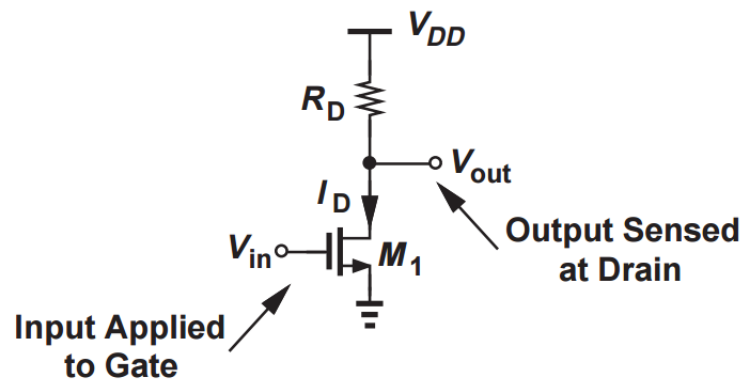


Figure 8: Common Source Amplifier

A8 When small signal ΔV is applied on input terminal, drain current change is :

$$\Delta I_D = I'_D \Delta V_{in} \quad (30)$$

From Krichhoff's Law,

$$V_{DD} = I_D R_D + V_{out} \quad (31)$$

In addition that V_{DD} is constant, i.e.

$$\Delta I_D R_D + \Delta V_{out} = 0 \quad (32)$$

Substitute (29) and (30) into (32), we can derive

$$\frac{\Delta V_{out}}{\Delta V_{in}} = -2k(V_{in} - V_{th})R_D. \quad (33)$$

Thus, gain of this amplifier is $2k(V_{in} - V_{th})R_D$, and output has a phase difference of π from Input.