

# CENG4480 Homework 2

## Solutions

**Q1** Given the following system as shown in Fig. 1.  $Q_1$  is so-call NPN bipolar device, which has following voltage-current characteristic:

$$I_C = I_S e^{\frac{kV_X}{T}} \quad (1)$$

where,  $T$  is temperature,  $k$  and  $I_S$  is constant. Suppose  $R_2$  is a temperature-sensitive resister and has resistor value of  $R_{2,0}$  at temperature  $T_0$ , determine the  $R_2$  in terms of  $T$ , so that  $V_Y$  is stable as temperature changes.

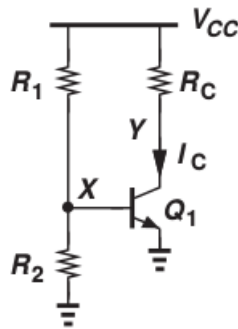


Figure 1: Resistive Divider Biased System

**A1** As required  $\frac{V_X}{T}$  is constant,

$$V_X = CT \quad (2)$$

Besides,

$$V_X = \frac{R_2}{R_1 + R_2} V_{CC} \quad (3)$$

We have,

$$C = \frac{R_{2,0}}{T_0 R_1 + T_0 R_{2,0}} \quad (4)$$

Combine Eq. (2)–(4),

$$R_{2,0} = \frac{R_1 R_{2,0} T}{T_0 (R_1 + R_{2,0}) - T R_{2,0}} \quad (5)$$

**Q2** A simple Infra-Red Sensor system to detect passing human is presented as in Fig. 2. A and B are IR Sensors which will generate different output voltages for different infra-red intensity, and higher voltage level corresponds to high light intensity.

- (1) Explain how this system works for counting passing pedestrians.
- (2) To increase counting accuracy, usually B is covered with materials that can reflect infra-red light. Explain why.

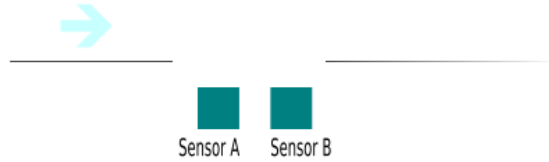


Figure 2: IR-System

**A2** (1) When pedestrians pass over IR Sensor, they will approach and deviate the sensor, which corresponds to voltage pulses  $V_A$  at the output of it. We can simply count pulse number for passing pedestrian.

(2) When Sensor B is covered with infra-red reflection materials, it can generate pulses  $V_B$  caused by non-infra-red wave. We can reduce wrongly counted number by subtract  $V_B$  from  $V_A$  to avoid counting noise signal.

**Q3** Considering the 4-bit DAC in Fig. 3, calculate the output scope of  $v_a$ , and the minimum voltage change it can generate.

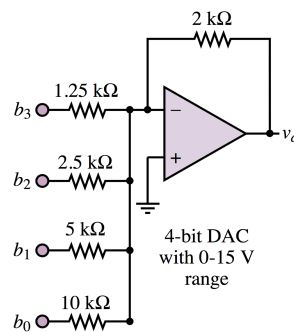


Figure 3: 4-bit DAC

**A3** Boundary of  $v_a$  occurs at digital input (0000) and (1111), thus the scope of output is 0–3V. Minimum voltage change occurs when the least significant bit changes, at this occasion,  $v_a$  has 0.2V change.

**Q4** Design a fully paralleled ADC, please provide ADC details. ADC should satisfy: (1) Detect input range 0–3V and (2) Generate 4-bit digital output.

**A4** Type: Flash ADC.

For 4-bit output, ADC should be able to sense 0.2V input change, thus total 15 comparators are needed with reference voltage 3.2V.

**Q5** For the 4-bit R-2R DAC, calculate  $V_0$  in terms of  $V_{b,0} - V_{b,4}$  if  $V_{ref}$  is grounded (Fig. 4).

**A5** As shown in Fig 5, first we calculate the equivalence seen from  $V_{o3}$ ,

$$R_{eq} = R \tag{6}$$

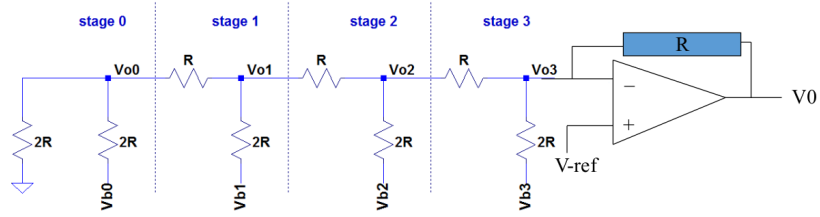


Figure 4: R-2R DAC

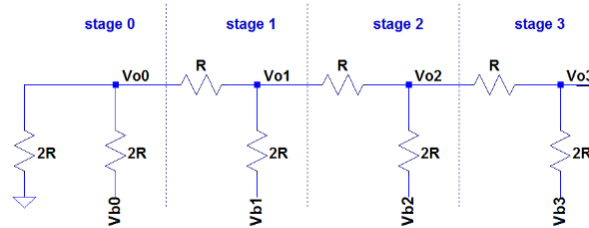


Figure 5: Load of R-2R ADC

Get contribution at  $V_{o3i}$  of each digital input  $V_{bi}$ ,  $i=0,1,2,3$  separately, it's easy to derive from Thevenin equivalent analysis,

$$V_{o30} = \frac{V_{b0}}{16} \quad (7)$$

$$V_{o31} = \frac{V_{b1}}{8} \quad (8)$$

$$V_{o32} = \frac{V_{b2}}{4} \quad (9)$$

$$V_{o33} = \frac{V_{b3}}{2} \quad (10)$$

$$(11)$$

then, we have,

$$V_{o3} = \frac{V_{b0}}{16} + \frac{V_{b1}}{8} + \frac{V_{b2}}{4} + \frac{V_{b3}}{2} \quad (12)$$

Using the quality of op amp,

$$V_o = \frac{V_{b0}}{16} + \frac{V_{b1}}{8} + \frac{V_{b2}}{4} + \frac{V_{b3}}{2} \quad (13)$$

**Q6** Briefly describe how PID affects motor control.

**A6** TRIVIAL

**Q7** Elaborate motion sensors you know.

**A7** TRIVIAL

**Q8** Describe how Sample and Hold Amp works.

**A8** When sampling signal comes, FET switch open, Capacitor will be charged by  $v_a$  and  $v_{SH}=v_a(t)$  Repeat previous procedure, continuous analog signal is converted into step signals for further quantization process.