

# CENG4480 Homework 3

- Q1** Elaborate and exemplify the differences between Combinational and Sequential Circuit.
- Q2** What is the modern memory hierarchy? Analysis the properties of each hierarchy level.
- Q3** For the given SR Latch Fig. 1. Draw the waveform of Q if S, R, and E(Clk) have the input shown in Fig. 2

 


Figure 1: Gated SR Latch

 


Figure 2: Gated SR Latch

- Q4** Show the differences between DRAM and SRAM and which level of hierarchy of memory are they employed.
- Q5** Design a finite state machine to detect the pattern of “11010” in the bit stream. How many states are required? Draw the state transition graph.
- Q6** (a) What is setup time?  
(b) How is clock skew generated? (c) How to alleviate clock skew?
- Q7** Explain the working principle of the following register (Fig. 3) and show that the circuit is not sensitive to clock skew.
- Q8** Explain cross-talk and approaches to eliminate cross-talk.

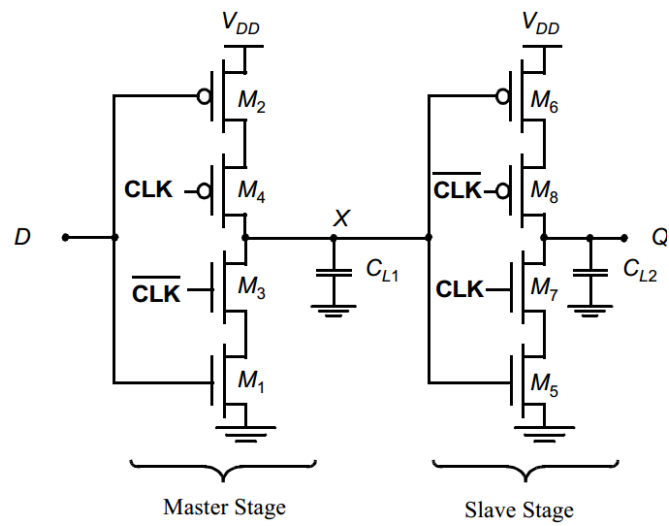


Figure 3: Sample Register.