

CENG4480

Lecture 02 Review

Bei Yu

2016 Fall

byu@cse.cuhk.edu.hk



香港中文大學

The Chinese University of Hong Kong

Voltage gain A

$$A = \frac{V_{out}}{V_{in}}$$


- ▶ Usually voltage gain may be either very large or very small
- ▶ Inconvenient to express as a simple ratio
- ▶ Therefore, **decibel** (dB):

Voltage gain in **dB**

$$A = 20 \cdot \log_{10} \frac{V_{out}}{V_{in}}$$



R_{in} & R_{out}

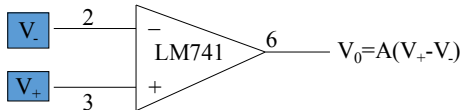

- ▶ R_{in} : input impedance (**High**)
- ▶ R_{out} : output impedance (**Low**)



Ideal Op-Amp Rules

Rule 1

No current flows in or out of the inputs

Rule 2

The Op-Amp tries to keep the inputs the **same** voltage

* only for negative feedback op-amp



Ideal Op-Amp v.s. Real Op-Amp

Open-Loop Gain A

Ideal: Infinite, thus $V^+ = V^-$

Real: Typical range (20,000, 200,000), thus $V_{out} = A(V^+ - V^-)$

Input Impedance

Ideal: Infinite. Since $Z_{in} = \frac{V_{in}}{I_{in}}$, zero input current

Real: No such rule.


Bandwidth

Ideal: Infinite Bandwidth

Real: Gain-Bandwidth product (GB).



Voltage follower

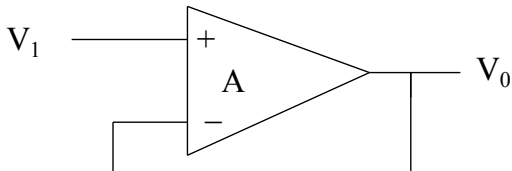


- ▶ Unit voltage gain
- ▶ Output $V_0 = V_1$
- ▶ high current gain, high input impedance

In real op-amp

$$V_0 = A(V_1 - V_0) \Rightarrow V_0 = \frac{V_1 A}{1 + A} \approx V_1$$



Non-inverting Amplifier

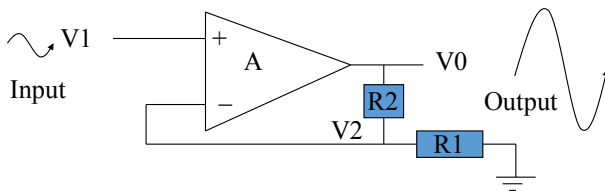


- R_{in} : High input impedance

In real op-amp

$$V_0 = A(V_1 - V_0) \text{ and } \frac{V_2}{V_0} = \frac{R_1}{R_1 + R_2}$$
$$\Rightarrow \frac{V_0}{V_1} = \frac{R_1 + R_2}{R_1 + (R_1 + R_2)/A} \approx \frac{R_1 + R_2}{R_1}$$




Question: Non-inverting Amplifier Gain

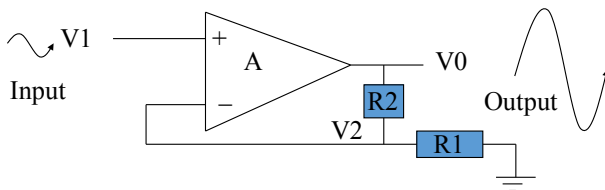

Calculate $\frac{V_0}{V_1} =$



Question: Non-inverting Amplifier Gain

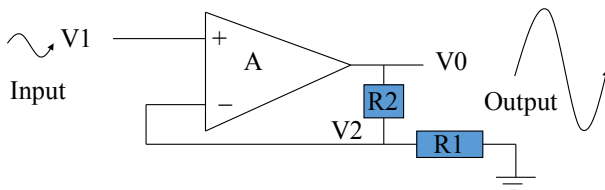


Calculate $\frac{V_0}{V_1} =$

$$1 + \frac{R_2}{R_1}$$




Current to Voltage Converter

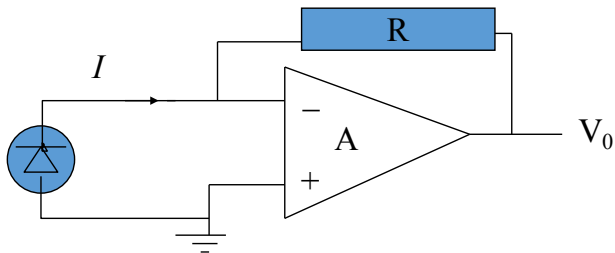

$$V_0 = I \cdot R$$



Inverting Amplifier

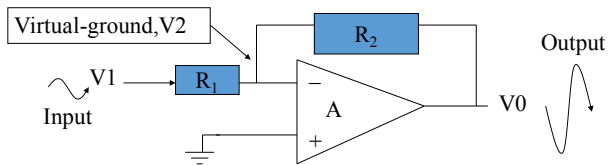


In real op-amp

$$V_0 = A(0 - V_2) \text{ and } \frac{V_0 - V_1}{R_1 + R_2} = \frac{V_2 - V_1}{R_1}$$
$$\Rightarrow \frac{V_0}{V_1} = \frac{R_2}{R_1} \cdot \frac{R_1 A}{R_1 A + R_1 + R_2} \approx -\frac{R_2}{R_1}$$




Inverting Amplifier

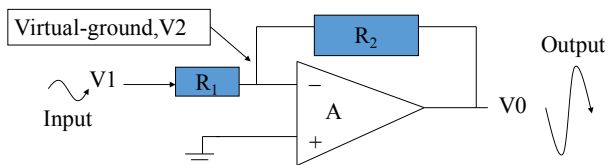


- ▶ $R_{in} = R_1$
- ▶ Gain (G) =

Inverting Amplifier

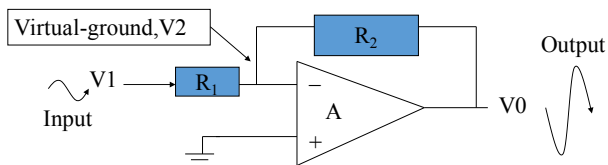

- ▶ $R_{in} = R_1$
- ▶ Gain (G) = $-\frac{R_2}{R_1}$

Inverting Amplifier

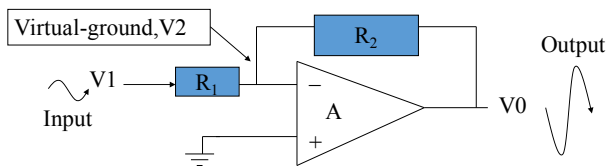


▶ $R_{in} = R_1$

▶ Gain (G) = $-\frac{R_2}{R_1}$

Question: How to increase input impedance?




Summing Amplifier

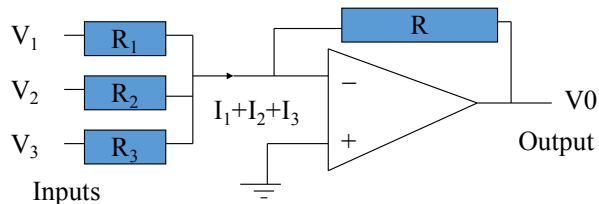

$$V_0 = -R \cdot \left\{ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right\}$$




Differential Amplifier

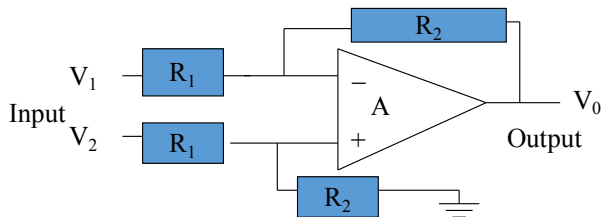

- ▶ Calculate the difference between V_1 and V_2
- ▶ Can control gain




Question: Differential Amplifier Gain

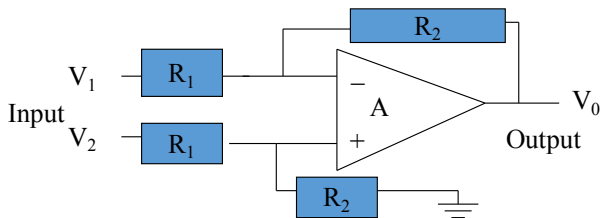

Calculate $V_0 =$



Question: Differential Amplifier Gain

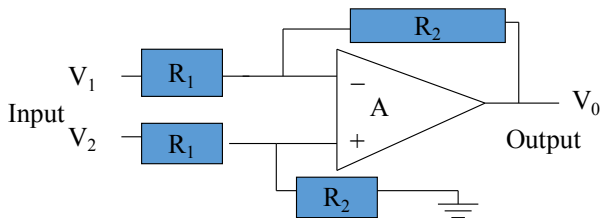


Calculate $V_0 =$

$$\frac{R_2}{R_1} \cdot (V_2 - V_1)$$




Instrumental Amplifier

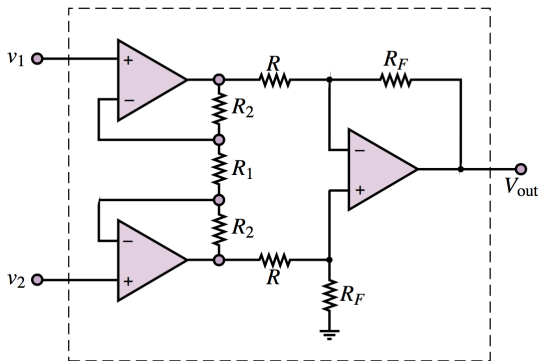

- ▶ To make a **better** DC amplifier from op-amps
- ▶ combine **2** noninverting amplifier & **1** differential amplifier



Instrumental Amplifier (cont.)

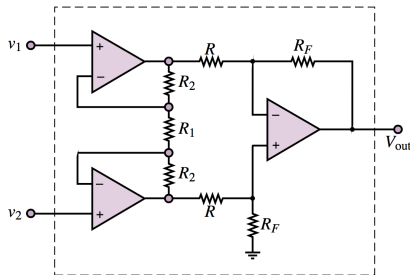

- ▶ For each non-inverting amplifier: $A = 1 + \frac{2R_2}{R_1}$
- ▶ Connecting to differential amplifier:

$$\begin{aligned} V_{out} &= \frac{R_F}{R} (A_{v1} - A_{v2}) \\ &= \frac{R_F}{R} \left(1 + \frac{2R_2}{R_1}\right) (v_1 - v_2) \end{aligned}$$

