

CENG4480

Lecture 03: Operational Amplifier – 2

Bei Yu

2016 Fall

byu@cse.cuhk.edu.hk



香港中文大學
The Chinese University of Hong Kong

Overview

Preliminaries

Integrator & Differentiator

Filters



Overview

Preliminaries

Integrator & Differentiator

Filters



Biasing

Biasing in electronics

The method of establishing predetermined voltages or currents at various points of an electronic circuit for the purpose of establishing proper operating conditions in electronic components

<https://en.wikipedia.org/wiki/Biasing>



Eulers Identity

$$e^{j\theta} = \cos\theta + j\sin\theta$$

- ▶ real component
- ▶ imaginary component
- ▶ magnitude

$$|e^{j\theta}| = \sqrt{\cos^2\theta + \sin^2\theta} = 1$$



Prove:


$$\left| \frac{1}{1+ja} \right| = \frac{1}{\sqrt{1+a^2}}$$



Sinusoidal Signal

$$x(t) = A \cos(\omega t + \phi)$$

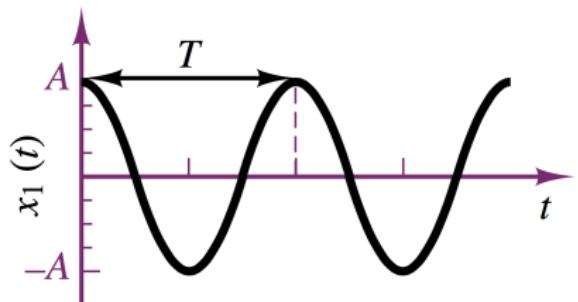- ▶ Periodic signals
- ▶ A : amplitude
- ▶ ω : radian frequency
- ▶ ϕ : phase




Time Domain

- ▶ Voltage gain against time

For sinusoidal signal:

$$v(t) = A\cos(\omega t + \phi)$$

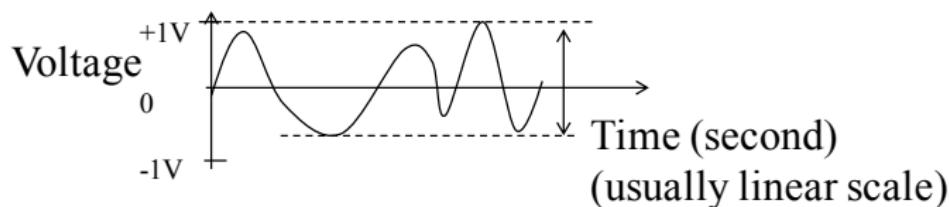

Frequency Domain

- ▶ Voltage gain against frequency


For sinusoidal signal:

$$\mathbf{V}(j\omega) = Ae^{j\phi} = A\angle\phi$$



Impedance

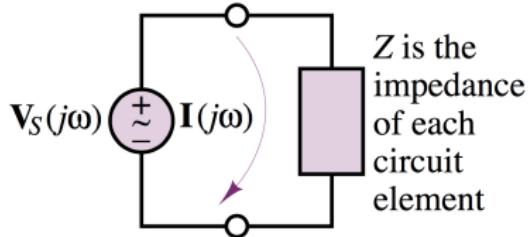A complex resistance or *frequency-dependent resistance*. That is, as resistors whose resistance is a function of the frequency of the sinusoidal excitation.




AC circuits in
phasor/impedance form



Resistor Impedance

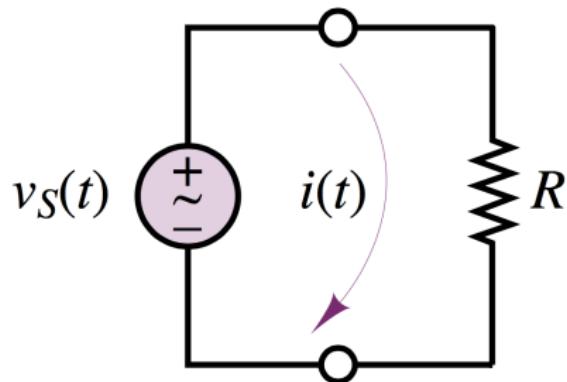- ▶ $\mathbf{V}(j\omega) = A\angle 0$
- ▶ $\mathbf{I}(j\omega) = \frac{A}{R}\angle 0$




Impedance of A Resistor

$$Z_R(j\omega) = \frac{\mathbf{V}(j\omega)}{\mathbf{I}(j\omega)} = R$$



Capacitor ABC

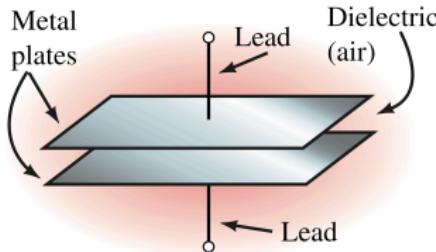

(a) Basic construction



(b) Symbol

Capacitance C


A measure of how much charge a capacitor can hold.

- ▶ Amount of charge $Q = C \cdot V$
- ▶ **current** is the rate of movement of charge: $I = \frac{dQ}{dt} = C \cdot \frac{dV}{dt}$



Capacitor Impedance
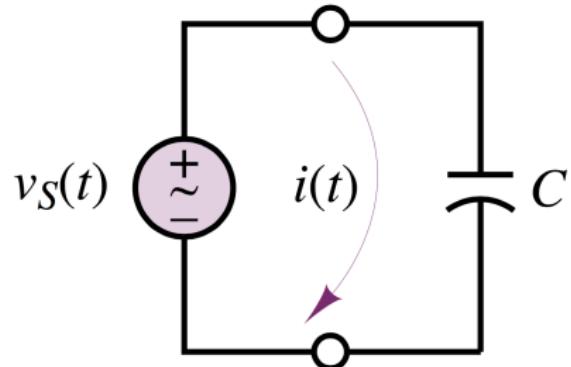
$$\mathbf{V}(j\omega) = A\angle 0$$
$$\mathbf{I}(j\omega) = \omega CA\angle\pi/2$$




Impedance of A Capacitor

$$Z_C(j\omega) = \frac{\mathbf{V}(j\omega)}{\mathbf{I}(j\omega)} =$$



$$Z_C(j\omega) = \frac{1}{j\omega C}$$

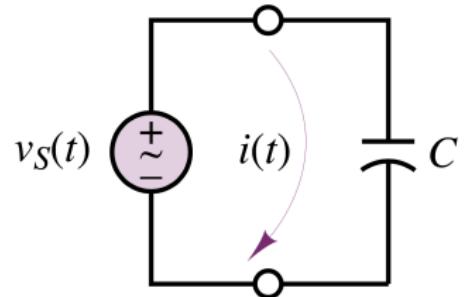

Capacitor Rule 1

Low Frequency \Rightarrow Open circuit

Capacitor Rule 2

High Frequency \Rightarrow Short circuit



Overview


Preliminaries

Integrator & Differentiator

Filters



Integrator

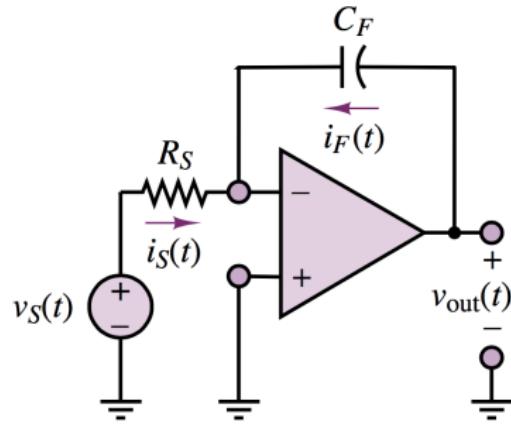


$$i_S(t) = -i_F(t)$$

$$i_S(t) = \frac{v_S(t)}{R_S}$$

$$i_F(t) = C_F \cdot \frac{dv_{out}(t)}{dt}$$



Integrator

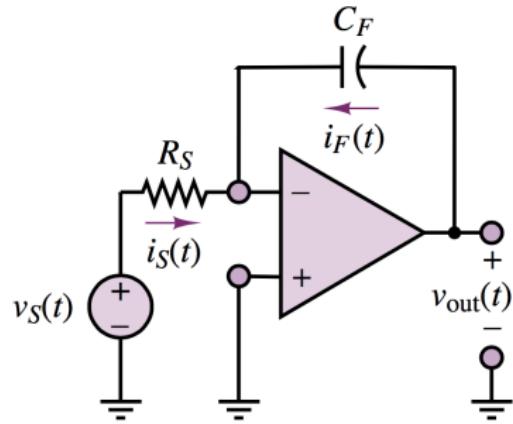

$$i_S(t) = -i_F(t)$$

$$i_S(t) = \frac{v_S(t)}{R_S}$$


$$i_F(t) = C_F \cdot \frac{dv_{out}(t)}{dt}$$

Therefore:

$$v_{out}(t) = -\frac{1}{R_S C_F} \int_{-\infty}^t v_S(t') dt'$$



Differentiator

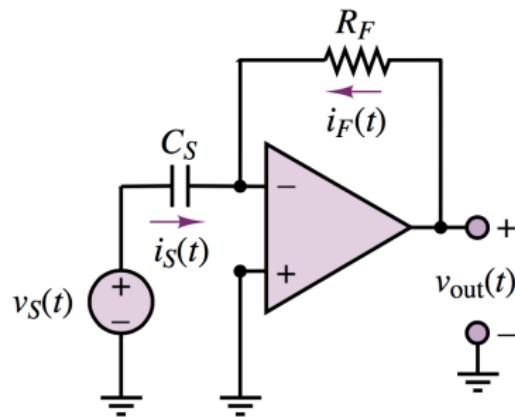


$$i_S(t) = C_S \cdot \frac{dv_S(t)}{dt}$$

$$i_F(t) = \frac{v_{out}(t)}{R_F}$$



Differentiator

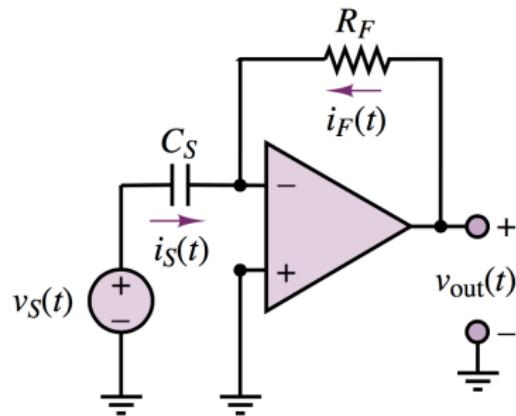

$$i_S(t) = C_S \cdot \frac{dv_S(t)}{dt}$$
$$i_F(t) = \frac{v_{out}(t)}{R_F}$$

Therefore:

$$v_{out}(t) = -R_F C_S \cdot \frac{dv_S(t)}{dt}$$



Overview


Preliminaries

Integrator & Differentiator


Filters



Frequency Response of An Op-Amp

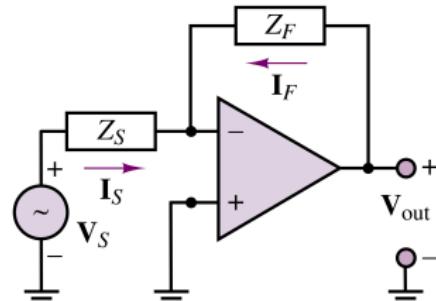


Inverting

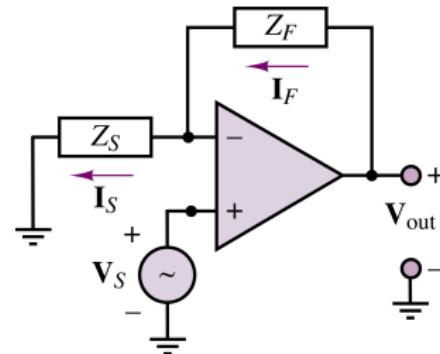


Noninverting



Frequency Response of An Op-Amp

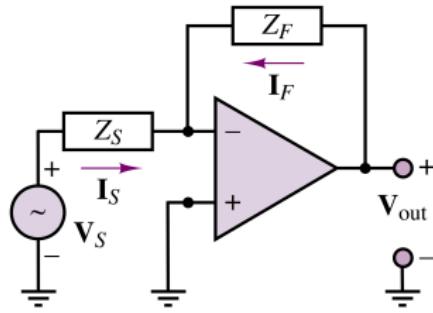

Inverting

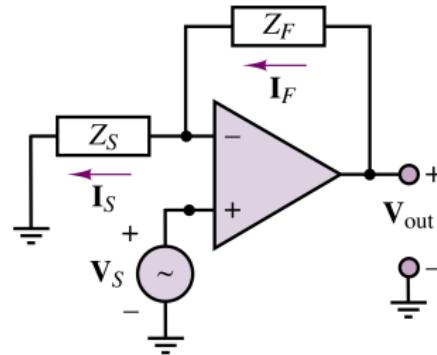


Noninverting


- Inverting amplifier: $\frac{V_{out}}{V_S}(j\omega) = -\frac{Z_F}{Z_S}$



Frequency Response of An Op-Amp

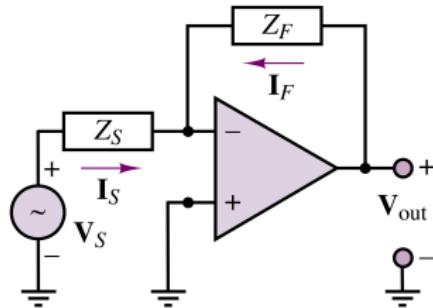

Inverting

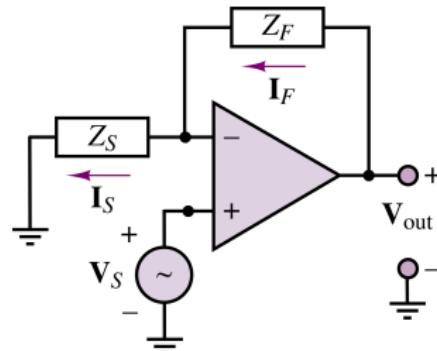


Noninverting

- ▶ Inverting amplifier: $\frac{V_{out}}{V_S}(j\omega) = -\frac{Z_F}{Z_S}$
- ▶ Non-Inverting amplifier: $\frac{V_{out}}{V_S}(j\omega) = 1 + \frac{Z_F}{Z_S}$



Low-Pass Filter

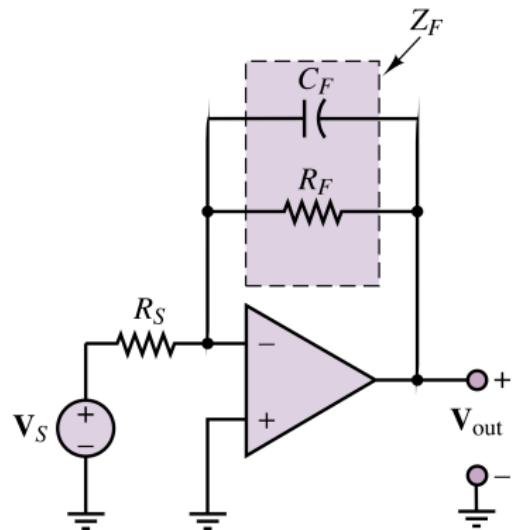


$$A(j\omega) = -\frac{Z_F}{Z_S}$$

$$Z_F = R_F \parallel \frac{1}{j\omega C_F} = \frac{R_F}{1 + j\omega C_F R_F}$$

$$Z_S = R_S$$



Low-Pass Filter

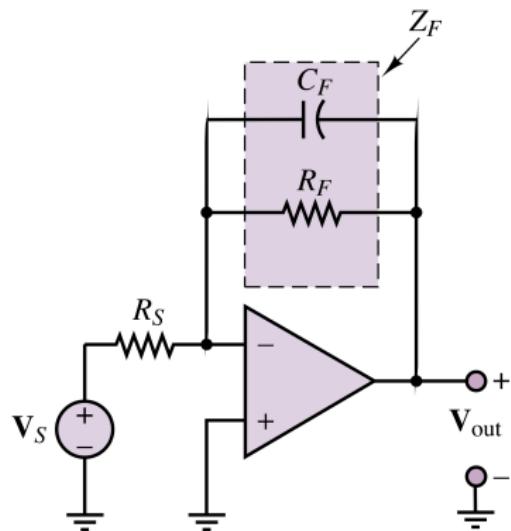

$$A(j\omega) = -\frac{Z_F}{Z_S}$$

$$Z_F = R_F \parallel \frac{1}{j\omega C_F} = \frac{R_F}{1 + j\omega C_F R_F}$$

$$Z_S = R_S$$

⇒

$$A(j\omega) = -\frac{Z_F}{Z_S} = -\frac{R_F/R_S}{1 + j\omega C_F R_F}$$



Given:

$$A(j\omega) = -\frac{Z_F}{Z_S} = -\frac{R_F/R_S}{1 + j\omega C_F R_F}$$


$$\omega_c = \frac{1}{R_F C_F}$$

Prove:


$$|A| = \frac{R_F}{R_S} \cdot \frac{1}{\sqrt{1 + w^2/w_c^2}}$$



Low-Pass Filter

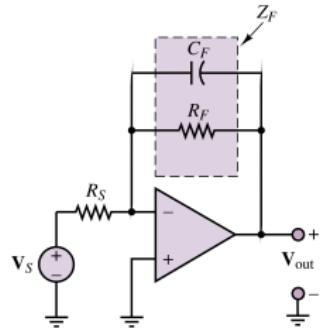

$$|A| = \frac{R_F}{R_S} \cdot \frac{1}{\sqrt{1 + w^2/w_c^2}}$$

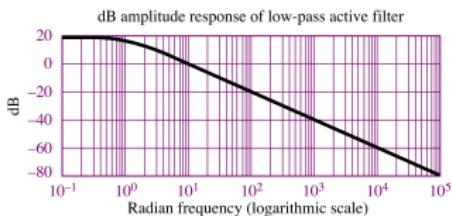


- ▶ $w_c = \frac{1}{R_F C_F}$
- ▶ **3-dB frequency**
- ▶ or **cutoff frequency**

BTW, $\lim_{\omega \rightarrow 0} |A| = \frac{R_F}{R_S}$, $\lim_{\omega \rightarrow \infty} |A| = 0$



High-Pass Filter

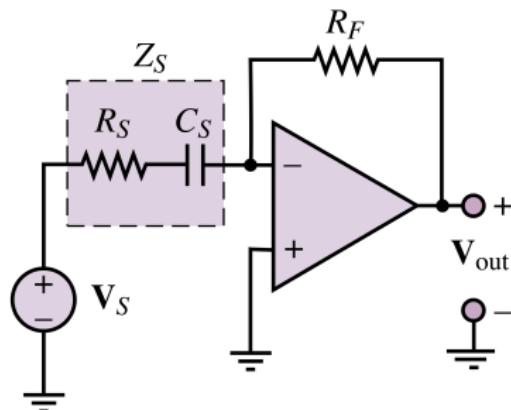

$$A(j\omega) = -\frac{Z_F}{Z_S}$$

$$Z_S = R_S + \frac{1}{j\omega C_S}$$


$$Z_F = R_F$$

⇒


$$A(j\omega) = -\frac{Z_F}{Z_S} = -\frac{j\omega C_S R_F}{1 + j\omega C_S R_S}$$



High-Pass Filter

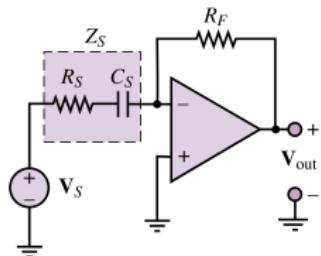
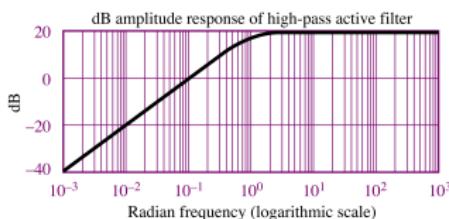
$$A(j\omega) = -\frac{Z_F}{Z_S} = -\frac{j\omega C_S R_F}{1 + j\omega C_S R_S}$$



$$\lim_{\omega \rightarrow 0} |A| = 0$$

$$\lim_{\omega \rightarrow \infty} |A| = \frac{R_F}{R_C}$$

High freq. cutoff unintentionally created by Op-amp



Band-Pass Filter

