



香港中文大學

The Chinese University of Hong Kong

*CENG3430 Rapid Prototyping of Digital Systems*

**Lecture 03:**

# **Combinational Circuit and Sequential Circuit**

 
**Ming-Chang YANG**

[mcyang@cse.cuhk.edu.hk](mailto:mcyang@cse.cuhk.edu.hk)






- **Combinational Circuit: no memory**
  - Outputs depend on the *present* inputs only.
  - **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
  - Outputs depend on *present* inputs and *previous* outputs.
  - **Rule: MUST** use sequential statements (i.e., `process`).


 
# Combinational Circuit



- **Combinational Circuit: no memory**
  - Outputs depend on the *present* inputs only.
    - As soon as inputs change, the values of previous outputs are **lost**.
  - **Rule:** You can build a combinational circuit using either concurrent statements (i.e., statements outside `process`) or sequential statements (i.e., statements inside `process`) .




# Modeling Combinational Circuit (1/3)



- Typical ways for modeling a combinational circuit:
  - 1) **Logic/Schematic Diagram** shows the **wiring** and **connections** of each individual logic gate.
  - 2) **Boolean Expression** is an expression in Boolean algebra that represents the logic circuit.
  - 3) **Truth Table** provides a concise list that shows all the output states for each possible combination of inputs

**Logic/Schematic Diagram**

 


```
architecture com_arch of comb is
  signal X, Y: std_logic;
begin
  X <= not (A and B);
  Y <= not (A or B);
  Q <= (X and C) and Y;
end com_arch;
```

# Modeling Combinational Circuit (2/3)



- Typical ways for modeling a combinational circuit:
  - 1) **Logic/Schematic Diagram** shows the wiring and connections of each individual logic gate.
  - 2) **Boolean Expression** is an **expression** in Boolean algebra that represents the logic circuit.
  - 3) **Truth Table** provides a concise list that shows all the output states for each possible combination of inputs

Logic/Schematic Diagram

 

Boolean Expression

$$Q = \overline{(A \cdot B)} \cdot \overline{(A + B)} \cdot C$$

```
architecture com_arch of comb is  
begin
```

```
    Q <= (not (A and B)) and  
        (not (A or B)) and C;
```

```
end com_arch;
```

# Modeling Combinational Circuit (3/3)



- Typical ways for modeling a combinational circuit:
  - 1) **Logic/Schematic Diagram** shows the wiring and connections of each individual logic gate.
  - 2) **Boolean Expression** is an expression in Boolean algebra that represents the logic circuit.
  - 3) **Truth Table** provides a **concise list** that shows all the output states for each possible combination of inputs

A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

```
process (A, B, C)
begin
  if( A = '0' and B = '0' and C = '1' ) then
    Q <= '1';
  else
    Q <= '0';
  end if;
end process;
```

# Comb. Circuit Example: Decoder (1/2)



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity decoder_ex is
port (in0,in1: in std_logic;
      out00,out01,out10,out11: out std_logic);
end decoder_ex;
architecture decoder_ex_arch of decoder_ex is
begin
  process (in0, in1)
  begin
```

```
    if in0 = '0' and in1 = '0' then
      out00 <= '1';
    else
      out00 <= '0';
    end if;
    if in0 = '0' and in1 = '1' then
      out01 <= '1';
    else
      out01 <= '0';
    end if;
```

in	in	out	out	out	out
0	1	00	01	10	11
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

# Comb. Circuit Example: Decoder (2/2)



...

```
if in0 = '1' and in1 = '0' then
  out10 <= '1';
else
  out10 <= '0';
end if;
if in0 = '1' and in1 = '1' then
  out11 <= '1';
else
  out11 <= '0';
end if;
```

```
end process;
end decoder_ex_arch;
```

in	in	out	out	out	out
0	1	00	01	10	11
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1



# Class Exercise 3.1

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_


- Re-implement the 2-to-4 decoder by referring the provided schematic diagram:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity decoder_ex is
    port( in0,in1: in std_logic;
          out00,out01,out10,out11:
            out std_logic);
```

```
end decoder_ex;
architecture decoder_ex_arch of
decoder_ex is
begin
```

```
end decoder_ex_arch;
```

in	in	out	out	out	out
0	1	00	01	10	11
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

# Comb. Circuit Example: Multiplexer



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity mux_ex is
port (in1,in2,sel: in std_logic;
      out1: out std_logic);
end mux_ex;
architecture mux_ex_arch of mux_ex is
begin
  process (in1, in2, sel)
  begin
    if sel = '0' then
      out1 <= in1; -- select in1
    else
      out1 <= in2; -- select in2
    end if;
  end process;
end mux_ex_arch;
```

sel	in1	in2	out1
0	0	0	0
	0	1	0
	1	0	1
	1	1	1
1	0	0	0
	0	1	1
	1	0	0
	1	1	1


# Class Exercise 3.2

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_


Name: \_\_\_\_\_

- Specify the I/O signals in the schematic diagram:
 
```
entity mux_ex is
port (in1,in2,sel: in std_logic;
      out1: out std_logic);
end mux_ex;
architecture mux_ex_arch of mux_ex is
begin
  process (in1, in2, sel)
  begin
    if sel = '0' then
      out1 <= in1; -- select in1
    else
      out1 <= in2; -- select in2
    end if;
  end process;
end mux_ex_arch;
```



# Recall: Tri-state Buffer

 


in1	enable	out1
0	0	Z
1	0	Z
0	1	0
1	1	1

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity tri_ex is
port (in1, enable: in std_logic;
      out1: out std_logic);
end tri_ex;
architecture tri_ex_arch of tri_ex is
begin
    out1 <= in1 when enable = '1' else 'Z';
end tri_ex_arch;
```



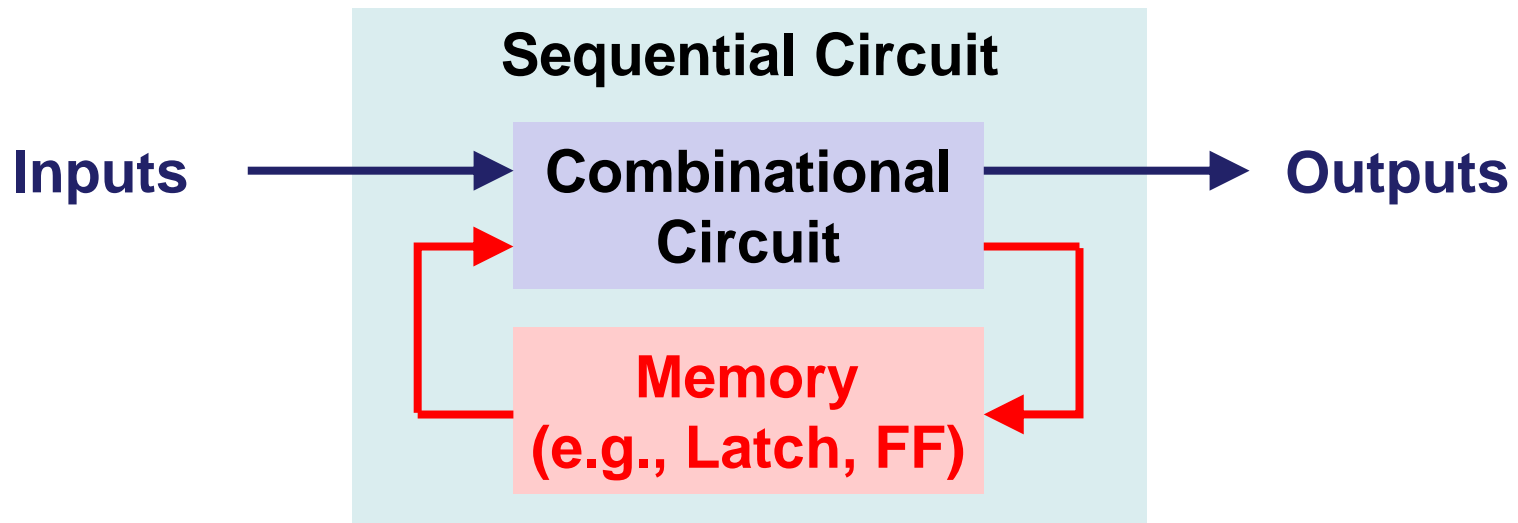
- **Combinational Circuit: no memory**
  - Outputs depend on the *present* inputs only.
  - **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
  - Outputs depend on *present* inputs and *previous* outputs.
  - **Rule: MUST** use sequential statements (i.e., `process`).


 
# Sequential Circuit




- **Sequential Circuit: has memory**
  - Outputs depend on present inputs and previous outputs.
    - The previous output(s) are kept in the **memory device(s)** and treated as the **present state**.
    - Two most common **memory devices**: **Latch** and **Flip-flop (FF)**, both can hold one bit of data (i.e., either low or high).
  - **Rule**: You **MUST** build a sequential circuit with **only sequential statements** (i.e., statements inside `process`).


 
# Memory Device: Latch



- Latch has **no** CLOCK signal.
  - It changes the output only in response to the input.
- **Case Study: D Latch**
  - When enable signal C is high, the output Q follows input D.
  - That is why D latch is also called as transparent latch.
    - When enable line C is asserted, the latch is said to be transparent.
  - When C falls, the last state of D is held (i.e., has memory)!




C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

<https://www.edgefx.in/digital-electronics-latches-and-flip-flops/>
 
# D Latch in VHDL



```
1 library IEEE;--(ok vivado 2014.4)
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity latch_ex is
4 port (C, D: in std_logic;
5       Q: out std_logic);
6 end latch_ex;
7 architecture latch_ex_arch of latch_ex is
8 begin
9     process(C, D) -- sensitivity list
10    begin
11        if ( C = '1' ) then
12            Q <= D;
13        end if;
14        -- no change (memory)
15    end process;
16 end latch_ex_arch;
```



C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state



# Class Exercise 3.3


Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

- Given a D latch, draw Q in the following figure:



Q

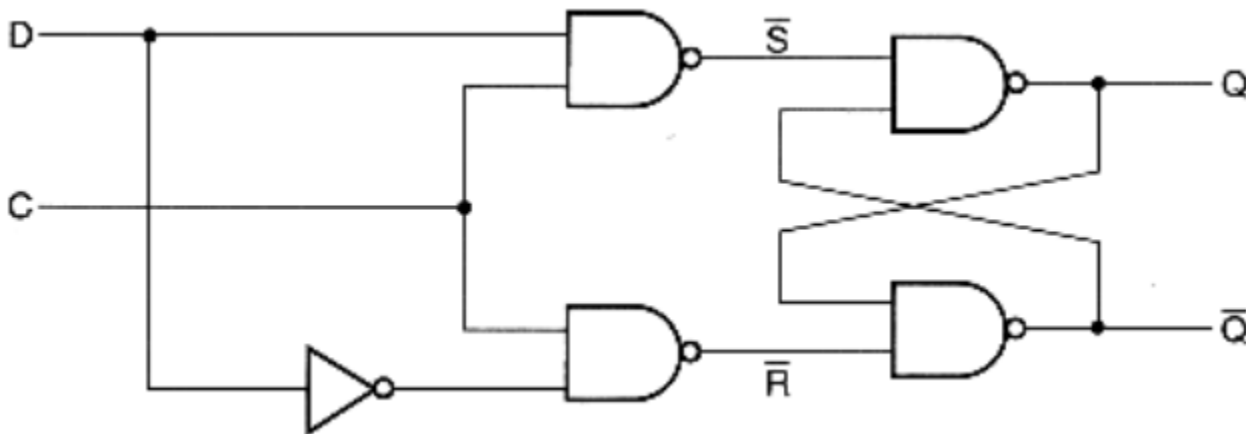


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

 
# Memory Device: Flip-flop (FF)



- Flip-flop **has** a clock signal (i.e., **CLK**).
  - It changes the output only at clock edges.




 - **Positive-Edge-Triggered**: At every **low to high** of CLOCK.
- **Negative-Edge-Triggered**: At every **high to low** of CLOCK.


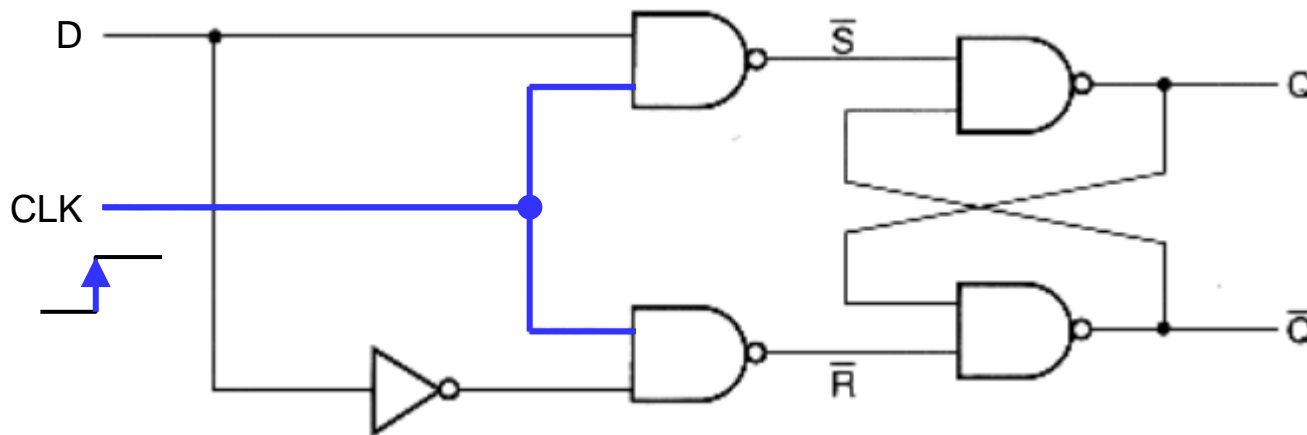
## • Case Study: Positive-Edge-Triggered D Flip Flop

- Whenever the clock rises, the output Q follows input D.
- Otherwise, the last state of D is held (i.e., has memory)!
- The held value can be **reset** asynchronously (i.e., anytime) or synchronously (i.e., only at clock edges).



CLK	D	Q <sub>next</sub>
<i>rising</i>	0	0
	1	1
<i>non-rising</i>	X	Q




# D Flip-flop with Async. Reset in VHDL

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity DFF_ASYNC is
4 port (D, CLK, RESET: in std_logic;
5       Q: out std_logic);
6 end dff_async;
7 architecture DFF_ASYNC_ARCH of DFF_ASYNC is
8 begin
9   process (CLK, RESET) -- sensitivity list
10  begin
11    if (RESET = '1') then
12      Q <= '0'; -- Reset Q anytime
13    elsif CLK = '1' and CLK'event then
14      Q <= D; -- Q follows input D
15    end if;
16    -- no change (so has memory)
17  end process;
18 end DFF_ASYNC_ARCH;

```

 


← Positive-edge-triggered
 
# Attribute



- An **attribute** provides information about items such as entities, architecture, signals, and types.
  - The syntax is an apostrophe ( ' ) and the attribute name.
  - There are several useful predefined value, signal, and range attributes (see [VHDL Predefined Attributes](#)).
- An important signal attribute is the **'event**.
  - This attribute yields a Boolean value of **TRUE** if an event has just occurred on the signal.
  - It is used primarily to determine if a **clock** has transitioned (i.e., either low-to-high or high-to-low).




`CLK = '1' and CLK'event`

# Class Exercise 3.4

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

 - Given a Positive-edge-triggered D Flip-flop with **async.** reset, draw the output Q.






# D Flip-flop with Sync. Reset in VHDL

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity DFF_SYNC is
4 port (D, CLK, RESET: in std_logic;
5       Q: out std_logic);
6 end DFF_SYNC;
7 architecture DFF_SYNC_ARCH of DFF_SYNC is begin

```

 

```

8   process (CLK) ← shall we put RESET in the sensitivity list?
9   begin

```

```

10      if CLK = '1' and CLK'event then
11          if (RESET = '1') then
12              Q <= '0'; -- Reset Q at edges
13          else
14              Q <= D; -- Q follows input D
15          end if;
16      end if;

```

Positive-edge-triggered ←

```

-- no change (so has memory)

```

```

17   end process;
18 end DFF_SYNC_ARCH;


```

# Class Exercise 3.5

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

 - Given a Positive-edge-triggered D Flip-flop with **sync.** reset, draw the output Q.



# Async. Reset vs. Sync. Reset (1/2)



- The order of the statements inside the process determines **asynchronous reset** or **synchronous reset**.

- **Asynchronous Reset** (check **RESET** first!)


```
11     if (RESET = '1') then
12         Q <= '0'; -- Reset Q anytime
13     elsif CLK = '1' and CLK'event then
14         Q <= D; -- Q follows input D
15     end if;
```

- **Synchronous Reset** (check **CLK** first!)

```
10     if CLK = '1' and CLK'event then
11         if (RESET = '1') then
12             Q <= '0'; -- Reset Q at edges
13         else
14             Q <= D; -- Q follows input D
15         end if;
16     end if;
```



# Async. Reset vs. Sync. Reset (2/2)

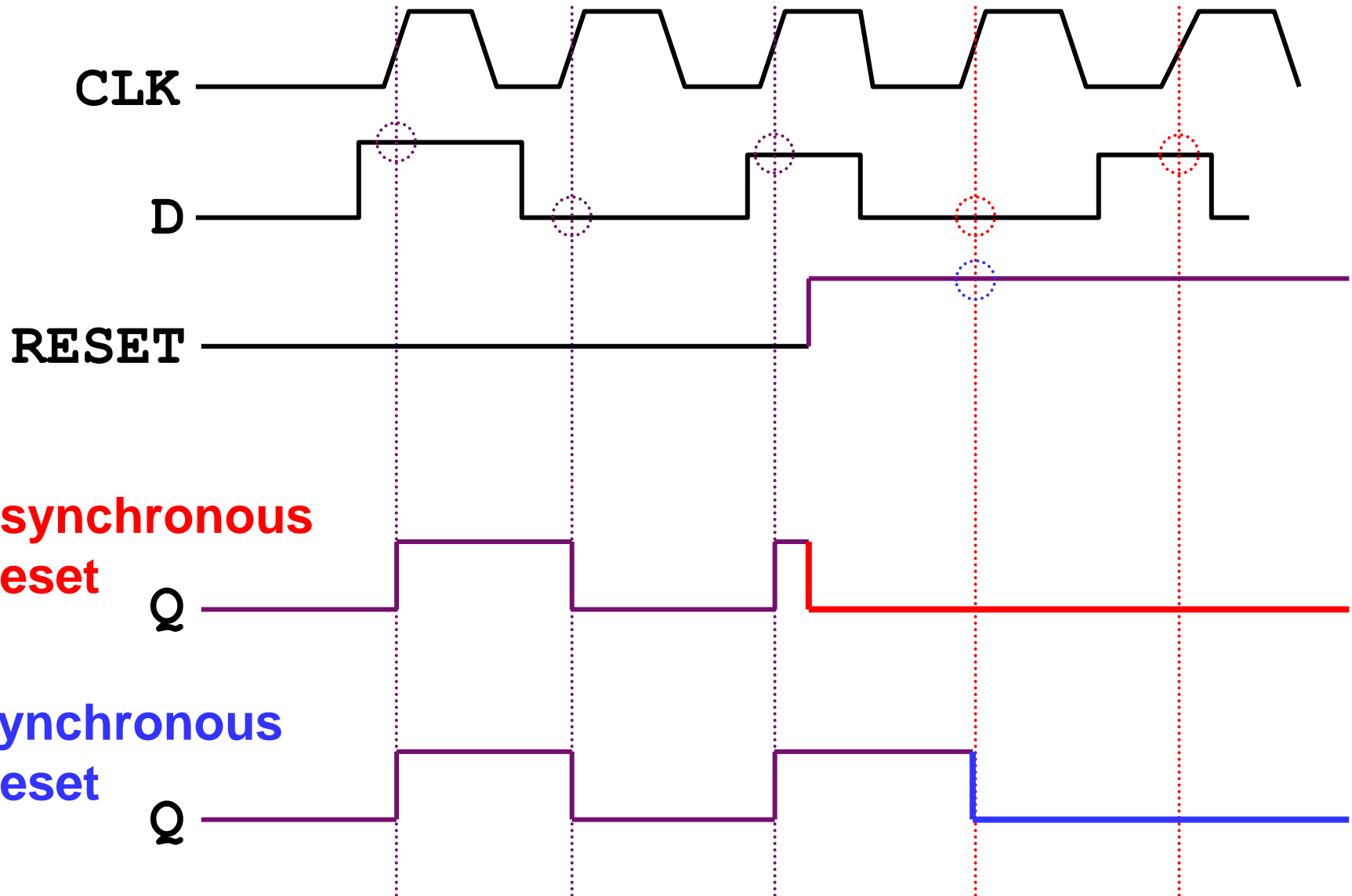

**Asynchronous  
Reset**

Q

**Synchronous  
Reset**

Q

# Latch vs. Flip-flop (FF)




- Latch and Flip-flop (FF) are both typical **memory devices** which can store one bit of data.
- Their major difference is that:
  - Latch has **no** clock signal and is **level-triggered**.
    - The output of a latch can be changed only when the **level of enable signal C** is high.
  - FF **has** a clock signal and is **edge-triggered**.
    - The output of an FF can only be changed whenever the clock signal goes from low to high and high to low (i.e., **clock edges**).
- FF can be found in a wide range of sequential circuits where time plays an essential role.
  - Common examples are **shift registers** (Lab03), **counters** (Lab04), **frequency divider circuits** (Lab04), etc.

# Seq. Circuit Example: Shift Register



- A **register** is a device that can be composed of a group of FFs to store multiple bits of data.
- A **shift register** allows the stored data being moved from one FF to another.
  - There are basically **four** types: ① Serial-In-Serial-Out (SISO), ② Serial-In-Parallel-Out (SIPO), ③ Parallel-In-Serial-Out (PISO), and ④ Parallel-In-Parallel-Out (PIPO).

## Ex: SIPO

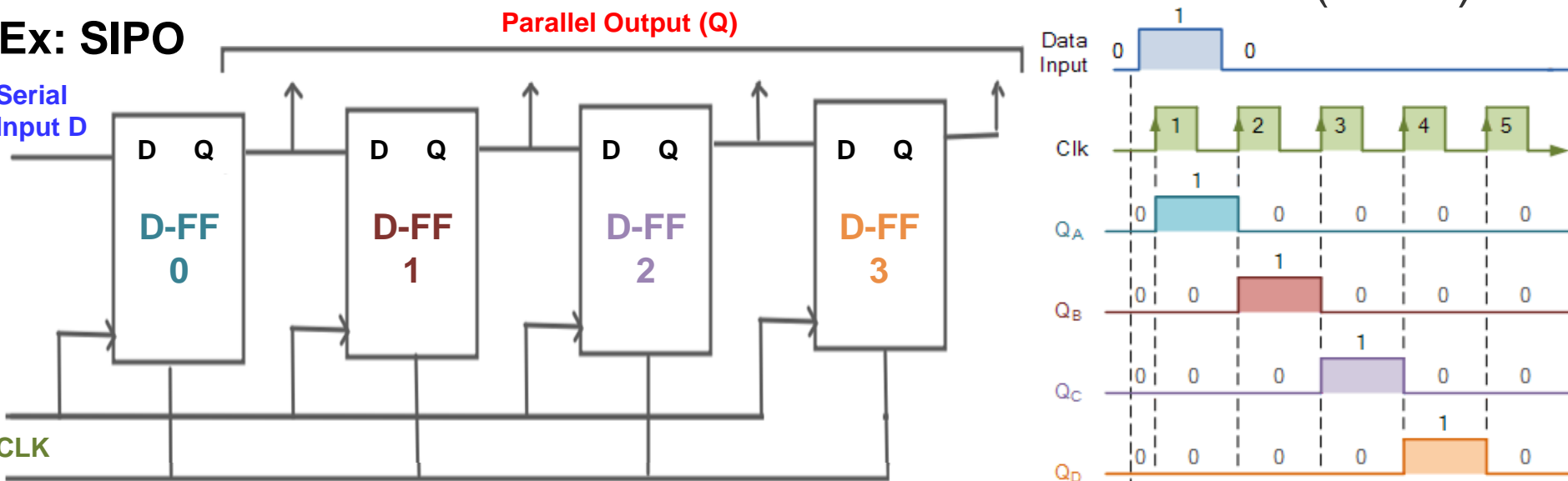

# SIPO Shift Register in VHDL



```
entity SIPO_ASYNC is
  port (D, CLK, RST : IN STD_LOGIC;
        Q : OUT STD_LOGIC_VECTOR(3 downto 0) );
end SIPO_ASYNC;
architecture SIPO_ASYNC_ARCH of SIPO_ASYNC is
```

```
  component DFF_ASYNC is
    port(D, clk, reset : in STD_LOGIC;
          Q : out STD_LOGIC );
  end component;
```

```
  signal dout : STD_LOGIC_VECTOR(3 downto 0); ← necessary?
```

```
begin
  DFF0: DFF_ASYNC port map(D, CLK, RST, dout(0));
  DFF1: DFF_ASYNC port map(dout(0), CLK, RST, dout(1));
  DFF2: DFF_ASYNC port map(dout(1), CLK, RST, dout(2));
  DFF3: DFF_ASYNC port map(dout(2), CLK, RST, dout(3));
```

```
  Q <= dout;
end SIPO_ASYNC_ARCH;
```

# Summary



- **Combinational Circuit: no memory**
  - Outputs depend on the *present* inputs only.
  - **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
  - Outputs depend on *present* inputs and *previous* outputs.
  - **Rule: MUST** use sequential statements (i.e., `process`).

