



香港中文大學

The Chinese University of Hong Kong

CENG3430 Rapid Prototyping of Digital Systems

Lecture 04:


Finite State Machine

Ming-Chang YANG

mcyang@cse.cuhk.edu.hk

Recall: Comb. vs. Seq. Circuits (Lec03)

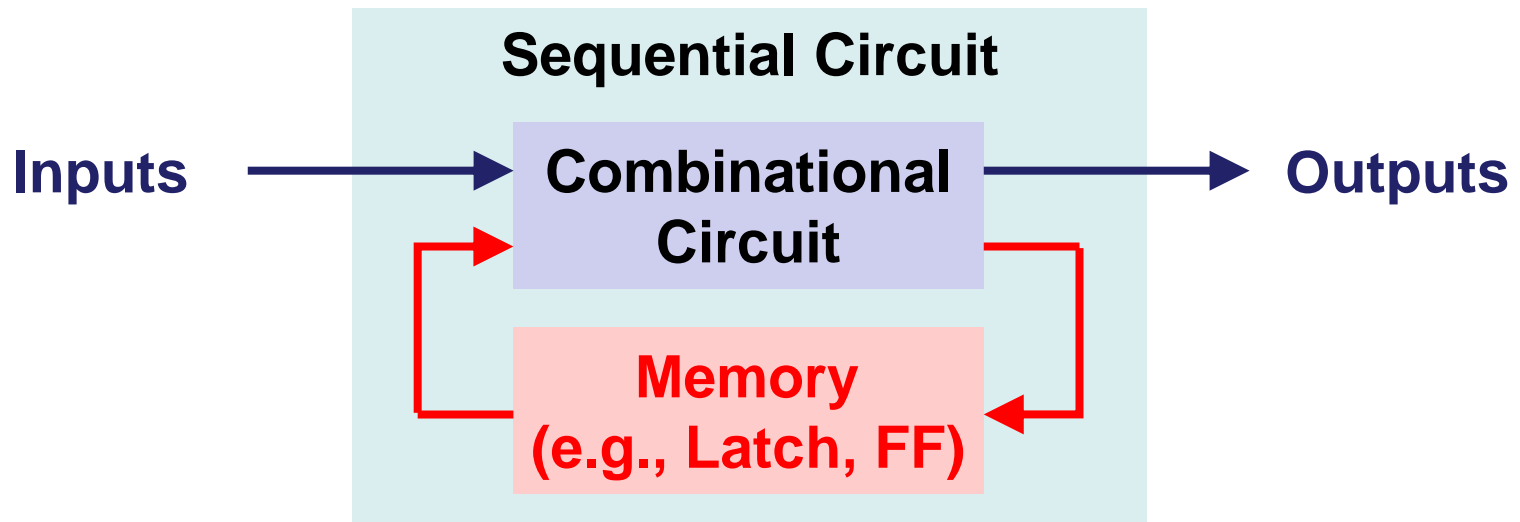- **Combinational Circuit: no memory**
 - Outputs depend on the *present* inputs only.
 - **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
 - Outputs depend on *present* inputs and *previous* outputs.
 - **Rule: MUST** use sequential statements (i.e., `process`).



Recall: SIPO Shift Register (Lab03)



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity SIPO_ASYNC is
    port(D, CLK, RST : IN STD_LOGIC;
         Q : OUT STD_LOGIC_VECTOR(3 downto 0) );
end SIPO_ASYNC;
architecture SIPO_ASYNC_ARCH of SIPO_ASYNC is
    component DFF_ASYNC is
        port(D, clk, reset : in STD_LOGIC;
             Q : out STD_LOGIC );
    end component;
```


```
    signal dout : STD_LOGIC_VECTOR(3 downto 0);
```

```
begin
```

```
    DFF0: DFF_ASYNC port map
        (D, CLK, RST, dout(0));
    DFF1: DFF_ASYNC port map
        (dout(0), CLK, RST, dout(1));
    DFF2: DFF_ASYNC port map
        (dout(1), CLK, RST, dout(2));
    DFF3: DFF_ASYNC port map
        (dout(2), CLK, RST, dout(3));
```

```
    Q <= dout;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity DFF_ASYNC is
    port(D, CLK, RESET: in std_logic;
         Q: out std_logic);
end DFF_ASYNC;
architecture DFF_ASYNC_ARCH of DFF_ASYNC is
begin
    process(CLK, RESET) -- sensitivity list
    begin
        if (RESET = '1') then
            Q <= '0'; -- Reset Q anytime
        elsif CLK = '1' and CLK'event then
            Q <= D; -- Q follows input D
        end if;
    end process;
end DFF_ASYNC_ARCH;
```

 


Can we model a sequential circuit in a more “abstract” way?

Recall: SIPO Shift Register (Lab03)



 - Bind the I/O ports and physical pins as following:
 - Input: **clk=SW7**, reset=SW6, D=SW0
 - Output: Q0~Q3=LD0~LD3



How to use a “real” clock?





- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- FSM Types
- Rule of Thumb: FSM Coding Tips
- FSM Examples
 - Up/Down Counter
 - Pattern Generator
- Use of Real Clock
 - Clock Sources of ZedBoard
 - Clock Divider

Finite State Machine (FSM)



  - **Finite State Machine (FSM)** is an abstract model of a sequential circuit that jumps from one state to another within a finite pool of states.
- Real-life Example of FSM: Traffic light



- Two crucial factors of FSM:

① **time controlling** and ② **state maintenance**


① Time Controlling



- Both “**wait until**” and “**if**” statements can be used to detect the clock edge (e.g., **CLK**):


- “**wait until**” statement:

 - **wait until** CLK = '1'; -- rising edge
- **wait until** CLK = '0'; -- falling edge




- “**if**” statement:

 - **if** CLK'event and CLK = '1' -- rising edge
- **if** CLK'event and CLK = '0' -- falling edge



OR

 - **if**(rising_edge (CLK)) -- rising edge
- **if**(falling_edge (CLK)) -- falling edge



When to use “wait until” or “if”? (1/2)

- **Synchronous Process:** Computes values only on clock edges (i.e., only sensitive/sync. to clock signal).
 - **Rule:** Use “**wait-until**” or “**if**” for **synchronous** process:

```
process ← NO sensitivity list implies that there is one clock signal.  
begin
```

Usage
of
“wait
until”

```
    wait until clk='1' ; ← The first statement must be wait until.  
    ...  
end process
```

*Note: IEEE VHDL requires that a process with a wait statement must not have a sensitivity list, and the first statement must be **wait until**.*

```
process (clk) ← The clock signal must be in the sensitivity list.  
begin
```

Usage
of
“if”

```
    ...  
    if ( rising_edge (clk) ) ← NOT necessary to be the first line.  
    ...  
end process
```


When to use “wait until” or “if”? (2/2)

- **Asynchronous Process:** Computes values on clock edges or when asynchronous conditions are TRUE.
 - That is, it must be sensitive to the clock signal (if any), and to all inputs that may affect the asynchronous behavior.
 - **Rule:** Only use “**if**” for **asynchronous** process:

```
process (clk, input_a, input_b, ...) ← The sensitivity list
begin
  ...
  if ( rising_edge (clk) )
  ...
end process
```

← The sensitivity list should include the clock signal, and all inputs that may affect asynchronous behavior.

Usage
of
“if”


Use “if” statement for both sync. and async. processes!

CLK'event VS. rising_edge (CLK) (1/2)

- Both “**wait until**” and “**if**” statements can be used to detect the clock edge (e.g., CLK):


- “**wait until**” statement:
 
```
- wait until CLK = '1'; -- rising edge  
- wait until CLK = '0'; -- falling edge
```




- “**if**” statement:
 
```
- if CLK'event and CLK = '1' -- rising edge  
- if CLK'event and CLK = '0' -- falling edge
```



OR
 
```
- if( rising_edge (CLK) ) -- rising edge  
- if( falling_edge (CLK) ) -- falling edge
```



CLK'event VS. rising_edge (CLK) (2/2)

- **rising_edge()** function in std_logic_1164 library


```
FUNCTION rising_edge (SIGNAL s : std_ulogic) RETURN BOOLEAN IS
BEGIN
    RETURN (s'EVENT AND (To_X01(s) = '1') AND
            (To_X01(s'LAST_VALUE) = '0'));
END;
```

- It results **TRUE** when there is an edge transition in the signal s, the present value is '1' and the last value is '0'.
 - If the last value is something like 'z' or 'U', it returns a **FALSE**.
- The statement (**clk'event** and **clk='1'**)
 - It results **TRUE** when there is an edge transition in the clk and the present value is '1'.
 - *It does not see whether the last value is '0' or not.*


Use rising/falling_edge() with “if” statement!

② State Maintenance

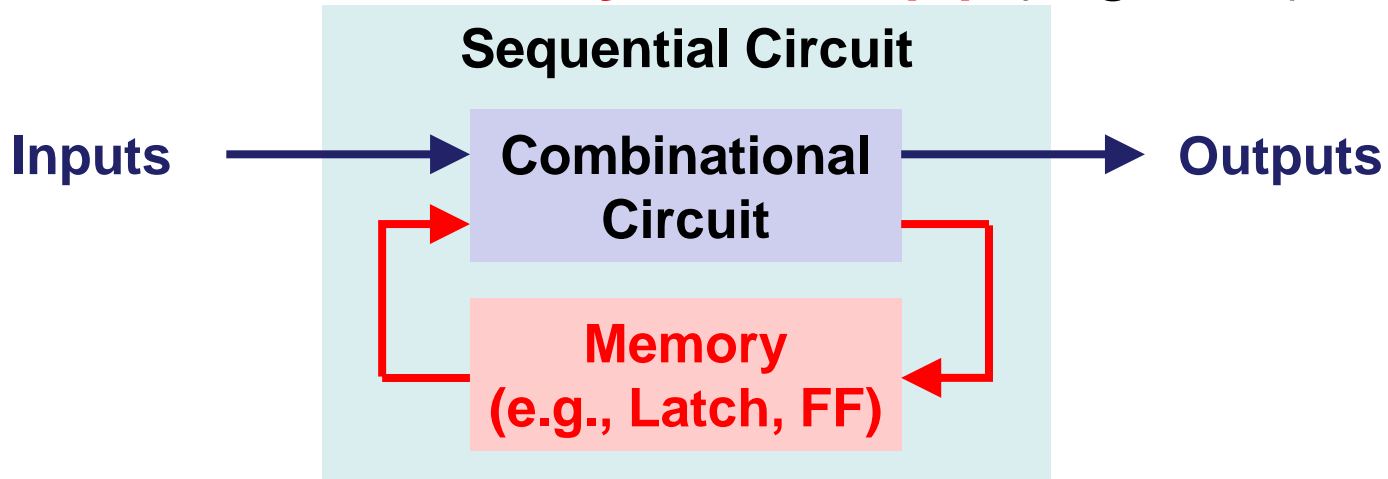- **Method 1:** Use **memory device(s)** (e.g., FF)



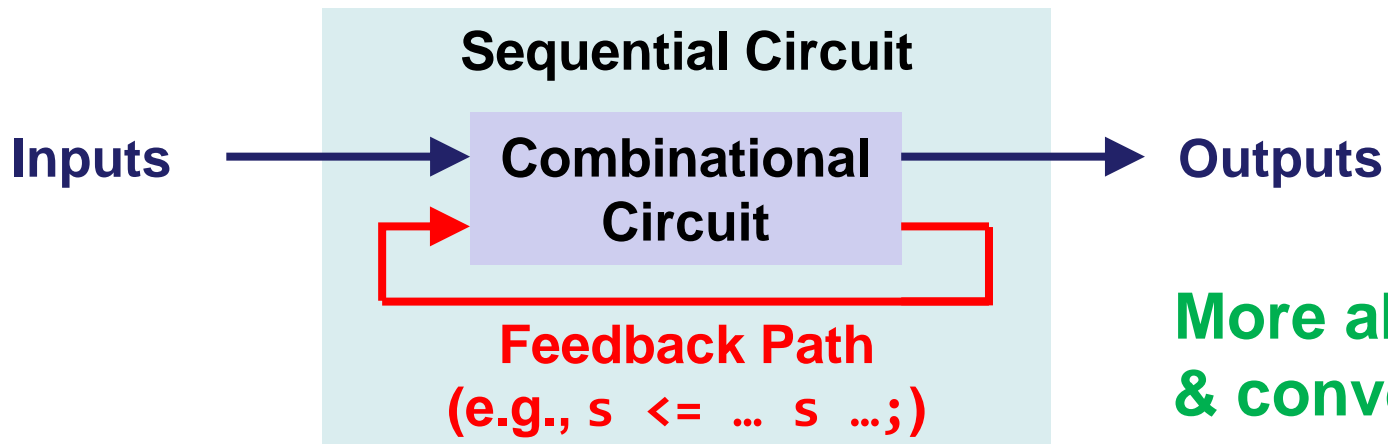
- **Method 2:** Form **feedback path(s)** in a clocked process (i.e., a process triggered by a clock)



**More abstract
& convenient!**

② State Maintenance
 
```
entity Method_1 is -- use D-FF
  port(D, CLK, RST : IN STD_LOGIC;
       Q : OUT STD_LOGIC );
end Method_1;
architecture Arch of Method_1 is
  component DFF_ASYNC is
    port(D, clk, reset : in STD_LOGIC;
         Q : out STD_LOGIC );
  end component;
  signal din, dout: STD_LOGIC;
begin
  din <= not ( D and dout );
  DFF_ASYNC port map(din,CLK,RST,dout);
  Q <= dout; -- output
end Arch;
```



```
entity Method_2 is -- form feedback path
  port(D, CLK, RST : IN STD_LOGIC;
       Q : OUT STD_LOGIC );
end Method_2;
architecture Arch of Method_2 is
  signal s: STD_LOGIC; -- state
begin
  process(CLK, RST) begin
    if (RST = '1') then
      s <= '0'; -- Async. reset s
    elsif rising_edge(CLK) then
      s <= not ( D and s ); -- feedback
    end if;
  end process; -- clocked process
  Q <= s; -- output
end Arch;
```

Signal **s** (i.e., state) forms a **feedback path** in a clocked process!

- **s** holds for one clock cycle.
- $\text{not}(D \text{ and } s)$ takes effect at the next edge.
- \leftarrow here can be treated as a flip-flop!




- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- **FSM Types**
- Rule of Thumb: FSM Coding Tips
- FSM Examples
 - Up/Down Counter
 - Pattern Generator
- Use of Real Clock
 - Clock Sources of ZedBoard
 - Clock Divider





- **Moore Machine:**

 - **Outputs** rely on the present **state** only.



- **Mealy Machine:**

  - **Outputs** rely on both the present **state** and **inputs**.



Example: An FSM that outputs a '0' (resp. to '1') if an even (resp. to odd) number of 1's have been received.

Moore Machine



- **Moore Machine:** *Outputs* rely on *present state* only.

architecture moore_arch of fsm is

```
signal s: std_logic; -- internal state
```

```
begin
```

```
process (s)
```

Combinational Logic

```
begin
```

```
OUTX <= s; -- output
```

```
end process;
```

```
process (CLOCK, RESET)
```

Sequential Logic

```
begin
```

```
if RESET = '1' then s <= '0';
```

```
elsif rising_edge(CLOCK) then
```

```
s <= INX xor s; -- feedback
```

```
end if;
```

```
end process;
```

```
end moore_arch;
```


Mealy Machine



- **Mealy Machine:** *Outputs* rely on both *state* and *inputs*.

architecture mealy_arch of fsm is

```
signal s: std_logic; -- internal state
```

```
begin
```

```
process (s, INX)
```

Combinational Logic

```
begin
```

```
    OUTX <= INX xor s; -- output
```

```
end process;
```

```
process (CLOCK, RESET)
```

Sequential Logic

```
begin
```

```
    if RESET = '1' then s <= '0';
```

```
    elsif rising_edge(CLOCK) then
```

```
        s <= INX xor s; -- feedback
```

```
    end if;
```

```
end process;
```

```
end mealy_arch;
```



- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- FSM Types
- **Rule of Thumb: FSM Coding Tips**
- FSM Examples
 - Up/Down Counter
 - Pattern Generator
- Use of Real Clock
 - Clock Sources of ZedBoard
 - Clock Divider

Rule of Thumb: FSM Coding Tips



- ① **Maintain the internal state(s) explicitly**
- ② **Separate combinational and sequential logics**
 - Write **at least two processes**: one for combinational logic, and the other for sequential logic
 - Maintain the **internal state(s)** using a sequential process
 - Drive the **output(s)** using a combination process
- ③ **Keep every process as simple as possible**
 - Partition a large process into **multiple small ones**
- ④ **Put every signal** (that your process must be sensitive to its changes) **in the sensitivity list.**
- ⑤ **Avoid assigning a signal from multi-processes**
 - It may cause the “**multi-driven**” issue.





- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- FSM Types
- Rule of Thumb: FSM Coding Tips
- **FSM Examples**
 - Up/Down Counter
 - Pattern Generator
- Use of Real Clock
 - Clock Sources of ZedBoard
 - Clock Divider

FSM Example 1) Up/Down Counter (1/3)

- **Up/Down Counter:** Generates a sequence of up/down counting patterns.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.Numeric_Std.ALL;
entity counter is
    port(
        CLK: in std_logic;
        RESET: in std_logic;
        COUNT: out std_logic_vector
            (3 downto 0) );
end counter;
architecture counter_arch of counter
is
    signal s: std_logic_vector(3 downto
0) := "0000"; -- state
```

```
begin
```

```
    process(CLK, RESET)
    begin
        if(RESET = '1') then s <= "0000";
        else
            if( rising_edge(CLK) ) then
                s <= std_logic_vector(
                    unsigned(s)+1); -- feedback
            end if;
        end if;
    end process;
```

Sequential Logic

Combinational Logic

```
COUNT <= s; -- Moore Machine
```


```
end counter_arch;
```

FSM Example 1) Up/Down Counter (2/3)

```
use IEEE.Numeric_Std.ALL;  
signal s: std_logic_vector(3 downto 0) := "0000"; -- state  
s <= std_logic_vector(unsigned(s)+1); -- feedback
```

- A `std_logic_vector` is merely a collection of `std_logic`.
 - The individual positions have no predefined meaning.
- The IEEE NUMERIC_STD package includes **overloading functions** for data types that are more convenient to use.
 - Such as **unsigned/signed** types and **integer** type.
- VHDL is a strongly-typed language.
 - Signals of different types **CANNOT** be assigned to each other without using **type casting/conversion**.

FSM Example 1) Up/Down Counter (3/3)

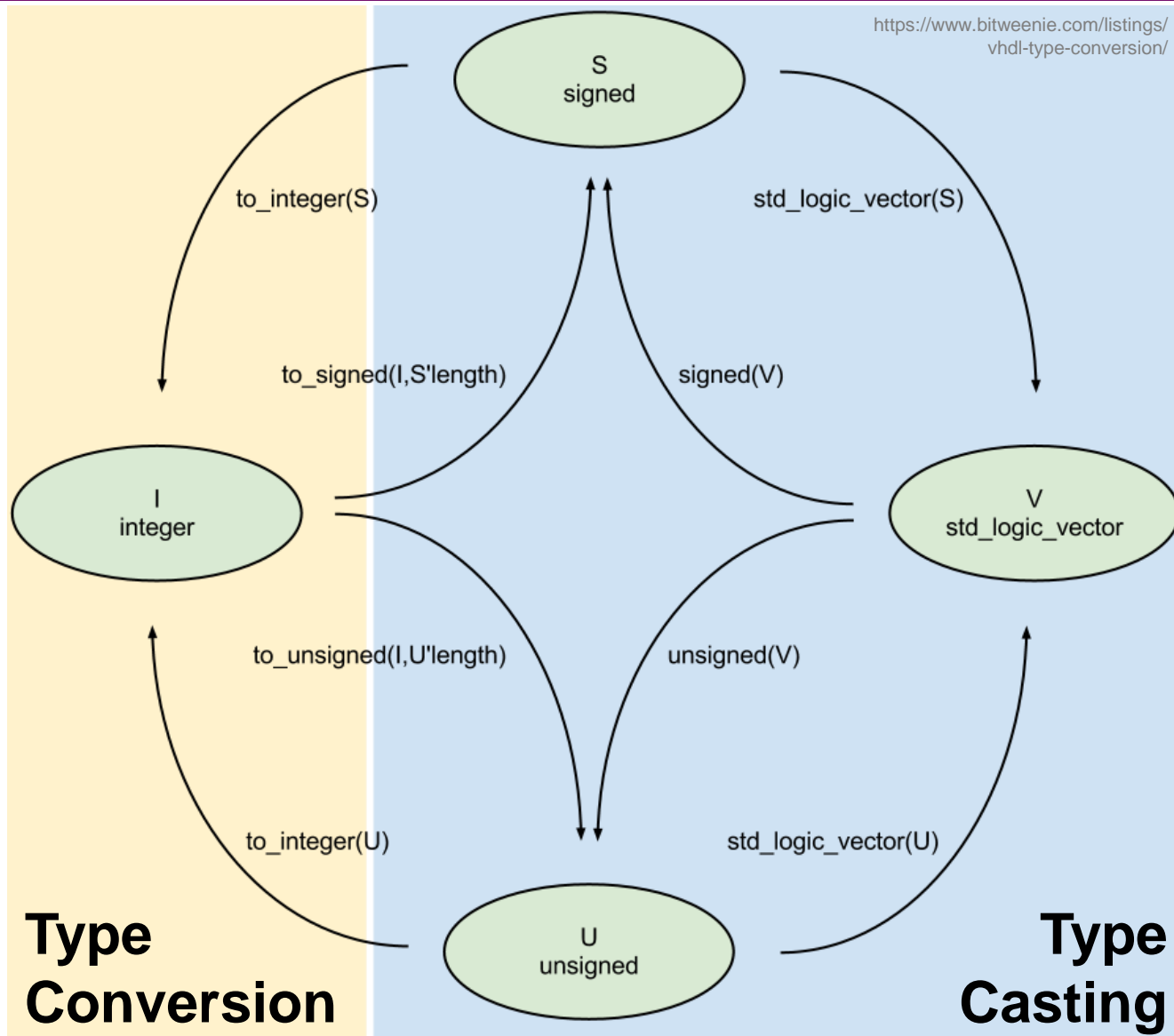

Remember to “use `IEEE.Numeric_Std.ALL`”!

Class Exercise 4.1

Student ID: _____ Date: _____
Name: _____

- Complete the counter FSM by filling in the missing line if the state is declared as an **unsigned** type:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.Numeric_Std.ALL;
entity counter is
    port(
        CLK: in std_logic;
        RESET: in std_logic;
        COUNT: out std_logic_vector
            (3 downto 0) );
end counter;
architecture counter_arch of counter
is
    signal s: unsigned(3 downto 0) :=
        "0000"; -- state
```

begin

```
process(CLK, RESET)
begin
    if(RESET = '1') then s <= "0000";
    else
        if( rising_edge(CLK) ) then
            s <= s + 1; -- feedback
        end if;
    end if;
end process;
```

**Sequential
Logic**

Combinational Logic

end counter_arch;

Class Exercise 4.2

Student ID: _____ Date: _____
Name: _____

- Complete the counter FSM by filling in the missing line if the state is declared as an **integer** type:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.Numeric_Std.ALL;
entity counter is
    port(
        CLK: in std_logic;
        RESET: in std_logic;
        COUNT: out std_logic_vector
            (3 downto 0) );
end counter;
architecture counter_arch of counter
is
    signal s: integer range 0 to 15
        := 0; -- state
begin
```

```
process(CLK, RESET)
begin
    if(RESET = '1') then s <= "0000";
    else
        if( rising_edge(CLK) ) then
            s <= s + 1; -- feedback
        end if;
    end if;
end process;
```

Combinational Logic

```
end counter_arch;
```

Integer Type




- An **integer type** can be defined with or without specifying a range.
 - If a range is not specified, VHDL allows integers to have a minimum range of
 - $-2,147,483,647$ to $2,147,483,647$
 - $-(2^{31} - 1)$ to $(2^{31} - 1)$
 - Or a range can be specified, e.g.,

```
signal int: integer range 0 to 255;
```

FSM Example 2) Pattern Generator (1/2)

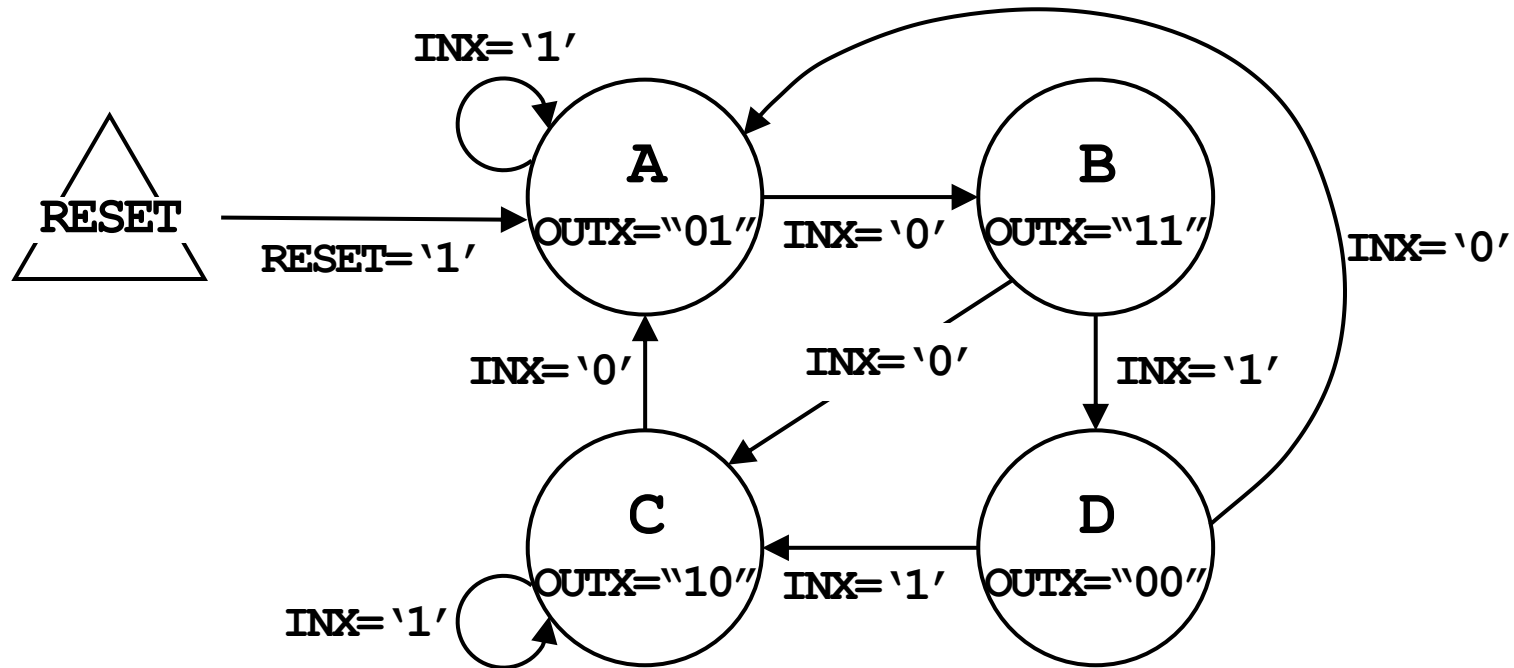- **Pattern Generator:** Generates **any pattern** we want.
- Given the following machine of 4 states: **A**, **B**, **C** and **D**.



- The machine has an asynchronous **RESET**, a clock signal **CLK**, and a 1-bit synchronous input signal **INX**.
- The machine also has a 2-bit output signal **OUTX**.

FSM Example 2) Pattern Generator (2/2)

```
library IEEE;
use IEEE.std_logic_1164.all;
entity pat_gen is port(
RESET,CLOCK,INX: in STD_LOGIC;
OUTX: out STD_LOGIC_VECTOR(1
downto 0));
end pat_gen;
architecture arch of pat_gen is
type state_type is (A,B,C,D);
signal s: state_type; -- state
begin
process(CLOCK, RESET)
begin
if RESET = '1' then
s <= A;
elsif rising_edge(CLOCK) then
-- feedback
case s is
when A =>
if INX = '1' then s <= A;
else s <= B; end if;
```

**Sequential
Logic**

```
when B =>
if INX = '1' then s <= D;
else s <= C; end if;
when C =>
if INX = '1' then s <= C;
else s <= A; end if;
when D =>
if INX = '1' then s <= C;
else s <= A; end if;
end case;
end if;
end process;
process(s)
begin
case s is
when A => OUTX <= "01";
when B => OUTX <= "11";
when C => OUTX <= "10";
when D => OUTX <= "00";
end case;
end process; -- Moore Machine
end arch;
```

**Combinational
Logic**

Enumeration Type



- An **enumeration type** introduces abstraction into circuits by allowing users defining a list of values.

- Example:

```
type colors is (RED, GREEN, BLUE);  
signal my_color: colors;
```

- An enumerated type is **ordered**.

- The order in which the values are listed in the type declaration defines their relation:

*Each values is greater than the one to the left,
and less than the one to the right.*

- Example: a comparison can be:

```
my_color > RED and my_color < BLUE
```

Class Exercise 4.3

Student ID: _____ Date: _____
Name: _____


- Complete the Mealy FSM that recognizes sequence "10":

architecture arch of mealy_fsm is

```

type state_type is (S0, S1);
signal s: std_logic; -- state
begin
process(CLK, RESET) -- seq
begin
if(RESET = '1') then s <= S0;
else
if( rising_edge(CLK) ) then
case s is
when S0 =>
if INX = '1' then
s <= S1; -- feedback
else
s <= S0; -- feedback
end if;

```

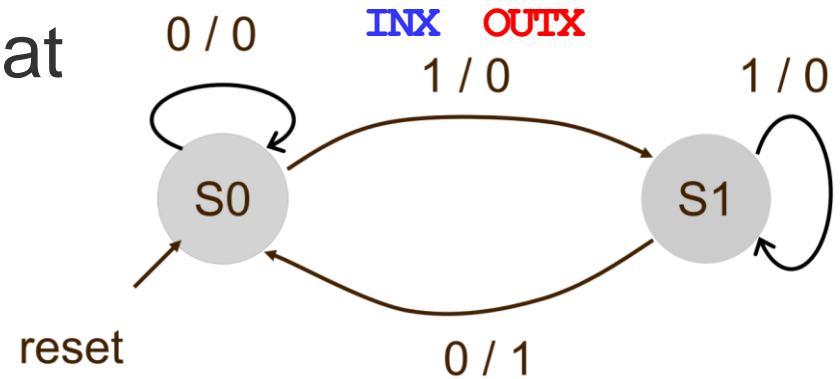

```

when S1 =>
if INX = '0' then
s <= S0; -- feedback
else
s <= S1; -- feedback
end if;
end case;
end if;
end process;
OUTX <= '1' when (s = S0 and INX = '1')
else '0'; -- Mealy
end arch;

```




- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- FSM Types
- Rule of Thumb: FSM Coding Tips
- FSM Examples
 - Up/Down Counter
 - Pattern Generator
- **Use of Real Clock**
 - Clock Sources of ZedBoard
 - Clock Divider

Clock Sources on ZedBoard (1/2)




- **Processing System**

 - PS subsystem uses a dedicated **33.3333 MHz clock source** with series termination.
 - IC18, Fox 767-33.333333-12
- PS subsystem can generate up to **four phase-locked loop (PLL) based clocks** for the PL system.



- **Programmable Logic**

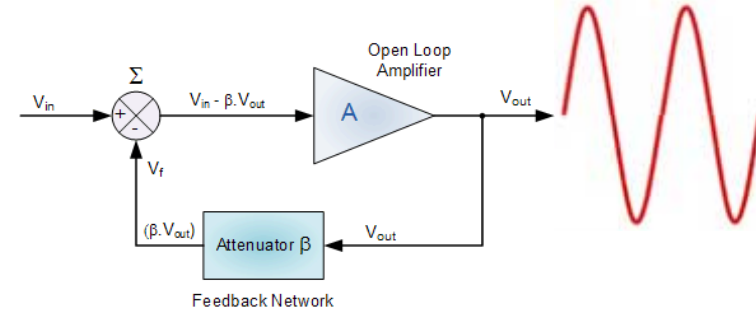- An on-board **100 MHz oscillator** supplies the PL subsystem clock input on bank 13, **pin Y9**.
 - IC17, Fox 767-100-136



Clock Sources on ZedBoard (2/2)



- To use the on-board 100 MHz clock input on bank 13, pin Y9, you need to include the following in your XDC constraint file:

```
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property PACKAGE_PIN Y9 [get_ports clk]
create_clock -period 10 [get_ports clk]
```


Note:

- The constraint *-period 10* is only used to inform the tool that clock period is 10 ns (i.e., 100 MHz).
- The constraint *-period 10* is **NOT** used specify or generate a different clock period from a given clock source.

Clock Divider (1/2)



 
- In practice, we often need clocks of **different rates**.
- Example: How to create a **1 KHz** clock from the on-board **100 MHz** oscillator (**c1k**)?




Clock Divider (2/2)



 - Trick:** If we make a counter (**count**) that counts n cycles, then we can generate a pulse (**ms_pulse**) when the counter is at any particular value n .


 
$$100 \text{ M} / 1 \text{ K} = 100,000 \times \uparrow$$



```
signal ms_pulse: STD_LOGIC:='0';
signal count: integer:=0;
process(clk)
```

```
begin
```

```
  if rising_edge(clk) then
```

```
    if (count = (50000-1)) then
```

```
      ms_pulse <= not ms_pulse;
```

```
      count <= 0; -- reset count
```

```
    else
```

```
      count <= count + 1;
```

```
    end if;
```

```
  end if;
```

```
end process;
```


ms_pulse



Class Exercise 4.4

Student ID: _____ Date: _____
Name: _____

 - Complete the code that creates a 50 Hz clock from the on-board 100 MHz oscillator (`clk`):



```
signal pulse: STD_LOGIC := '0';
signal count: integer := 0;
process(clk)
begin
  if rising_edge(clk) then
    if (count = (_____-1)) then
      pulse <= not pulse;
      count <= 0; -- reset count
    else
      count <= count + 1;
    end if;
  end if;
end process;
```

Generating Multi-Clocks (1/2)



- **Method 1: Create entity/process for each of clocks**

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.Numeric_Std.all;
entity clk_1hz is
  port( clk : in std_logic;
        clk_out : out std_logic );
end clk_1hz;
architecture arch_clk_1hz of clk_1hz is
  signal pulse : std_logic := '0';
  signal count : integer := 0;
begin
  process (clk)
  begin
    if rising_edge(clk) then
      if (count = (50000000 - 1)) then
        pulse <= not pulse;
        count <= 0; -- reset count
      else
        count <= count + 1;
      end if;
    end if;
  end process;
  clk_out <= pulse;
end arch_clk_1hz;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.Numeric_Std.all;
entity clk_4hz is
  port( clk : in std_logic;
        clk_out : out std_logic );
end clk_4hz;
architecture arch_clk_4hz of clk_4hz is
  signal pulse : std_logic := '0';
  signal count : integer := 0;
begin
  process (clk)
  begin
    if rising_edge(clk) then
      if (count = (12500000 - 1)) then
        pulse <= not pulse;
        count <= 0; -- reset count
      else
        count <= count + 1;
      end if;
    end if;
  end process;
  clk_out <= pulse;
end arch_clk_4hz;
```

Drawback: Most of the codes are redundant!

Generating Multi-Clocks (2/2)



- **Method 2: Use generic**

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.Numeric_Std.all;
entity generic_ex is
    port( clk : in std_logic );
end generic_ex;
architecture arch_generic_ex of generic_ex is
    signal clk_1, clk_4 : std_logic;
    component clock_divider is
        generic (N : integer);
        port( clk : in std_logic;
              clk_out : out std_logic );
    end component;
begin
    clk_1hz: clock_divider
        generic map (N => 50000000)
        port map(clk, clk_1);
        -- instantiation
    clk_4hz: clock_divider
        generic map(N => 12500000)
        port map(clk, clk_4);
        -- instantiation
end arch_generic_ex;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.Numeric_Std.all;
entity clock_divider is
    generic (N : integer);
    port( clk : in std_logic;
          clk_out : out std_logic );
end clock_divider;
architecture arch_clock_divider of
clock_divider is
    signal pulse : std_logic := '0';
    signal count : integer := 0;
begin
    process (clk)
    begin
        if rising_edge(clk) then
            if (count = (N - 1)) then
                pulse <= not pulse;
                count <= 0; -- reset count
            else
                count <= count + 1;
            end if;
        end if;
    end process;
    clk_out <= pulse;
end arch_clock_divider;
```

generic: Key to Parameterized Entity



- In VHDL, you can create a “parameterized entity” by including a **generic clause** that lists all supported parameters (i.e., **generics**) in the entity declaration.

```
generic ( PARA_NAME: <type> [ := <value> ] );
```

– *Note: Default values are **optional** for generics and can be given in the entity declaration or the component declaration.*

- You can then instantiate a parameterized entity with a **component instantiation statement** in a similar way as instantiating an unparameterized entity.
 - Generics can be set (via **generic map**) in the instantiation.

```
generic map ( PARA_NAME => <value> )
```



- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- FSM Types
- Rule of Thumb: FSM Coding Tips
- FSM Examples
 - Up/Down Counter
 - Pattern Generator
- Use of Real Clock
 - Clock Sources of ZedBoard
 - Clock Divider