



香港中文大學

The Chinese University of Hong Kong

CENG3430 Rapid Prototyping of Digital Systems

Lecture 04:

Combinational Circuit and Sequential Circuit

Ming-Chang YANG

mcyang@cse.cuhk.edu.hk






- Combinational Circuit and Sequential Circuit
 - Combinational Circuit: No Memory
 - Decoder
 - Multiplexer
 - Bi-directional Bus
 - Sequential Circuit: Has Memory
 - Latch
 - Flip-flop
 - Asynchronous Reset and Synchronous Reset
 - Finite State Machine (FSM)
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples

Combinational Circuit



- **Combinational Circuit: no memory**
 - Outputs are a function of the *present* inputs only.
 - As soon as inputs change, the values of previous outputs are **lost**.
 - It has **no** internal state (i.e., has **no memory**).
 - Common Examples: *Comparator, Encoder/Decoder, Full/Half Adder, Multiplexer, Bi-directional Bus*, etc.
 - **Rule:** You can build a combinational circuit using **either concurrent statements** (i.e., statements outside `process`) **or sequential statements** (i.e., statements inside `process`).

 


Modeling Combinational Logic (1/3)



- Three typical ways for modeling a combinational logic:
 - 1) **Logic/Schematic Diagram** shows the **wiring** and **connections** of each individual logic gate.
 - 2) **Boolean Expression** is an expression in Boolean algebra that represents the logic circuit.
 - 3) **Truth Table** provides a concise list that shows all the output states for each possible combination of inputs

Logic/Schematic Diagram

 


```
architecture com_arch of comb is
  signal X, Y: std_logic;
begin
  X <= not (A and B);
  Y <= not (A or B);
  Q <= (X and C) and Y;
end com_arch;
```

Modeling Combinational Logic (2/3)



- Three typical ways for modeling a combinational logic:
 - 1) **Logic/Schematic Diagram** shows the wiring and connections of each individual logic gate.
 - 2) **Boolean Expression** is an **expression** in Boolean algebra that represents the logic circuit.
 - 3) **Truth Table** provides a concise list that shows all the output states for each possible combination of inputs

Logic/Schematic Diagram

 


Boolean Expression

$$Q = \overline{(A \cdot B)} \cdot \overline{(A + B)} \cdot C$$

```
architecture com_arch of comb is  
begin
```

```
    Q <= (not (A and B)) and  
        (not (A or B)) and C;
```

```
end com_arch;
```

 

Modeling Combinational Logic (3/3)



- Three typical ways for modeling a combinational logic:
 - 1) **Logic/Schematic Diagram** shows the wiring and connections of each individual logic gate.
 - 2) **Boolean Expression** is an expression in Boolean algebra that represents the logic circuit.
 - 3) **Truth Table** provides a **concise list** that shows all the output states for each possible combination of inputs


A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

```
process (A, B, C)
begin
  if( A = '0' and B = '0' and C = '1' ) then
    Q <= '1';
  else
    Q <= '0';
  end if;
end process;
```

Sequential Circuit




- **Sequential Circuit: has memory**
 - Outputs are a function of the present inputs and the previous outputs (i.e., the **internal state**).
 - It changes outputs based on inputs; but the outputs also depend upon previous outputs (i.e., the **internal state**) (i.e., has **memory**).
 - Example: *Latch, Flip-Flop, Finite State Machine*, etc.
 - **Rule:** You **must** build a sequential circuit with **only** sequential statements (i.e., statements inside `process`).

 

Combinational vs. Sequential Circuit



 - **Combinational Circuit: no memory**
 - ① Outputs are a function of the *present* inputs only.
 - ② **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
 - ① Outputs are a function of the *present* inputs and the *previous* outputs (i.e., the **internal state**).
 - ② **Rule: Must use sequential statements** (i.e., `process`).






- **Combinational Circuit and Sequential Circuit**
 - **Combinational Circuit: No Memory**
 - **Decoder**
 - **Multiplexer**
 - **Bi-directional Bus**
 - **Sequential Circuit: Has Memory**
 - **Latch**
 - **Flip-flop**
 - Asynchronous Reset and Synchronous Reset
 - **Finite State Machine (FSM)**
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples

Recall: Combinational Circuit



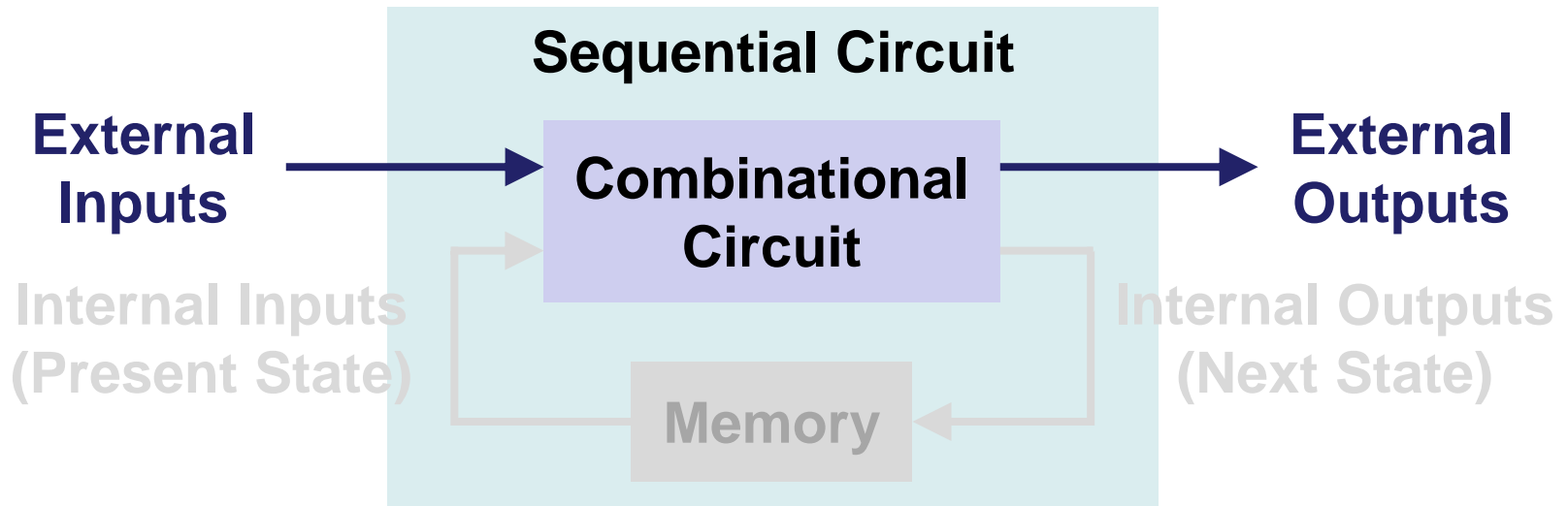- **Combinational Circuit: no memory**
 - ① Outputs are a function of the *present* inputs only.
 - ② **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
 - ① Outputs are a function of the *present* inputs and the *previous* outputs (i.e., the **internal state**).
 - ② **Rule:** Must use sequential statements (i.e., `process`).



Combinational Logic as a Process



- Consider a simple combinational logic:

$$c \leq a \text{ and } b;$$

- This logic can be also modeled as a **process**:

- All signals **referenced** in process must be in **sensitivity list**.

```
entity And_Good is
```

```
  port (a, b: in std_logic; c: out std_logic);
```

```
end And_Good;
```

```
architecture Synthesis_Good of And_Good is
```

```
begin
```

```
  process (a, b) -- sensitive to signals a and/or b
```

```
  begin
```

```
    c <= a and b; -- c updated
```

```
  end process;
```

```
end;
```

Combinational Circuit: Decoder (1/2)



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity decoder_ex is
port (in0,in1: in std_logic;
      out00,out01,out10,out11: out std_logic);
end decoder_ex;
architecture decoder_ex_arch of decoder_ex is
begin
  process (in0, in1)
  begin
```

```
    if in0 = '0' and in1 = '0' then
      out00 <= '1';
    else
      out00 <= '0';
    end if;
```

out00

```
    if in0 = '0' and in1 = '1' then
      out01 <= '1';
    else
      out01 <= '0';
    end if;
```

out01

in	in	out	out	out	out
0	1	00	01	10	11
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Combinational Circuit: Decoder (2/2)




...

```
if in0 = '1' and in1 = '0' then
  out10 <= '1';
else
  out10 <= '0';
end if;
if in0 = '1' and in1 = '1' then
  out11 <= '1';
else
  out11 <= '0';
end if;
```

```
end process;
end decoder_ex_arch;
```

in	in	out	out	out	out
0	1	00	01	10	11
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

<https://www.allaboutcircuits.com/textbook/digital/chpt-9/decoder/>

Class Exercise 4.1

Student ID: _____ Date: _____

Name: _____

- Implement the **Encoder** based on the given table:

```
port (
    ) ;
```

```
...
architecture encoder_ex_arch of encoder_ex is
begin
    process (
    )
    begin
```

```
        end process;
    end encoder_ex_arch;
```

in	in	in	in	out	out
00	01	10	11	0	1
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1




- **Combinational Circuit and Sequential Circuit**
 - **Combinational Circuit: No Memory**
 - Decoder
 - **Multiplexer**
 - Bi-directional Bus
 - Sequential Circuit: Has Memory
 - Latch
 - Flip-flop
 - Asynchronous Reset and Synchronous Reset
 - Finite State Machine (FSM)
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples


Combinational Circuit: Multiplexer


 
```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity mux_ex is
port (in1,in2,sel: in std_logic;
      out1: out std_logic);
end mux_ex;
architecture mux_ex_arch of mux_ex is
begin
  process (in1, in2, sel)
  begin
    if sel = '0' then
      out1 <= in1; -- select in1
    else
      out1 <= in2; -- select in2
    end if;
  end process;
end mux_ex_arch;
```



Recall: Tri-state Buffer

 

in1	enable	out1
0	0	Z
1	0	Z
0	1	0
1	1	1


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity tri_ex is
port (in1, enable: in std_logic;
      out1: out std_logic);
end tri_ex;
architecture tri_ex_arch of tri_ex is
begin
    out1 <= in1 when enable = '1' else 'Z';
end tri_ex_arch;
```

Class Exercise 4.2

Student ID: _____ Date: _____
Name: _____

- Specify the I/O signals in the circuit:
 
```
entity mux_ex is
port (in1,in2,sel: in std_logic;
      out1: out std_logic);
end mux_ex;
architecture mux_ex_arch of mux_ex is
begin
  process (in1, in2, sel)
  begin
    if sel = '0' then
      out1 <= in1;
    else
      out1 <= in2;
    end if;
  end process;
end mux_ex_arch;
```






- **Combinational Circuit and Sequential Circuit**
 - **Combinational Circuit: No Memory**
 - Decoder
 - Multiplexer
 - **Bi-directional Bus**
 - **Sequential Circuit: Has Memory**
 - Latch
 - Flip-flop
 - Asynchronous Reset and Synchronous Reset
 - **Finite State Machine (FSM)**
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples

Combinational Circuit: Bi-directional Bus

```
entity inout_ex is
port (io1, io2: inout std_logic;
      ctrl: in std_logic);
end inout_ex;
architecture inout_ex_arch of inout_ex is
begin
  process (io1, io2, ctrl) is begin
    if (ctrl = '1') then io1 <= io2;
    else io1 <= 'Z';
    end if;
  end process;
  process (io1, io2, ctrl) is begin
    if (ctrl = '0') then io2 <= io1;
    else io2 <= 'Z';
    end if;
  end process;
end inout_ex_arch;
```

 

io1 follows "io2.in"



io2 follows "io1.in"

Class Exercise 4.3

Student ID: _____ Date: _____
Name: _____

```
entity inout_ex is
port (io1, io2: inout std_logic;
      ctrl: in std_logic);
end inout_ex;
architecture inout_ex_arch of inout_ex is
begin
  process (io1, io2, ctrl) is begin
    if (ctrl = '1') then io1 <= io2;
    else io1 <= 'Z';
    end if;
  end process;
  process (io1, io2, ctrl) is begin
    if (ctrl = '0') then io2 <= io1;
    else io2 <= 'Z';
    end if;
  end process;
end inout_ex_arch;
```

- Specify I/O signals:

  




- **Combinational Circuit and Sequential Circuit**
 - Combinational Circuit: No Memory
 - Decoder
 - Multiplexer
 - Bi-directional Bus
 - **Sequential Circuit: Has Memory**
 - Latch
 - **Flip-flop**
 - Asynchronous Reset and Synchronous Reset
 - **Finite State Machine (FSM)**
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples

Recall: Sequential Circuit



 - **Combinational Circuit: no memory**
 - ① Outputs are a function of the *present* inputs only.
 - ② **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
 - ① Outputs are a function of the *present* inputs and the *previous* outputs (i.e., the **internal state**).
 - ② **Rule: Must use sequential statements** (i.e., `process`).



Latches and Flip Flops



- Latches and Flip-flops (FF) are the basic elements used to store information.
 - Each latch and flip flop can keep one bit of data.
- The main difference between latch and flip-flop:
 - A latch continuously checks input and changes the output whenever there is a change in input.
 - A latch has **no** clock signal.
 - A flip-flop continuously checks input and changes the output only at times determined by the clock signal.
 - A flip flop has a clock signal.




- **Combinational Circuit and Sequential Circuit**
 - Combinational Circuit: No Memory
 - Decoder
 - Multiplexer
 - Bi-directional Bus
 - **Sequential Circuit: Has Memory**
 - Latch
 - Flip-flop
 - Asynchronous Reset and Synchronous Reset
 - Finite State Machine (FSM)
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples

Sequential Circuit: Latch (1/2)



- Latches are **asynchronous** (**no** CLOCK signal).
 - It changes output **only in response to input**.
- Case Study: D Latch**
 - When enable line C is high, the output Q follows input D.
 - That is why D latch is also called as **transparent latch**.
 - When enable line C is asserted, the latch is said to be transparent.
 - When C falls, the last state of D input is trapped and held.
 - That is why the latch **has memory!**

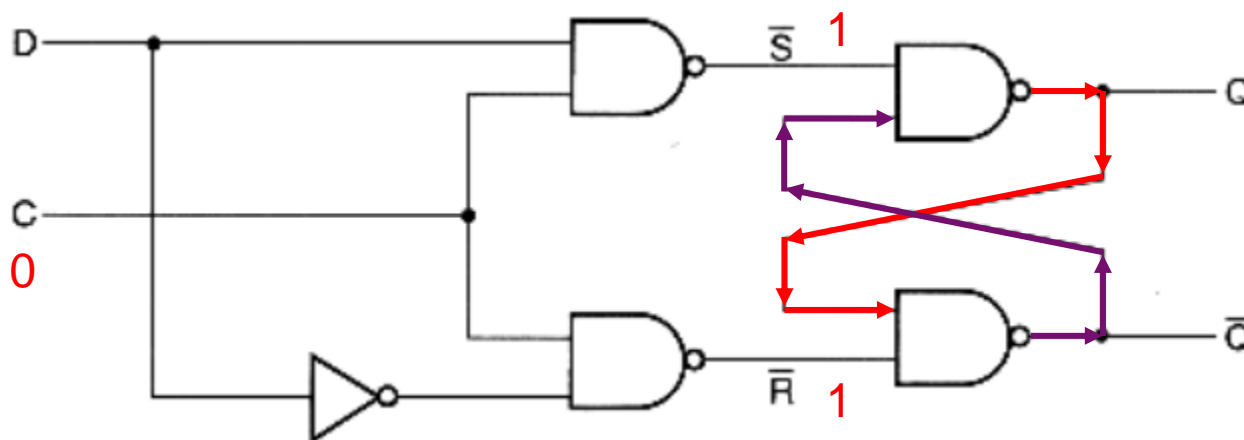

Data need to be held.


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

<https://www.edgefx.in/digital-electronics-latches-and-flip-flops/>

Sequential Circuit: Latch (2/2)



```
1 library IEEE;--(ok vivado 2014.4)
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity latch_ex is
4 port (C, D: in std_logic;
5       Q: out std_logic);
6 end latch_ex;
7 architecture latch_ex_arch of latch_ex is
8 begin
9     process(C, D) -- sensitivity list
10    begin
11        if (C = '1') then
12            Q <= D;
13        end if;
14        -- no change (memory)
15    end process;
16 end latch_ex_arch;
```

 

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

Class Exercise 4.4


Student ID: _____ Date: _____

Name: _____

- Given a D latch, draw Q in the following figure:



Q

 

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state




- **Combinational Circuit and Sequential Circuit**
 - Combinational Circuit: No Memory
 - Decoder
 - Multiplexer
 - Bi-directional Bus
 - **Sequential Circuit: Has Memory**
 - Latch
 - **Flip-flop**
 - Asynchronous Reset and Synchronous Reset
 - Finite State Machine (FSM)
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples

Sequential Circuit: Flip-flop



- A **Latch** is a non-clock-controlled memory device.

 - ① It has **no** CLOCK signal.
- ② It changes output only in response to data input (i.e., the value is set **asynchronously**).



- A **Flip-flop (FF)** is a **clock-controlled** memory device.

- ① Different from a Latch, it **has** a CLOCK signal as input.
- ② It stores the input value (i.e., low or high) and **outputs** the stored value **only in response to** the CLOCK signal.


- **Positive-Edge-Triggered**: At every **low to high** of CLOCK.
- **Negative-Edge-Triggered**: At every **high to low** of CLOCK.

- ③ The value can be **reset** **asynchronously** or **synchronously**.

- **Async. Reset**: Reset the value **anytime**.
- **Sync. Reset**: Reset the value on **positive** or **negative** clock edges.

Positive-Edge-Triggered FF with Async. Reset

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity dff_async is
4 port (D, CLK, RESET: in std_logic;
5       Q: out std_logic);
6 end dff_async;
7 architecture dff_async_arch of dff_async is
8 begin
9     process (CLK, RESET) -- sensitivity list
10    begin
11        if (RESET = '1') then
12            Q <= '0'; -- Reset Q immediately
13        elsif CLK = '1' and CLK'event then
14            Q <= D; -- Q follows input D
15        end if;
16        -- no change (so has memory)
17    end process;
18 end dff_async_arch;
```

 

Positive-
edge-
triggered

Recall: Attributes (Lec01)



- Another important signal attribute is the '**event**'.
 - This attribute yields a Boolean value of TRUE if an event has just occurred on the signal.
 - It is used primarily to determine if a **clock** has transitioned.
- Example (*more in Lec04*):

```
...  
port (my_in,  clock: in std_logic;  
      my_out: out std_logic);  
...  
if clock = '1' and clock'event then  
    my_out <= my_in;
```


Class Exercise 4.5

Student ID: _____ Date: _____
Name: _____

- Consider the following VHDL implementation of a positive-edge-triggered FF with asynchronous reset:

```
...
9   process (CLK, RESET) -- sensitivity list
10  begin
11      if (RESET = '1') then
12          Q <= '0'; -- Reset Q
13      elsif CLK = '1' and CLK'event then
14          Q <= D; -- Q follows input D
15      end if;
16      -- no change (so has memory)
17  end process;
```

...

- When will line 9 be executed?

Answer: _____

- Which signal is more “powerful”? CLK or RESET?



Answer: _____

Class Exercise 4.6

Student ID: _____ Date: _____


Name: _____

  - Given a Positive-edge-triggered D Flip-flop with **async.** reset, draw the output Q.



Positive-Edge-Triggered FF with Sync. Reset
 
```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity dff_sync is
4 port (D,CLK,RESET: in std_logic;
5       Q: out std_logic);
6 end dff_sync;
```



```
7 architecture dff_sync_arch of dff_sync is begin
8 process (CLK) ← RESET can be removed (why?)
```

```
9   begin
10     if CLK = '1' and CLK'event then
11       if (RESET = '1') then
12         Q <= '0'; -- Reset Q
13       else
14         Q <= D; -- Q follows input D
15       end if;
16     end if;
```

Positive-
edge-
triggered

```
    -- no change (so has memory)
```



```
17   end process;
18 end dff_sync_arch;
```

Class Exercise 4.7

Student ID: _____ Date: _____

Name: _____

  - Given a Positive-edge-triggered D Flip-flop with **sync.** reset, draw the output Q.



Async. Reset vs. Sync. Reset (1/2)



- The order of the statements inside the process determines **asynchronous reset** or **synchronous reset**.


- **Asynchronous Reset** (check **RESET** first!)

```
11     if (RESET = '1') then
12         Q <= '0'; -- Reset Q
13     elsif CLK = '1' and CLK'event then
14         Q <= D; -- Q follows input D
15     end if;
```

- **Synchronous Reset** (check **CLK** first!)

```
10     if CLK = '1' and CLK'event then
11         if (RESET = '1') then
12             Q <= '0'; -- Reset Q
13         else
14             Q <= D; -- Q follows input D
15         end if;
16     end if;
```

Async. Reset vs. Sync. Reset (2/2)

 

**Asynchronous
Reset**

Q

**Synchronous
Reset**

Q





- **Combinational Circuit and Sequential Circuit**
 - Combinational Circuit: No Memory
 - Decoder
 - Multiplexer
 - Bi-directional Bus
 - **Sequential Circuit: Has Memory**
 - Latch
 - Flip-flop
 - Asynchronous Reset and Synchronous Reset
 - **Finite State Machine (FSM)**
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples

Finite State Machine (FSM)



  - **Finite State Machine (FSM):** A system jumps from one **state** to another:
 - Within a pool of finite states, and
 - Upon clock edges and/or input transitions.
- Example of FSM: traffic light, digital watch, CPU, etc.



- Two crucial factors: *time (clock edge)* and *state (feedback)*



- **Combinational Circuit and Sequential Circuit**
 - Combinational Circuit: No Memory
 - Decoder
 - Multiplexer
 - Bi-directional Bus
 - **Sequential Circuit: Has Memory**
 - Latch
 - Flip-flop
 - Asynchronous Reset and Synchronous Reset
 - **Finite State Machine (FSM)**
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples


Clock Edge Detection



- Both “**wait until**” and “**if**” statements can be used to detect the clock edge (e.g., **CLK**):


- “**wait until**” statement:

 - **wait until** CLK = '1'; -- rising edge
- **wait until** CLK = '0'; -- falling edge




- “**if**” statement:

 - **if** CLK'event and CLK = '1' -- rising edge
- **if** CLK'event and CLK = '0' -- falling edge



OR

 - **if**(rising_edge (CLK)) -- rising edge
- **if**(falling_edge (CLK)) -- falling edge



rising_edge (CLK) VS. CLK'event



- **rising_edge ()** function in std_logic_1164 library

```
FUNCTION rising_edge (SIGNAL s : std_ulogic) RETURN BOOLEAN IS
BEGIN
    RETURN (s'EVENT AND (To_X01(s) = '1') AND
            (To_X01(s'LAST_VALUE) = '0'));
END;
```

- It results **TRUE** when there is an edge transition in the signal s, the present value is '1' and the last value is '0'.
 - If the last value is something like 'z' or 'U', it returns a **FALSE**.
- The statement (**clk'event** and **clk='1'**)
 - It results **TRUE** when there is an edge transition in the clk and the present value is '1'.
 - *It does not see whether the last value is '0' or not.*

Use rising_edge () / falling_edge () with “if” statements!

When to use “wait until” or “if”? (1/2)

- **Synchronous Process:** Computes values only on clock edges (i.e., only sensitive/sync. to clock signal).
 - **Rule:** Use “**wait-until**” or “**if**” for **synchronous** process:

```
process ← NO sensitivity list implies that there is one clock signal.  
begin
```

Usage
of
“wait
until”

```
    wait until clk='1' ; ← The first statement must be wait until.  
    ...  
end process
```

*Note: IEEE VHDL requires that a process with a wait statement must not have a sensitivity list, and the first statement must be **wait until**.*

```
process (clk) ← The clock signal must be in the sensitivity list.  
begin
```

Usage
of
“if”

```
    ...  
    if ( rising_edge (clk) ) ← NOT necessary to be the first line.  
    ...  
end process
```

When to use “wait until” or “if”? (2/2)

- **Asynchronous Process:** Computes values on clock edges or when asynchronous conditions are TRUE.
 - That is, it must be sensitive to the clock signal (if any), and to all inputs that may affect the asynchronous behavior.
 - **Rule:** Only use “**if**” for **asynchronous** process:

```
process (clk, input_a, input_b, ...) ← The sensitivity list
begin
  ...
  if ( rising_edge (clk) )
  ...
end process
```

← The sensitivity list should include the clock signal, and all inputs that may affect asynchronous behavior.

Usage
of
“if”

Simply use “if” statements for both sync. and async. processes!




- **Combinational Circuit and Sequential Circuit**
 - Combinational Circuit: No Memory
 - Decoder
 - Multiplexer
 - Bi-directional Bus
 - **Sequential Circuit: Has Memory**
 - Latch
 - Flip-flop
 - Asynchronous Reset and Synchronous Reset
 - **Finite State Machine (FSM)**
 - Clock Edge Detection
 - **Direct Feedback Path**
 - Types and Examples

Feed-forward and Feedback Paths



 - So far, we mostly focus on logic with **feed-forward** (or **open-loop**) paths.



- Now, we are going to learn **feedback** (or **closed-loop**) **paths**—*the key step of making a finite state machine.*

Direct Feedback Path



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity feedback_1 is
port (a, clk, reset: in std_logic;
      c: buffer std_logic);
end feedback_1;
```

```
architecture feedback_1_arch of feedback_1 is
begin
```

```
  process (clk, reset) -- async.
  begin
```


```
    if reset = '1' then c <= '0';
    elsif rising_edge(clk) then
```

```
      c <= not (a and c);
```

```
    end if;
```

```
  end process;
```

```
end feedback_1_arch ;
```

 

① Signal **c** forms a **closed loop**.

- **not (a and c)** takes effect at the next rising clock edge.
- The current **c** holds for one cycle.


② “**<=**” is like a flip-flop.

Internal Feedback: inout or buffer



- Recall (*Lec01*): There are 4 modes of I/O pins:

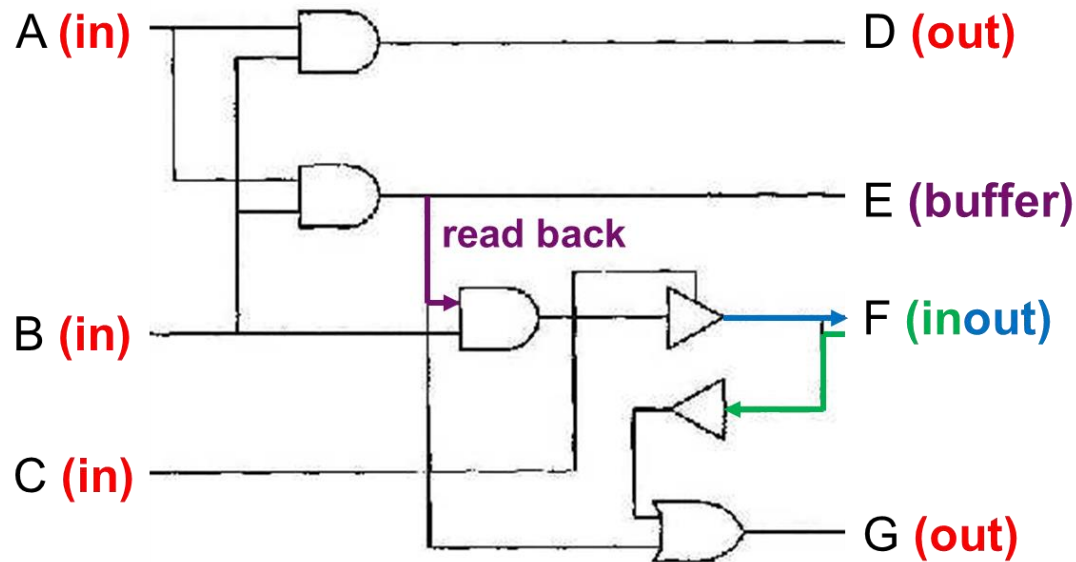- 1) **in**: Data flows **in** only
- 2) **out**: Data flows **out** only (cannot be read back by the entity)
- 3) **inout**: Data flows **bi-directionally** (i.e., in or out)
- 4) **buffer**: Similar to **out** but it can be **read back** by the entity



- Both **buffer** and **inout** can be **read back** internally.
 - **inout** can also read external input signals.




- **Combinational Circuit and Sequential Circuit**
 - Combinational Circuit: No Memory
 - Decoder
 - Multiplexer
 - Bi-directional Bus
 - **Sequential Circuit: Has Memory**
 - Latch
 - Flip-flop
 - Asynchronous Reset and Synchronous Reset
 - **Finite State Machine (FSM)**
 - Clock Edge Detection
 - Direct Feedback Path
 - **Types and Examples**

Types of Finite State Machines





- **Moore Machine:**

 - **Outputs** are a function of the present **state** only.



- **Mealy Machine:**

  - **Outputs** are a function of the present **state** and the present **inputs**.



Suggestion: Maintain the internal state explicitly!

Moore Machine



- **Moore Machine:** *outputs* rely on *present state* only.

architecture moore_arch of fsm is

signal s: bit; -- internal state

begin

```
process (s)
```

Combinational Logic

```
begin
```

```
    OUTX <= not s; -- output
```

```
end process;
```

```
process (CLOCK, RESET)
```

Sequential Logic

```
begin
```

```
    if RESET = '1' then s <= '0';
```

```
    elsif rising_edge(CLOCK) then
```

```
        s <= not (INX and s); -- feedback
```

```
    end if;
```

```
end process;
```

```
end moore_arch;
```

Mealy Machine



- **Mealy Machine:** *outputs* depend on *state* and *inputs*.

architecture mealy_arch of fsm is

```
signal s: bit; -- internal state
```

```
begin
```

```
process (INX, s) Combinational Logic
```

```
begin
```

```
OUTX <= (INX or s); -- output
```

```
end process;
```

```
process (CLOCK, RESET) Sequential Logic
```

```
begin
```

```
if RESET = '1' then s <= '0';
```

```
elsif rising_edge(CLOCK) then
```

```
s <= not (INX and s); -- feedback
```

```
end if;
```

```
end process;
```

```
end mealy_arch;
```

FSM Example 1) Up/Down Counter



- **Up/Down Counters:** Generate a sequence of counting patterns according to the clock and inputs.

```
use IEEE.Numeric_Std.ALL;
```

```
entity counter is
```

```
  port(CLK: in std_logic;
```

```
        RESET: in std_logic;
```

```
        COUNT: out std_logic_vector(3 downto 0));
```

```
end counter;
```

```
architecture counter_arch of counter is
```

```
  signal s: std_logic_vector(3 downto 0); -- internal state
```

```
begin
```

```
  COUNT <= s; -- output
```

Combinational Logic

```
  process (CLK, RESET)
```

Sequential Logic

```
  begin
```

```
    if(RESET = '1') then s <= "0000";
```

```
    else
```

```
      if( rising_edge(CLK) ) then
```

```
        s <= std_logic_vector(unsigned(s) + 1); -- feedback
```

```
      end if;
```


```
    end if;
```

```
  end process;
```

```
end counter_arch;
```


FSM Example 1) Up/Down Counter (2/2)

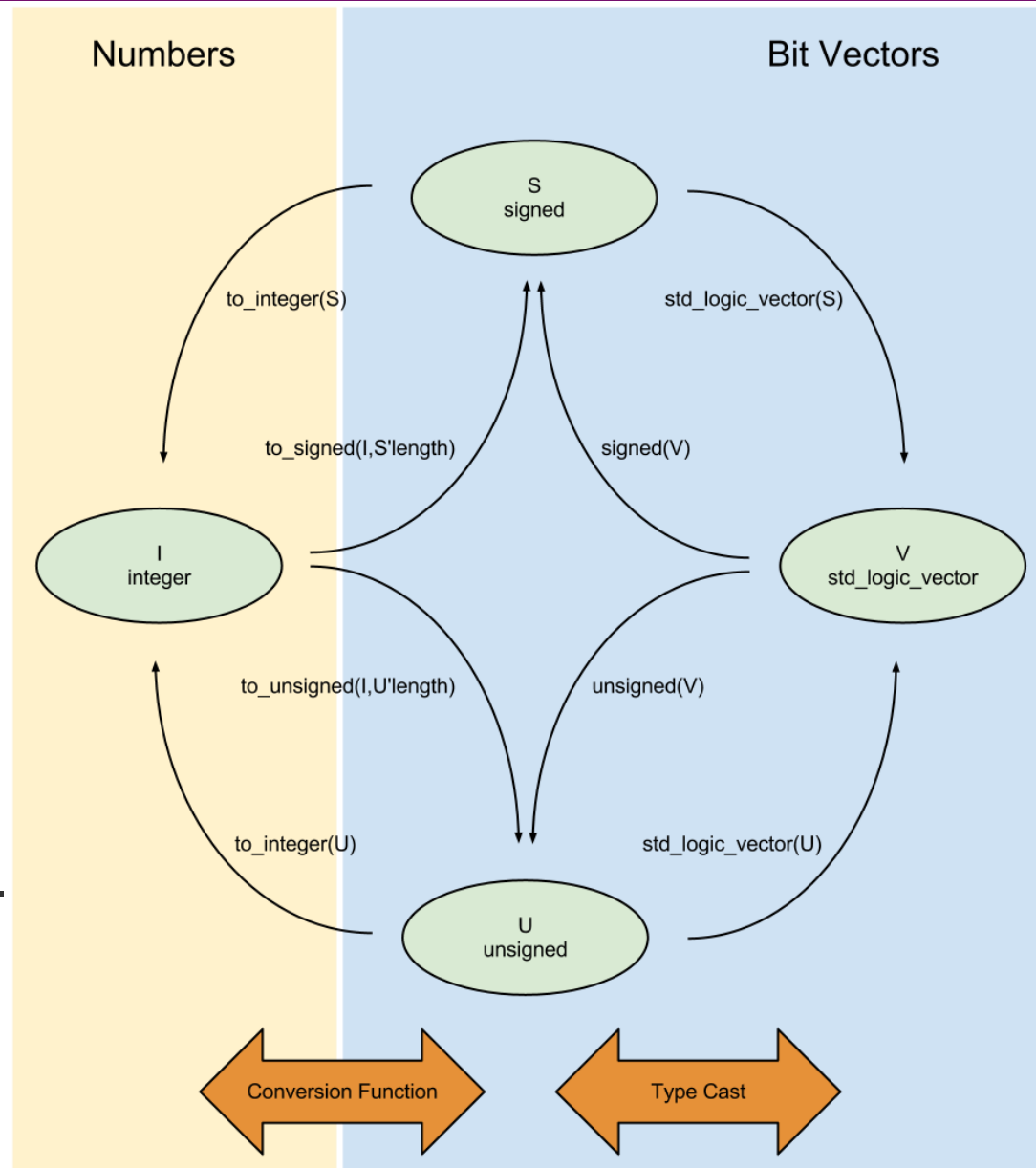- VHDL is **strongly-typed** language.
 - Data objects of different base types **CANNOT** to assigned to each other without using **type-casting** or **type-conversion**.
 - **Type-casting:** Move between `std_logic_vector` and `signed/unsigned`.
 - **Type-conversion:** Move between `signed/unsigned` and `integer`.



FSM Example 2) Pattern Generator (1/3)

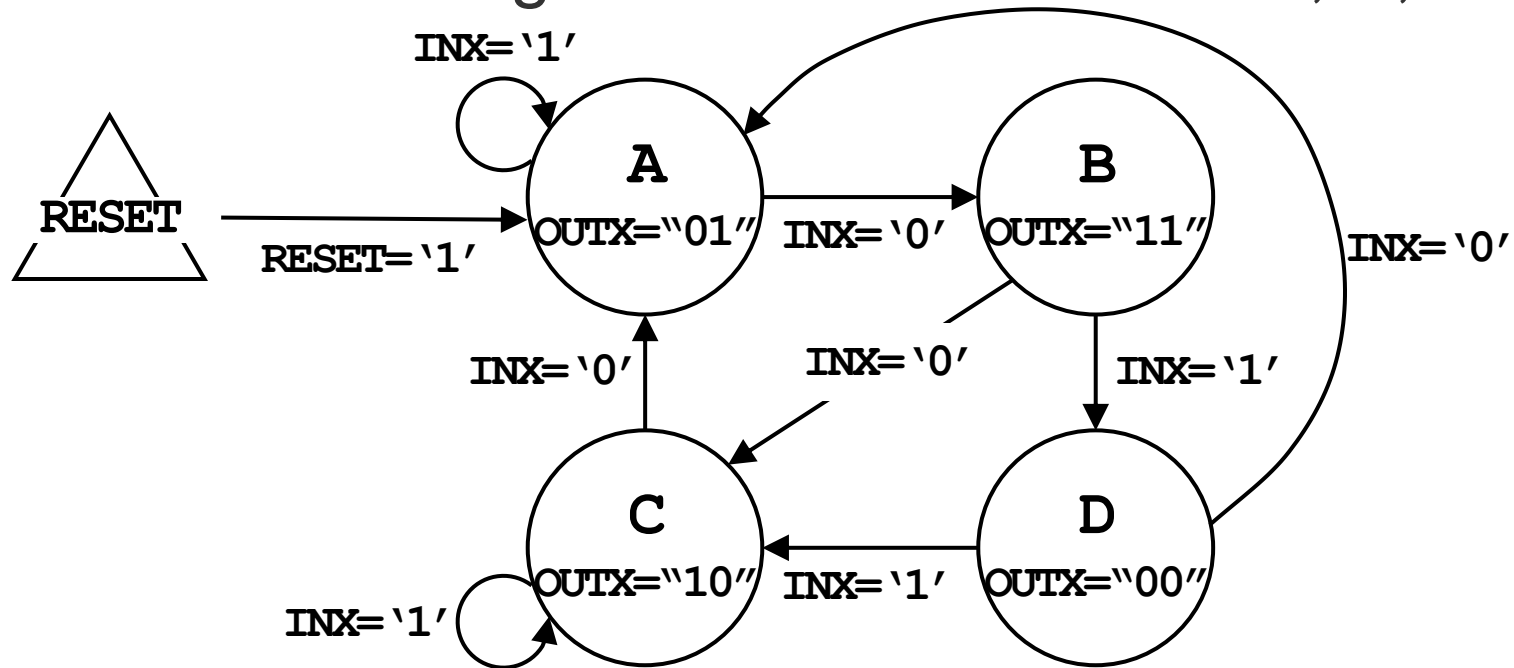- **Pattern Generator:** Generates **any pattern** we want.
 - Example: the control unit of a CPU, traffic light, etc.
- Given the following machine of 4 states: **A**, **B**, **C** and **D**.



- The machine has an asynchronous **RESET**, a clock signal **CLK** and a 1-bit synchronous input signal **INX**.
- The machine also has a 2-bit output signal **OUTX**.

FSM Example 2) Pattern Generator (2/3)

```
library IEEE;
use IEEE.std_logic_1164.all;
entity pat_gen is port(
RESET,CLOCK,INX: in STD_LOGIC;
OUTX: out STD_LOGIC_VECTOR(1 downto 0));
end pat_gen;
architecture arch of pat_gen is
type state_type is (A,B,C,D);
signal s: state_type; -- state
begin
```

```
process(CLOCK, RESET)
begin
    if RESET = '1' then
        s <= A;
    elsif rising_edge(CLOCK) then
        -- feedback
        case s is
        when A =>
            if INX = '1' then s <= A;
            else s <= B; end if;
```

**Sequential
Logic**

```
        when B =>
            if INX = '1' then s <= D;
            else s <= C; end if;
        when C =>
            if INX = '1' then s <= C;
            else s <= A; end if;
        when D =>
            if INX = '1' then s <= C;
            else s <= A; end if;
        end case;
```

```
    end if;
end process;
```

```
process(s)
begin
```

```
    case s is
        when A => OUTX <= "01";
        when B => OUTX <= "11";
        when C => OUTX <= "10";
        when D => OUTX <= "00";
    end case;
```

**Combinational
Logic**

```
end process;
```

```
end arch;
```


FSM Example 2) Pattern Generator (3/3)

- Encoding methods for representing patterns/states:
 - **Binary Encoding**: Using N flip-flops to represent 2^N states.
 - Less flip-flops but more combinational logics
 - **One-hot Encoding**: Using N flip-flops for N states.
 - More flip-flops but less combination logic
 - *Xilinx default setting is one-hot encoding.*
 - *Change at synthesis → options*
 - *<http://www.xilinx.com/itp/xilinx4/data/docs/sim/vtex9.html>*

Class Exercise 4.8

Student ID: _____ Date: _____
 Name: _____

 - Complete a Mealy Machine that recognizes sequence "10":



architecture arch of mealy_fsm is

```

type state_type is (S0, S1);
signal s: std_logic; -- state
begin
process (CLK, RESET) -- seq
begin
    if (RESET = '1') then s <= __;
    else
        if ( rising_edge(CLK) ) then
            case s is
            when S0 =>
                if input = __ then
                    s <= __; -- feedback
                else
                    s <= __; -- feedback
                end if;
            
```

```

            when S1 =>
                if input = __ then
                    s <= __; -- feedback
                else
                    s <= __; -- feedback
                end if;
            end case;
        end if;
    end if;
end process;
OUTX <= __ when (s=__ and INX=__ )
else __; -- output
end arch;

```

Rule of Thumb: VHDL Coding Tips



- ① **Maintain the internal state(s) explicitly**
- ② **Separate combinational and sequential logics**
 - Write **at least two processes**: one for combinational logic, and the other for sequential logic
 - Maintain the **internal state(s)** using a sequential process
 - Drive the **output(s)** using a combination process
- ③ **Keep every process as simple as possible**
 - Partition a large process into **multiple small ones**
- ④ **Put every signal** (that your process must be sensitive to its changes) **in the sensitivity list.**
- ⑤ **Avoid assigning a signal from multi-processes**
 - It may cause the “**multi-driven**” issue.





- Combinational Circuit and Sequential Circuit
 - Combinational Circuit: No Memory
 - Decoder
 - Multiplexer
 - Bi-directional Bus
 - Sequential Circuit: Has Memory
 - Latch
 - Flip-flop
 - Asynchronous Reset and Synchronous Reset
 - Finite State Machine (FSM)
 - Clock Edge Detection
 - Direct Feedback Path
 - Types and Examples