

CENG4480

Lecture 03 Review

Bei Yu

2016 Fall

byu@cse.cuhk.edu.hk




香港中文大學

The Chinese University of Hong Kong

Sinusoidal Signal

$$x(t) = A\cos(\omega t + \phi)$$

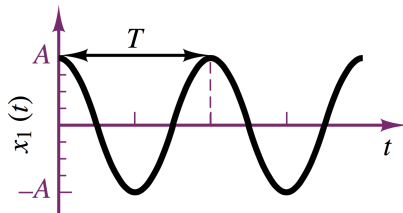- ▶ Periodic signals
- ▶ A : amplitude
- ▶ ω : radian frequency
- ▶ ϕ : phase




Time Domain

- ▶ Voltage gain against **time**

For sinusoidal signal:

$$v(t) = A\cos(\omega t + \phi)$$

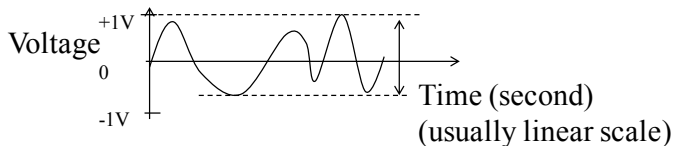


Frequency Domain

- ▶ Voltage gain against frequency


For sinusoidal signal:
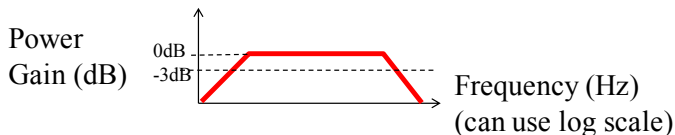
$$\mathbf{V}(j\omega) = Ae^{j\phi} = A\angle\phi = A\cos\phi + jA\sin\phi$$



Impedance

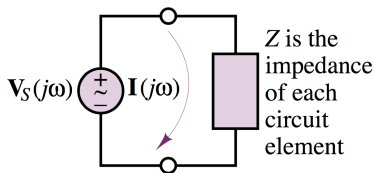A complex resistance or *frequency-dependent resistance*. That is, as resistors whose resistance is a function of the frequency of the sinusoidal excitation.




AC circuits in
phasor/impedance form



Resistor Impedance

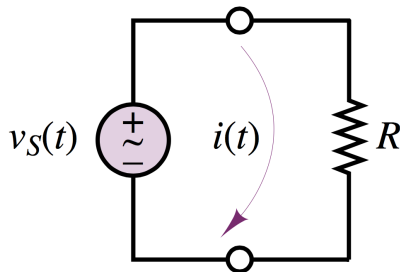- ▶ $\mathbf{V}(j\omega) = A\angle 0$
- ▶ $\mathbf{I}(j\omega) = \frac{A}{R}\angle 0$



Impedance of A Resistor


$$Z_R(j\omega) = \frac{\mathbf{V}(j\omega)}{\mathbf{I}(j\omega)} = R\angle 0 = R$$



Capacitor Impedance

$$\mathbf{V}(j\omega) = A\angle 0$$
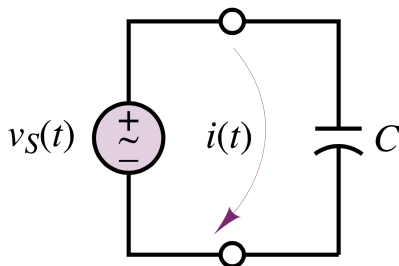
$$\mathbf{I}(j\omega) = \omega CA\angle \pi/2$$



Impedance of A Capacitor


$$Z_C(j\omega) = \frac{\mathbf{V}(j\omega)}{\mathbf{I}(j\omega)}$$



Capacitor Impedance

$$\mathbf{V}(j\omega) = A\angle 0$$
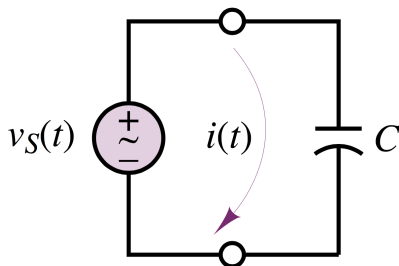
$$\mathbf{I}(j\omega) = \omega C A \angle \pi/2$$




Impedance of A Capacitor

$$\begin{aligned} Z_C(j\omega) &= \frac{\mathbf{V}(j\omega)}{\mathbf{I}(j\omega)} \\ &= \frac{1}{\omega C} \angle -\pi/2 = \frac{1}{\omega C} (\cos -\pi/2 + j \sin -\pi/2) \\ &= \frac{-j}{\omega C} = \frac{1}{j\omega C} \end{aligned}$$



$$Z_C(j\omega) = \frac{1}{j\omega C}$$

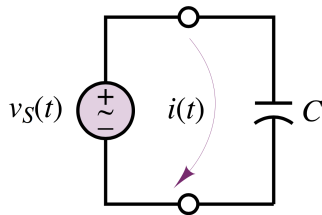

Capacitor Rule 1


Low Frequency \Rightarrow Open circuit

Capacitor Rule 2


High Frequency \Rightarrow Short circuit



Frequency Response of An Op-Amp

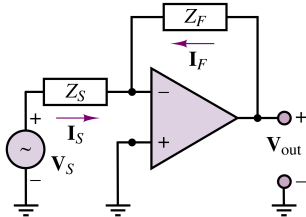



Inverting

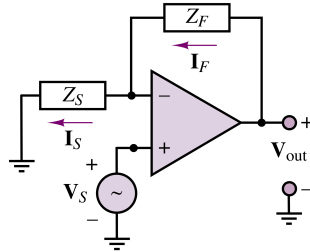

Noninverting





Frequency Response of An Op-Amp

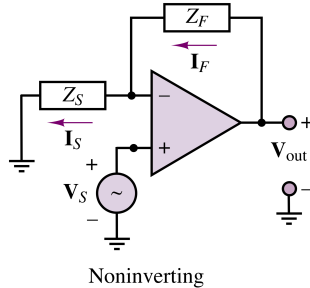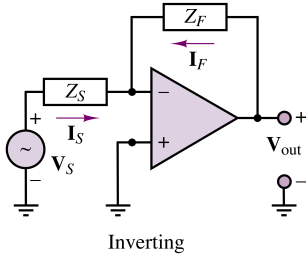

- ▶ Inverting amplifier: $\frac{V_{out}}{V_S}(j\omega) = -\frac{Z_F}{Z_S}$



Frequency Response of An Op-Amp

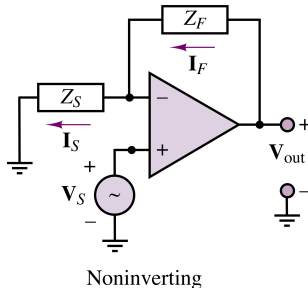
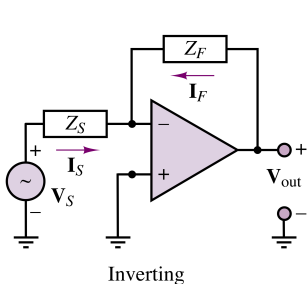


▶ Inverting amplifier: $\frac{V_{out}}{V_S}(j\omega) = -\frac{Z_F}{Z_S}$

▶ Non-Inverting amplifier: $\frac{V_{out}}{V_S}(j\omega) = 1 + \frac{Z_F}{Z_S}$



Low-Pass Filter

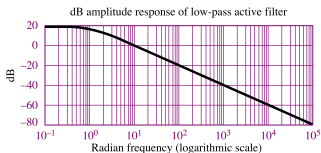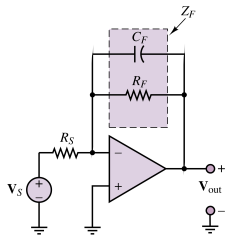


$$\text{BTW, } \lim_{\omega \rightarrow 0} |A| = \frac{R_F}{R_S}, \lim_{\omega \rightarrow \infty} |A| = 0$$

$$|A| = \frac{R_F}{R_S} \cdot \frac{1}{\sqrt{1 + \omega^2 / \omega_c^2}}$$


- ▶ $\omega_c = \frac{1}{R_F C_F}$
- ▶ **3-dB** frequency
- ▶ or **cutoff** frequency



High-Pass Filter

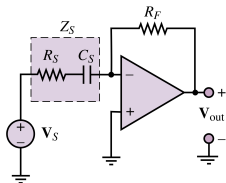
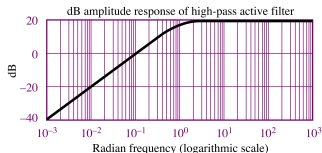
$$A(j\omega) = -\frac{Z_F}{Z_S} = -\frac{j\omega C_S R_F}{1 + j\omega C_S R_S}$$



$$\lim_{\omega \rightarrow 0} |A| = 0$$

$$\lim_{\omega \rightarrow \infty} |A| = \frac{R_F}{R_S}$$

High freq. cutoff unintentionally created by Op-amp

