



CENG4480

## Lecture 09: Memory 2

**Bei Yu**

[byu@cse.cuhk.edu.hk](mailto:byu@cse.cuhk.edu.hk)

(Latest update: November 26, 2020)

Fall 2020



香港中文大學

The Chinese University of Hong Kong

# CENG4480 v.s. CENG3420




## CENG3420:

- ▶ architecture perspective
- ▶ memory coherent
- ▶ data address

## CENG4480:

- ▶ more details on how data is stored


# Memory Arrays

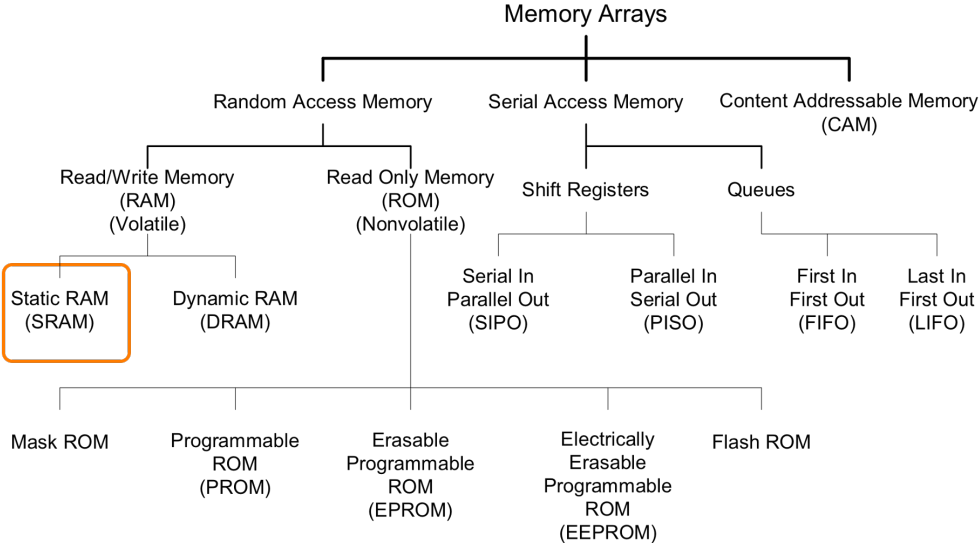

 
# Memory Arrays



- ▶ What if we add feedback to a pair of inverters?




 
- ▶ Usually drawn as a ring of **cross-coupled** inverters
- ▶ Stable way to store one bit of information (w. power)


  
# How to change the value stored?



- ▶ Replace inverter with NAND gate
- ▶ RS Latch





| A | B | A nand B |
|---|---|----------|
| 0 | 0 | 1        |
| 0 | 1 | 1        |
| 1 | 0 | 1        |
| 1 | 1 | 0        |


  
# 12T SRAM Cell

- ▶ Basic building block: SRAM Cell
  - ▶ Holds one bit of information, like a latch
  - ▶ Must be read and written
- ▶ 12-transistor (**12T**) SRAM cell
  - ▶ Use a simple latch connected to bitline
  - ▶  $46 \times 75 \lambda$  unit cell



# nMOS, pMOS, Inverter



- ▶ nMOS:



- ▶ Gate = 1, transistor is ON
- ▶ Then electric current path

- ▶ pMOS:

- ▶ Gate = 0, transistor is ON
- ▶ Then electric current path

- ▶ Inverter:


- ▶  $Q = \text{NOT}(A)$

  
 
# 6T SRAM Cell



- ▶ Used in most commercial chips
- ▶ A pair of **weak** cross-coupled inverters
- ▶ Data stored in cross-coupled inverters
- ▶ Compared with 12T SRAM, 6T SRAM:
  - ▶ (+) reduce area
  - ▶ (-) much more complex control






  
# 6T SRAM Read



- ▶ Precharge both bitlines high
- ▶ Then turn on wordline
- ▶ One of the two bitlines will be pulled down by the cell
- ▶ Read stability
  - ▶ A must not flip
  - ▶  $N1 \gg N2$






  
# 6T SRAM Write




- ▶ Drive one bitline high, the other low
- ▶ Then turn on wordline
- ▶ Bitlines overpower cell with new value
- ▶ **Writability**
  - ▶ Must overpower feedback inverter
  - ▶  $N4 \gg P2$
  - ▶  $N2 \gg P1$  (symmetry)


 
# EX: 6T SRAM Write




- ▶ **Question 1:**  $A = 0, A_b = 1$ , discuss the behavior:
  
- ▶ **Question 2:** At least how many bit lines to finish write?





# Memory Arrays

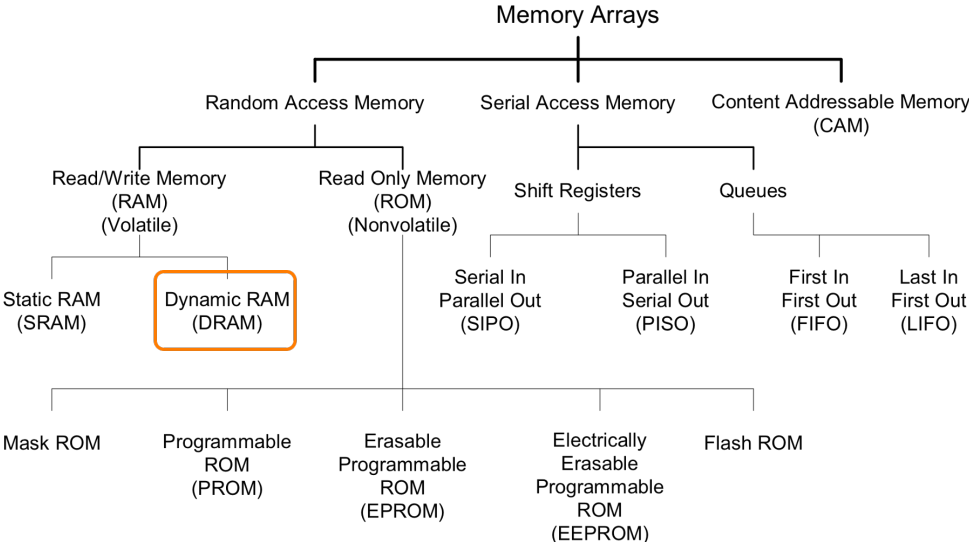

# Dynamic RAM (DRAM)




- ▶ Basic Principle: Storage of information on **capacitors**
- ▶ **Charge & discharge** of capacitor to change stored value
- ▶ Use of transistor as "switch" to:
  - ▶ Store charge
  - ▶ Charge or discharge
 
# 4T DRAM Cell



Remove the two p-MOS transistors from static RAM cell, to get a four-transistor dynamic RAM cell.





- ▶ Data must be refreshed regularly
- ▶ Dynamic cells must be designed very carefully
- ▶ Data stored as charge on gate capacitors (complementary nodes)



 
 
# 3T DRAM Cell



- ▶ No constraints on device ratios
- ▶ Reads are non-destructive
- ▶ Value stored at node X when writing a "1" =  $V_{DD} - V_T$




# 3T DRAM Layout

  


[1970: Intel 1003]

- ▶ 576  $\lambda$  3T DRAM v.s. 1092  $\lambda$  6T SRAM
- ▶ Further simplified


# 1T1R1C DRAM Cell

 


(a)

 


(b)

 


(c)

 


(d)

 

(e)

 


(f)

 

(g)

► Need sense amp helping reading

# 1T1R1C1 DRAM Cell

 



## ▶ Read

- ▶ Pre-charge large tank to  $VDD2$
- ▶ If  $T_s = 0$ , for large tank:  $VDD2 - V1$
- ▶ If  $T_s = 1$ , for large tank:  $VDD2 + V1$
- ▶  $V1$  is very insignificant
  
# 1T1R1C1 DRAM Cell



- ▶ **Write:**  $C_s$  is charged or discharged by asserting WL and BL
- ▶ **Read:** Charge redistribution takes place between bit line and storage capacitance
- ▶ Voltage swing is small; typically around 250 mV



Trench-capacitor cell [Mano87]

# EX. 1T DRAM Cell



- ▶ **Question:**  $V_{DD}=4\text{V}$ ,  $C_S=100\text{pF}$ ,  $C_{BL}=1000\text{pF}$ . What's the voltage swing value?
- ▶ **Note:**  $\Delta V = \frac{V_{DD}}{2} \cdot \frac{C_S}{C_S+C_{BL}}$

# SRAM v.s. DRAM



## ▶ **Static (SRAM)**

- ▶ Data stored as long as supply is applied
- ▶ Large (6 transistors/cell)
- ▶ Fast
- ▶ Compatible with current CMOS manufacturing


## ▶ **Dynamic (DRAM)**

- ▶ Periodic refresh required
- ▶ Small (1-3 transistors/cell)
- ▶ Slower
- ▶ Require additional process for trench capacitance
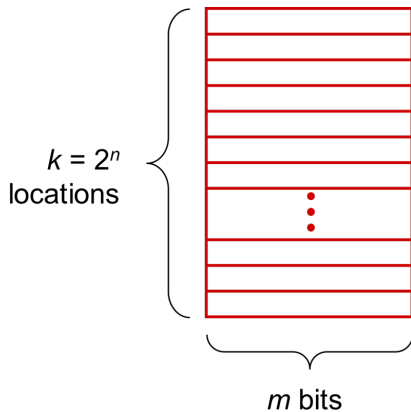
# Array Architecture



- ▶  $2^n$  words of  $2^m$  bits each
- ▶ Good regularity - easy to design






# SRAM Memory Structure




▶ Latch based memory

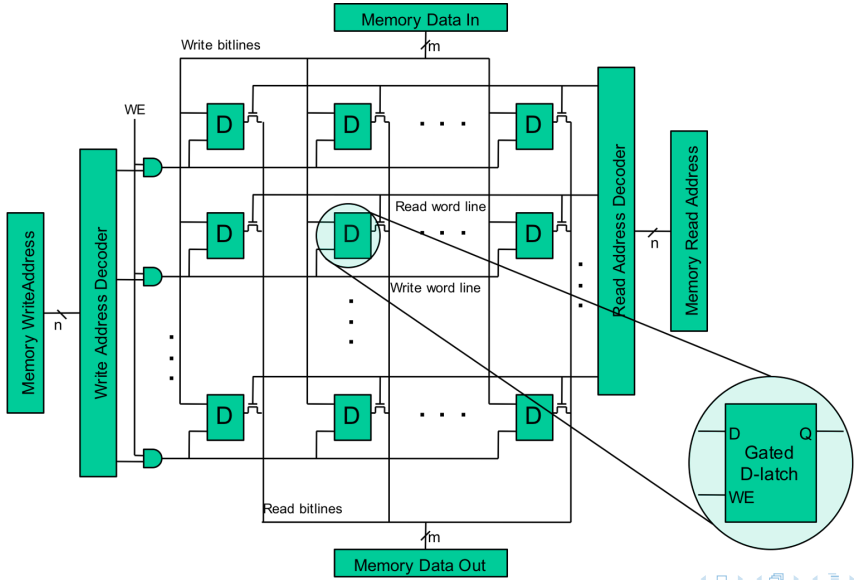
 
# Array Architecture




- ▶  $2^n$  words of  $2^m$  bits each
- ▶ How to design if  $n \gg m$ ?
- ▶ Fold by  $2^k$  into fewer rows of more columns



 
# Decoders




- ▶  $n:2^n$  decoder consists of  $2^n$  n-input AND gates
  - ▶ One needed for each row of memory
  - ▶ Build **AND** with **NAND** or **NOR** gates



## Static CMOS

 


## Using **NOR** gates

 
 
# EX. Decoder




- ▶ Question: AND gates => NAND gate structure


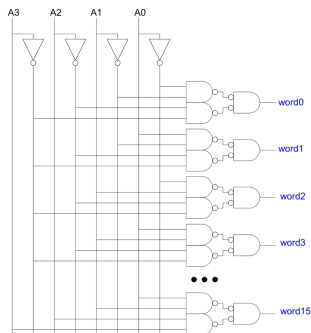
# Larger Decoder




- ▶ For  $n > 4$ , NAND gates become slow
  - ▶ Break large gates into multiple smaller gates


 
# Predecoding



- ▶ Many of these gates are redundant
  - ▶ Factor out common gates
  - ▶ => Predecoder
  - ▶ Saves area
  - ▶ Same path effort




▶ **Question:** How many NANDs can be saved?
 
# \*Decoder Layout




- ▶ Decoders must be pitch-matched to SRAM cell
  - ▶ Requires very skinny gates




 
# \*Column Circuitry

- ▶ Some circuitry is required for each column
  - ▶ Bitline conditioning
  - ▶ Column multiplexing
  - ▶ Sense amplifiers (DRAM)







# \*Bitline Conditioning



- ▶ Precharge bitlines high before reads

 

 
- ▶ Equalize bitlines to minimize voltage difference when using sense amplifiers




 
# \*Twisted Bitlines



- ▶ Sense amplifiers also amplify noise
  - ▶ Coupling noise is severe in modern processes
  - ▶ Try to couple equally onto bit and bit\_b
  - ▶ Done by twisting bitlines



# \*SRAM Column Example

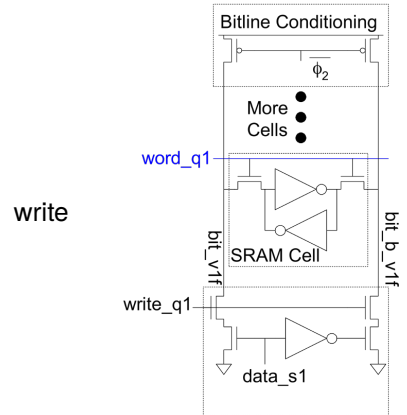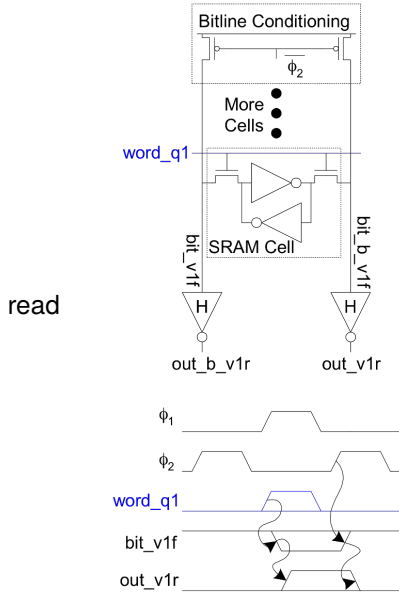


# \*Column Multiplexing



- ▶ Recall that array may be folded for good aspect ratio
- ▶ Ex: 2 kword x 16 folded into 256 rows x 128 columns
  - ▶ Must select 16 output bits from the 128 columns
  - ▶ Requires 16 8:1 column multiplexers




# \*Ex: 2-way Muxed SRAM

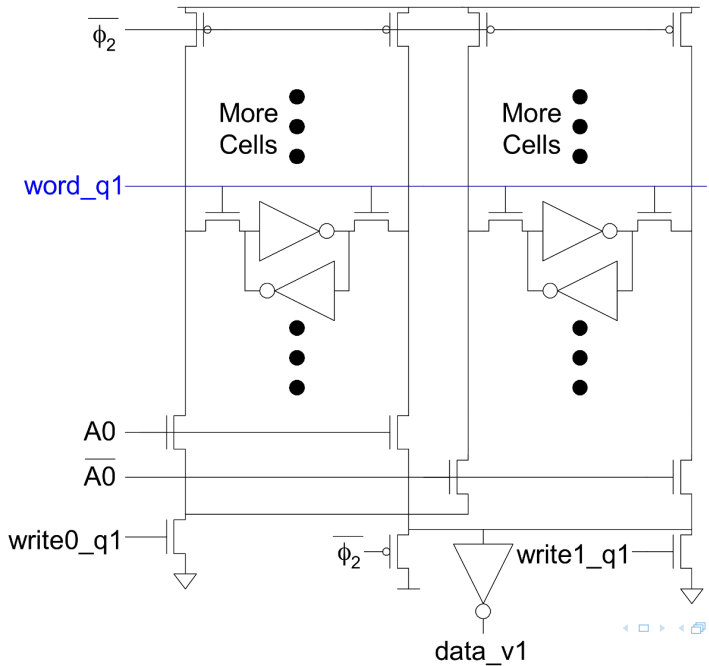



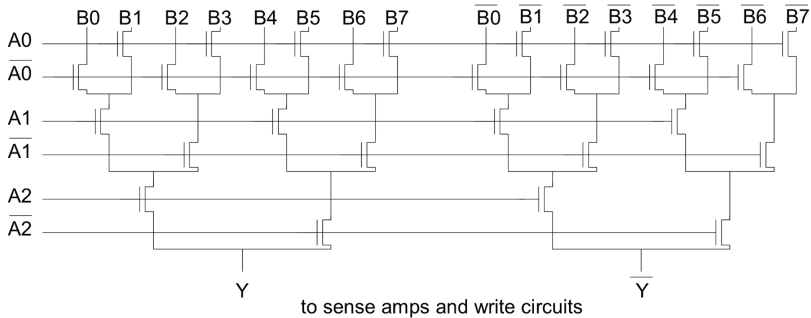
# \*Tree Decoder Mux


- ▶ Column mux can use pass transistors
  - ▶ Use nMOS only, precharge outputs
- ▶ One design is to use k series transistors for  $2^k:1$  mux
  - ▶ No external decoder logic needed



# \*SRAM from ARM

 

# Sense Amp Operation for 1T DRAM

 

- ▶ 1T DRAM read is destructive
- ▶ Read and refresh for 1T DRAM



# \*Sense Amplifiers (DRAM)




- ▶ Bitlines have many cells attached
  - ▶ Ex: 32-kbit SRAM has 256 rows x 128 cols
  - ▶ 256 cells on each bitline
- ▶  $t_{pd} \propto (C/I)\Delta V$ 
  - ▶ Ex: Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
  - ▶ Discharged slowly through small transistors (small I)
- ▶ Sense amplifiers are triggered on small voltage swing (reduce  $\Delta V$ )




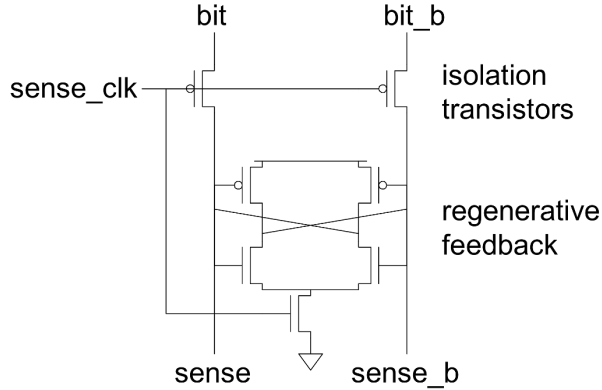
# \*Clocked Sense Amp

- ▶ Clocked sense amp saves power
- ▶ Requires sense\_clk after enough bitline swing
- ▶ Isolation transistors cut off large bitline capacitance





Thank You :)