

B3. Memory—1

Bei Yu


Reference:

- **Chapter 11 Memories**
- **CMOS VLSI Design—A Circuits and Systems Perspective**
- **by H.E.Weste and D.M.Harris**

CEG4480 v.s. CEG3420

- CEG3420:
 - ◆ architecture perspective
 - ◆ memory coherent
 - ◆ data address
- CEG4480: more details on how data is stored


Memory Arrays

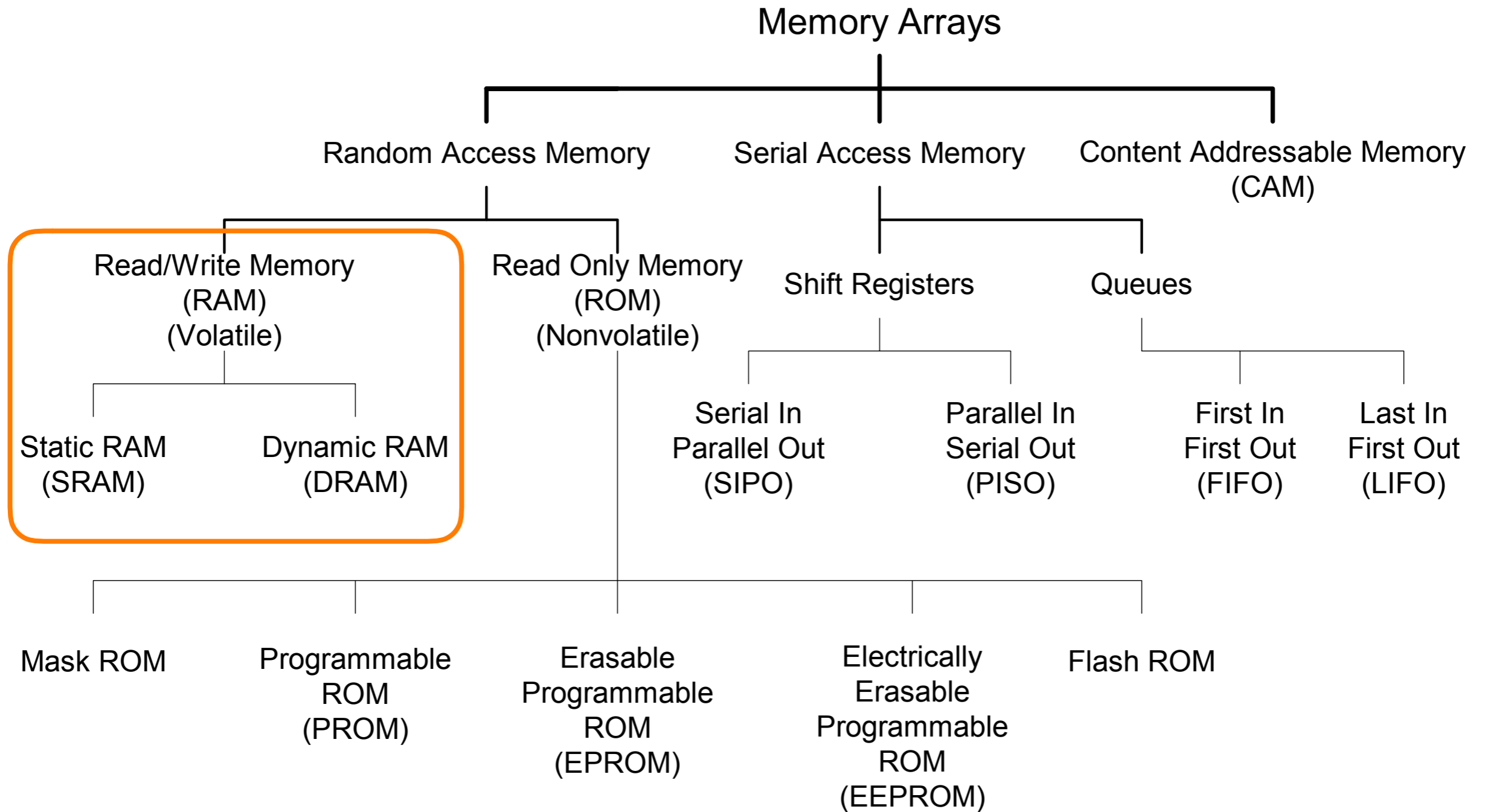

Combinational v.s. Sequential


- **Combinational Circuit**
 - ◆ Always gives the same output for a given set of inputs
 - ◆ E.g., adders
- **Sequential Circuit**
 - ◆ Store information
 - ◆ Output depends on stored information
 - ◆ E.g., counter
 - ◆ Need a **storage** element

Memory Arrays

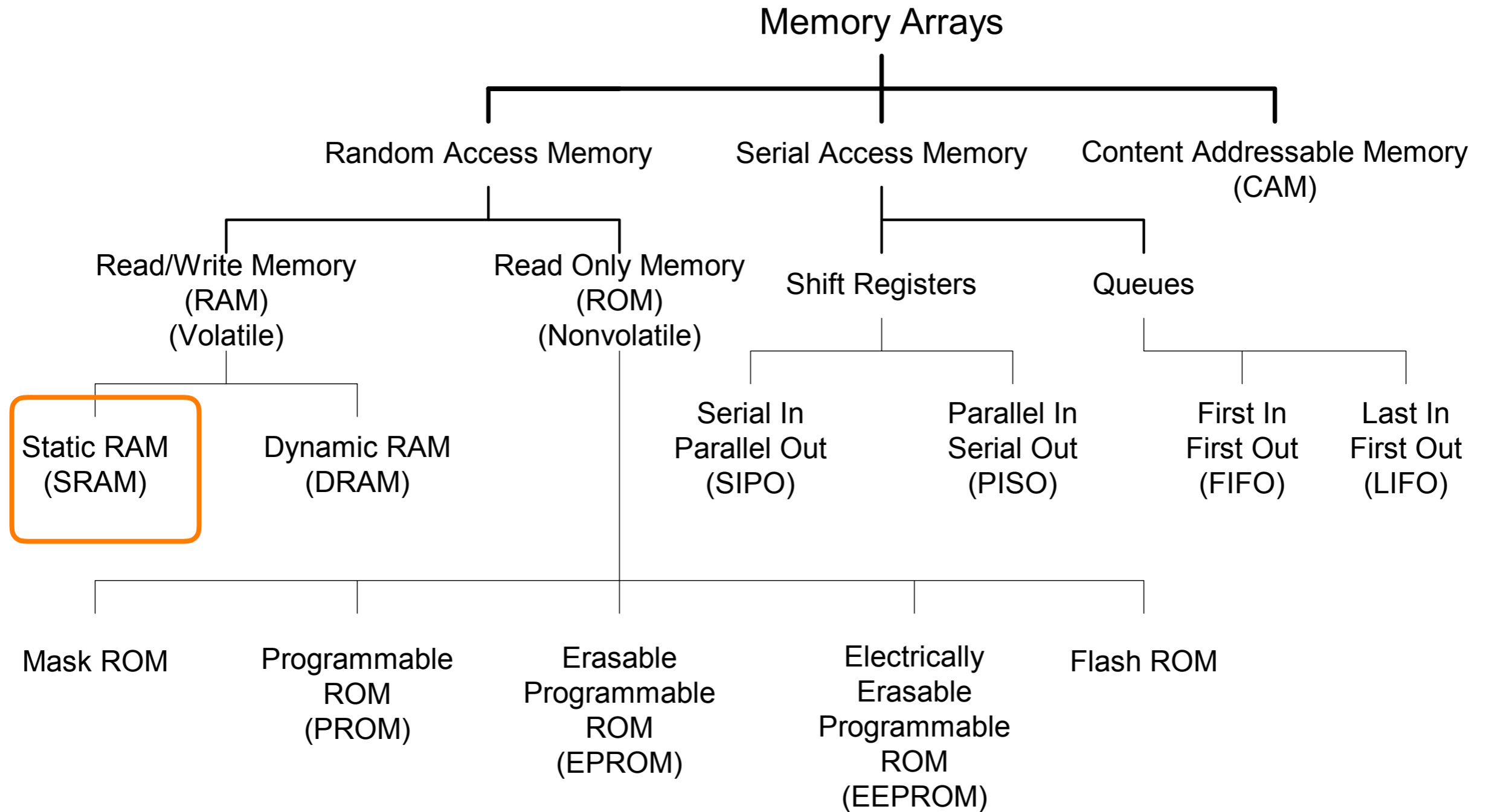


Storage based on Feedback

 - What if we add feedback to a pair of inverters?




 
- Usually drawn as a ring of **cross-coupled** inverters
- Stable way to store one bit of information (**w. power**)



How to change the value stored?

- Replace inverter with NAND gate
- RS Latch


A	B	A nand B
0	0	1
0	1	1
1	0	1
1	1	0

  

EX. RS Latch Summary


- **Question:** What's the Q value based on different R, S input.
 - ♦ R=S=1:
 - ♦ S=0, R=1:
 - ♦ S=1, R=0:
 - ♦ R=S=0:

A	B	A nand B
0	0	1
0	1	1
1	0	1
1	1	0

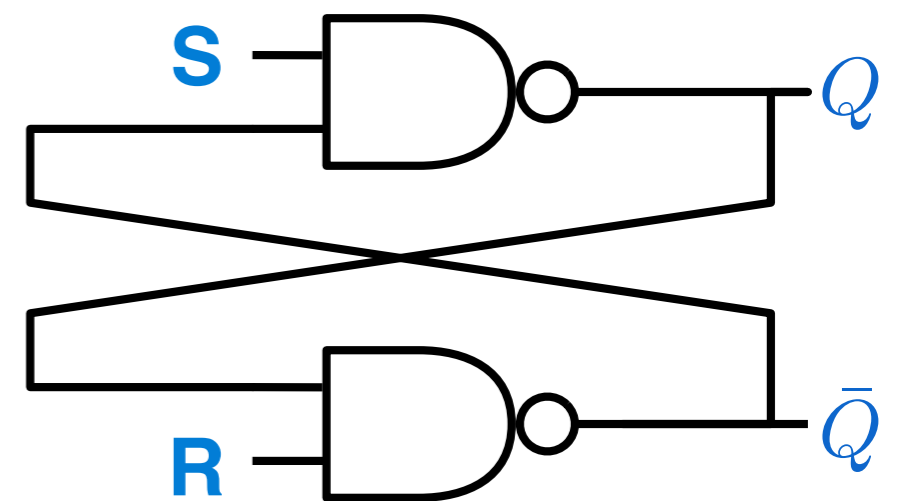


Gated D-Latch

 - Two inputs: **D** (data) & **WE** (write enable)
- When $WE=1$, $S=NOT(D)$, $R=D$;
- When $WE=0$, $S=R=1$





EX. Gated D-Latch

 

 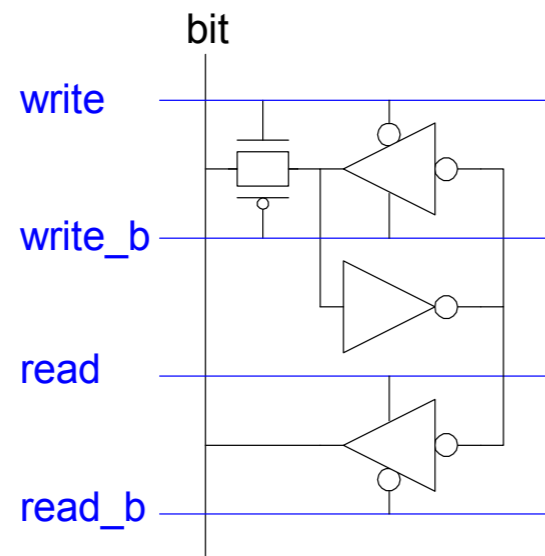- **Question 1:** will S & R be zero at the same time?
- **Question 2:** out values when
 - ♦ WE=1:
 - ♦ WE=0:

12T SRAM Cell

- Basic building block: SRAM Cell
 - ♦ Holds one bit of information, **like a latch**
 - ♦ Must be read and written
- 12-transistor (**12T**) SRAM cell
 - ♦ Use a simple latch connected to bitline
 - ♦ 46 x 75 λ unit cell



nMOS, pMOS, Inverter

- nMOS:



- ◆ Gate = 1, transistor is ON
- ◆ Then electric current path

- pMOS:

- ◆ Gate = 0, transistor is ON
- ◆ Then electric current path


- Inverter:

- ◆ $Q = \text{NOT}(A)$

 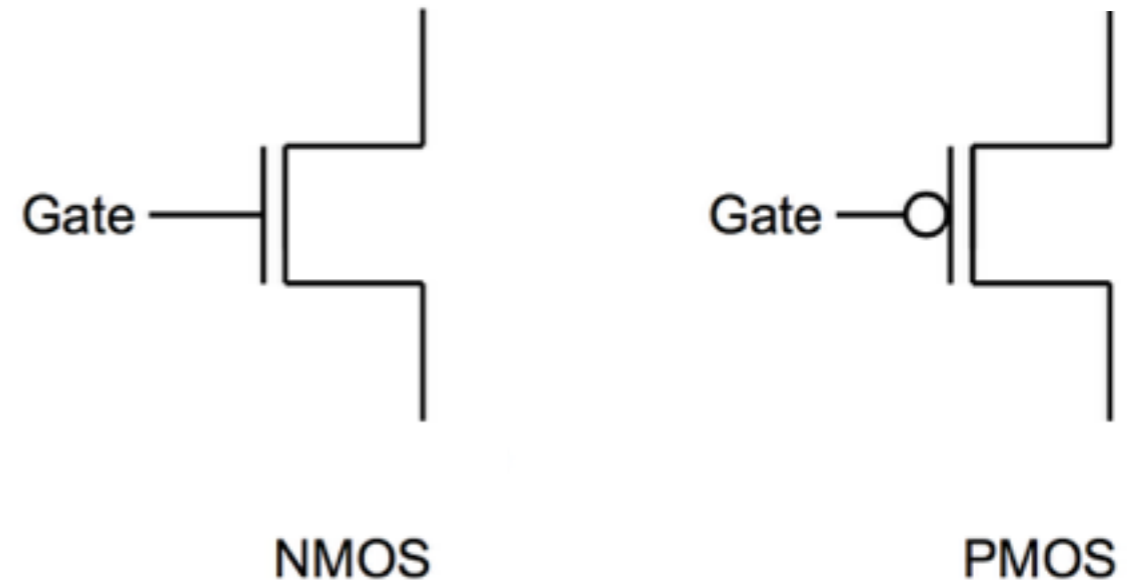



6T SRAM Cell

 - Used in most commercial chips
- A pair of **weak** cross-coupled inverters
- Data stored in cross-coupled inverters
- Compared with 12T SRAM, 6T SRAM:
 - ◆ (+) reduce area
 - ◆ (-) much more complex control




6T SRAM Read

  - Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- **Read stability**
 - A must not flip
 - $N1 \gg N2$





EX: 6T SRAM Read

 - **Question 1:** $A = 0$, $A_b = 1$, discuss the behavior:
- **Question 2:** At least how many bit lines to finish read?




6T SRAM Write

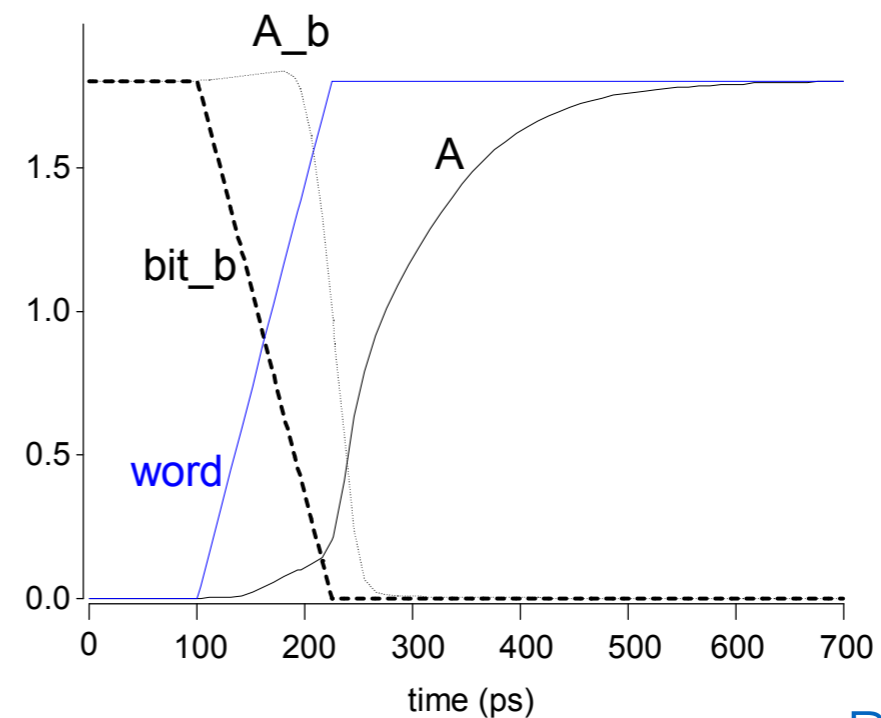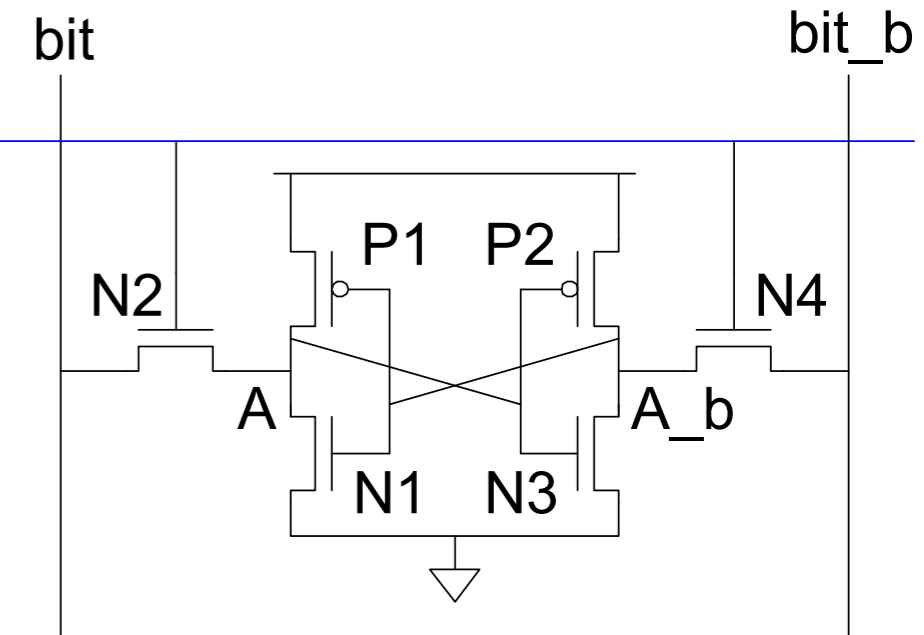- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- **Writability**
 - Must overpower feedback inverter
 - $N4 \gg P2$
 - $N2 \gg P1$ (symmetry)




6T SRAM Sizing

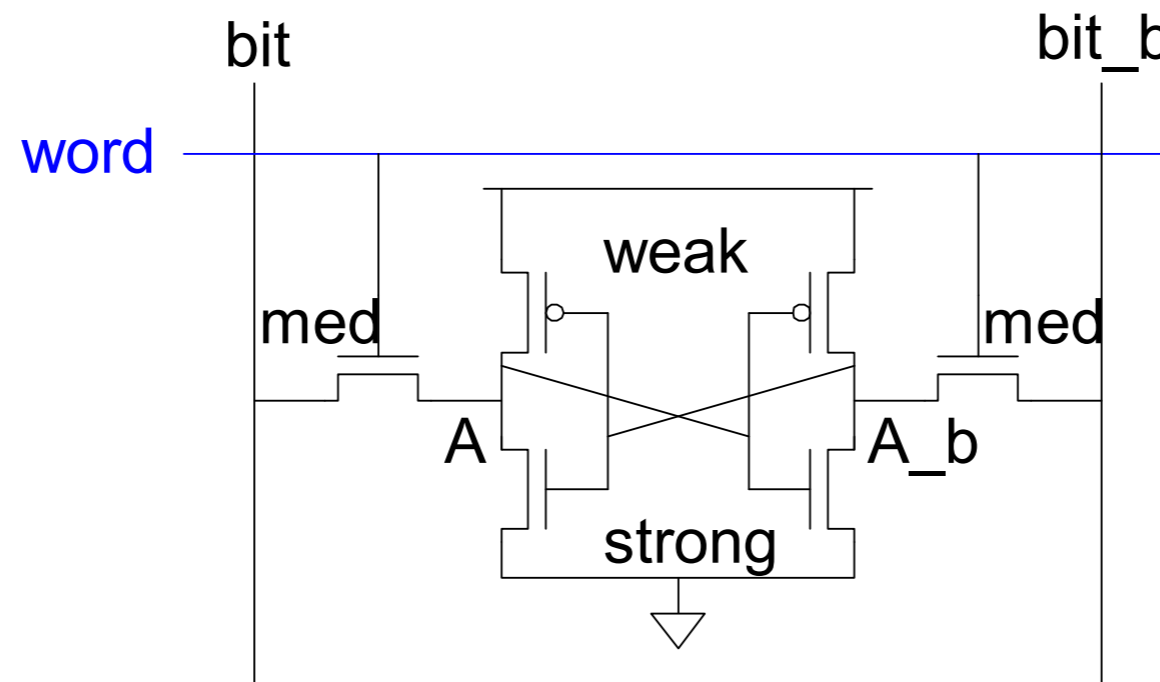- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell



Memory Arrays

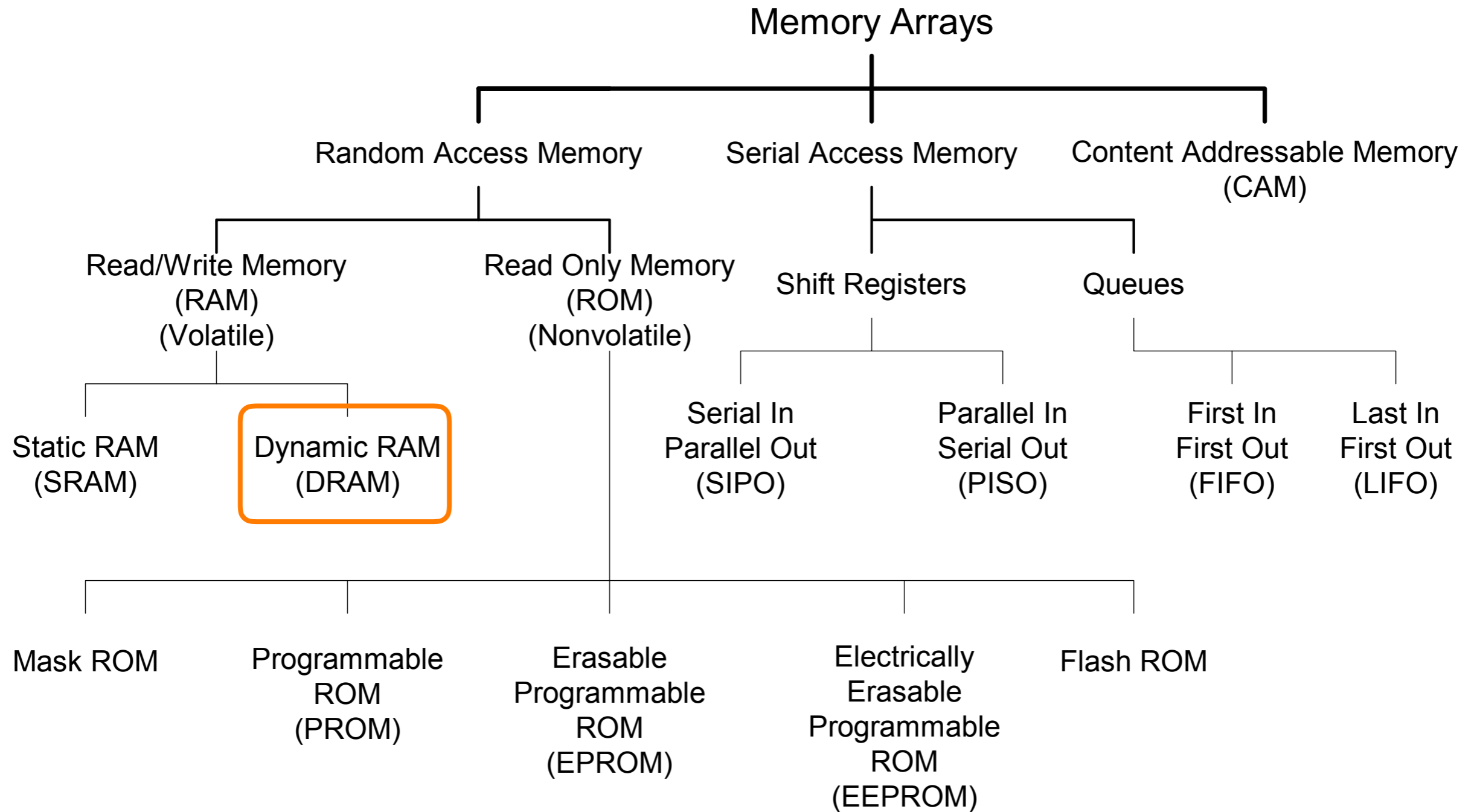


Dynamic RAM (DRAM)

- Basic Principle: Storage of information on **capacitors**
- **Charge & discharge** of capacitor to change stored value
- Use of transistor as “switch” to:
 - ♦ Store charge
 - ♦ Charge or discharge

4T DRAM Cell


 
Remove the two p-MOS transistors from static RAM cell, to get a four-transistor dynamic RAM cell.





- Data must be refreshed regularly
- Dynamic cells must be designed very carefully
- Data stored as charge on gate capacitors (complementary nodes)

3T DRAM Cell

 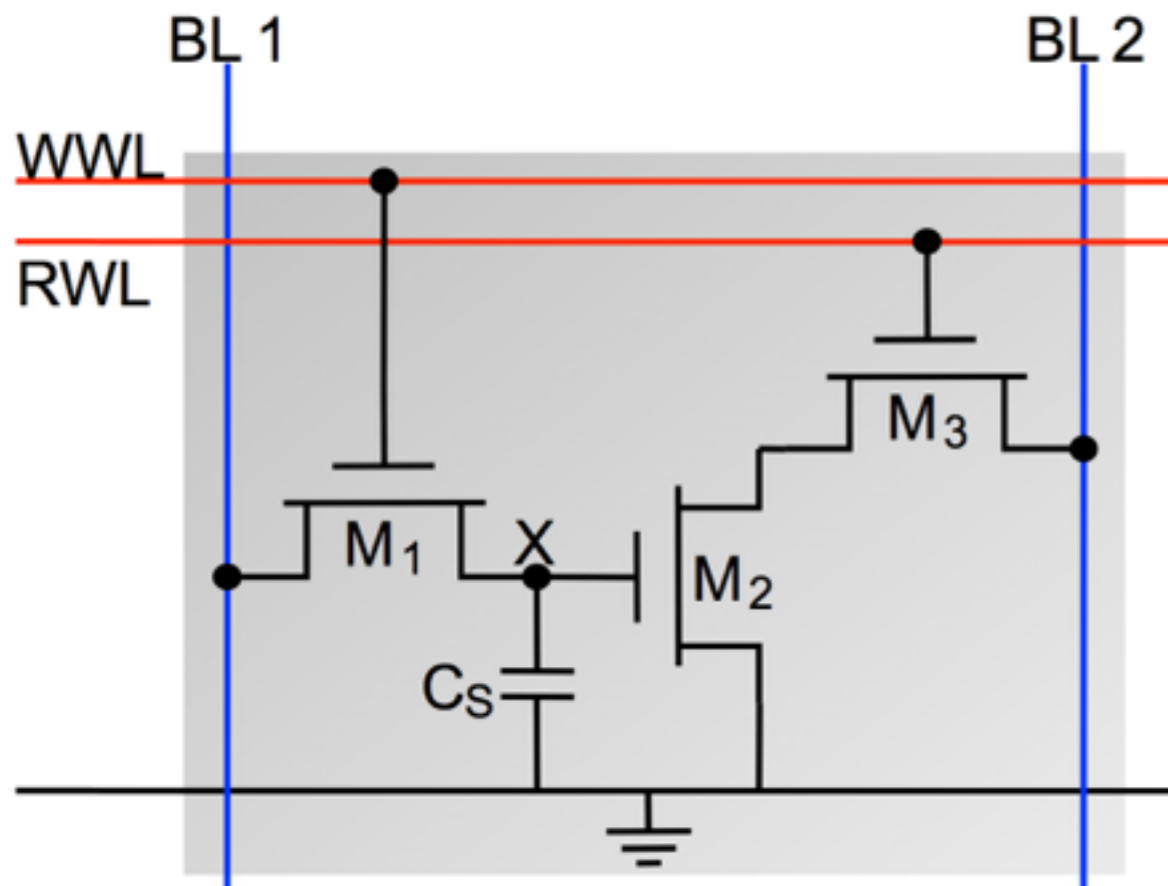- No constraints on device ratios
- Reads are non-destructive
- Value stored at node X when writing a “1” = $V_{DD} - V_T$




3T DRAM Layout

  


[1970: Intel 1003]

- 576 λ 3T DRAM v.s. 1092 λ 6T SRAM
- Further simplified


1T DRAM Cell

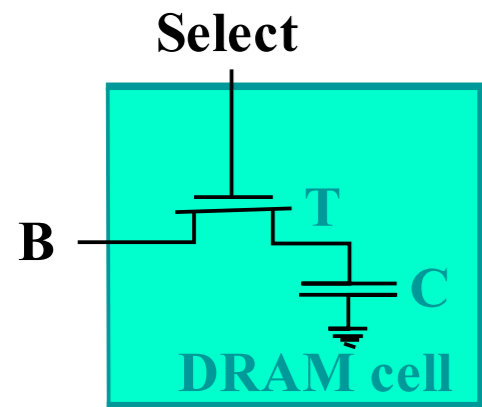


(a)

 


(b)

 


(c)

 


(d)

 

(e)

 


(f)

 

(g)



- Need sense amp helping reading

 

- Read:
 - ◆ Pre-charge large tank to $V_{DD}/2$
 - ◆ If $T_s = 0$, for large tank : $V_{DD}/2 - V_1$
 - ◆ If $T_s = 1$, for large tank: $V_{DD}/2 + V_1$
 - ◆ V_1 is very insignificant
 - ◆ Need sense amp

1T1R DRAM Cell

  - **Write:** C_s is charged or discharged by asserting WL and BL
- **Read:** Charge redistribution takes place between bit line and storage capacitance
- Voltage swing is small; typically around 250 mV



Trench-capacitor cell [Mano87]

EX. 1T DRAM Cell

- **Question:** $V_{DD}=4V$, $C_S=100pF$, $C_{BL}=1000pF$. What's the voltage swing value?
- **Note:**
$$\Delta V = \frac{V_{DD}}{2} \cdot \frac{C_S}{C_S + C_{BL}}$$

SRAM v.s. DRAM

Static (SRAM)


- Data stored as long as supply is applied
- Large (6 transistors/cell)
- Fast
- Compatible with current CMOS manufacturing

Dynamic (DRAM)

- Periodic refresh required
- Small (1-3 transistors/cell)
- Slower
- Require additional process for trench capacitance


Array Architecture

 - 2^n words of 2^m bits each
- Good regularity – easy to design




SRAM Memory Structure

- Latch based memory

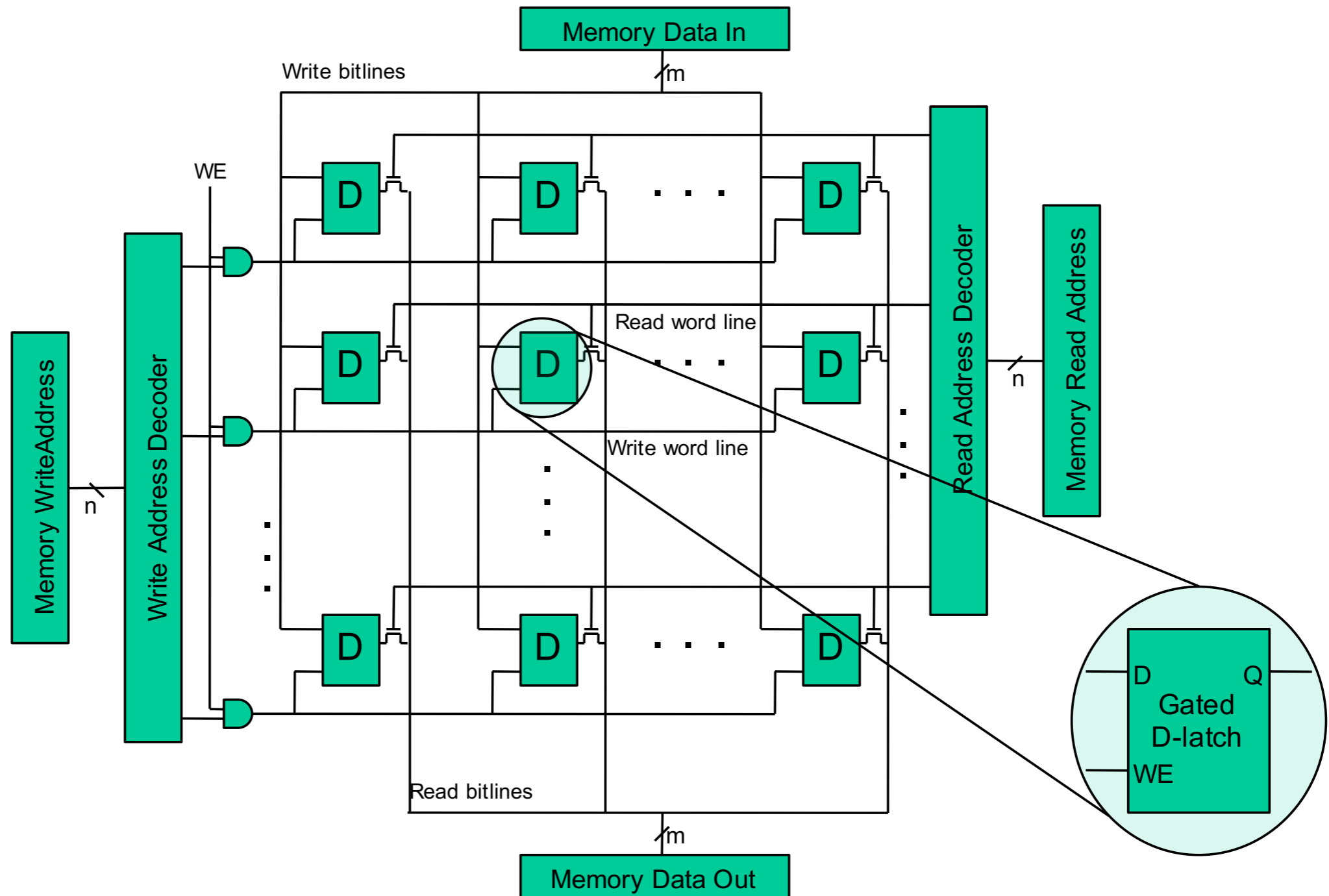

Array Architecture

 - 2^n words of 2^m bits each
- How to design if $n \gg m$?
- Fold by 2^k into fewer rows of more columns





Decoders

- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND with **NAND** or **NOR** gates


Static CMOS

Using **NOR** gates

  


EX. Decoder

 - **Question:** AND gates \Rightarrow NAND gate structure




Large Decoders

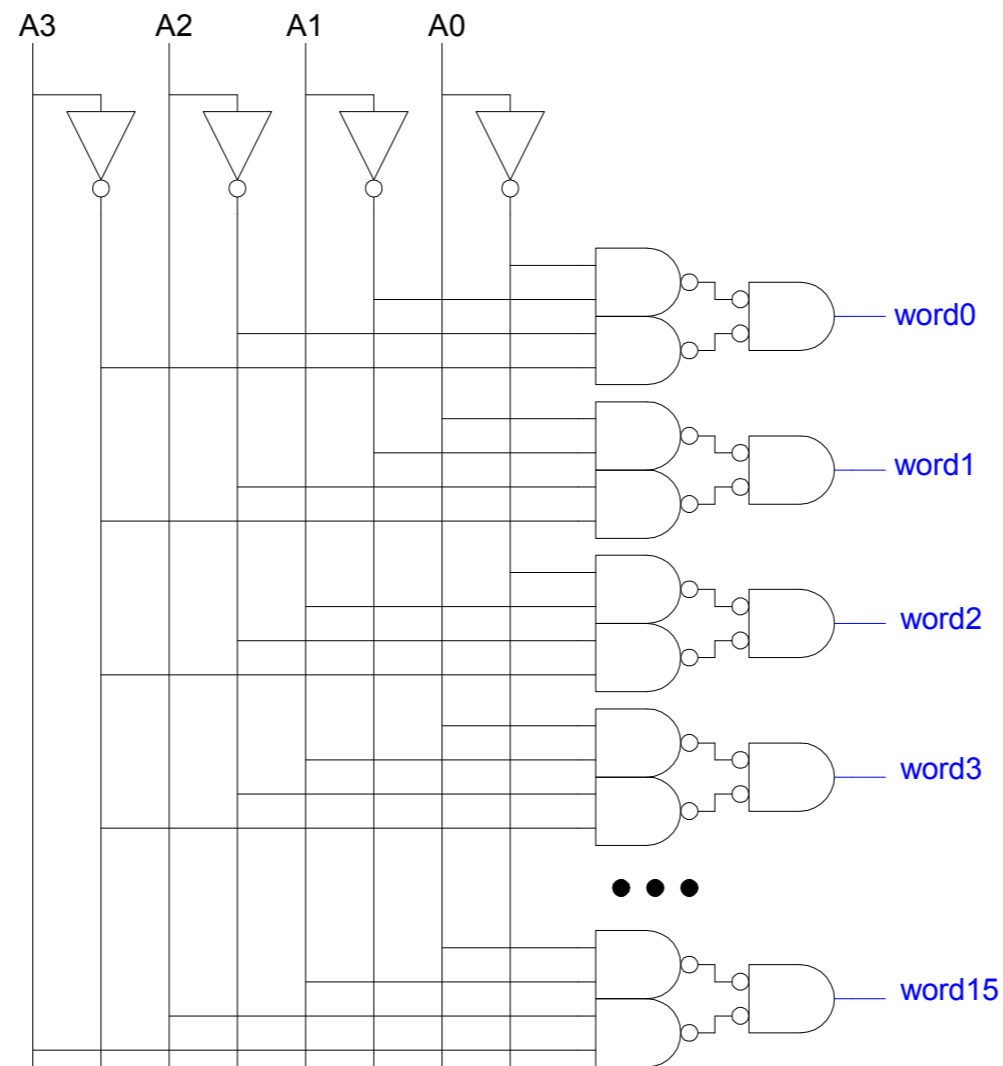- For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates



Predecoding

 
- Many of these gates are redundant
 - Factor out common gates
 - => Predecoder
 - Saves area
 - Same path effort



 - **Question:** How many NANDs can be saved?


Decoder Layout

- Decoders must be pitch-matched to SRAM cell
 - Requires very skinny gates




Column Circuitry

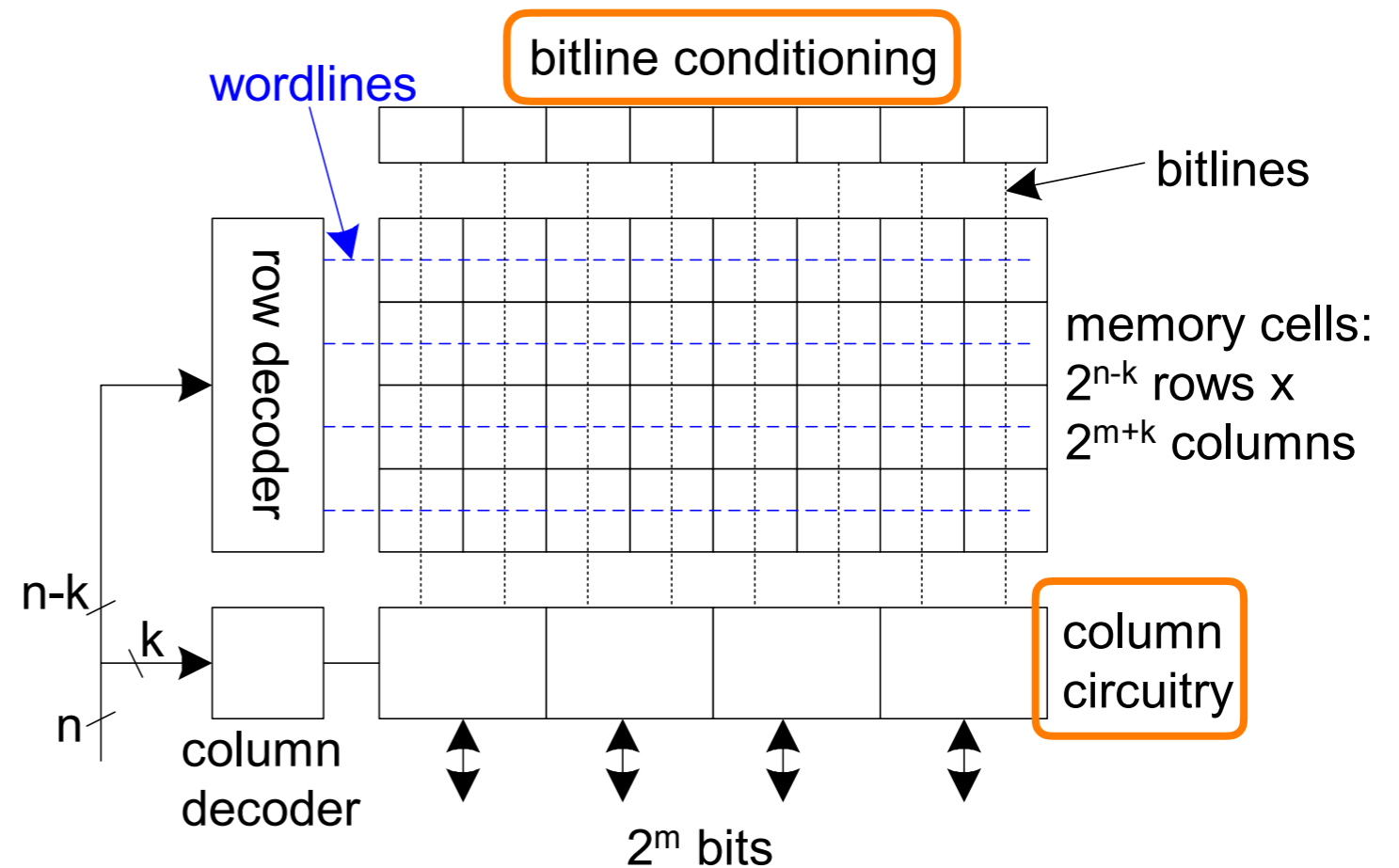- Some circuitry is required for each column
 - Bitline conditioning
 - Column multiplexing
 - *Sense amplifiers (DRAM)




Bitline Conditioning

- Precharge bitlines high before reads

 


 - Equalize bitlines to minimize voltage difference when using sense amplifiers





Twisted Bitlines

 - Sense amplifiers also amplify noise
 - Coupling noise is severe in modern processes
 - Try to couple equally onto bit and bit_b
 - Done by *twisting* bitlines




SRAM Column Example

  

Column Multiplexing


- Recall that array may be folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
 - Must select 16 output bits from the 128 columns
 - Requires 16 8:1 column multiplexers

Ex: 2-way Muxed SRAM

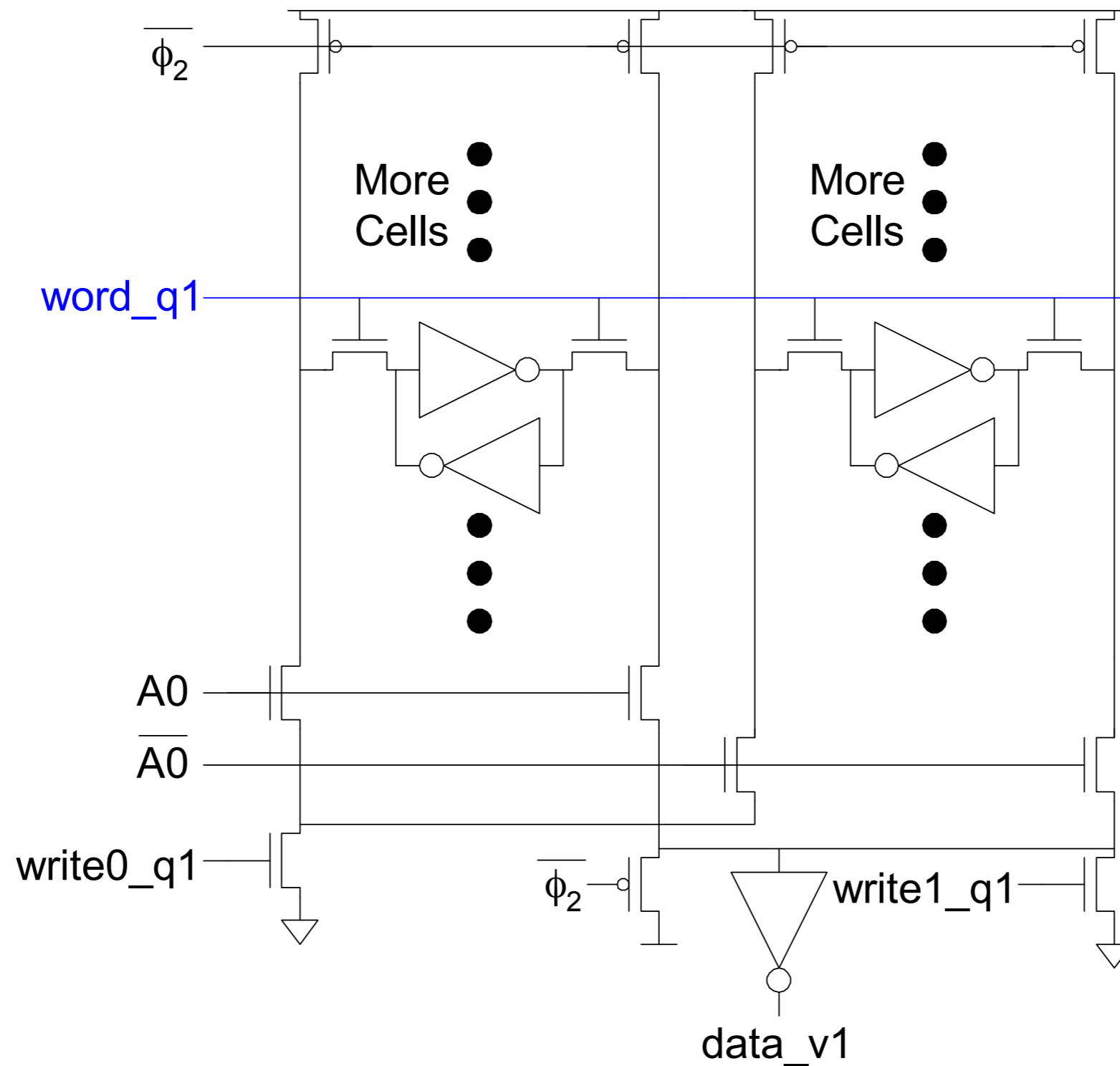

Tree Decoder Mux

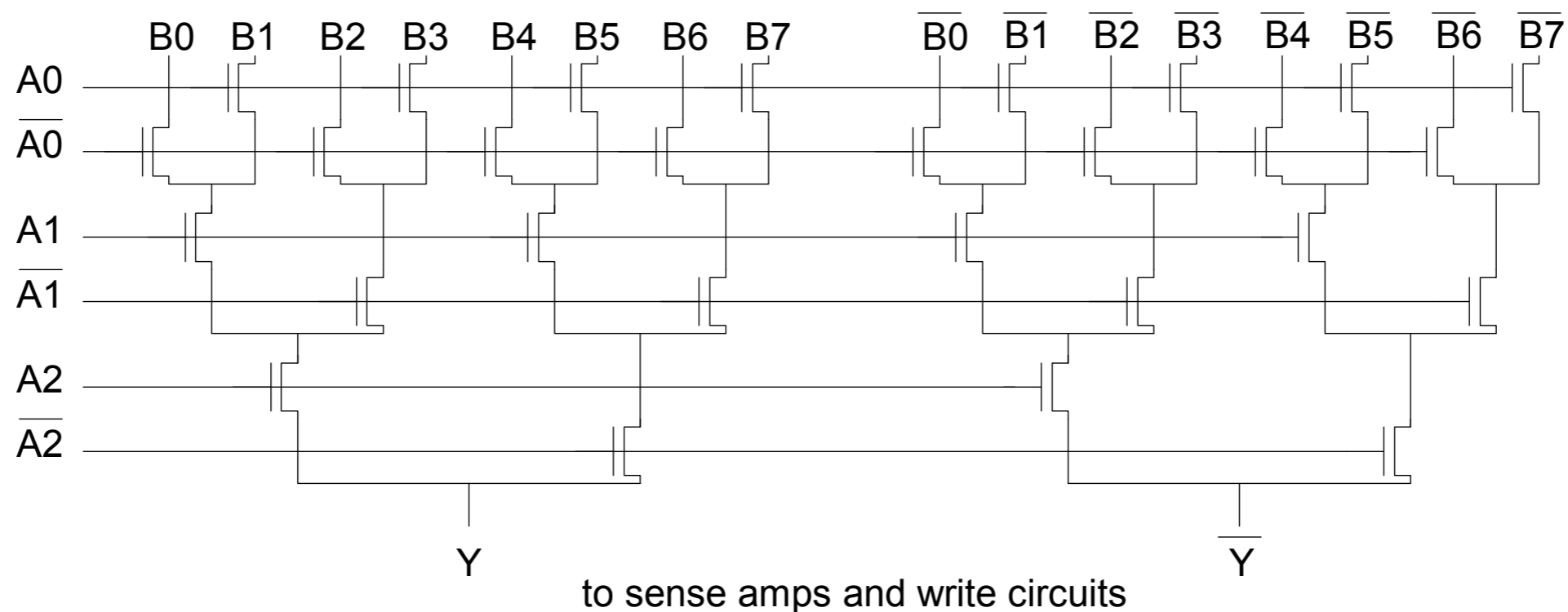- Column mux can use pass transistors
 - Use nMOS only, precharge outputs
- One design is to use k series transistors for $2^k:1$ mux
 - No external decoder logic needed




*Sense Amplifiers (DRAM)


- Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 256 rows x 128 cols
 - 256 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- Sense amplifiers are triggered on small voltage swing (reduce ΔV)

*Differential Pair Amp

 - Differential pair requires no clock
- But always dissipates static power



*Sense Amp Operation for 1T DRAM

 

- 1T DRAM read is destructive
- Read and refresh for 1T DRAM

Thank You :-)