

CENG4480 2021F Homework 1

Due: Oct. 24, 2021

Solutions

All solutions should be submitted to the blackboard in the format of **PDF/MS Word**.

- Q1** (10%) The following circuit Figure 1 is a difference amplifier circuit. $U_1 = 40V$, $U_2 = 25V$, $R_1 = 6\Omega$, $R_2 = 4\Omega$, $R_3 = 15\Omega$, $R_4 = 20\Omega$. Please calculate the output voltage of U_o .

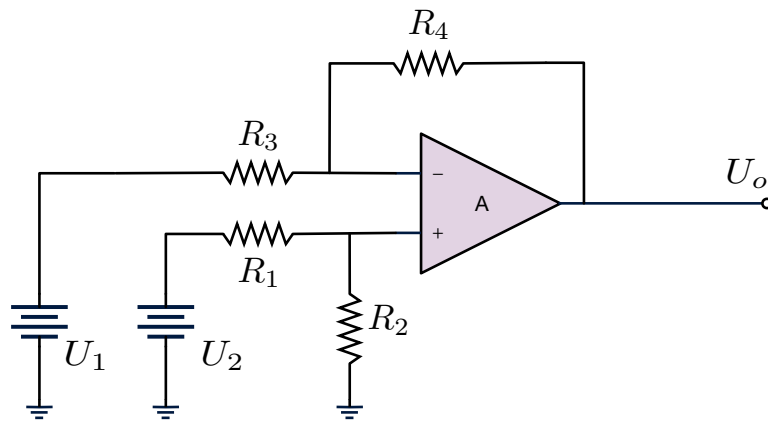


Figure 1: Q1 Circuit

A1 By voltage division,

$$U_{in+} = U_2 \times \frac{R_2}{R_1 + R_2} = 25V \times \frac{4\Omega}{6\Omega + 4\Omega} = 10V$$

By the virtual short circuit between the input terminals, $U_{in-} = U_{in+} = 10V$, the current through the 15Ω is

$$I_3 = \frac{U_1 - U_{in-}}{R_3} = \frac{40V - 10V}{15\Omega} = 2A$$

The input impedance is infinite; therefore, $I_{in-} = 0$ and $I_3 = I_4 = 2A$. Based on Kirchoff's voltage law to find the output voltage

$$U_o = U_{in-} - R_4 \times I_4 = 10V - 20\Omega \times 2A = -30V$$

- Q2** (20%) Given an ideal op-amp circuit below where $R_1 = 1k\Omega$, $R_2 = 2k\Omega$, $R_3 = 3k\Omega$, if I want to obtain a gain of 5, what's the value of the resistor R_4 as shown in the circuit?

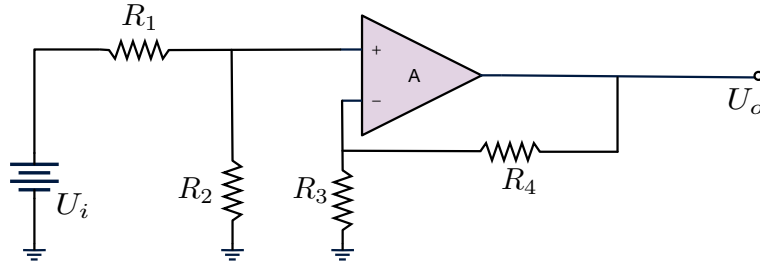


Figure 2: Q2 Circuit

A2 By voltage division,

$$U_{in+} = U_i \times \frac{R_2}{R_1 + R_2} = U_i \times \frac{2\text{k}\Omega}{3\text{k}\Omega} = \frac{2}{3}U_i \quad (1)$$

By the virtual short circuit,

$$U_{in-} = U_{in+} = \frac{2}{3}U_i \quad (2)$$

$$I_3 = \frac{U_{in-}}{3\text{k}\Omega} = \frac{\frac{2}{3}U_i}{3\text{k}\Omega} \quad (3)$$

And

$$\frac{U_o - U_{in-}}{R_4} = \frac{\frac{2}{3}U_i}{3\text{k}\Omega} \quad (4)$$

$$U_o = 5U_i \quad (5)$$

Therefore

$$R_4 = 19.5\text{k}\Omega$$

Q3 (20%) Given the following amplifier circuit as shown in Figure 3. $R_1 = 1\text{M}\Omega$, $R_2 = 500\text{k}\Omega$ and $R_3 = 100\Omega$. Also, I want to acquire a voltage gain $U_o/U_i = -120$, how to choose the value of R_4 ?

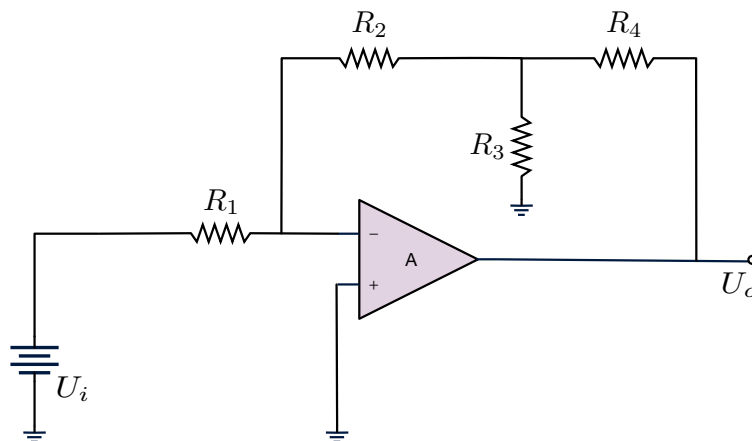


Figure 3: Q3 Circuit

A3 U_{in+} is grounded, so U_{in-} is also a virtual ground. So

$$U_{in-} = 0$$

Since $U_{in-} = 0$, $U_i = I_1 R_1$ and $I_1 = U_i / R_1$. Since $U_{in+} = 0$, $U_x = -I_2 R_2$ and $I_2 = -U_x / R_2$. Similarly

$$U_x = -I_3 R_3 \quad (6)$$

$$U_x - U_o = I_4 R_4 \quad (7)$$

From Kirchhoff's current law,

$$I_4 = I_2 + I_3 \quad (8)$$

$$\frac{U_x - U_o}{R_4} = \frac{-U_x}{R_2} + \frac{-U_x}{R_3} \quad (9)$$

$$U_o = -120U_i \quad (10)$$

Also,

$$I_1 = I_2 \quad (11)$$

So,

$$\frac{U_i}{R_1} = \frac{-U_x}{R_2} \quad (12)$$

$$U_x = -\frac{R_2}{R_1} U_i \quad (13)$$

$$\frac{-\frac{R_2}{R_1} U_i - (-120U_i)}{R_4} = \frac{\frac{R_2}{R_1} U_i}{R_2} + \frac{\frac{R_2}{R_1} U_i}{R_3} \quad (14)$$

Therefore

$$R_4 = \frac{120 \frac{R_1}{R_2} - 1}{\frac{R_2 + R_3}{R_2 R_3}} = 2.39 \times 10^4 \Omega \quad (15)$$

Q4 (20%) The diagram of amplifier circuit is shown in fig. 4. Given $R_1 = 4\text{k}\Omega$, $R_2 = 6\text{k}\Omega$ and $R_3 = 12\text{k}\Omega$, answer the following questions.

1. Find the output voltage U_o if $U_a = 4\text{V}$ and $U_b = -12\text{V}$.
2. When $U_b = -12\text{V}$, determine the range of U_a for linear operation if the saturation voltage of op-amp is $\pm 12\text{V}$.

A4 1. Obviously this is a summing amplifier.

$$U_o = -\left(\frac{R_3}{R_1} U_a + \frac{R_3}{R_2} U_b\right) \quad (16)$$

$$= -\left(\frac{12}{4} \times 4 + \frac{12}{6} \times (-12)\right) \quad (17)$$

$$= 12\text{V} \quad (18)$$

2. For linear operation,

$$\pm 12 = -\left(\frac{12}{4} U_a + \frac{12}{6} \times (-12)\right) \quad (19)$$

$$= -3U_a + 24 \quad (20)$$

Therefore, $4\text{V} < U_a < 12\text{V}$.

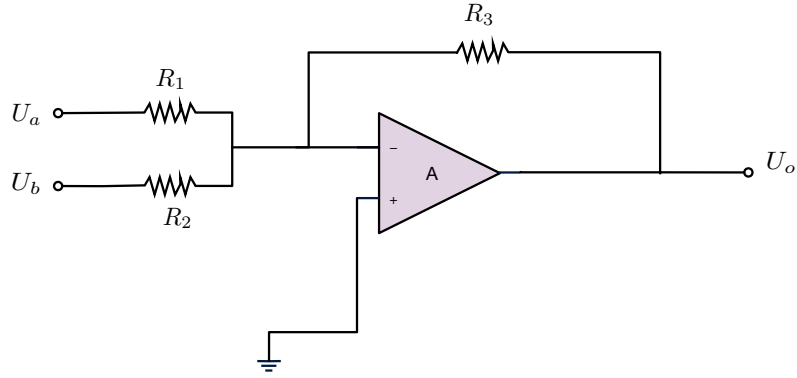


Figure 4: Q4 Circuit Diagram

Q5 (20%) In the circuit of Figure 5, $R_3 = R_4 = R_5 = R_6 = R_7 = R = 2R_1 = 2R_2 = 100\text{k}\Omega$ and $C = 1\mu\text{F}$. Assume the op-amps are ideal. What is the relationship between U_i and U_o ?

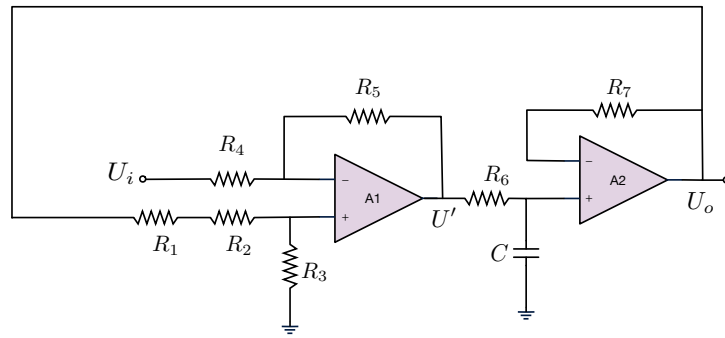


Figure 5: Q5 Circuit Diagram

A5 1. As the amplifier is ideal,

$$\frac{R_3}{R_1 + R_2 + R_3} \times U_o = U_i - \frac{U_i - U'}{R_4 + R_5} \times R_4 \quad (21)$$

Therefore,

$$\frac{U_o}{2} = U_1 - \frac{U_i - U'}{2} \quad (22)$$

$$U_o = U_i + U' \quad (23)$$

The voltage on the capacitance $U_c = U_o$, so the current of the capacitance is

$$i_C = \frac{U' - U_o}{R} = -\frac{U_i}{R} \quad (24)$$

And

$$U_o(t) = \frac{1}{C} \int_{-\infty}^t i_c(\lambda) d\lambda = -\frac{1}{RC} \int_{-\infty}^t U_i(\lambda) d\lambda = -10 \int_{-\infty}^t U_i(\lambda) d\lambda \quad (25)$$

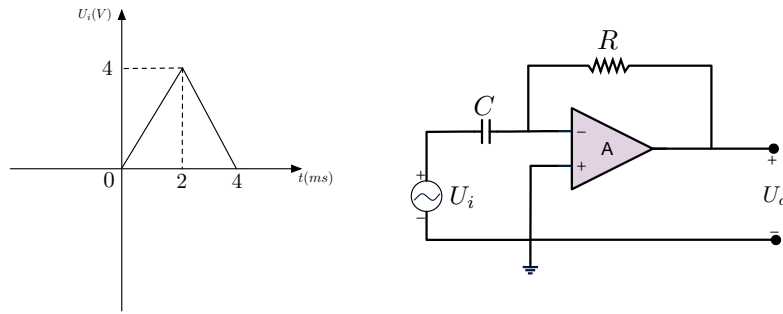


Figure 6: Q6 Circuit and Input Voltage Waveform

Q6 (10%) Draw the output voltage waveform given the input voltage waveform and the circuit in Figure 6. In the circuit, $R = 5k\Omega$ and $C = 0.2\mu F$.

A6 The input voltage is:

$$U_i = \begin{cases} 2000t, & 0 < t < 2 \text{ ms} \\ 8 - 2000t, & 2 \leq t < 4 \text{ ms} \end{cases}$$

The output voltage is given by:

$$U_o = -RC \frac{dU_i}{dt} = \begin{cases} -2V, & 0 < t < 2 \text{ ms} \\ 2V, & 2 \leq t < 4 \text{ ms} \end{cases}$$

The waveform is as follows:

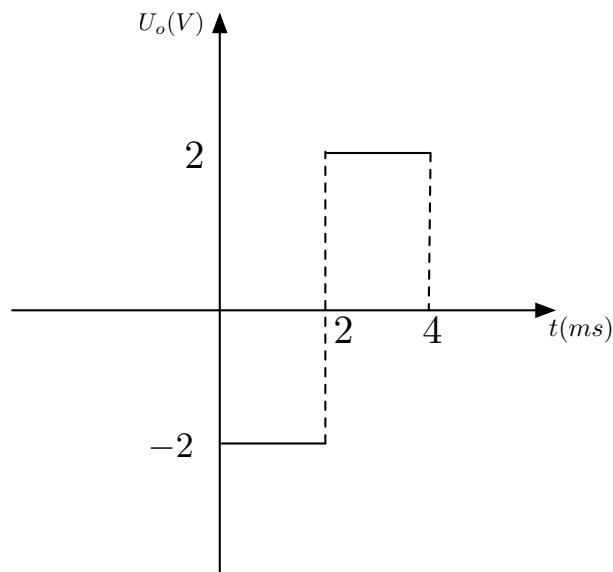


Figure 7: Q6 solution