

CENG 4480 Midterm (Fall 2021)

Name: _____

ID: _____

Solutions

Q1 (30%) Check or fill the correct answer:

1. A circuit where the input signal power is less than the output signal power is called **amplifier/attenuator**.
2. In an ideal op amplifier, $V_{in+} > / = / < V_{in-}$, since it has **infinite/finite** open-loop gain.
3. An amplifier with input voltage of 1mv and output voltage 1V has gain ___ dB.
4. A capacitor can be regarded as a short circuit when a **high/low** frequency signal is input.
5. A 5-bit D/A converter has a voltage output. For a binary input of 10100, an output voltage of 12 mV is produced. When the binary input is 11100, the output voltage is ___ mV
6. ___ is the minimum number of bits required to digitize an analog signal with a resolution of 0.5%. (Resolution is the ratio between minimum voltage that can be sensed and the input voltage range.)
7. Given a differentiator circuit and a triangular wave as input signal, the waveform of the output is **cosine/square**.
8. Bandwidth is defined as the frequency range over which the voltage gain of the amplifier is above 70.7% or ___dB of its maximum output value.
9. The sampling rate of the ADC used depends on the maximum frequency f_{max} of input signal. According to Nyquist sampling theorem, the sampling frequency f_s should be greater or equal to **two/three** times f_{max} .
10. In PID control, decreasing proportional gain will lead to the **faster/slower** response. And we will get **faster/slower** elimination of steady state error by adding integral gain, while **increasing/decreasing** settling time and overshoot with a larger derivative gain.

A1 1. amplifier

2. =, infinite

3. 60

4. high

5. 16.8

6. 8

7. square

8. -3

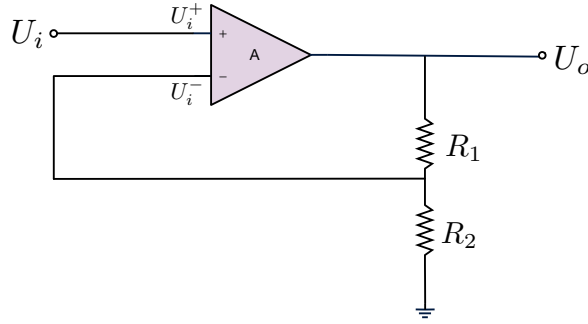


Figure 1: Non-inverting Amplifier.

9. two

10. slower, faster, decreasing

Q2 (20%) Given a non-inverting amplifier as shown in Figure 1. $R_1 = 3R_2$ and $A = 1000$.

(1) Calculate the voltage gain $G = \frac{U_o}{U_i}$.

(2) If the amplifier is ideal ($A = \infty$), compute the voltage gain defined in (1).

A2 From the properties of Op Amplifier,

$$U_o = A_0(U_i^+ - U_i^-) \quad (1)$$

Given that,

$$U_i^- = \frac{R_2}{R_1 + R_2} U_o \quad (2)$$

Substituting into (1) we have,

$$G_{real} = \frac{U_o}{U_i} = \frac{A}{1 + \frac{R_2}{R_1 + R_2} A} \quad (3)$$

Besides,

$$G_{ideal} = \left(1 + \frac{R_1}{R_2}\right) \quad (4)$$

Substituting data into Eqs. (3) and (4),

$$G_{real} = 3.98, G_{ideal} = 4 \quad (5)$$

Q3 (10%) In the circuit of Figure 2, $R_1 = R_2 = 10\text{k}\Omega$, $R_3 = R_4 = 3\text{k}\Omega$, $C_1 = 0.1\mu\text{F}$, $C_2 = 0.05\mu\text{F}$. Calculate the bandwidth of the RC band pass filter.

1.

$$f_l = \frac{1}{2\pi(R_1 // R_2)C_1} = 318.3\text{Hz} \quad (6)$$

$$f_h = \frac{1}{2\pi(R_3 + R_4)C_2} = 530.5\text{Hz} \quad (7)$$

$$\text{bandwidth} = f_h - f_l = 212.2\text{Hz} \quad (8)$$

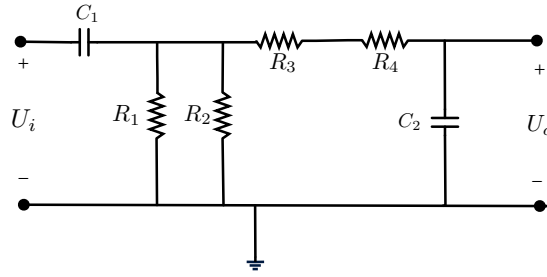


Figure 2: Band Pass Filter

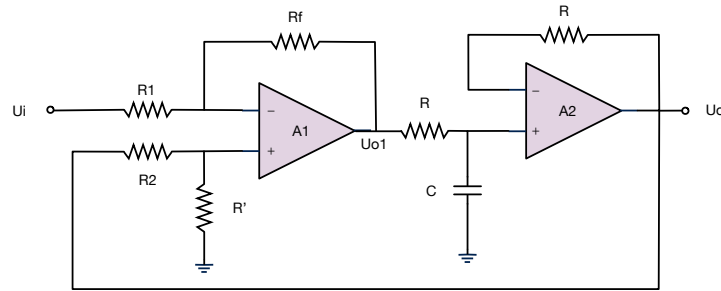


Figure 3: Voltage Follower.

Q4 (20%) In the circuit of Figure 3, $R_1 = R = R' = 100\text{k}\Omega$, $R_2 = R_f = 200\text{k}\Omega$ and $C = 1\mu\text{F}$. Assume the op-amps are ideal.

1. The relationship between U_i and U_o (U_{o1} is unknown).
2. Assume that when the time $t = 0$, $U_o = 0\text{V}$ and U_i jumps from 0V to -1V . How long will the U_o take to change from 0V to 6V ?

1. Because A_2 is a voltage follower (the voltage on the capacitance $U_c = U_o$), so we can obtain U_{o1}

$$U_{o1} = -\frac{R_f}{R_1}U_i + \left(1 + \frac{R_f}{R_1}\right) \frac{R'}{R_2 + R'}U_o = U_o - 2U_i \quad (9)$$

The voltage on the capacitance $U_c = U_o$, so the current of the capacitance is

$$i_C = \frac{U_{o1} - U_o}{R} = -\frac{2U_i}{R} \quad (10)$$

And

$$U_o = \frac{1}{C} \int_{-\infty}^t i_C dt = -\frac{2}{RC} \int_{-\infty}^t U_i dt = -20 \int_{-\infty}^t U_i dt \quad (11)$$

2. We can get $U_o = -20 \int_0^t U_i dt = 20t = 6$. So $t = 0.3\text{sec}$

Q5 (20%) Try to use discrete incremental PID formulations to calculate $\Delta u(t)$. Some notations and values of parameters are given:

- $u(t)$ is the output of a controller in the t th measurement interval.

- $e(t)$ is the error between the target value and measurement value in the t th measurement interval. The error is measured every T time interval ($T = 0.001$).
And $e(t) = 2$, $e(t - 2) = 5$ and $e(t - 1) = 3$.
- The numerical values of PID parameters, K_p , K_i and K_d , are 1, 50, 0.001 respectively.
(Hint: The formulation of continuous PID is $u(t) = K_p e(t) + K_i \int_0^t e(t) dt + K_d \frac{de(t)}{dt}$)

A5

$$u(t) = K_p * e(t) + K_i * \sum e(t) * T + K_d * \frac{e(t) - e(t - 1)}{T} \quad (12)$$

$$u(t - 1) = K_p * e(t - 1) + K_i * \sum e(t - 1) * T + K_d * \frac{e(t - 1) - e(t - 2)}{T} \quad (13)$$

$$\Delta u(t) = K_p * (e(t) - e(t - 1)) + K_i * e(t) * T + K_d * \frac{e(t) - 2e(t - 1) + e(t - 2)}{T} \quad (14)$$

So $\Delta u(t) = 0.1$