



# CENG 4480

## Embedded System Development & Applications

### Lecture 10: Memory 2

Bei Yu

CSE Department, CUHK

[byu@cse.cuhk.edu.hk](mailto:byu@cse.cuhk.edu.hk)

(Latest update: October 27, 2021)

Fall 2021




## CENG3420:

- architecture perspective
- memory coherent
- data address

## CENG4480:

- more details on how data is stored

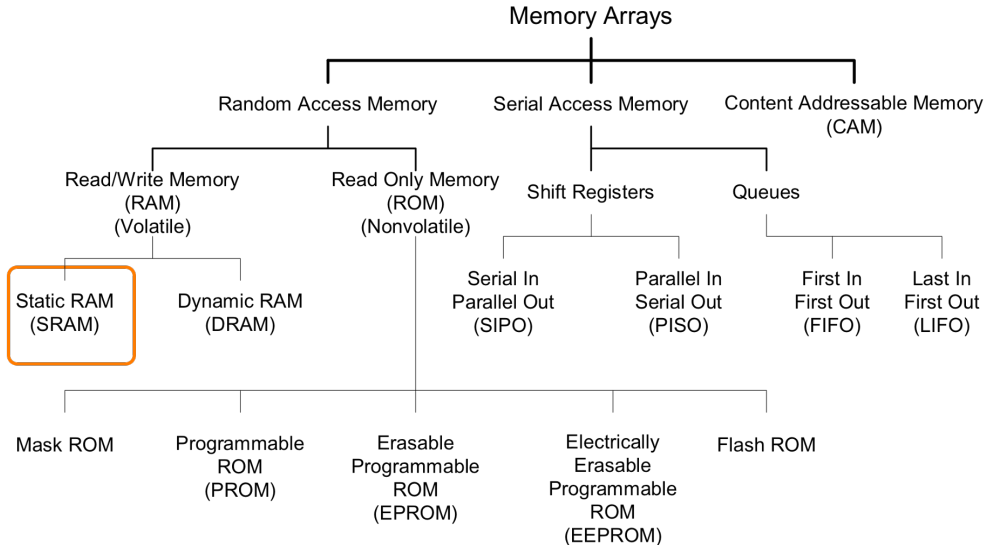




 
# SRAM



- What if we add feedback to a pair of inverters?




 
- Usually drawn as a ring of **cross-coupled** inverters
- Stable way to store one bit of information (w. power)


  
# How to change the value stored?





- Replace inverter with NAND gate
- RS Latch



A	B	A nand B
0	0	1
0	1	1
1	0	1
1	1	0





  - Basic building block: SRAM Cell
  - Holds one bit of information, like a latch
  - Must be read and written
- 12-transistor (12T) SRAM cell
  - Use a simple latch connected to bitline
  - $46 \times 75 \lambda$  unit cell





  
- nMOS:
  - Gate = 1, transistor is ON
  - Then electric current path
- pMOS:
  - Gate = 0, transistor is ON
  - Then electric current path
- Inverter:
  - $Q = \text{NOT}(A)$









 - Used in most commercial chips
- A pair of **weak** cross-coupled inverters
- Data stored in cross-coupled inverters
- Compared with 12T SRAM, 6T SRAM:
  - (+) reduce area
  - (-) much more complex control






  - Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- Read stability
  - A must not flip
  - $N1 \gg N2$







 - **Question 1:**  $A = 0$ ,  $A_b = 1$ , discuss the behavior:
- **Question 2:** At least how many bit lines to finish read?





  
- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- **Writability**
  - Must overpower feedback inverter
  - $N4 \gg P2$
  - $N2 \gg P1$  (symmetry)








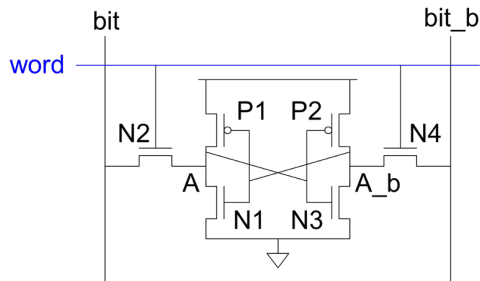- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell



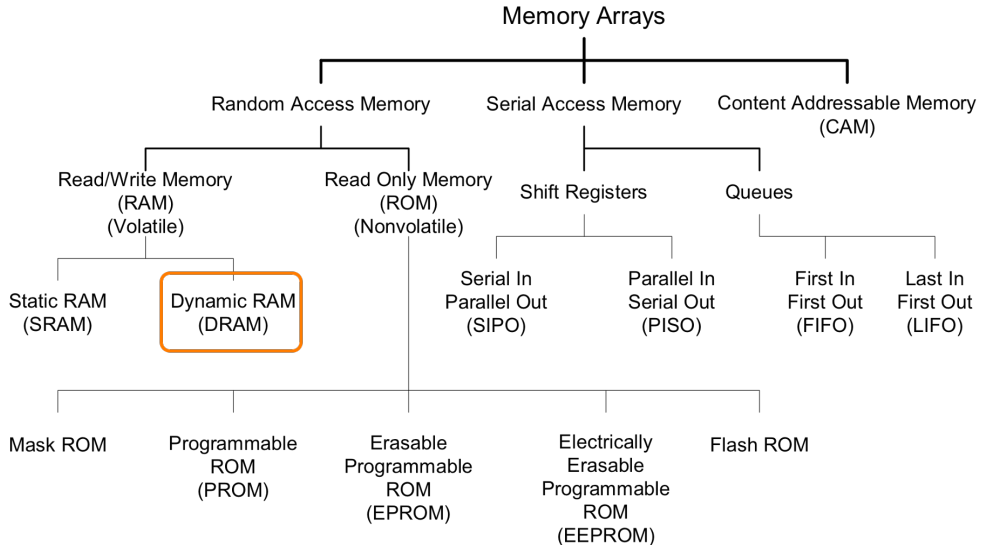



DRAM






- Basic Principle: Storage of information on [capacitors](#)
- [Charge & discharge](#) of capacitor to change stored value
- Use of transistor as "switch" to:
  - Store charge
  - Charge or discharge




 
Remove the two p-MOS transistors from static RAM cell, to get a four-transistor dynamic RAM cell.





- Data must be refreshed regularly
- Dynamic cells must be designed very carefully
- Data stored as charge on gate capacitors (complementary nodes)



  
- No constraints on device ratios
- Reads are non-destructive
- Value stored at node X when writing a "1" =  $V_{DD} - V_T$



  


[1970: Intel 1003]

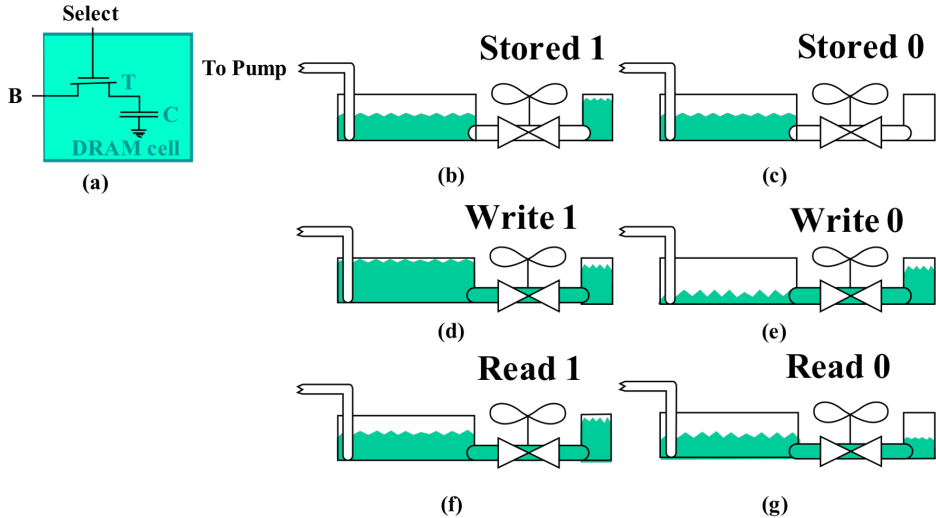- $576 \lambda$  3T DRAM v.s.  $1092 \lambda$  6T SRAM
- Further simplified





- Need sense amp helping reading

 

- Read
  - Pre-charge large tank to  $V_{DD2}$
  - If  $T_s = 0$ , for large tank:  $V_{DD2} - V_1$
  - If  $T_s = 1$ , for large tank:  $V_{DD2} + V_1$
  - $V_1$  is very insignificant
  - Need sense amp

  - **Write:**  $C_s$  is charged or discharged by asserting WL and BL
- **Read:** Charge redistribution takes place between bit line and storage capacitance
- Voltage swing is small; typically around 250 mV



Trench-capacitor cell [Mano87]



- **Question:**  $V_{DD}=4V$ ,  $C_S=100\text{pF}$ ,  $C_{BL}=1000\text{pF}$ . What's the voltage swing value?
- **Note:**  $\Delta V = \frac{V_{DD}}{2} \cdot \frac{C_S}{C_S+C_{BL}}$





- **Static (SRAM)**

- Data stored as long as supply is applied
- Large (6 transistors/cell)
- Fast
- Compatible with current CMOS manufacturing

- **Dynamic (DRAM)**


- Periodic refresh required
- Small (1-3 transistors/cell)
- Slower
- Require additional process for trench capacitance


 
# Array Architecture




- $2^n$  words of  $2^m$  bits each
- Good regularity - easy to design



# SRAM Memory Structure




- Latch based memory

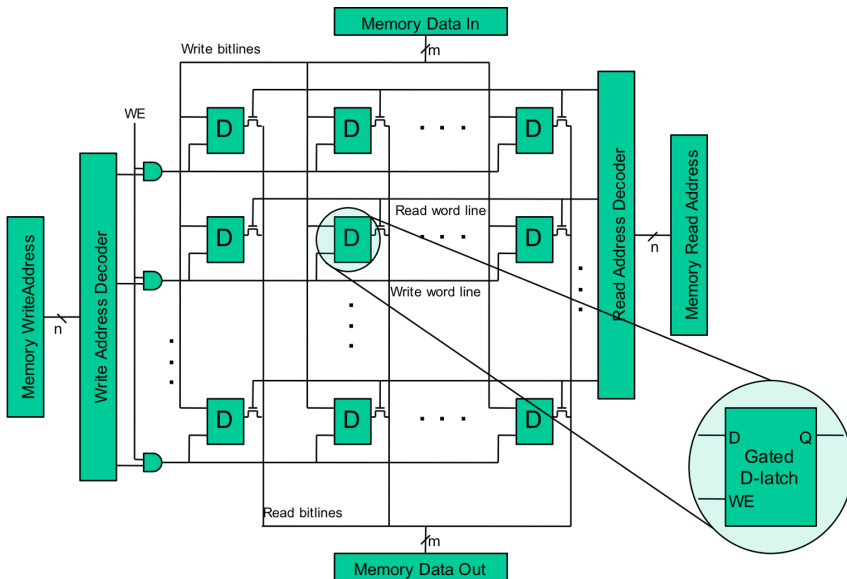




 - $2^n$  words of  $2^m$  bits each
- How to design if  $n \gg m$ ?
- Fold by  $2^k$  into fewer rows of more columns






 
- $n:2^n$  decoder consists of  $2^n$   $n$ -input AND gates
  - One needed for each row of memory
  - Build **AND** with **NAND** or **NOR** gates



## Static CMOS

 


## Using **NOR** gates

 




 - **Question:** AND gates => NAND gate structure





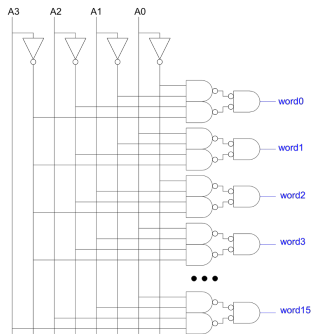
- For  $n > 4$ , NAND gates become slow
  - Break large gates into multiple smaller gates







 - Many of these gates are redundant
  - Factor out common gates
  - => Predecoder
  - Saves area
  - Same path effort




- **Question:** How many NANDs can be saved?


 
# Appendix




- Decoders must be pitch-matched to SRAM cell
  - Requires very skinny gates






 - Some circuitry is required for each column
  - Bitline conditioning
  - Column multiplexing
  - Sense amplifiers (DRAM)






- Precharge bitlines high before reads

 


 - Equalize bitlines to minimize voltage difference when using sense amplifiers





 
- Sense amplifiers also amplify noise
  - Coupling noise is severe in modern processes
  - Try to couple equally onto bit and bit\_b
  - Done by twisting bitlines




# \*SRAM Column Example



read

 

write

 




- Recall that array may be folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
  - Must select 16 output bits from the 128 columns
  - Requires 16 8:1 column multiplexers





# \*Ex: 2-way Muxed SRAM

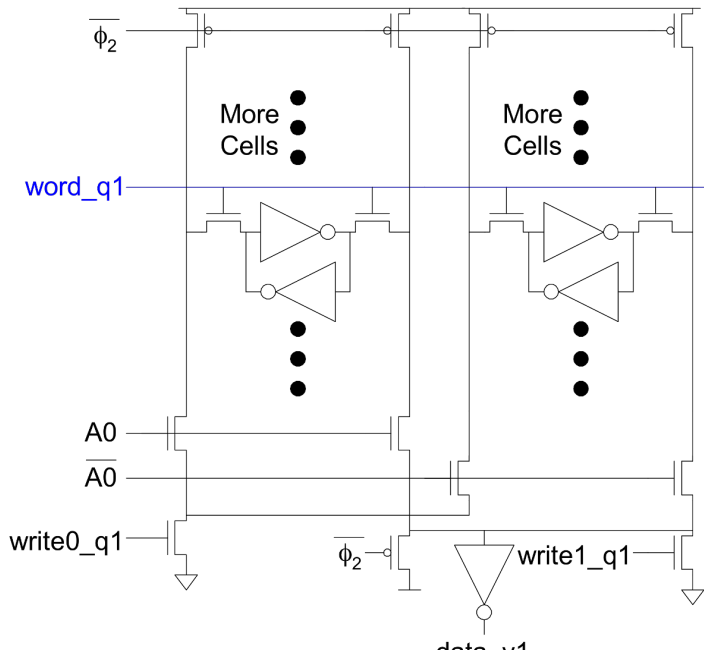




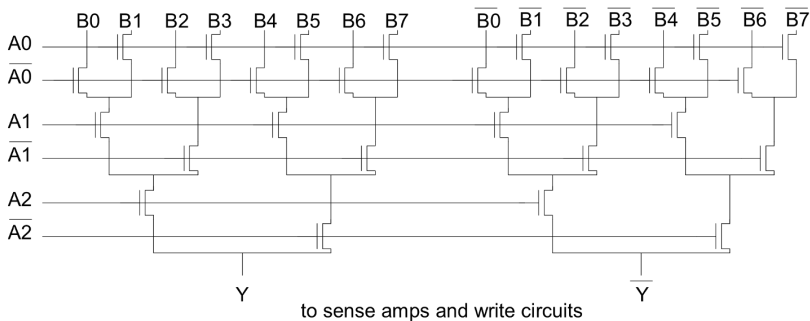- Column mux can use pass transistors
  - Use nMOS only, precharge outputs
- One design is to use k series transistors for  $2^k:1$  mux
  - No external decoder logic needed



 

# Sense Amp Operation for 1T DRAM

 

- 1T DRAM read is destructive
- Read and refresh for 1T DRAM




- Bitlines have many cells attached
  - Ex: 32-kbit SRAM has 256 rows x 128 cols
  - 256 cells on each bitline
- $t_{pd} \propto (C/I)\Delta V$ 
  - Ex: Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
  - Discharged slowly through small transistors (small I)
- Sense amplifiers are triggered on small voltage swing (reduce  $\Delta V$ )


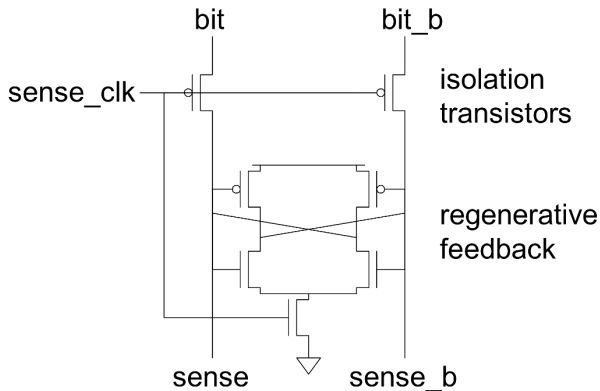
## \*Clocked Sense Amp



- Clocked sense amp saves power
- Requires sense\_clk after enough bitline swing
- Isolation transistors cut off large bitline capacitance





**Thank You :-)**