
CENG 3420

Lecture 02: Digital Logic Review

Bei Yu


byu@cse.cuhk.edu.hk




香港中文大學

The Chinese University of Hong Kong

Review: Major Components of a Computer

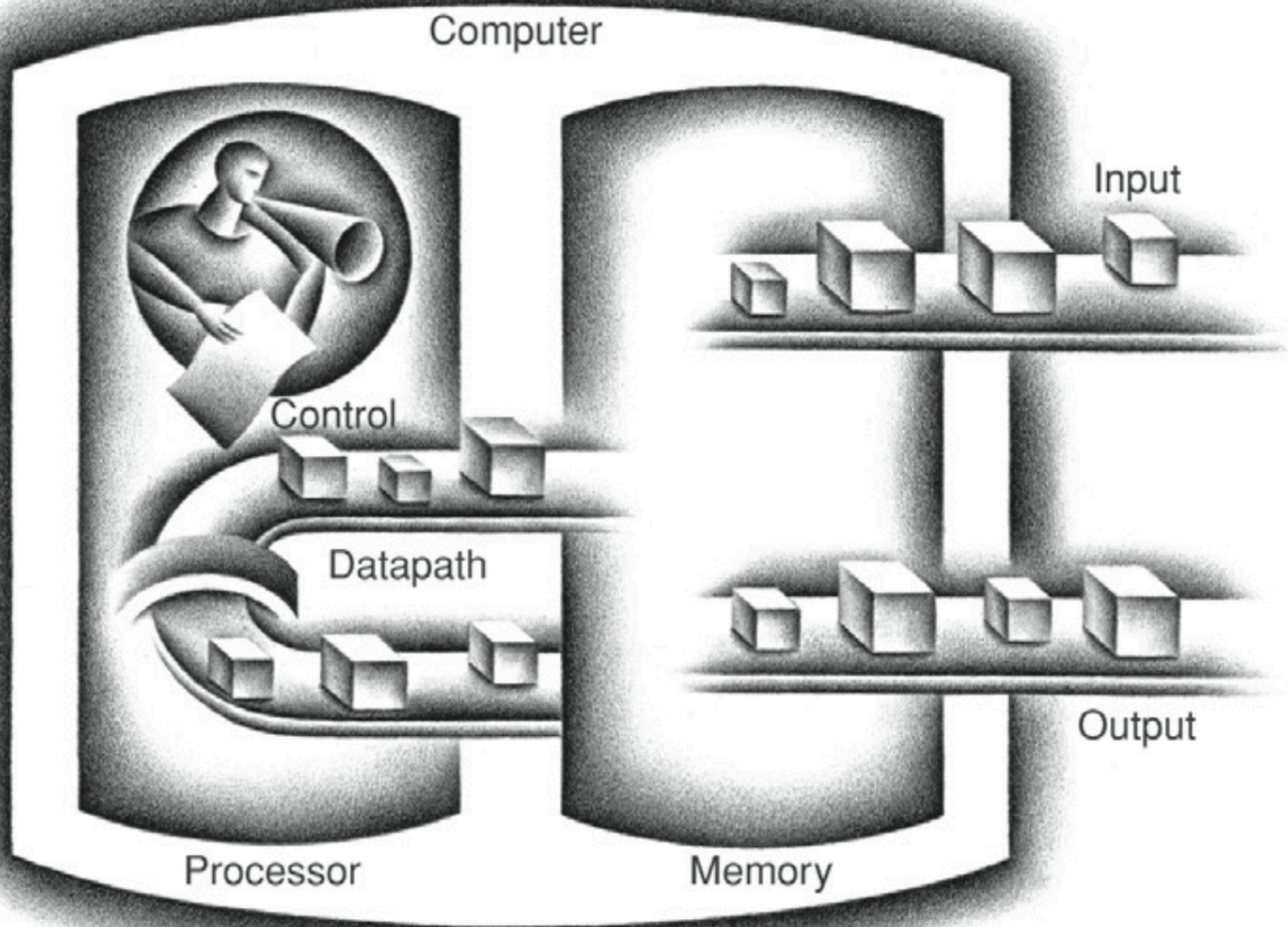

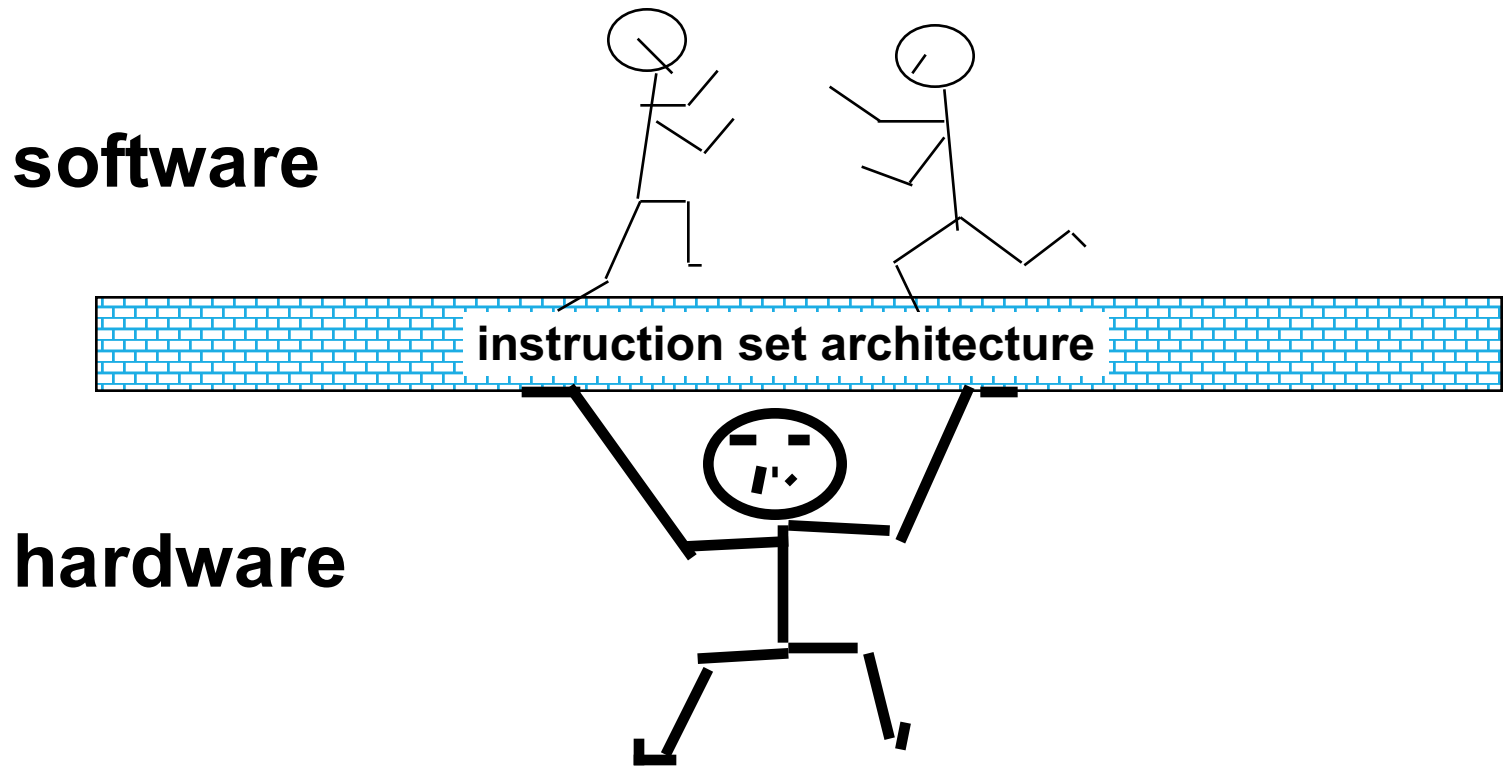Review: The Instruction Set Architecture (ISA)




The interface description separating the software and hardware

Analog vs. Digital


Analog Signal

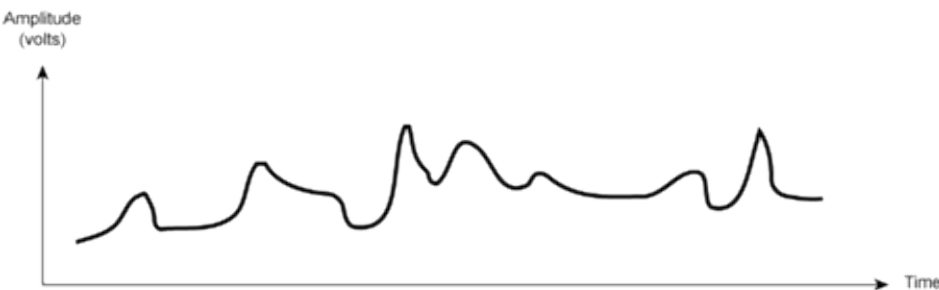- Vary in a smooth way over time
- Analog data are continuous valued
 - Example: audio, video



Digital Signal

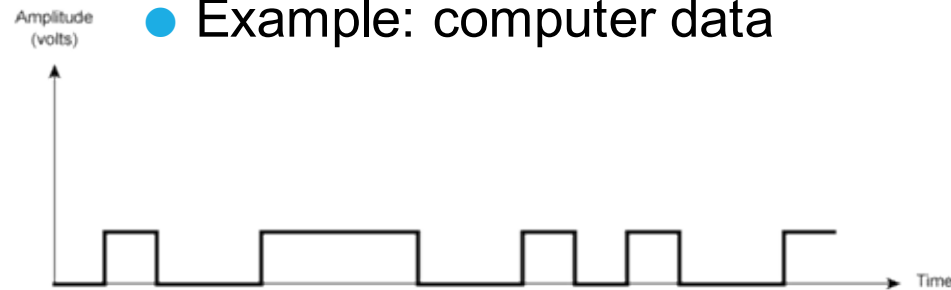- Maintains a constant level then changes to another constant level (generally operate in one of the two states)
- Digital data are discrete valued
 - Example: computer data



Number Systems

- ❑ An ordered set of symbols, called digits, with relations defined for addition, subtraction, multiplication, and division
- ❑ **Radix** or **base** of the number system is the total number of digits allowed in the number system
- ❑ Commonly used numeral systems

System Name	Decimal	Binary	Octal	Hexadecimal
Radix	10	2	8	16
First seventeen positive integers	0	0	0	0
	1	1	1	1
	2	10	2	2
	3	11	3	3
	4	100	4	4
	5	101	5	5
	6	110	6	6
	7	111	7	7
	8	1000	10	8
	9	1001	11	9
	10	1010	12	A
	11	1011	13	B
	12	1100	14	C
	13	1101	15	D
	14	1110	16	E
	15	1111	17	F
16	10000	20	10	

-
- In the 2009 film Avatar, Na'vi race employs an **octal** numeral system.



Conversion from Decimal Integer


- ❑ Step 1: Divide the decimal number by the radix (number base)
- ❑ Step 2: Save the remainder (first remainder is the least significant digit)
- ❑ Repeat steps 1 and 2 until the quotient is zero
- ❑ Result is in reverse order of remainders

EX: L02-1

- ❑ EX1: Convert 36_8 to binary value
- ❑ EX2: Convert 36_{10} to binary value

Unsigned Binary Representation

Hex	Binary	Decimal
0x00000000	0...0000	0
0x00000001	0...0001	1
0x00000002	0...0010	2
0x00000003	0...0011	3
0x00000004	0...0100	4
0x00000005	0...0101	5
0x00000006	0...0110	6
0x00000007	0...0111	7
0x00000008	0...1000	8
0x00000009	0...1001	9
	...	
0xFFFFFFFFC	1...1100	$2^{32} - 4$
0xFFFFFFFDD	1...1101	$2^{32} - 3$
0xFFFFFFFDE	1...1110	$2^{32} - 2$
0xFFFFFFFFF	1...1111	$2^{32} - 1$

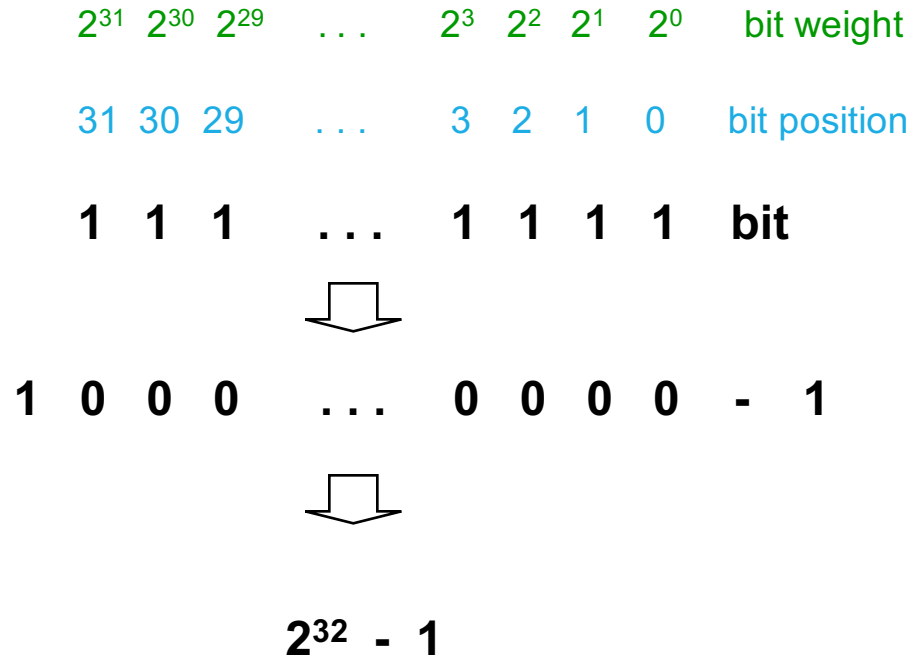

Signed Binary Representation

	2'sc binary	decimal
$-2^3 =$	1000	-8
$-(2^3 - 1) =$	1001	-7
	1010	-6
	1011	-5
	1100	-4
	1101	-3
	1110	-2
	1111	-1
	0000	0
	0001	1
	0010	2
	0011	3
	0100	4
	0101	5
	0110	6
	0111	7

complement all the bits

0101

1011

and add a 1

and add a 1

0110

1010

complement all the bits

$2^3 - 1 =$

EX: L02-2

- For an n -bit signed binary numeral system, what's the largest positive number and the smallest negative number?


Digital Circuits

- Digital circuits generally contain two parts:
 - Combinational logic
 - Sequential logic
- **Combinational** circuits consist of logic gates with inputs and outputs
 - The outputs at any instance of time depend only on the combination of the input values based on logic operations such as AND, OR etc.
- **Sequential** circuits, in addition to inputs and outputs also have storage elements, therefore the output depends on both the current inputs as well as the stored values


Digital Signal Representation

- ❑ Active HIGH
 - High voltage means On


- ❑ Active LOW
 - Low voltage means On

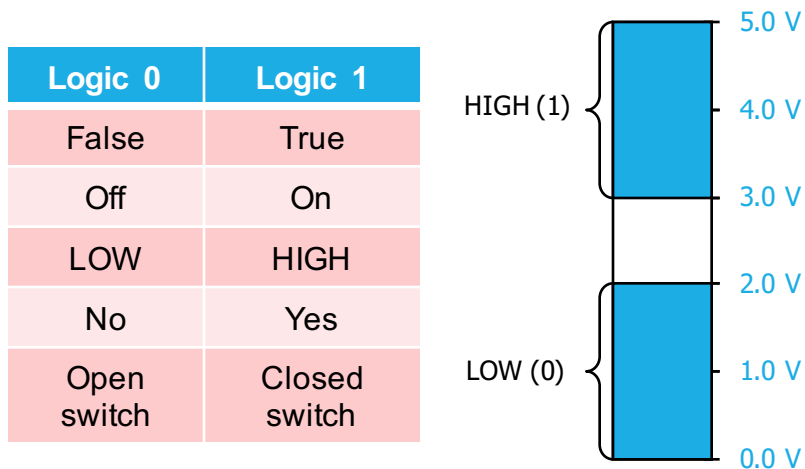


Logic Gates

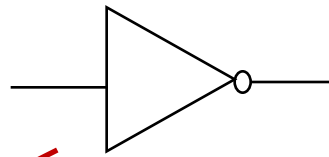


NOT (Invertor)

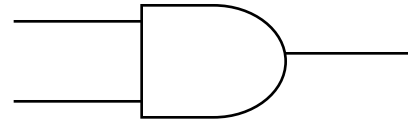



AND

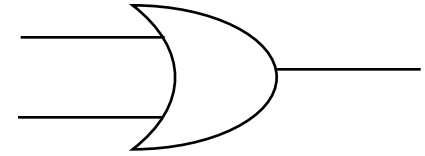


OR

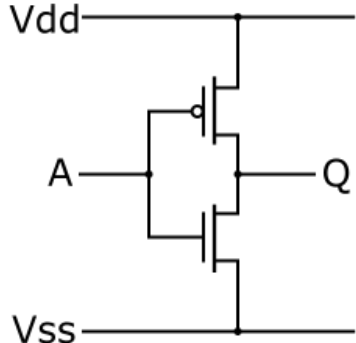


Invertor schematic view

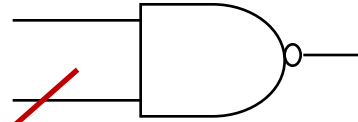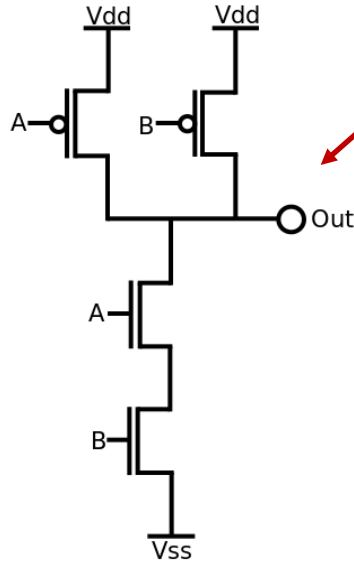


NAND

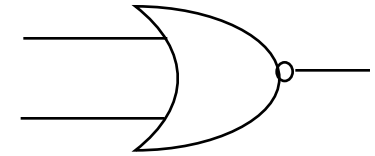

NOR

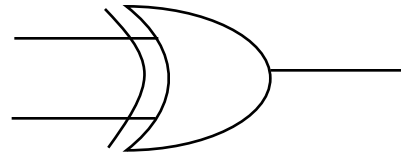

XOR

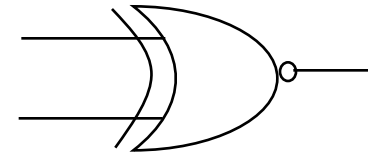

XNOR


❑ What is the schematic view of an AND gate?

EX: L02-3

- Please draw NOR gate schematic view

Truth Table

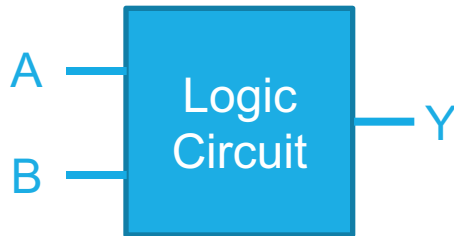- A means for describing how a logic circuit's output depends on the logic levels present at the circuit's inputs
- The number of input combinations will equal 2^N for an N-input truth table




Inputs		Output
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

EX: L02-4

Determine the true table of a three-input AND gate


Combinational Circuits

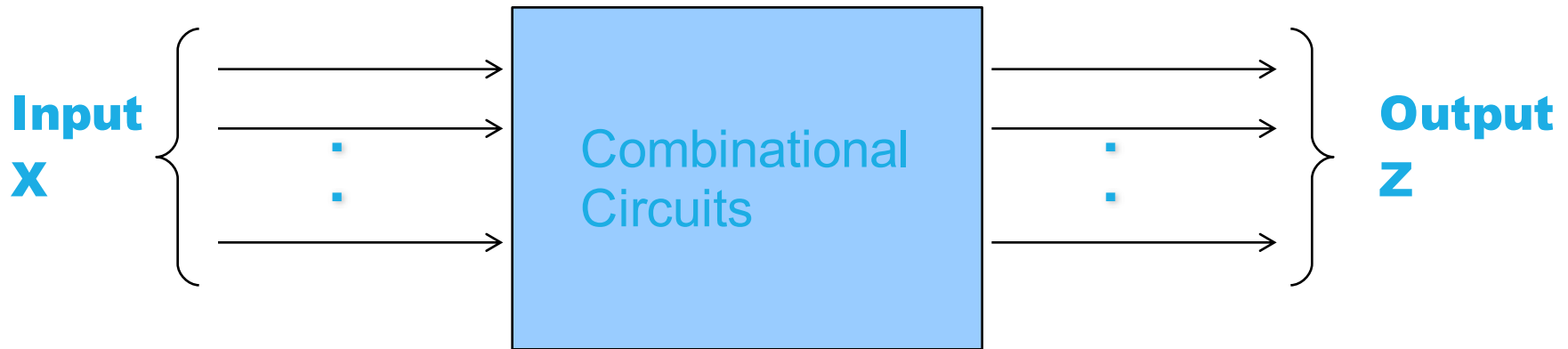

$$Z = F(X)$$

In combinational circuits, the output at any time is a direct function of the applied external inputs

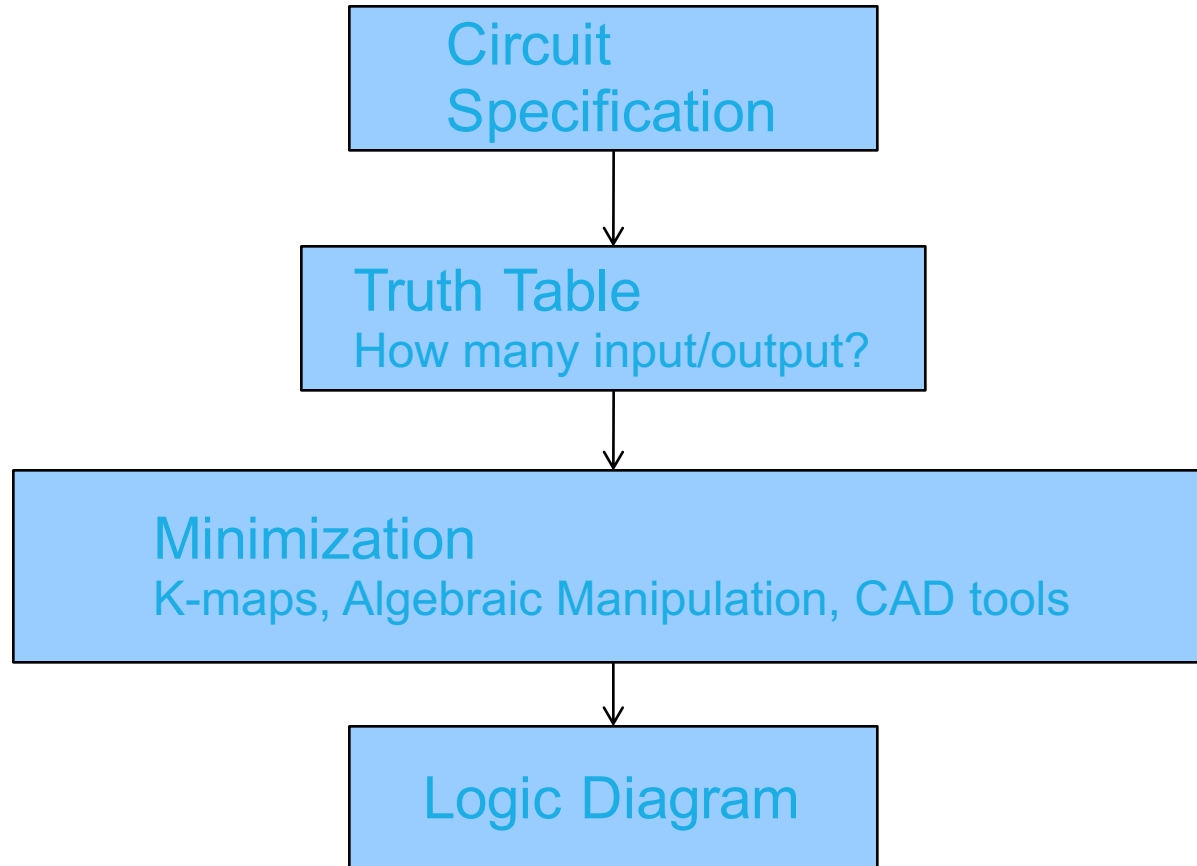Design Procedure of Combinational Circuits




EX: L02-5

- Implement $AB+CD$ using NAND gates only

Propagation Delay

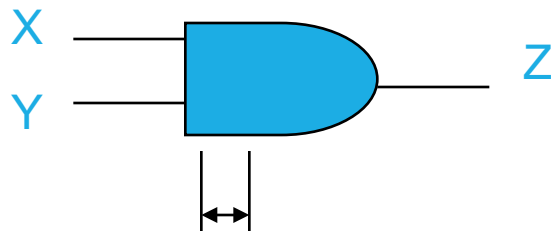
- ❑ The delay when the signal arrives at the input of a circuit, and when the output of the circuit changes, is called the propagation delay
- ❑ A circuit is considered to be fast, if its propagation delay is small (ideally as close to 0 as possible)




Delay between input (X, Y) and change in output Z

Timing Diagram

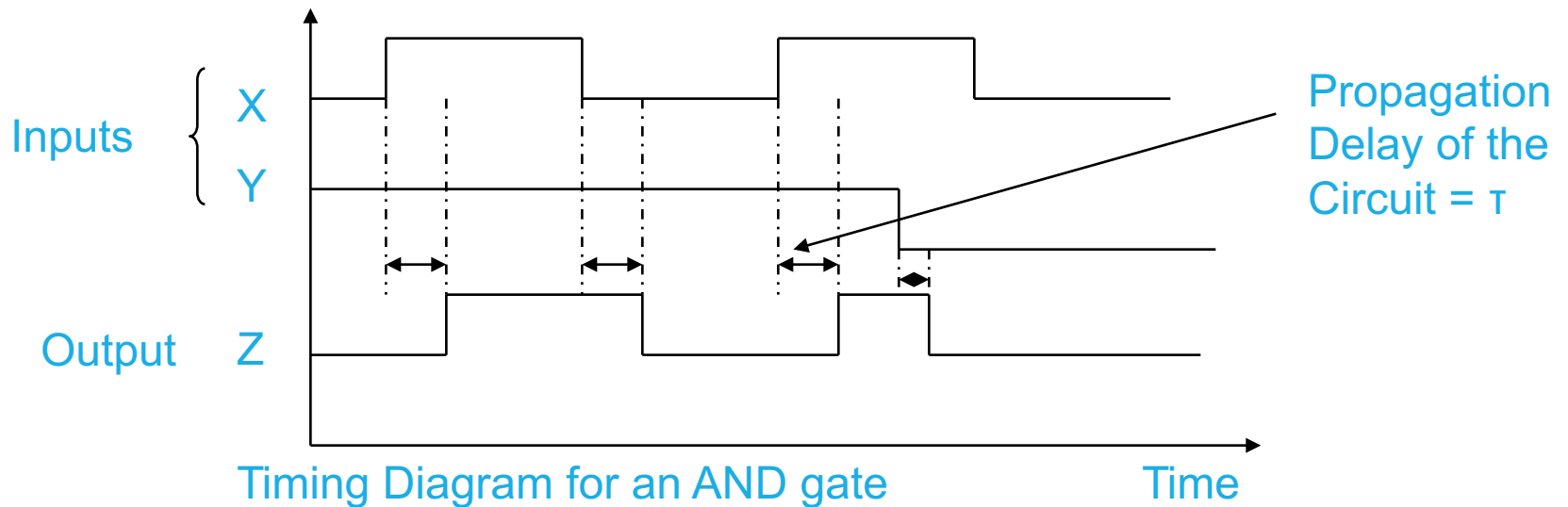- ❑ The inputs to a circuit can be changed over time.
- ❑ The timing diagram shows the values of the input signals to a circuit with the passage of time, in the form of a waveform
- ❑ It also shows a waveform for the output



Power Consumption

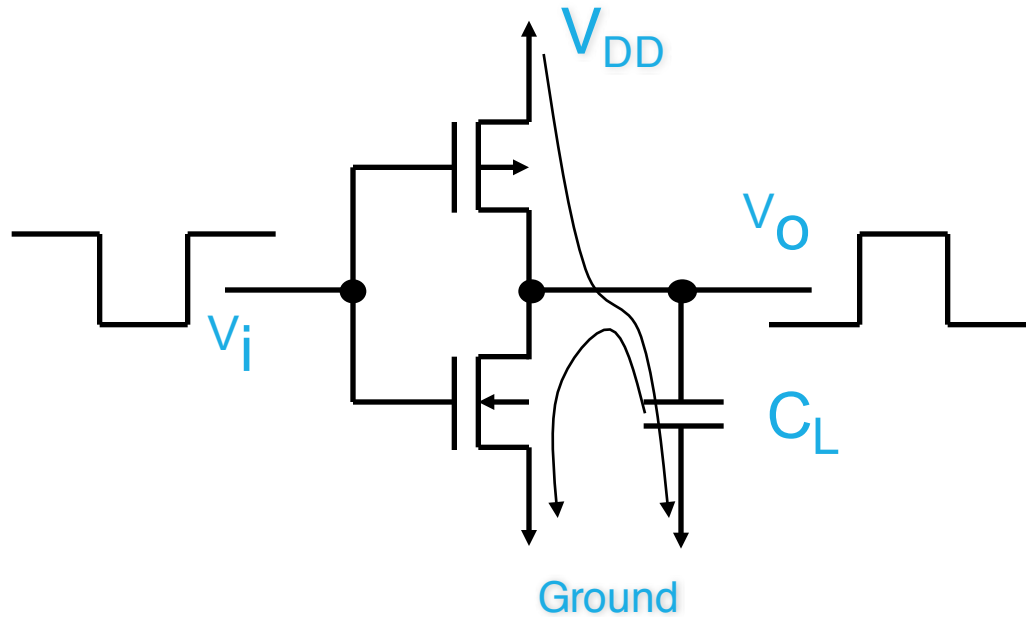

Dynamic Power


$$\approx C_L V_{DD}^2 / 2$$

Fanin

- ❑ Fanin of a gate is the number of inputs to the gate
- ❑ For a 3-input OR gate, the fanin = 3
- ❑ There is a limitation on the fanin for any gate
- ❑ In CMOS IC technology, higher fanin implies **slower** gates (higher propagation delays)


Fanout

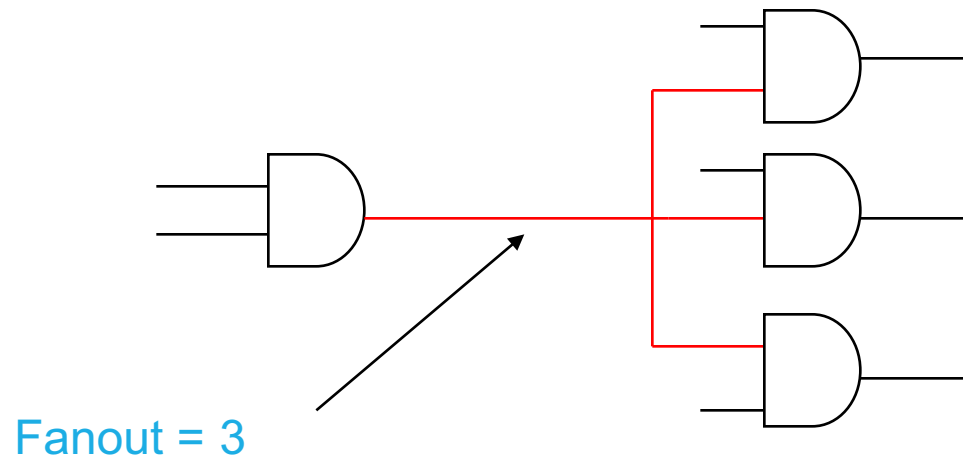- ❑ Fanout is the number of gates that can be driven by a driver gate
- ❑ The driven gate is called the load gate
- ❑ There is a limit to the number of load gates that can be driven by a driver gate




Buffers

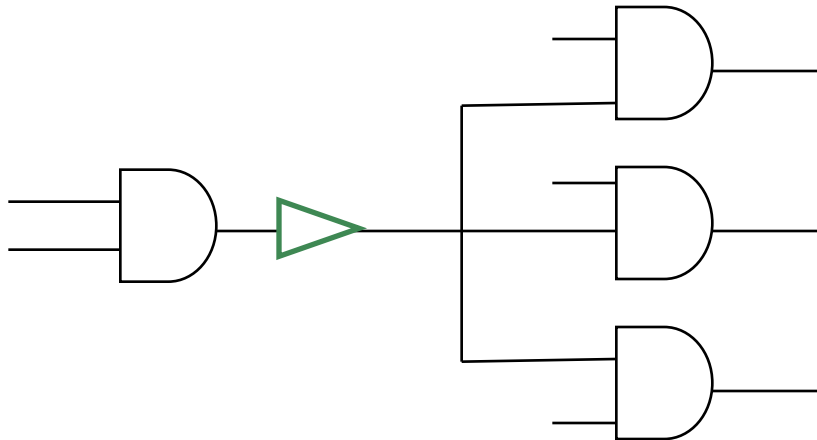- ❑ Buffers have a single input and a single output, where output = input
- ❑ Buffers help increase the driving capability of a circuit by increasing the fanout
- ❑ **Drive strength**: how much load a gate can drive
- ❑ Greater drive strength, fanout gates (dis)charged quickly




How to increase drive strength?

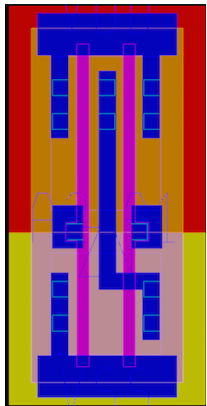
- Reduce resistance -> Increase output current
 - Increase transistor size with gate
 - Parallel a number of transistors




NAND

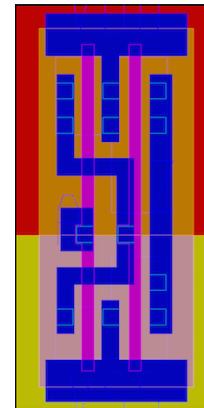

BUF_X1

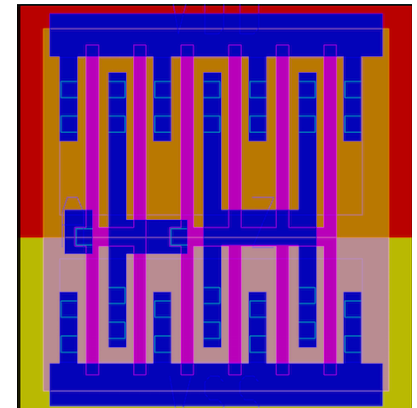


BUF_X4

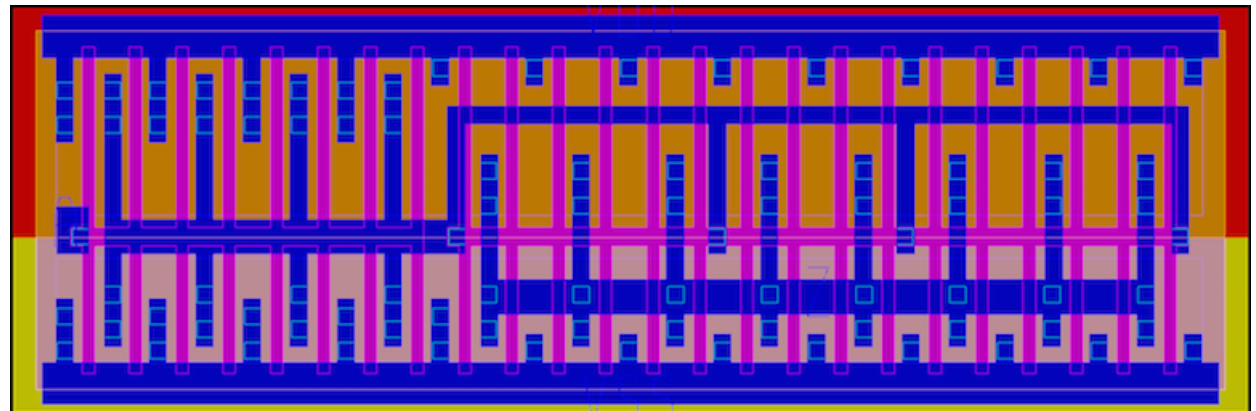

BUF_X16


Decoder

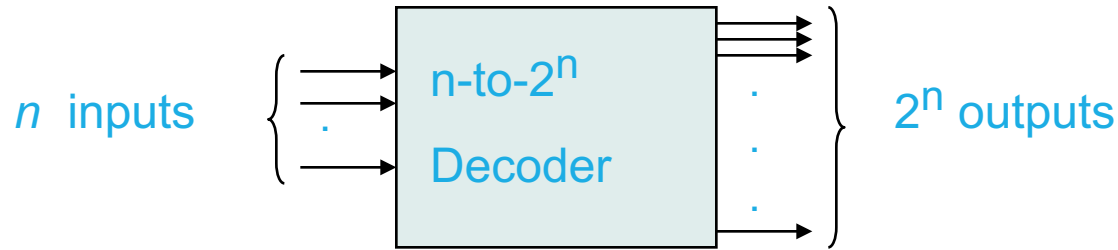

- ❑ Information is represented by binary codes
- ❑ Decoding - the conversion of an n -bit input code to an m -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- ❑ Circuits that perform decoding are called decoders
- ❑ A decoder is a **minterm generator**


Decoder (Use Cases)

□ Decode a 3-bit op-codes:

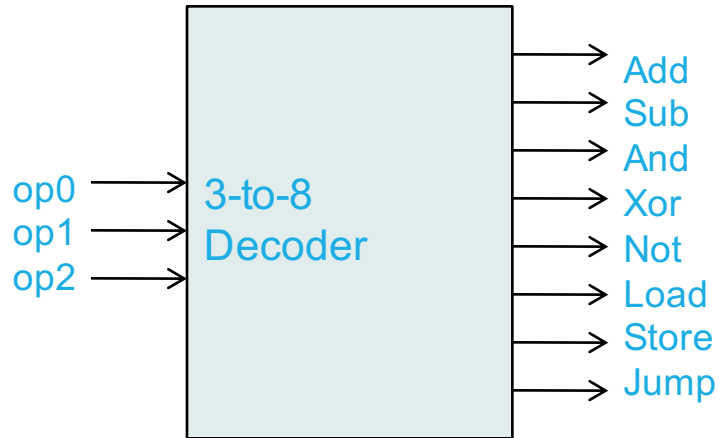

Load a
Add b
Store c
:
:

□ Home automation:

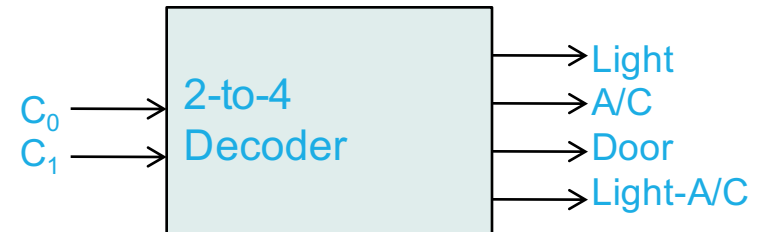

Decoder-Based Circuits


X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \sum (1,2,4,7)$$

$$C = \sum (3,5,6,7)$$


3 inputs and 8 possible minterms

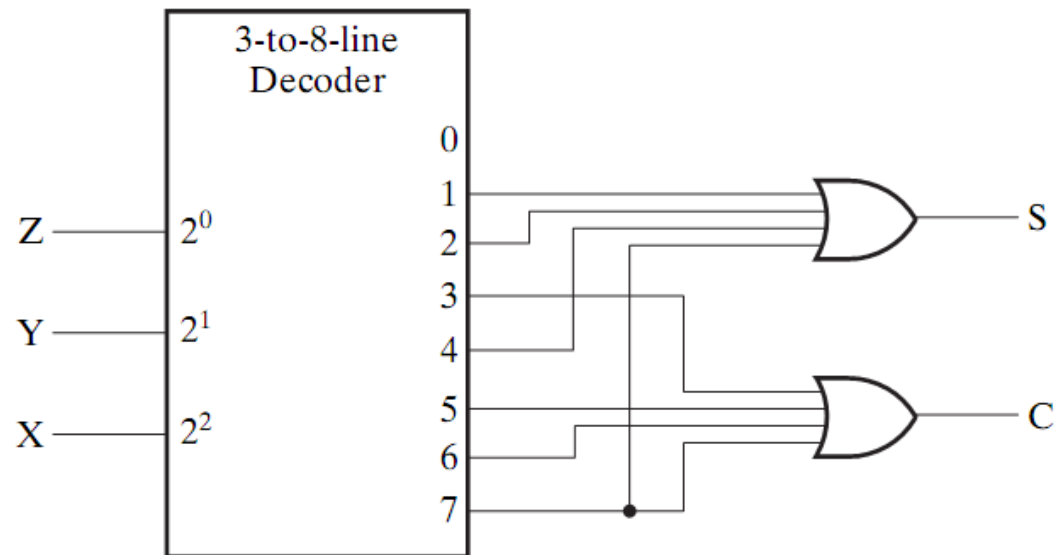3-to-8 decoder can be used for implementing this circuit



Src: Mano's book


Encoder

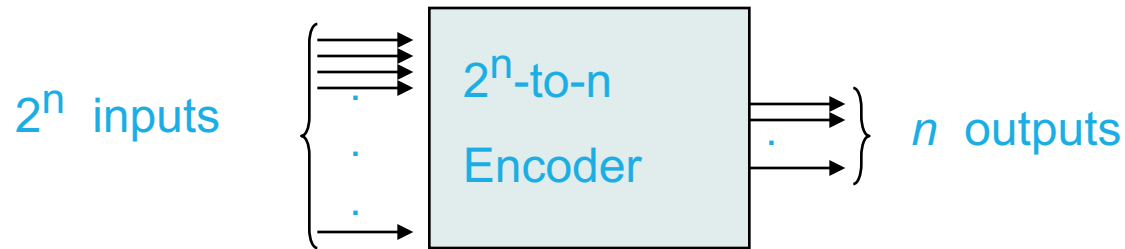

- ❑ Encoding - the opposite of decoding - the conversion of an m -bit input code to a n -bit output code such that each valid code word produces a unique output code
- ❑ Circuits that perform encoding are called encoders
- ❑ An encoder has 2^n (or fewer) input lines and n output lines which generate the binary code corresponding to the input values
- ❑ Typically, an encoder converts a code containing exactly one bit that is 1 to a binary code corresponding to the position in which the 1 appears.

Multiplexers

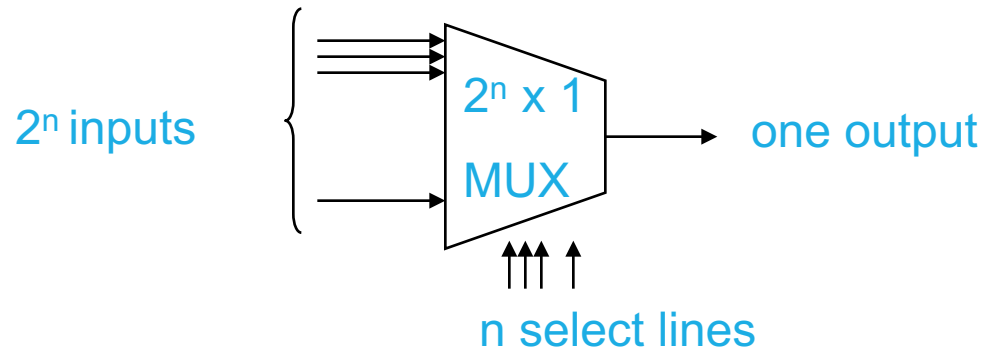- ❑ Directs one of 2^n input to the output
- ❑ Input to output direction is done based on a set of n select bits



MUX-based Design (n-1 Select lines)

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


$$F = C$$

$$F = C'$$


$$F = 0$$

$$F = 1$$

$$F(A,B,C) = \sum(1,2,6,7)$$

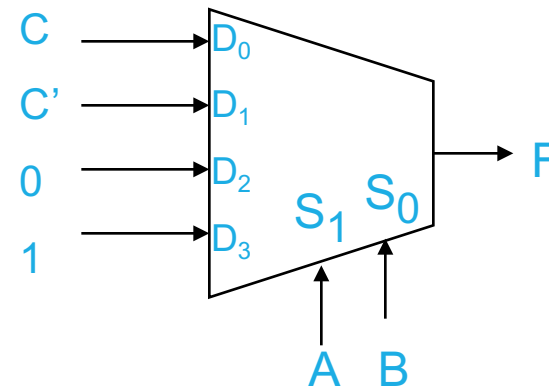


Combinational vs Sequential

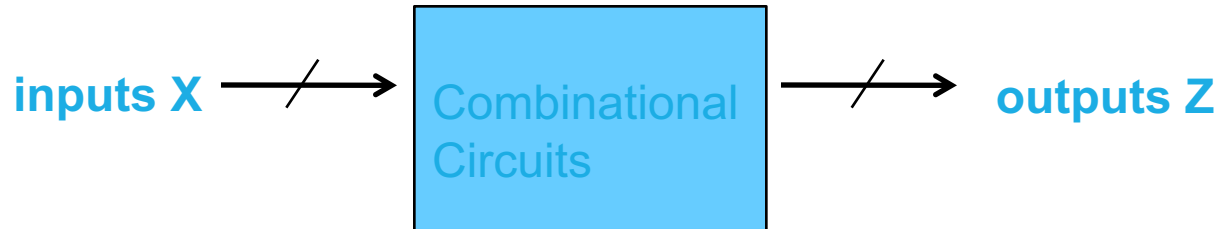


- ❑ A combinational circuit:
- ❑ At any time, outputs depends only on inputs
 - Changing inputs changes outputs
- ❑ History is ignored !

Combinational vs Sequential

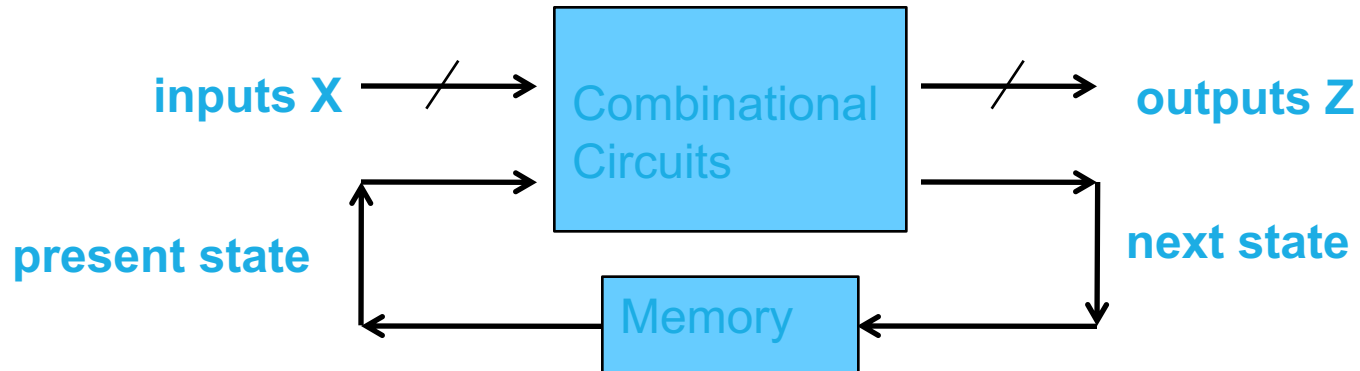

- ❑ A sequential circuit:
- ❑ outputs depends on inputs and previous inputs
 - Previous inputs are stored as binary information into memory
 - The stored information at any time defines a state
- ❑ next state depends on inputs and present state

Examples of sequential systems

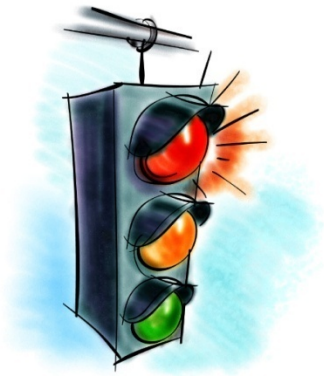

Traffic light



ATM




Vending machine

Types of Sequential Circuits


- Two types of sequential circuits:
 - Synchronous: The behavior of the circuit depends on the input signal values at discrete intervals of time (also called clocked)
 - Asynchronous: The behavior of the circuit depends on the order of change of the input signals at any instance of time (continuous)

Design A Latch

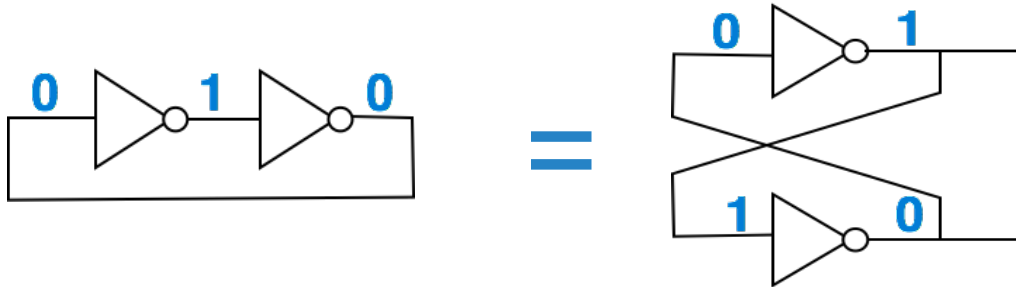- Store one bit of information: cross-coupled invertor



- How to change the value stored?

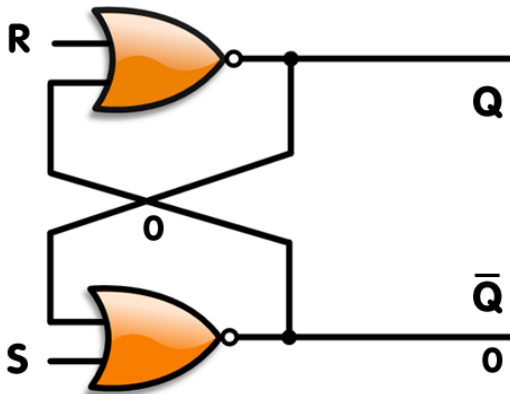


R: reset signal
S: set signal

SR-Latch

EX: L02-6

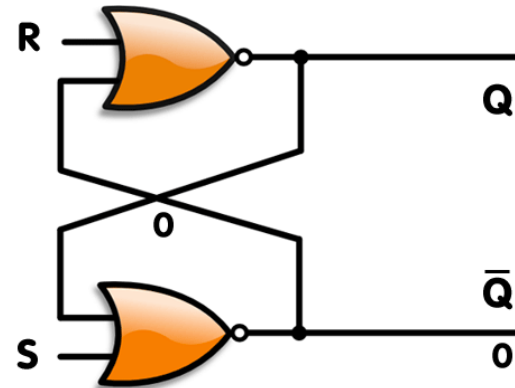
- What's the Q value based on different R, S inputs?



- $S=R=1$:
- $S=0, R=1$:
- $S=1, R=0$:
- $S=R=0$:

Latch and Flip-Flop






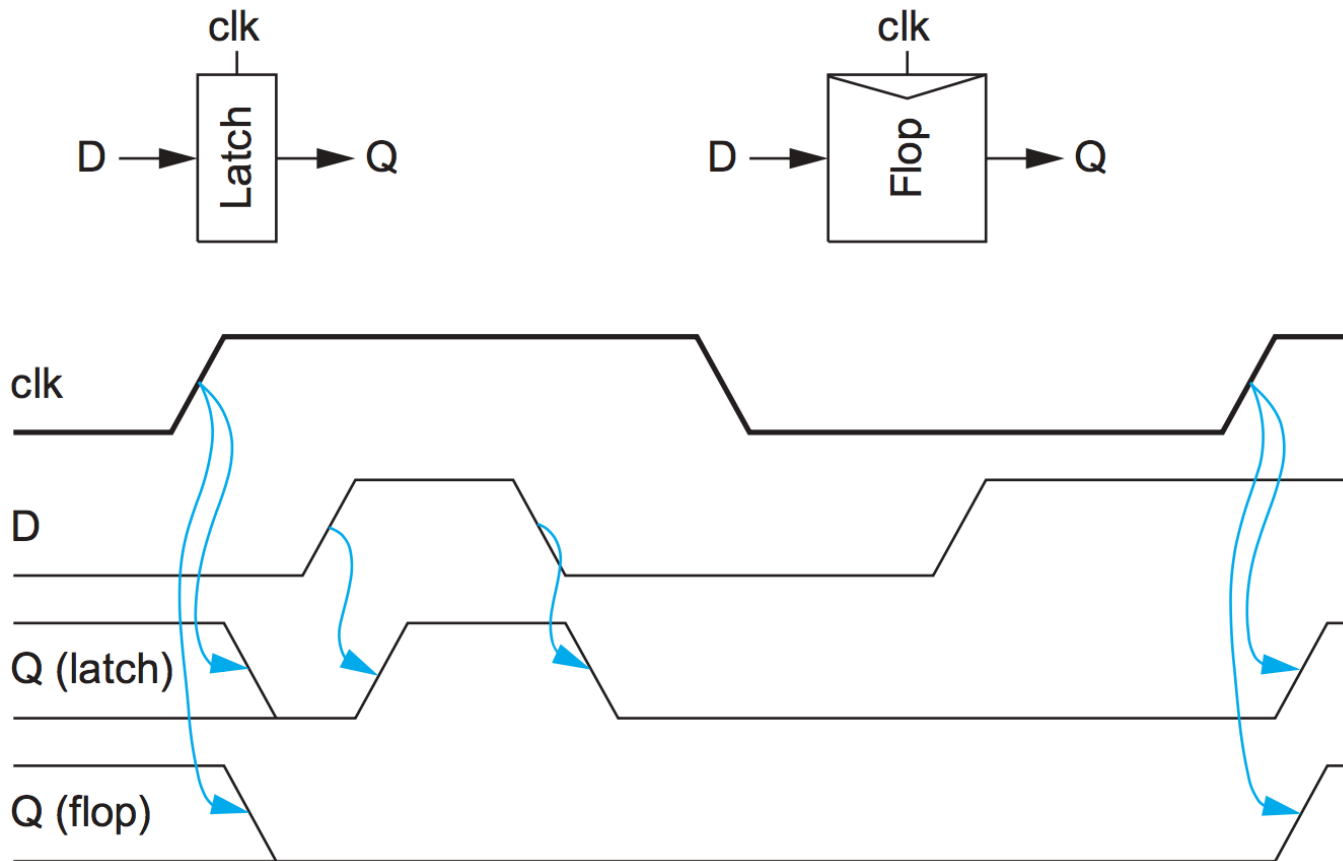
- ❑ Latch is level-sensitive
- ❑ Flip-flop is edge triggered




Timing Diagrams (optional)

Contamination and Propagation Delays

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk-Q Prop Delay
t_{ccq}	Latch/Flop Clk-Q Cont. Delay
t_{pdq}	Latch D-Q Prop Delay
t_{pcq}	Latch D-Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

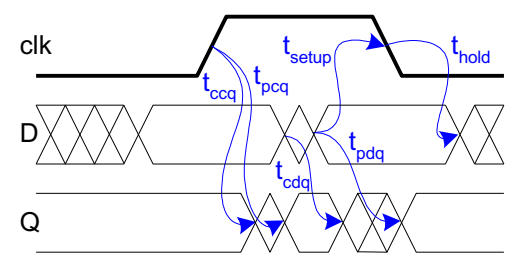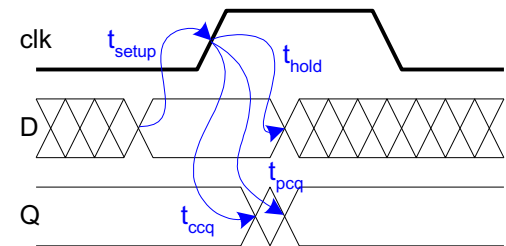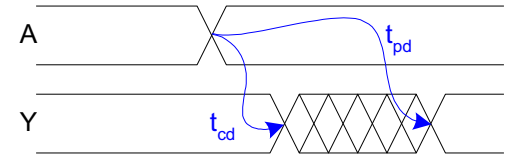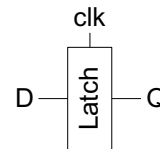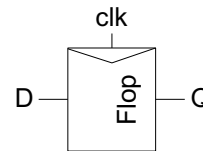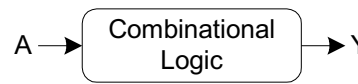


Registers

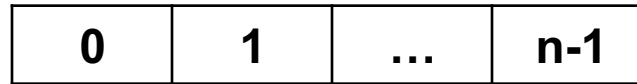

- ❑ A register is a group of flip-flops.
- ❑ An n-bit register is made of n flip-flops and can store n bits
- ❑ A register may have additional combinational gates to perform certain operations


4-Bit Register

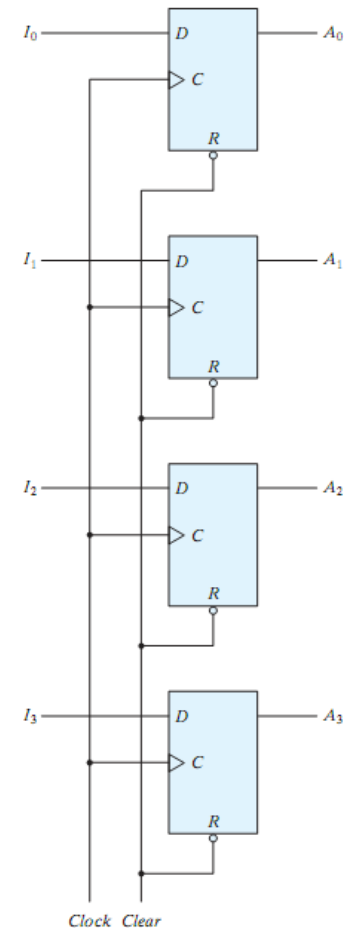- ❑ A simple 4-bit register can be made with 4 D-FF
- ❑ Common Clock
 - At each positive-edge, 4 bits are loaded in parallel
 - Previous data is overwritten
- ❑ Common Clear
 - Asynchronous clear
 - When Clear = 0, all FFs are cleared; i.e. 0 is stored.





4-bit Shift Register

Serial-in and Serial-out (SISO)

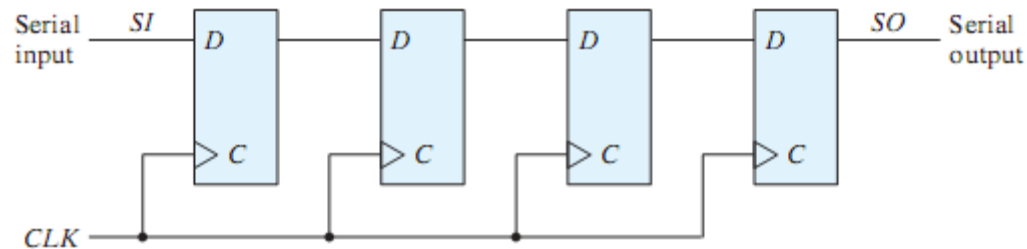

- ❑ A simple 4-bit shift register can be made with 4 D-FF
- ❑ Common Clock
 - At each positive-edge, 1 bit is shifted in
 - Rightmost bit is discarded
- ❑ Which direction this register is shifting?

Universal Shift Register (cont.)

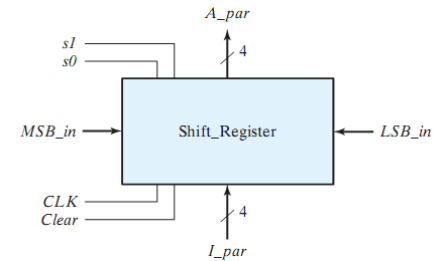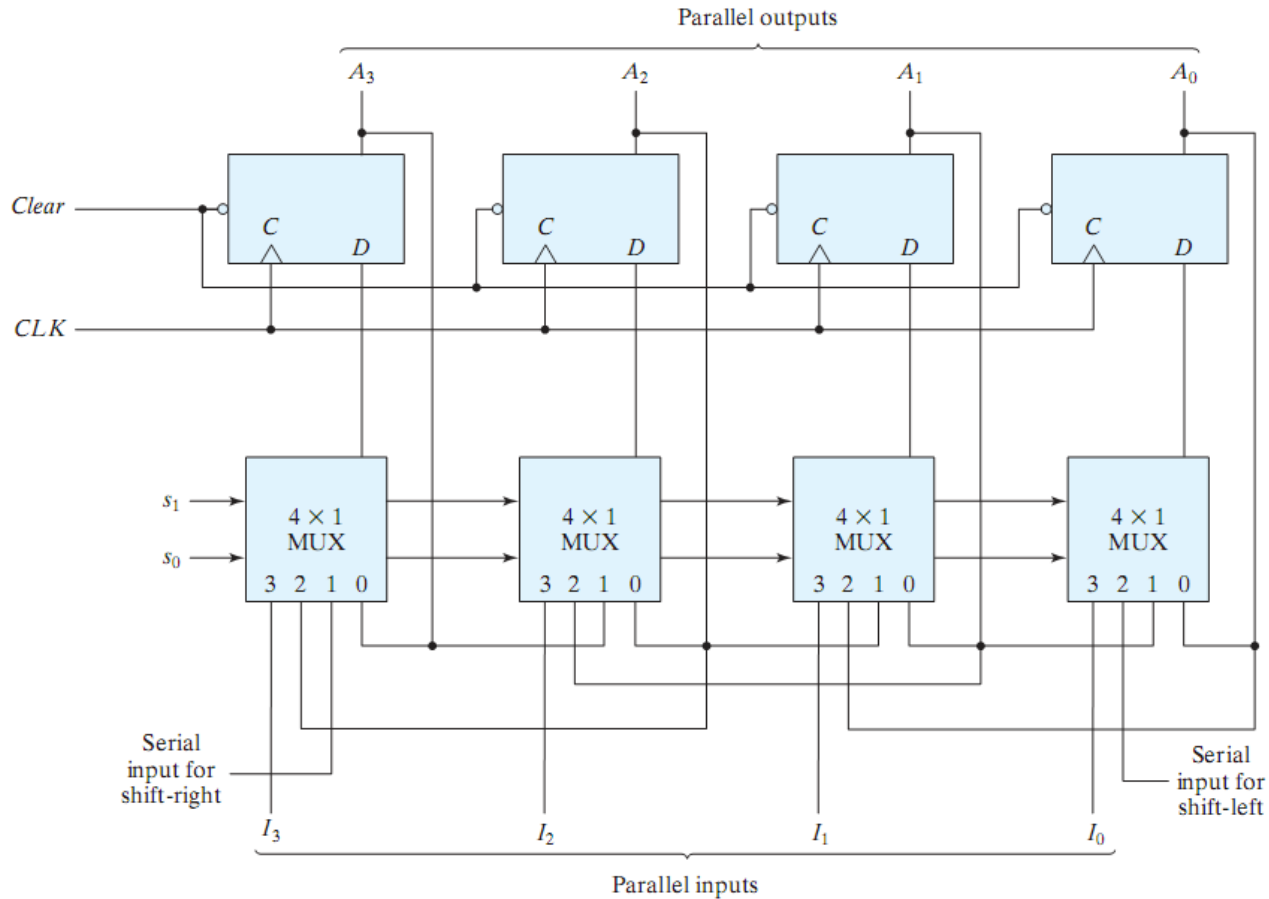

Mode Control

s_1	s_0	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load