

# CENG4480 Homework 1

**Due:** Oct. 21, 2018

- **Small-Signal Gain:** For given amp circuits, small changes of input  $\Delta V_{in}$  will cause output change of  $\Delta V_{out}$ . Small-signal gain is defined by  $\frac{\Delta V_{out}}{\Delta V_{in}}$ .

**Q1** (10%) Given a non-inverting amplifier as shown in Figure 1,  $R_1 = 3R_2$  and  $A_0 = 1000$ , calculate the exact finite gain. Then determine the gain difference if the circuit is expected to have an ideal gain under  $A_0 = \infty$ .

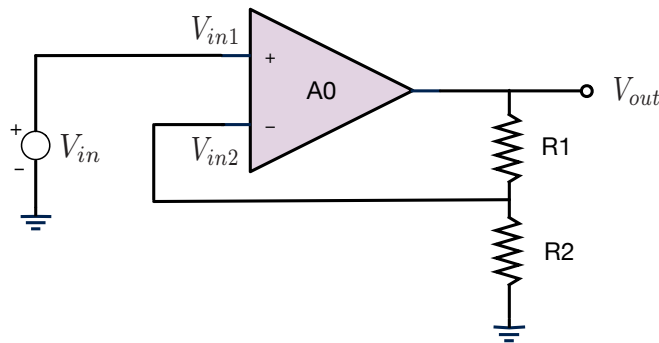


Figure 1: Non-inverting Amplifier.

**Q2** (10%) An op-amp exhibits the following nonlinear characteristic:

$$V_{out} = \alpha \arctan[\beta(V_{in1} - V_{in2})]. \quad (1)$$

Determine the small-signal gain of the op amp in the case  $V_{in1} \approx V_{in2}$ . (Hint: use Taylor expansion of  $\arctan$  and definition of aforementioned small-signal gain.)

**Q3** (10%) In the circuit of Figure 2,  $R_1 = R_2 = R' = R_f = R = 100\text{k}\Omega$  and  $C = 1\mu\text{F}$ . Assume the op-amps are ideal.

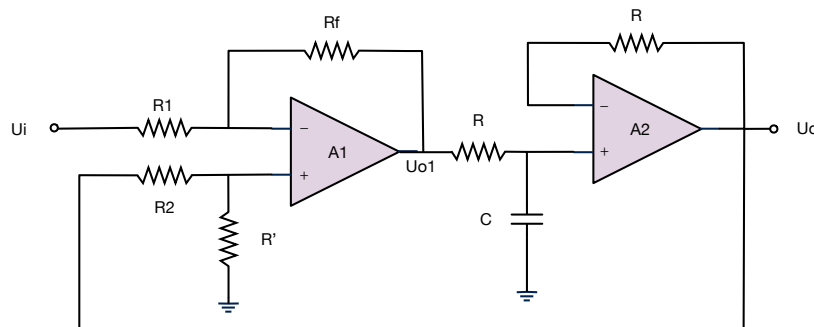


Figure 2: Voltage Follower.

- (6%) The relationship between  $U_i$  and  $U_o$  ( $U_{o1}$  is unknown).
- (4%) Assume that when the time  $t = 0$ ,  $U_o = 0V$  and  $U_i$  jumps from  $0V$  to  $-1V$ . How long will the  $U_o$  take to change from  $0V$  to  $6V$ ?

**Q4** (15%) Determine the output voltage (i.e. the mathematical expression of  $V_{out}(t)$ ) for the integrator circuit of Figure 3a if the input is a square wave of amplitude  $\pm A$  and period  $T$  shown in Figure 3b. Assume  $T = 10ms$ ,  $C_F = 1\mu F$ ,  $R_s = 10k\Omega$  and ideal op-amp. The square wave starts at  $t = 0$  and therefore  $V_{out}(0) = 0$ .

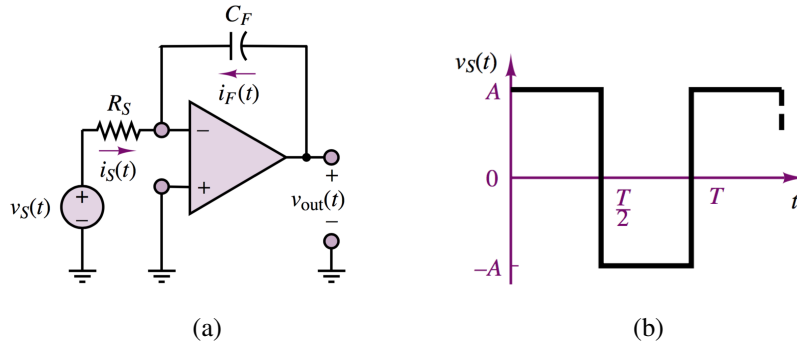


Figure 3: (a) Op-amp integrator; (b) Input of a square wave.

**Q5** (20%) Assume op-amps are ideal. Given  $R_1 = 0.4M\Omega$ ,  $R_2 = R_3 = R_5 = 1M\Omega$ ,  $R_4 = 2.5k\Omega$  and  $C_1 = C_2 = 1\mu F$ , derive the differential equation corresponding to the analog computer simulator of Figure 4, i.e. the mathematical relationship between  $f$  and  $x$ . Note that  $f(t)$  is input signal,  $y$  and  $z$  are outputs of corresponding op-amps.

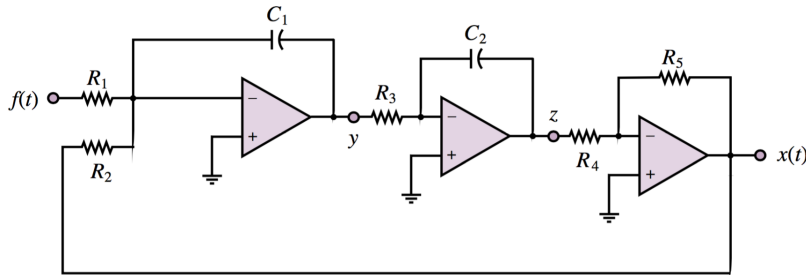


Figure 4: Analog computer simulation of unknown system.

**Q6** (10%) Let us consider the Schmitt Trigger shown in Figure 5

- (5%) Due to the manufacturing defects, a parasitic resistor  $R_3$  occurs between the output node and ground, calculate the reference voltages.
- (5%) If the parasitic device is a capacitor  $C$ , sketch  $v_{out}$  versus  $v_{in}$ . Label the key coordinates on the curve.

**Q7** (10%) Compute and sketch the output voltage of the op-amp in Fig. 6. Given  $R_S = 1k\Omega$ ,  $R_F = 10k\Omega$ ,  $R_L = 1k\Omega$ ,  $V_S^+ = 15V$ ,  $V_S^- = -15V$ ,  $v_s(t) = 2\sin(1000t)$ . Repeat the problem if  $V_S^+ = 20V$  and  $V_S^- = -20V$ . Assume the op-amp is supply voltage-limited.

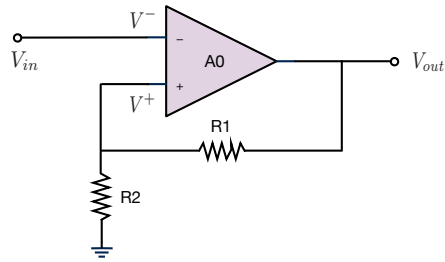


Figure 5: Schmitt Trigger.

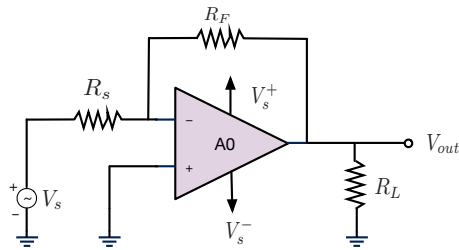


Figure 6: Inverting Amplifier.

**Q8** (15%) Determine the closed-loop voltage gain as a function of frequency (i.e.  $A(j\omega) = \frac{V_{out}(j\omega)}{V_s(j\omega)}$ ) for the op-amp circuit of Fig. 7. Assume the op-amp is ideal. Given only  $R_1$ ,  $R_2$  and  $\omega_0$ ,  $R_2C = \frac{L}{R_1} = \omega_0$ . (Hint: the impedance of a inductor  $L$  equals to  $j\omega L$ .)

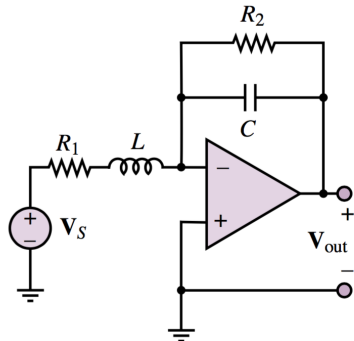


Figure 7: A second-order low-pass filter.