

# CENG4480 Homework 2

**Due:** Nov. 13, 2018

**Q1** The circuit shown in Figure 1 represents a simple 4-bit digital-to-analog converter. Each switch is controlled by the corresponding bit of the digital number if the bit is 1 the switch is up; if the bit is 0 the switch is down. Let the digital number be represented by  $b_3b_2b_1b_0$ . Please answer the following two questions:

- (1) Determine an expression relating  $v_o$  to the binary input bits.
- (2) Use this converter, design another 4-bit digital-to-analog converter whose output is given by

$$v_o = -\frac{1}{10}(8b_3 + 4b_2 + 2b_1 + b_0)V. \quad (1)$$

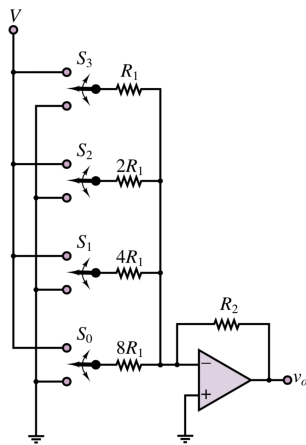


Figure 1: 4-bit DAC.

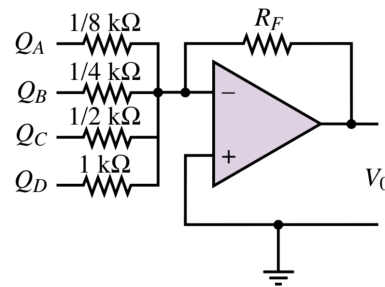


Figure 2: RF DAC.

**Q2** For the DAC circuit shown in Figure 2 (using an ideal op-amp), what value of  $R_F$  will give an output range of  $-10 \leq V_0 \leq 0V$ ? Assume that logic 0 = 0V and logic 1 = 5V.

**Q3** A simple Infra-Red Sensor system to detect passing human is presented as in Figure 3. A and B are IR Sensors which will generate different output voltages for different infra-red intensity, and higher voltage level corresponds to high light intensity.

- (1) Explain how this system works for counting passing pedestrians.
- (2) To increase counting accuracy, usually B is covered with materials that can reflect infra-red light. Explain why.



Figure 3: IR-System.

**Q4** Exemplify the working principles of sensors that measure: (1) Flow; (2) Temperature; (3) Pressure; (4) Motion; (5) Liquid Level.

**Q5** Briefly describe how PID affects motor control.

**Q6** Given a linear system

$$\begin{cases} \mathbf{x}_t = \mathbf{A}_{t-1}\mathbf{x}_{t-1} + \boldsymbol{\omega}_{t-1}, \\ \mathbf{z}_t = \mathbf{B}_t\mathbf{x}_t + \mathbf{v}_t, \\ \mathbf{v}_t = \mathbf{C}_{t-1}\mathbf{v}_{t-1} + \mathbf{n}_{t-1}, \end{cases} \quad (2)$$

where  $\boldsymbol{\omega}_t$  and  $\mathbf{n}_t$  are independent and obey Gaussian distribution zero-mean and covariance  $\mathbf{Q}_t$  and  $\mathbf{R}_t$ , respectively. Please give the estimate equation and measurement equation of the system.

**Q7** Given two Gaussian distributions  $N(x_0; \mu_0, \sigma_0)$  and  $N(x_1; \mu_1, \sigma_1)$ , try to give the expectation and variance of a new distribution which is the product of these two Gaussian distributions.

**Q8** For the 4-bit R-2R DAC, calculate  $V_0$  in terms of  $V_{b,0} - V_{b,4}$  if  $V_{ref}$  is grounded (Figure 4).

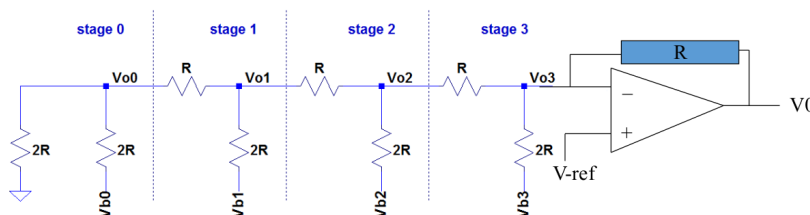


Figure 4: R-2R DAC.

**Q9** (Discrete-time random walk) Suppose that we wish to estimate the position of a particle that is undergoing a random walk in one dimension (i.e., along a line). We model the position of the particle as

$$x[k + 1] = x[k] + u[k],$$

where  $x$  is the position of the particle and  $u$  is a white noise processes with  $E\{u[i]\} = 0$  and  $E\{u[i]u[j]\} = R_u\theta(i - j)$ . We assume that we can measure  $x$  subject to additive, zero-mean, Gaussian white noise with covariance 1.

Construct a Kalman filter to estimate the position of the particle given the noisy measurements of its position. Compute the steady-state expected value and covariance of the error of your estimate.