



香港中文大學

The Chinese University of Hong Kong

CENG3430 Rapid Prototyping of Digital Systems

Lecture 04:


Finite State Machine

Ming-Chang YANG

mcyang@cse.cuhk.edu.hk

Recall: Comb. vs. Seq. Circuits (Lec03)

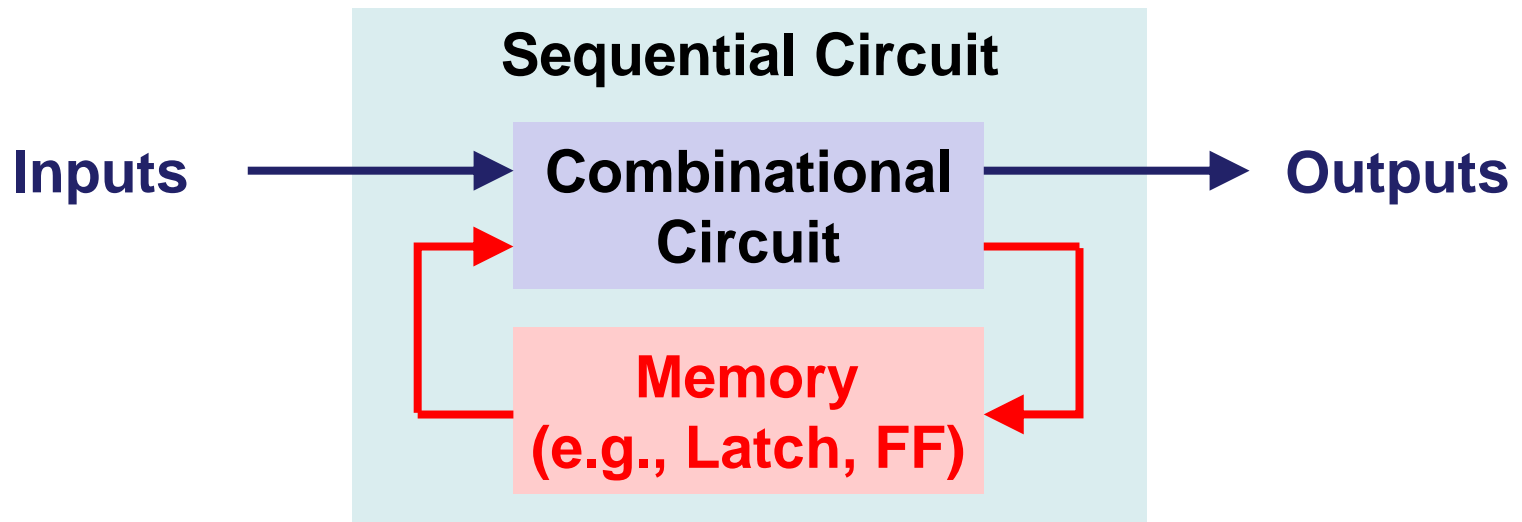- **Combinational Circuit: no memory**
 - Outputs depend on the *present* inputs only.
 - **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
 - Outputs depend on *present* inputs and *previous* outputs.
 - **Rule: MUST** use sequential statements (i.e., `process`).



Recall: SIPO Shift Register (Lab03)



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity SIPO_ASYNC is
  port(D, CLK, RST : IN STD_LOGIC;
       Q : OUT STD_LOGIC_VECTOR(3 downto 0) );
end SIPO_ASYNC;
```

```
architecture SIPO_ASYNC_ARCH of SIPO_ASYNC is
```

```
  component DFF_ASYNC is
    port(D, clk, reset : in STD_LOGIC;
         Q : out STD_LOGIC );
  end component;
```

```
  signal dout : STD_LOGIC_VECTOR(3 downto 0);
begin
```

```
  DFF0: DFF_ASYNC port map
    (D, CLK, RST, dout(0));
```


```
  DFF1: DFF_ASYNC port map
    (dout(0), CLK, RST, dout(1));
```

```
  DFF2: DFF_ASYNC port map
    (dout(1), CLK, RST, dout(2));
```

```
  DFF3: DFF_ASYNC port map
    (dout(2), CLK, RST, dout(3));
```

```
  Q <= dout;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity DFF_ASYNC is
  port(D, CLK, RESET: in std_logic;
       Q: out std_logic);
end DFF_ASYNC;
architecture DFF_ASYNC_ARCH of DFF_ASYNC is
begin
  process(CLK, RESET) -- sensitivity list
  begin
    if (RESET = '1') then
      Q <= '0'; -- Reset Q anytime
    elsif CLK = '1' and CLK'event then
      Q <= D; -- Q follows input D
    end if;
  end process;
end DFF_ASYNC_ARCH;
```

 

Can we model a sequential circuit in a more “abstract” way?





- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- FSM Types
 - Moore Machine
 - Mealy Machine
- FSM Examples
 - Up/Down Counter
 - Pattern Generator
- Rule of Thumb: FSM Coding Tips

Finite State Machine (FSM)



 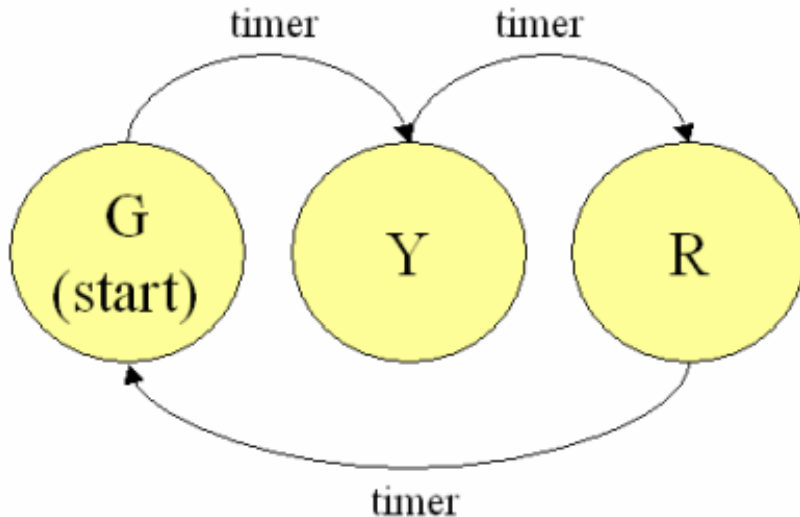- **Finite State Machine (FSM)** is an abstract model of a sequential circuit.
 - It jumps from one state to another within a finite pool.
 - Real-life example: Traffic light



- Two crucial factors of FSM:

① **time controlling** and ② **state maintenance**


① Time Controlling



- Both “**wait until**” and “**if**” statements can be used to detect the clock edge (e.g., **CLK**):


- “**wait until**” statement:

 - **wait until** CLK = '1'; -- rising edge
- **wait until** CLK = '0'; -- falling edge




- “**if**” statement:

 - **if** CLK'event and CLK = '1' -- rising edge
- **if** CLK'event and CLK = '0' -- falling edge



OR

 - **if**(rising_edge(CLK)) -- rising edge
- **if**(falling_edge(CLK)) -- falling edge



When to use “wait until” or “if”? (1/2)

- **Synchronous Process:** Computes values only on clock edges (i.e., only sensitive/sync. to clock signal).
 - **Rule:** Use “**wait-until**” or “**if**” for **synchronous** process:

process ← NO sensitivity list implies that there is one clock signal.

begin

wait until **clk**='1' ; ← The first statement must be **wait until**.

...

end process

*Note: IEEE VHDL requires that a process with a wait statement must not have a sensitivity list, and the first statement must be **wait until**.*

process (**clk**) ← The clock signal must be in the sensitivity list.

begin

...

if (**rising_edge** (**clk**)) ← NOT necessary to be the first line.

...

end process

Usage
of
“wait
until”

Usage
of
“if”

When to use “wait until” or “if”? (2/2)

- **Asynchronous Process:** Computes values on clock edges or when asynchronous conditions are TRUE.
 - That is, it must be sensitive to the clock signal (if any), and to all inputs that may affect the asynchronous behavior.
 - **Rule:** Only use “**if**” for **asynchronous** process:

```
process (clk, input_a, input_b, ...) ← It should include the
begin                                  clock signal and all
...                                    inputs that involve.
    if ( rising_edge (clk) ) ← The clock edge detection doesn't
...                                  have to be the first statement of this
end process                          process.
```

Usage
of
“if”


Simply use “if” statement for both sync/async process!

CLK'event VS. rising_edge (CLK) (1/2)

- Both “**wait until**” and “**if**” statements can be used to detect the clock edge (e.g., CLK):


- “**wait until**” statement:
 
```
- wait until CLK = '1'; -- rising edge  
- wait until CLK = '0'; -- falling edge
```




- “**if**” statement:
 
```
- if CLK'event and CLK = '1' -- rising edge  
- if CLK'event and CLK = '0' -- falling edge
```



OR
 
```
- if ( rising_edge (CLK) ) -- rising edge  
- if ( falling_edge (CLK) ) -- falling edge
```



CLK'event VS. rising_edge (CLK) (2/2)

- **rising_edge()** function in std_logic_1164 library


```
FUNCTION rising_edge (SIGNAL s : std_ulogic) RETURN BOOLEAN IS
BEGIN
    RETURN (s'EVENT AND (To_X01(s) = '1') AND
            (To_X01(s'LAST_VALUE) = '0'));
END;
```

- It results **TRUE** when there is an edge transition in the signal s, the present value is '1' and the last value is '0'.
 - If the last value is something like 'z' or 'U', it returns a **FALSE**.
- The statement (**clk'event** and **clk='1'**)
 - It results **TRUE** when there is an edge transition in the clk and the present value is '1'.
 - *It does not see whether the last value is '0' or not.*


Suggested to use rising/falling_edge() with “if”!

② State Maintenance (1/2)

 - **Method 1:** Use “**memory device(s)**” (e.g., FF)



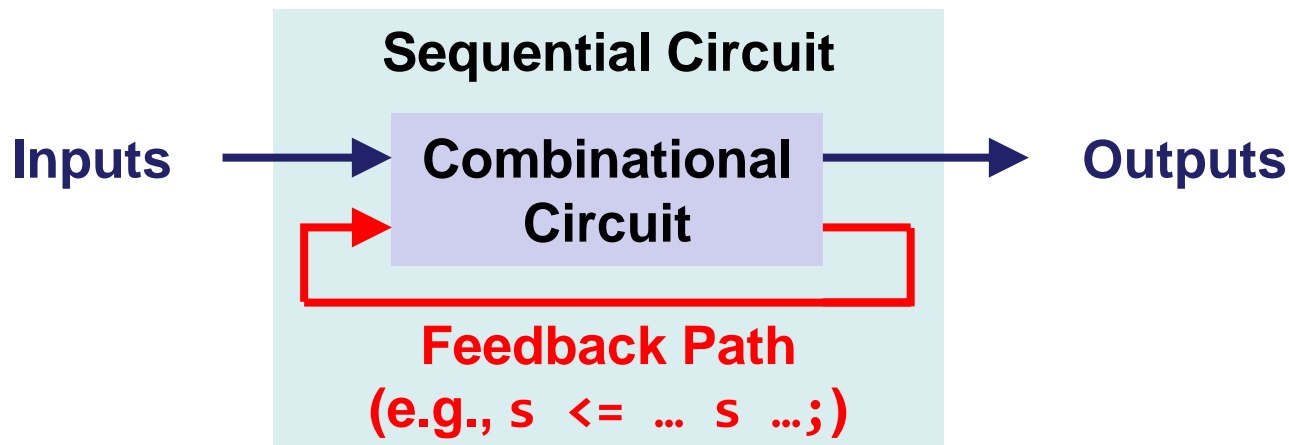
- **Method 2:** Form “**feedback path(s)**” in a clocked process (i.e., sensitive to the clock signal)



**More abstract
& convenient!**

② State Maintenance (2/2)
 
```
entity Method_1 is -- use D-FF
  port(D, CLK, RST : IN STD_LOGIC;
       Q : OUT STD_LOGIC );
end Method_1;
architecture Arch of Method_1 is
  component DFF_ASYNC is
    port(D, clk, reset : in STD_LOGIC;
         Q : out STD_LOGIC );
  end component;
  signal din, dout: STD_LOGIC;
begin
  din <= not ( D and dout );
  DFF_ASYNC port map(din,CLK,RST,dout);
  Q <= dout; -- output
end Arch;
```



```
entity Method_2 is -- form feedback path
  ... -- same as Method_1
end Method_2;
architecture Arch of Method_2 is
  signal s: STD_LOGIC; -- state
begin
  process(CLK, RST) -- clocked process
  begin
    if (RST = '1') then
      s <= '0'; -- async. Reset
    elsif rising_edge(CLK) then
      s <= not ( D and s ); -- feedback
    end if;
  end process;
  Q <= s; -- output
end Arch;
```



Signal **s** (i.e., state) forms a **feedback path** in a clocked process!

- The value of **s** will last for one clock cycle.
 - i.e., $\text{not}(D \text{ and } s)$ will take effect at the next edge.
- **<=** here can be treated as a flip-flop!

Class Exercise 4.1



- Determine the signal **Q**:

  

```
entity Method_2 is -- form feedback path
  port(D, CLK, RST : IN STD_LOGIC;
        Q : OUT STD_LOGIC );
```

```
end Method_2;
```

```
architecture Arch of Method_2 is
```

```
  signal s: STD_LOGIC; -- state
```

```
begin
```

```
  process(CLK, RST) -- clocked process
```

```
  begin
```

```
    if (RST = '1') then
```

```
      s <= '0'; -- async. Reset
```

```
    elsif rising_edge(CLK) then
```

```
      s <= not ( D and s ); -- feedback
```

```
    end if;
```

```
  end process;
```

```
  Q <= s; -- output
```

```
end Arch;
```




- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- **FSM Types**
 - Moore Machine
 - Mealy Machine
- FSM Examples
 - Up/Down Counter
 - Pattern Generator
- Rule of Thumb: FSM Coding Tips

FSM Types





- **Moore Machine:**

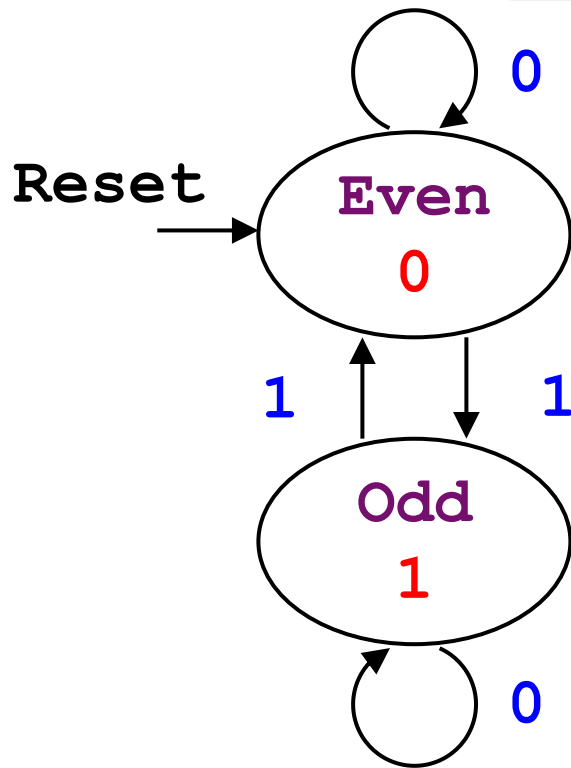- **Outputs** rely on the present **state** only.



- **Mealy Machine:**

 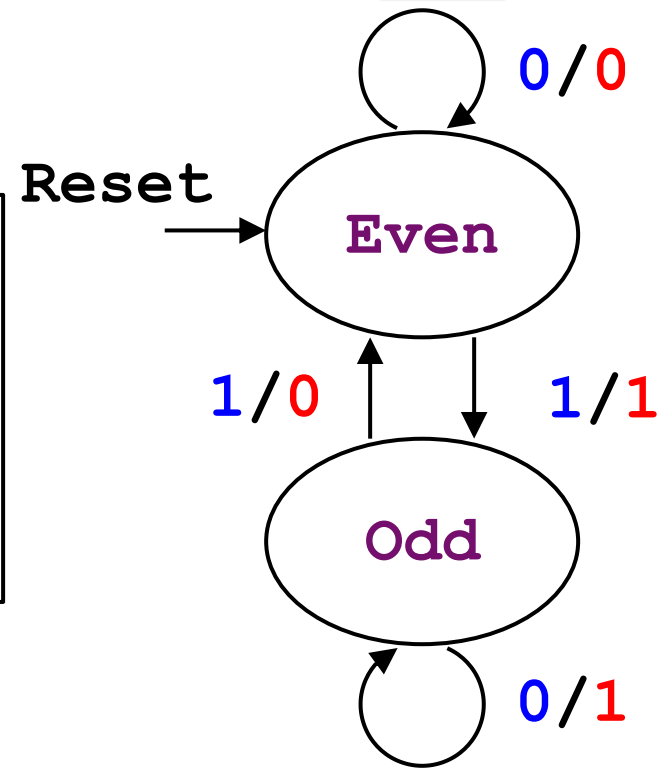- **Outputs** rely on both the present **state** and **inputs**.



Example: An FSM that outputs a '0' (resp. to '1') if an even (resp. to odd) number of 1's have been received.

Moore Machine



- Moore Machine: *Outputs* rely on *present state* only.

architecture moore_arch of fsm is

```
signal s: std_logic := '0'; -- internal state  
begin
```

```
process (s)
```

Combinational Logic

```
begin
```

```
OUTX <= s; -- output
```

```
end process;
```

```
process (CLOCK, RESET)
```

Sequential Logic

```
begin
```

```
if RESET = '1' then s <= '0';
```


```
elsif rising_edge(CLOCK) then
```

```
s <= INX xor s; -- feedback
```

```
end if;
```

```
end process;
```

```
end moore_arch;
```

 

Mealy Machine



- **Mealy Machine:** *Outputs* rely on both *state* and *inputs*.

architecture mealy_arch of fsm is

```
signal s: std_logic := '0'; -- internal state
begin
```

```
process (s, INX) Combinational Logic
begin
```

```
    OUTX <= INX xor s; -- output
```

```
end process;
process (CLOCK, RESET) Sequential Logic
begin
```

```
    if RESET = '1' then s <= '0';
```


```
    elsif rising_edge(CLOCK) then
```

```
        s <= INX xor s; -- feedback
```

```
    end if;
```

```
end process;
```

```
end mealy_arch;
```

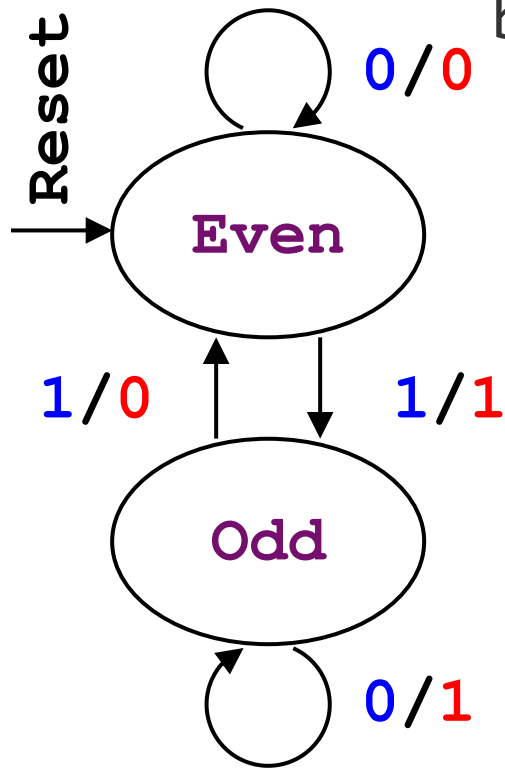



- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- FSM Types
 - Moore Machine
 - Mealy Machine
- **FSM Examples**
 - Up/Down Counter
 - Pattern Generator
- Rule of Thumb: FSM Coding Tips

FSM Example 1) Up/Down Counter (1/3)

- **Up/Down Counter:** Generates a sequence of up/down counting patterns.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.Numeric_Std.ALL;
entity counter is
    port(
        CLK: in std_logic;
        RESET: in std_logic;
        COUNT: out std_logic_vector
            (3 downto 0) );
end counter;
architecture counter_arch of counter
is
    signal s: std_logic_vector(3 downto
0) := "0000"; -- state
```

```
begin
```

```
    process(CLK, RESET)
    begin
        if(RESET = '1') then s <= "0000";
        else
            if( rising_edge(CLK) ) then
                s <= std_logic_vector(
                    unsigned(s)+1); -- feedback
            end if;
        end if;
    end process;
```

Sequential Logic

Combinational Logic

```
COUNT <= s; -- Moore or Mealy?
```


```
end counter_arch;
```

FSM Example 1) Up/Down Counter (2/3)

```
use IEEE.Numeric_Std.ALL;  
signal s: std_logic_vector(3 downto 0) := "0000"; -- state  
s <= std_logic_vector(unsigned(s)+1); -- feedback
```

- A `std_logic_vector` is merely a collection of `std_logic`.
 - The individual positions have no predefined meaning.
- The IEEE NUMERIC_STD package includes **overloading functions** for data types that are more convenient to use.
 - Such as **unsigned/signed** types and **integer** type.
- VHDL is a strongly-typed language.
 - Signals of different types **CANNOT** be assigned to each other without using **type casting/conversion**.

FSM Example 1) Up/Down Counter (3/3)

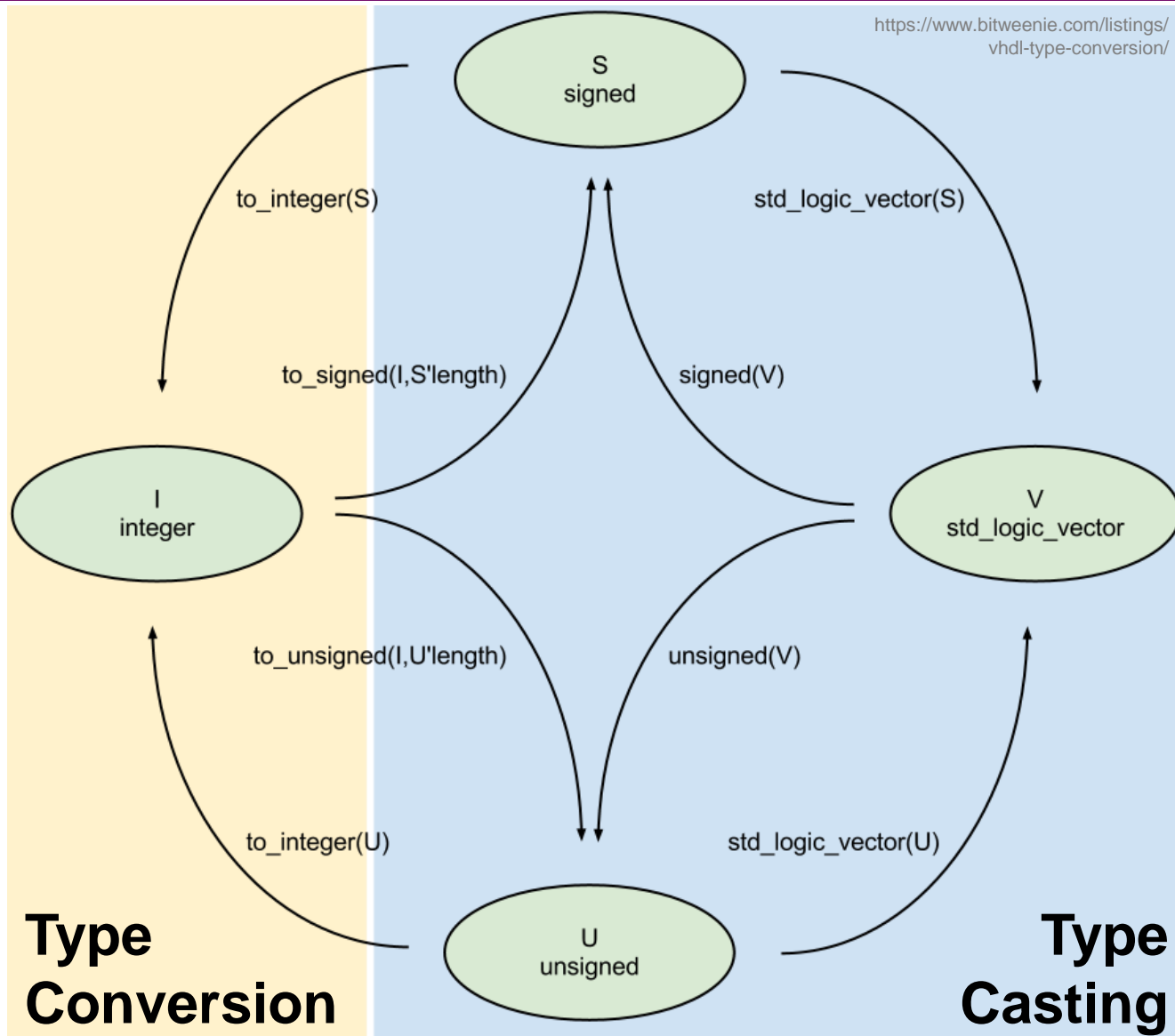

Remember to “use `IEEE.Numeric_Std.ALL`”!

Class Exercise 4.2



- Complete the counter FSM by filling in the missing line if the state is declared as an **unsigned** type:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.Numeric_Std.ALL;
entity counter is
    port(
        CLK: in std_logic;
        RESET: in std_logic;
        COUNT: out std_logic_vector
            (3 downto 0) );
end counter;
architecture counter_arch of counter
is
    signal s: unsigned(3 downto 0) :=
        "0000"; -- state
```

```
begin
```

```
    process(CLK, RESET)
    begin
        if(RESET = '1') then s <= "0000";
        else
            if( rising_edge(CLK) ) then
                s <= s + 1; -- feedback
            end if;
        end if;
    end process;
```

**Sequential
Logic**

Combinational Logic

```
end counter_arch;
```

Class Exercise 4.3



- Complete the counter FSM by filling in the missing line if the state is declared as an **integer** type:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.Numeric_Std.ALL;
entity counter is
    port(
        CLK: in std_logic;
        RESET: in std_logic;
        COUNT: out std_logic_vector
            (3 downto 0) );
end counter;
architecture counter_arch of counter
is
    signal s: integer range 0 to 15
        := 0; -- state
```

begin

```
process(CLK, RESET)
begin
    if(RESET = '1') then s <= "0000";
    else
        if( rising_edge(CLK) ) then
            s <= s + 1; -- feedback
        end if;
    end if;
end process;
```

Sequential Logic

Combinational Logic

end counter_arch;

Integer Type



- An **integer type** can be defined with or without specifying a range.
 - If a range is not specified, VHDL allows integers to have a minimum range of

$-2,147,483,647$ to $2,147,483,647$


$-(2^{31} - 1)$ to $(2^{31} - 1)$

- Or a range can be specified, e.g.,

```
signal int: integer range 0 to 255;
```


FSM Example 2) Pattern Generator (1/2)

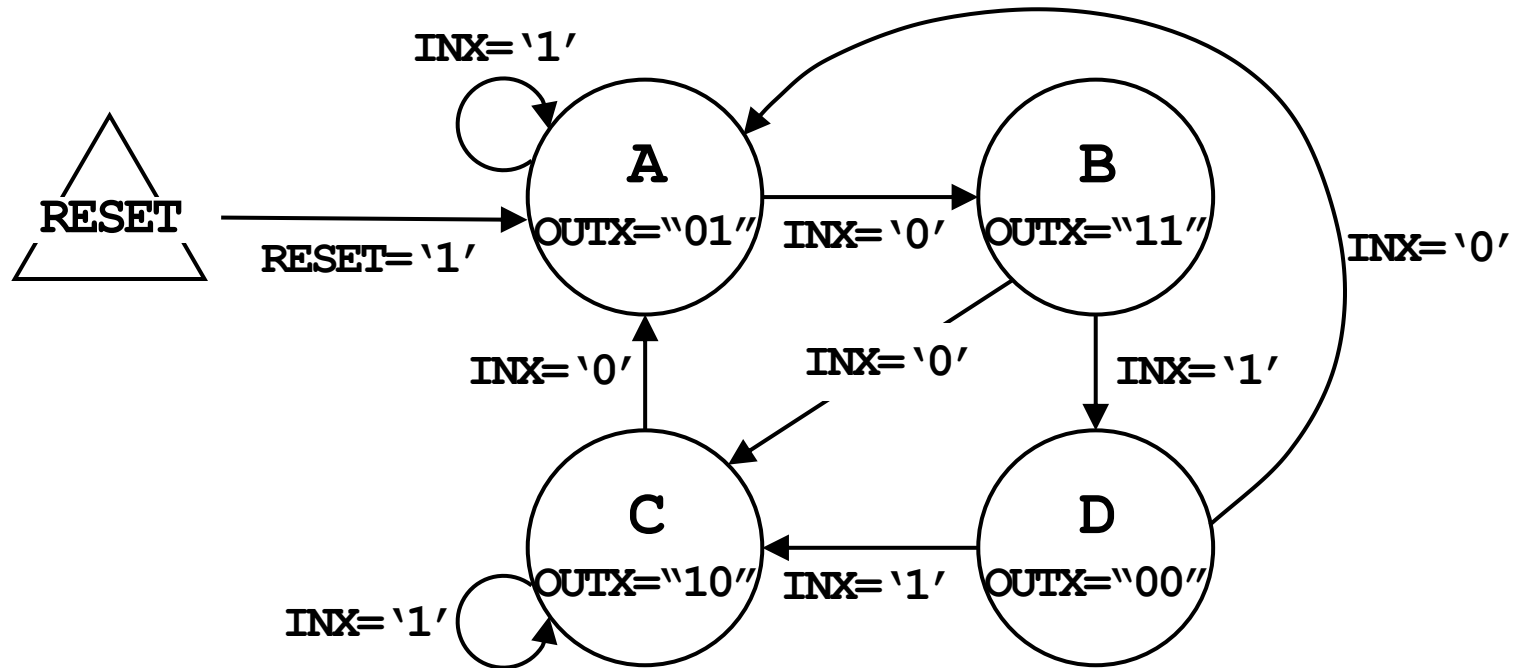- **Pattern Generator:** Generates **any pattern** we want.
- Given the following machine of 4 states: **A**, **B**, **C** and **D**.



- The machine has an asynchronous **RESET**, a clock signal **CLK**, and a 1-bit synchronous input signal **INX**.
- The machine also has a 2-bit output signal **OUTX**.

FSM Example 2) Pattern Generator (2/2)

```
library IEEE;
use IEEE.std_logic_1164.all;
entity pat_gen is port(
RESET,CLOCK,INX: in STD_LOGIC;
OUTX: out STD_LOGIC_VECTOR(1
downto 0));
end pat_gen;
architecture arch of pat_gen is
type state_type is (A,B,C,D);
signal s: state_type; -- state
begin
process(CLOCK, RESET)
begin
if RESET = '1' then
s <= A;
elsif rising_edge(CLOCK) then
-- feedback
case s is
when A =>
if INX = '1' then s <= A;
else s <= B; end if;
```

**Sequential
Logic**

```
when B =>
if INX = '1' then s <= D;
else s <= C; end if;
when C =>
if INX = '1' then s <= C;
else s <= A; end if;
when D =>
if INX = '1' then s <= C;
else s <= A; end if;
end case;
end if;
end process;
process(s)
begin
case s is
when A => OUTX <= "01";
when B => OUTX <= "11";
when C => OUTX <= "10";
when D => OUTX <= "00";
end case;
end process; -- Moore Machine
end arch;
```

**Combinational
Logic**

Enumeration Type



- An **enumeration type** introduces abstraction into circuits by allowing users defining a list of values.

- Example:

```
type colors is (RED, GREEN, BLUE);  
signal my_color: colors;
```

- An enumerated type is **ordered**.

- The order in which the values are listed in the type declaration defines their relation:

*Each values is greater than the one to the left,
and less than the one to the right.*

- Example: a comparison can be:

```
my_color > RED and my_color < BLUE
```

Class Exercise 4.4

Student ID: _____ Date: _____
Name: _____

- Complete the Mealy FSM that recognizes sequence "10":

architecture arch of mealy_fsm is

```
type state_type is (S0, S1);
```

```
signal s: std_logic; -- state
```

```
begin
```

```
process(CLK, RESET) -- seq
```

```
begin
```

```
if(RESET = '1') then s <= S0;
```

```
else
```

```
if( rising_edge(CLK) ) then
```

```
case s is
```

```
when S0 =>
```


```
if INX = '1' then
```

```
s <= S1; -- feedback
```

```
else
```

```
s <= S0; -- feedback
```

```
end if;
```

 

```
when S1 =>
```

```
if INX = '0' then
```

```
s <= S0; -- feedback
```

```
else
```

```
s <= S1; -- feedback
```

```
end if;
```

```
end case;
```

```
end if;
```

```
end if;
```

```
end process;
```

```
OUTX <= '1' when (s = S0 and INX = '1')
```

```
else '0'; -- Mealy
```

```
end arch;
```



- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- FSM Types
 - Moore Machine
 - Mealy Machine
- FSM Examples
 - Up/Down Counter
 - Pattern Generator
- **Rule of Thumb: FSM Coding Tips**

Rule of Thumb: FSM Coding Tips



- ① **Maintain/define the internal state(s) explicitly**
- ② **Separate combinational and sequential logics**
 - Write **at least two processes**: one for combinational logic, and the other for sequential logic
 - Maintain the **internal state(s)** using a sequential process
 - Drive the **output(s)** using a combination process
- ③ **Keep every process as simple as possible**
 - Partition a large process into **multiple small ones**
- ④ **Put every signal (*that your process must be sensitive to its changes*) in the sensitivity list**
- ⑤ **Avoid assigning a signal from **multi-processes****
 - It may cause the “**multi-driven**” issue.





- Finite State Machine (FSM)
 - Time Controlling
 - State Maintenance
- FSM Types
 - Moore Machine
 - Mealy Machine
- FSM Examples
 - Up/Down Counter
 - Pattern Generator
- Rule of Thumb: FSM Coding Tips