



香港中文大學

The Chinese University of Hong Kong


*CSCI2510 Computer Organization*

**Lecture 09:**

**Basic Processing Unit**

 
**Ming-Chang YANG**

[mcyang@cse.cuhk.edu.hk](mailto:mcyang@cse.cuhk.edu.hk)




Reading: Chap. 2.13, 5

# Basic Functional Units of a Computer

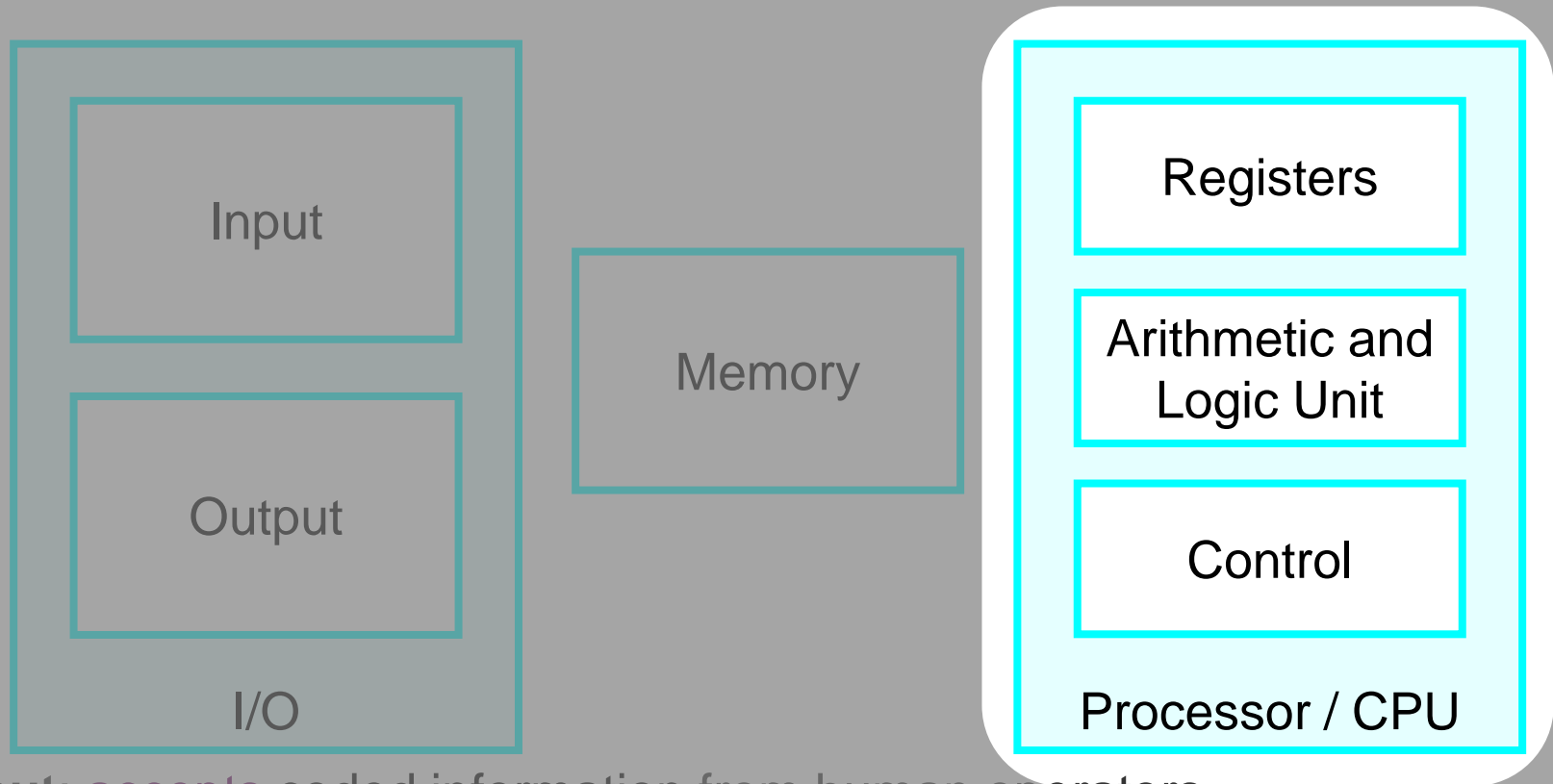

- **Input:** accepts coded information from human operators.
- **Memory:** stores the received information for later use.
- **Processor:** executes the instructions of a program stored in the memory.
- **Output:** reacts to the outside world.
- **Control:** coordinates all these actions.

 
- Main Components of a Processor
- RISC-Style Processor Design
  - Five-Stage Organization
  - Instruction Execution
- CISC-Style Processor Design
  - Multi-Bus Interconnect
  - Instruction Execution
- Control Signal Generation


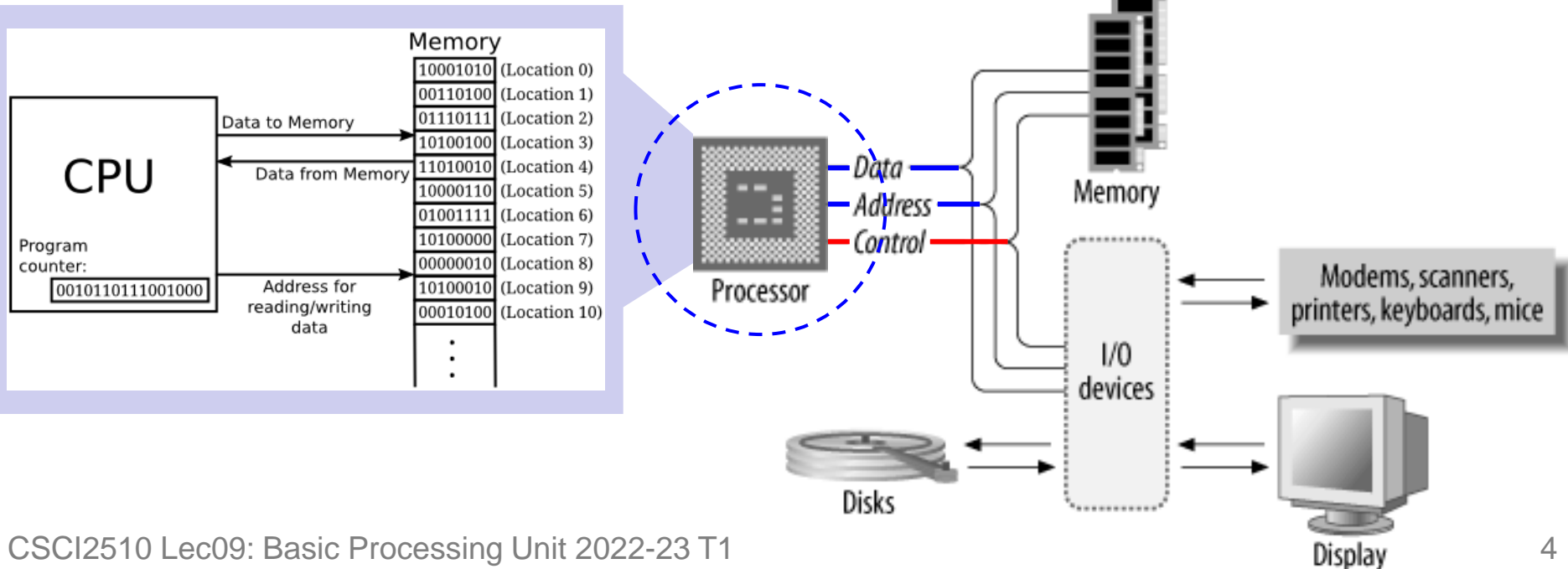
# Basic Processing Unit: Processor



- **Executing** machine-language instructions.
- **Coordinating** other units in a computer system.
- Used to be called the **central processing unit (CPU)**.
  - The term “central” is no longer appropriate today.
  - Today’s computers often include several processing units.
    - E.g., multi-core processor, graphic processing unit (GPU), etc.



# Main Components of a Processor



## Control Circuitry

*Interpret/decode* the fetched instruction & issue *control signals* to coordinate all the other units

## Register File (i.e., $R_0 \sim R_{n-1}$ )

Served as the processor's *general-purpose registers*

## Arithmetic and Logic Unit (ALU)

Perform *arithmetic or logic operations*

## Instruction Address Generator

### Program Counter (PC)

Keep the address of the next instruction to be fetched and executed (*special register*)

*Update the contents of PC* after every instruction is fetched

### Instruction Register (IR)

Hold the instruction until its execution is completed (*special register*)

### Other Special Registers

*E.g., memory address register, memory data register, condition code register, stack pointer register, link register, etc.*


## Processor–Memory Interface

Allow *communication between processor and memory* through two special registers: *memory address register (MAR)* and *memory data register (MDR)*
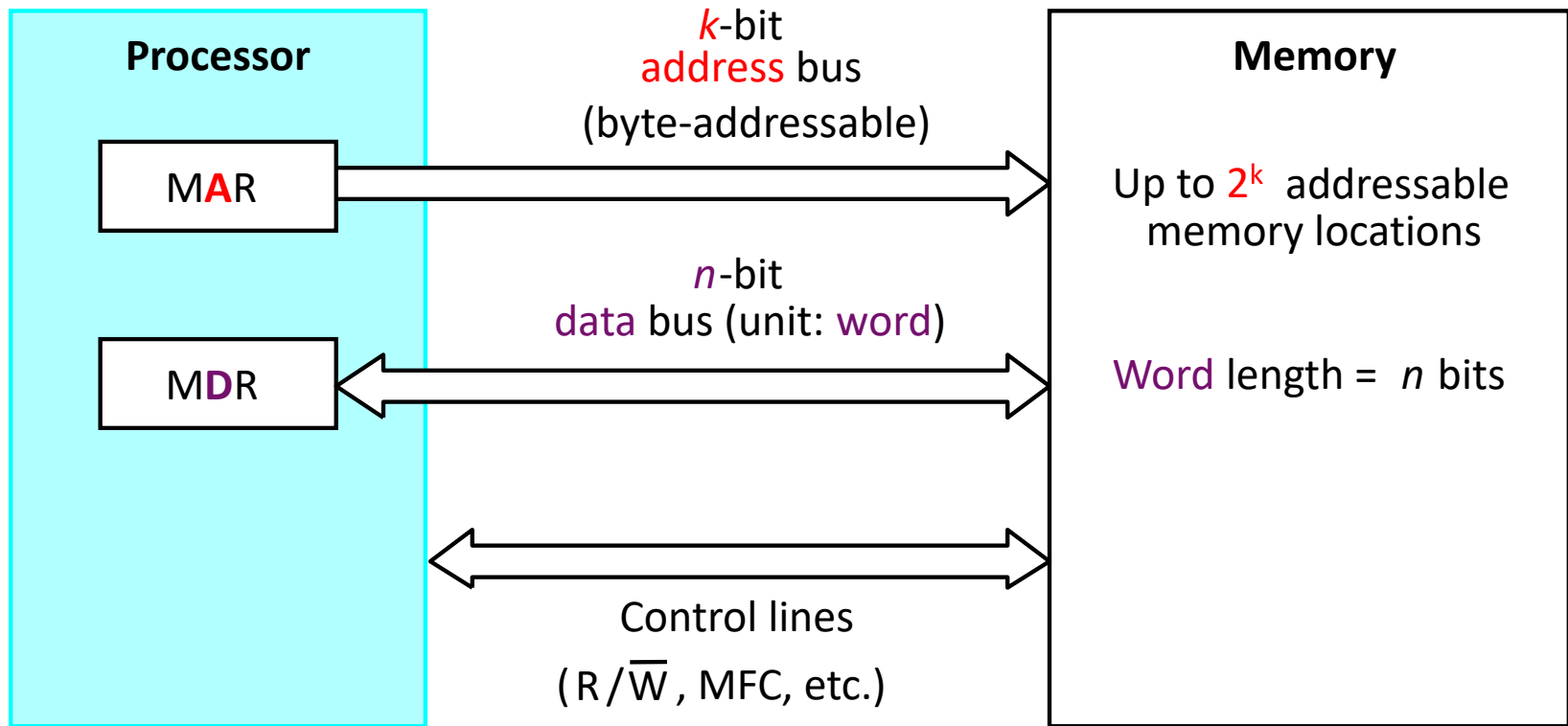
# Recall: Processor-Memory



- Data transferring takes place through MAR and MDR.
  - **MAR**: Memory **A**ddress Register
  - **MDR**: Memory **D**ata Register



*\*MFC (Memory Function Completed): Indicating the requested operation has been completed.*

# Recall: RISC vs. CISC Styles



- There are two fundamentally different approaches in the design of instruction sets for modern computers:
  - 1) **Reduced Instruction Set Computer (RISC)** reduces the **complexity/types** of instructions for **higher performance**.
    - Each instruction fits in a **single word** in memory.
    - A **load/store architecture** is adopted.
      - Memory operands are accessed only using Load/Store instructions.
      - The operands involved in arithmetic/logic operations must be either in registers or given explicitly within the instruction.
  - 2) **Complex Instruction Set Computer (CISC)** allows **more complicated** but **powerful** instructions to be designed.
    - Each instruction may span **more than one word** in memory.
    - The operands involved in arithmetic/logic operations can be in **both registers and memory** or given explicitly within the instruction.
    - **Two-operand** format is usually used.

**The processor design is affected by the instruction set design!**



- Main Components of a Processor
- **RISC-Style Processor Design**
  - Five-Stage Organization
  - Instruction Execution
- CISC-Style Processor Design
  - Multi-Bus Interconnect
  - Instruction Execution
- Control Signal Generation




# Five-Stage Organization (RISC CPU)



- The execution of **RISC instructions** can be *generally* organized into a **five-stage** sequence of actions:

- ① Fetch an instruction and increment the PC.
- ② Decode the instruction & read source registers.
- ③ Perform an ALU operation.
- ④ Read or write memory data if memory operand is involved.
- ⑤ Write the result into the destination register.

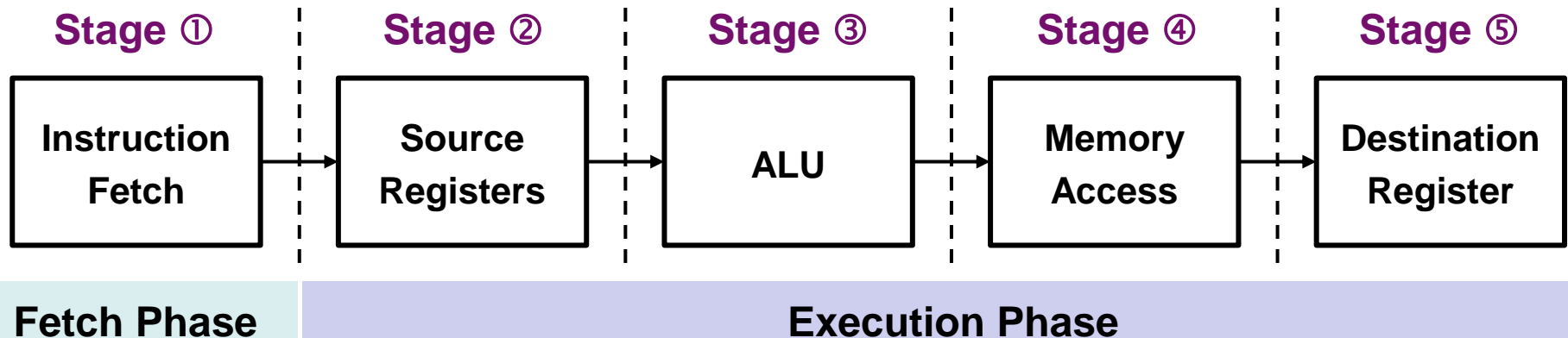
*Note: **Not** all these actions have to be carried out by every instruction.*


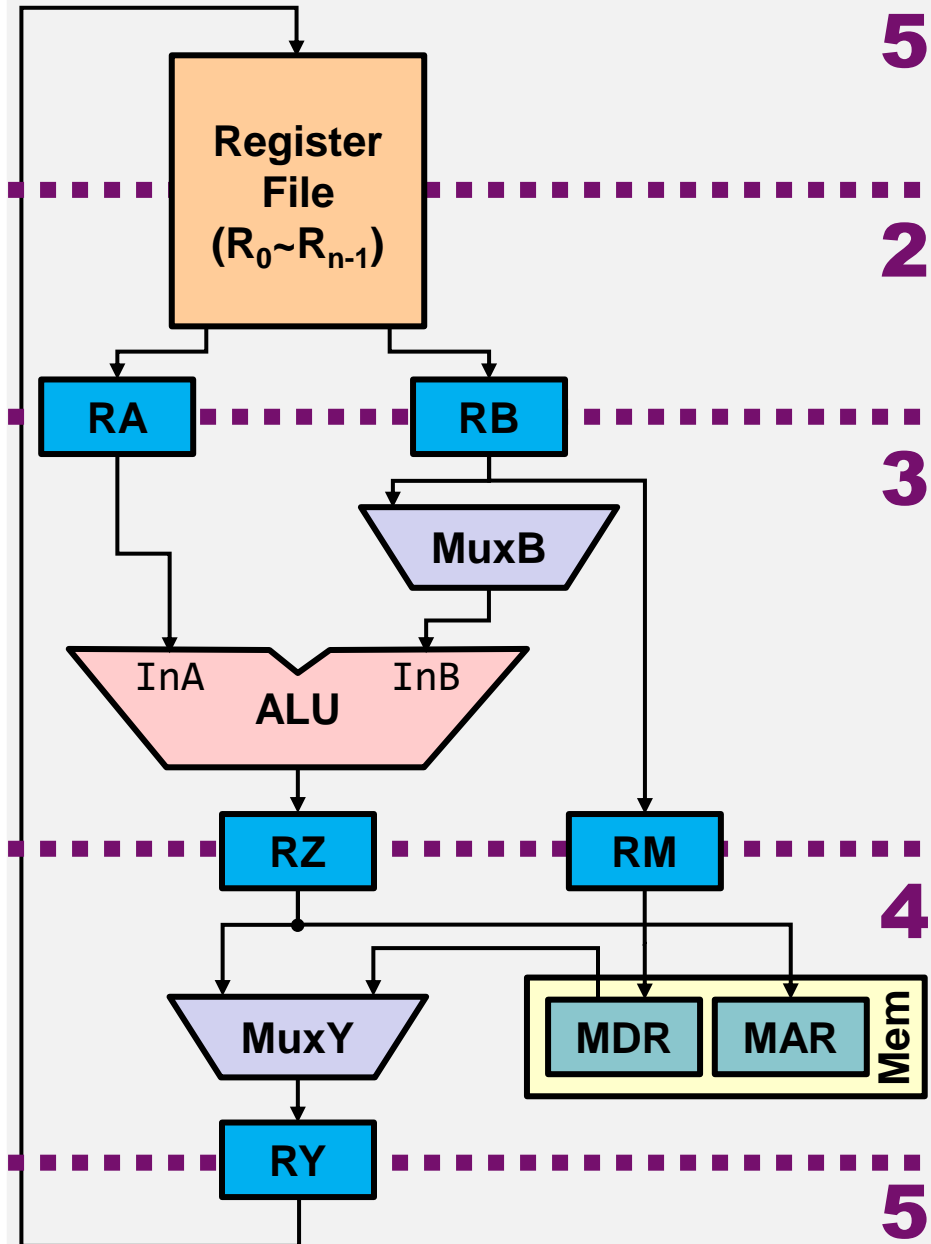
# Multi-Stage Structure: Datapath



- The processor's hardware can also be organized into **multiple stages**.
  - The actions taken in each stage can be completed **independently** and in **one clock cycle** (hopefully).
- It is necessary to insert **inter-stage registers** to:
  - Hold the produced results;
  - Work as inputs to the next.
- This multi-stage structure is often called **datapath**.





- Main Components of a Processor
- **RISC-Style Processor Design**
  - Five-Stage Organization
  - **Instruction Execution**
- CISC-Style Processor Design
  - Multi-Bus Interconnect
  - Instruction Execution
- Control Signal Generation




# Execution Phase: Stage ②



- The **execution phase** is generally of four stages:
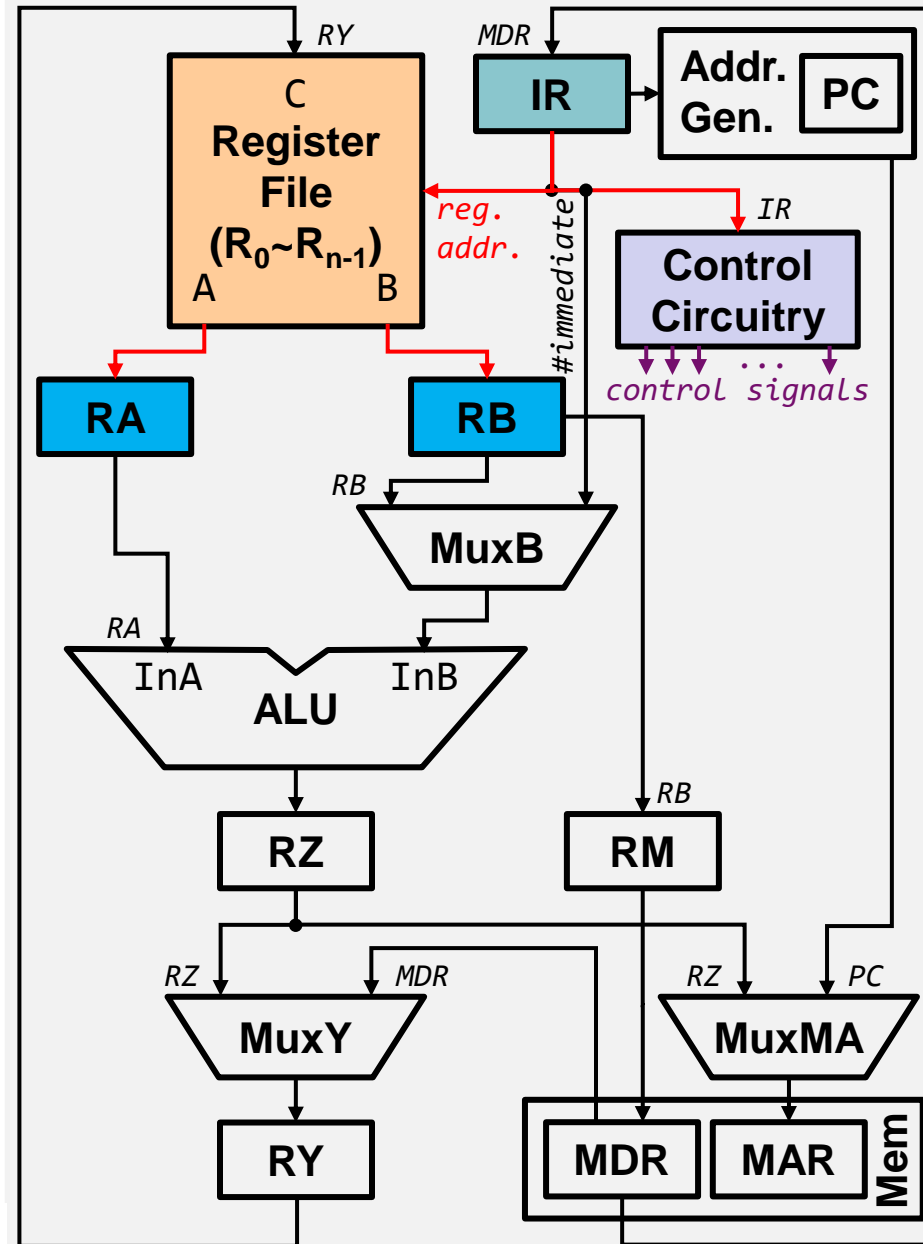
## ② Decode the instruction & read source registers.

- [IR]** must be firstly **decoded** by **Control Circuitry**.
  - It is for generating **signals** to **control** all the hardware.
- Two source registers can be read from **Register File** at the same time.
  - How? The source register addresses are supplied by **IR** directly (w/o decoding).
  - Two source registers are always read and placed into **RA** and **RB** (no matter whether they are needed).




# Instruction Encoding



- Consider a **RISC-style** processor that
  - Has **32 general-purpose registers**;
  - Represents every instruction by a **32-bit word**.
- Representative encoding formats include:


## ① Three-Operand Format

- E.g., Add, Rdst, Rsrc1, Rsrc2

 
 
## ② Immediate-Operand Format

- E.g., Add Rdst, Rsrc, #Value
- E.g., Load/Store instruction using register indirect or index modes
- E.g., Branch instruction using offset



## ③ Address-Operand Format

- E.g., Branch instruction
- E.g., Call instruction




**The instruction encoding varies (a lot) from machine to machine!**
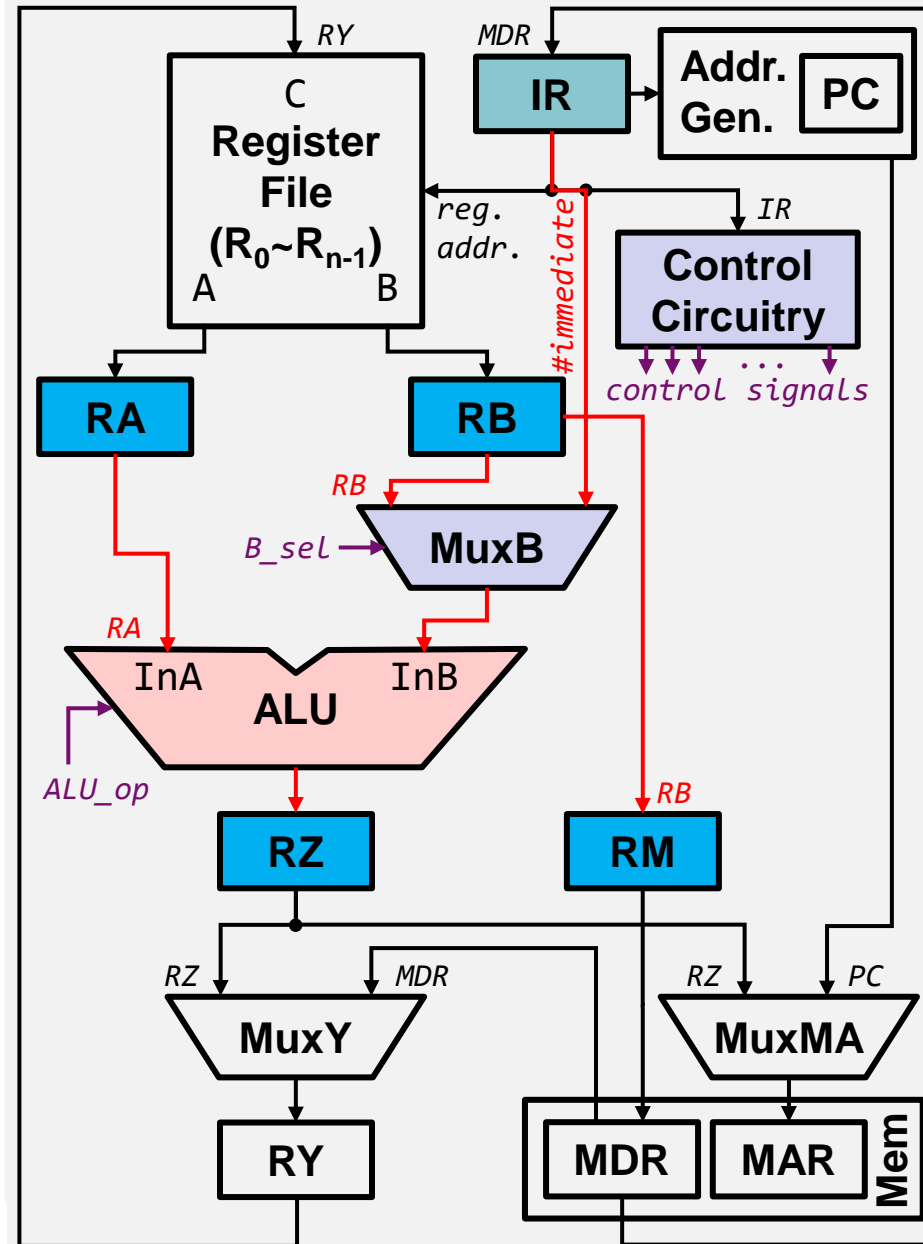
# Execution Phase: Stage ③




- The **execution phase** is generally of four stages:
  - ③ **Perform ALU operation.**
    - The input InA of **ALU** is supplied by **RA**.
    - The input InB of **ALU** is supplied by the multiplexer **MuxB** which forwards:
      - Either the contents of **RB**;
      - Or the immediate value specified in **IR**.
    - ALU** performs the operation.
    - The computed result is placed in **RZ**.
    - Note: **[RB]** is always forwarded to **RM** (though it's only needed by **Store**).


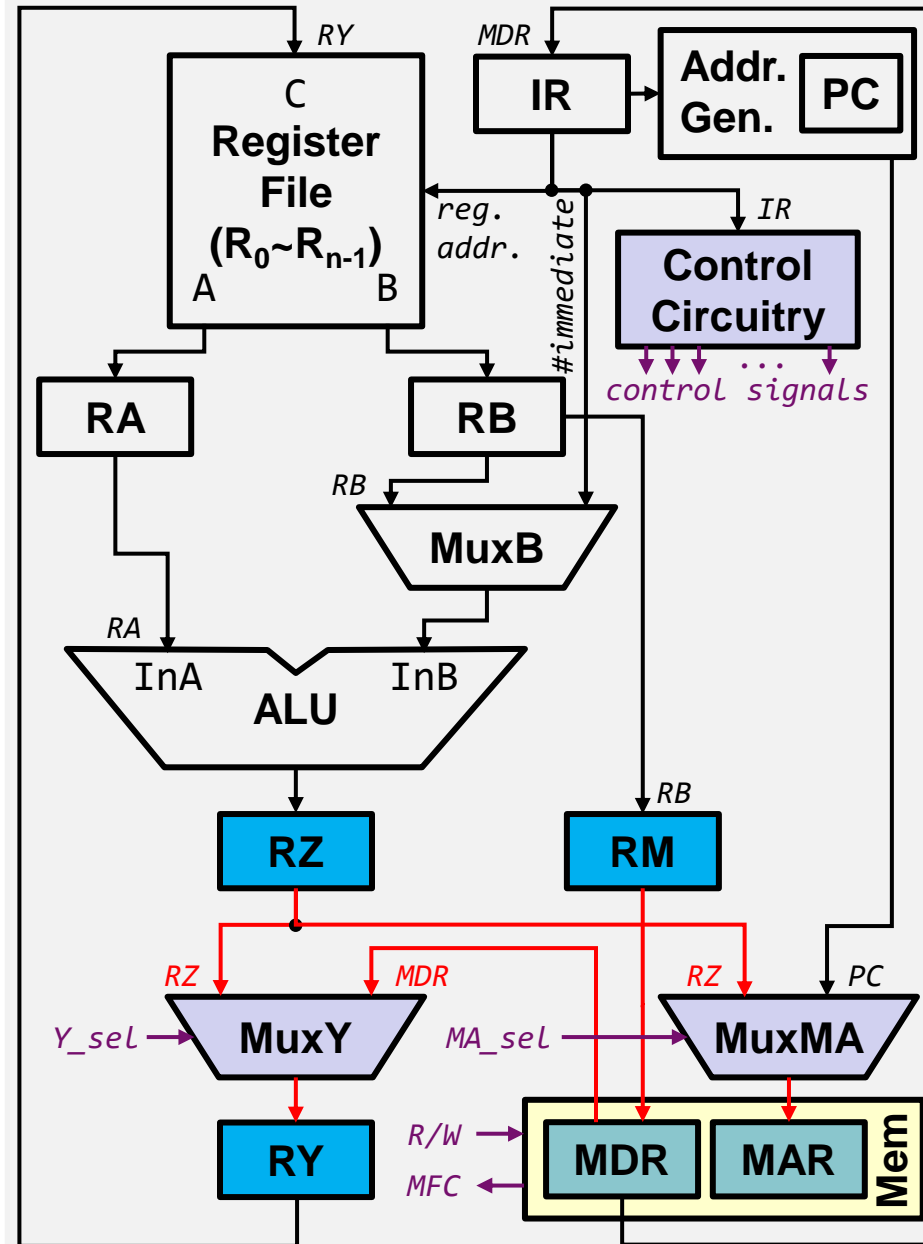
# Execution Phase: Stage ④



- The **execution phase** is generally of four stages:
  - ④ **Read/write memory data.**
    - The memory read/write takes place via [Processor-Mem Interface](#).
      - The **effective address** is derived by **ALU** and kept in **RZ** in Stage ③.
      - The “loaded” data are put into **RY** (with the multiplexer **MuxY** properly set).
      - The “to-be-stored” data are available in **RM**.
    - Note: For non-Load and non-Store instructions, the data in **RZ** are forwarded to **RY**.







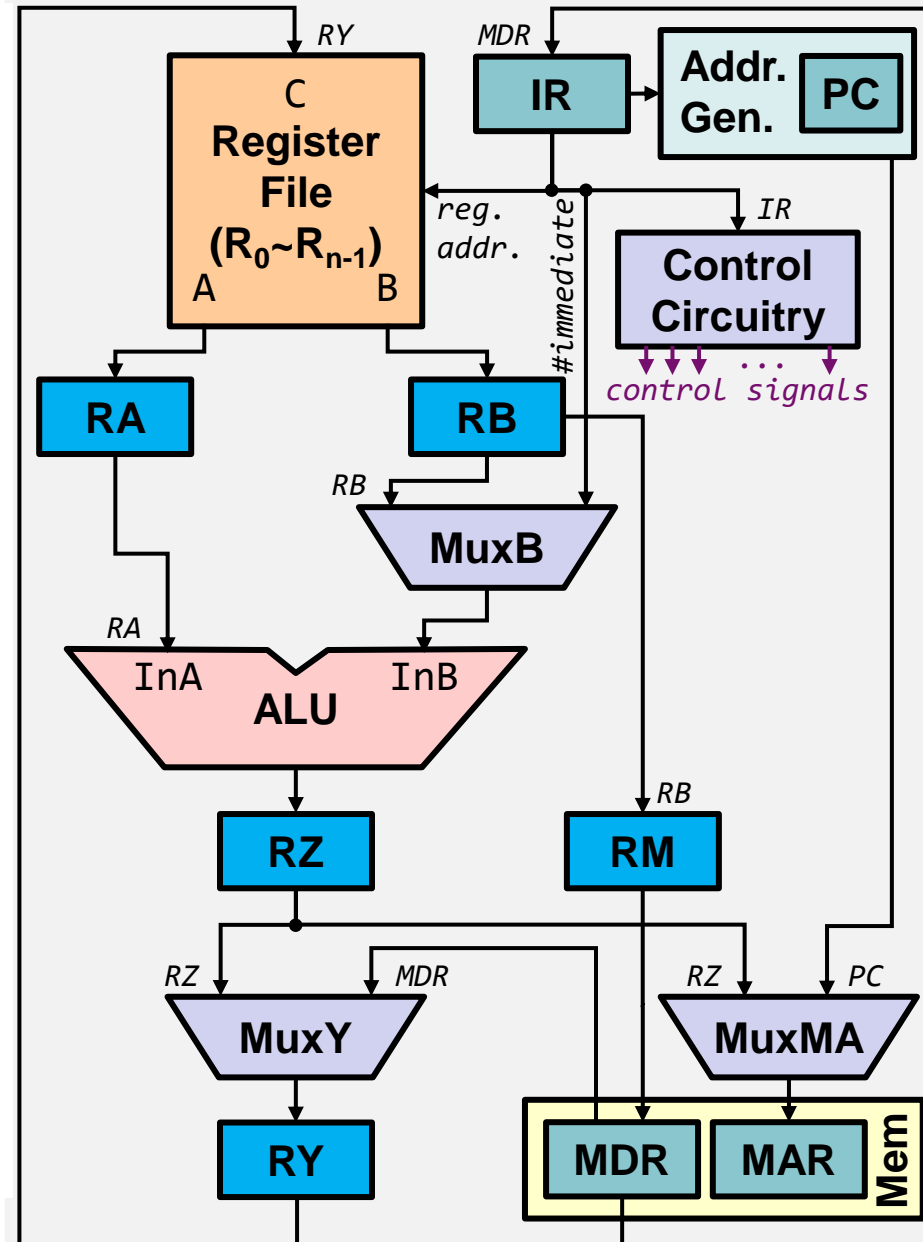
# Observations



- The datapath is designed to be **independent** and **versatile**.
- But **not all actions/stages have to be carried out** by every instructions.
- Let's examine the actual execution of the following typical instructions:
  - Add R3, R4, R5
  - Load R5, X(R7)
  - Store R6, X(R8)
  - Branch



# Recall: Register Transfer Notation



- Register Transfer Notation (RTN) describes the data transfer from one location in computer to another.
  - Possible locations: memory locations, processor registers.
    - Locations can be identified **symbolically** with names (e.g., LOC).


**Ex.**

**R2** ← **[LOC]**

- *Transferring the contents of memory LOC into register R2.*

- ① **Contents of any location**: denoted by placing square brackets **[ ]** around its location name (e.g. **[LOC]**).
- ② **Right-hand side** of RTN: always denotes a **value**
- ③ **Left-hand side** of RTN: the name of a **location** where the value is to be placed (by overwriting the old contents)

# Ex 1: Add R3, R4, R5

 

①  $MAR \leftarrow [PC]$ , Read memory, Wait\_MFC,  $IR \leftarrow [MDR]$ ,  $PC \leftarrow [PC] + 4$  (shown [here](#))

② Decode instruction,  $RA \leftarrow [R4]$ ,  $RB \leftarrow [R5]$

- The source register addresses are available in  $IR_{31-27}$  and  $IR_{26-22}$ .
- As a result,  $[R4]$  and  $[R5]$  can be read into **RA** and **RB** in Stage ②.

③  $RZ \leftarrow [RA] + [RB]$


- **MuxB** is set to select input from **RB**.
- **ALU** is set to perform an **Add**.

④  $RY \leftarrow [RZ]$

- **MuxY** is set to select input from **RZ**.

⑤  $R3 \leftarrow [RY]$

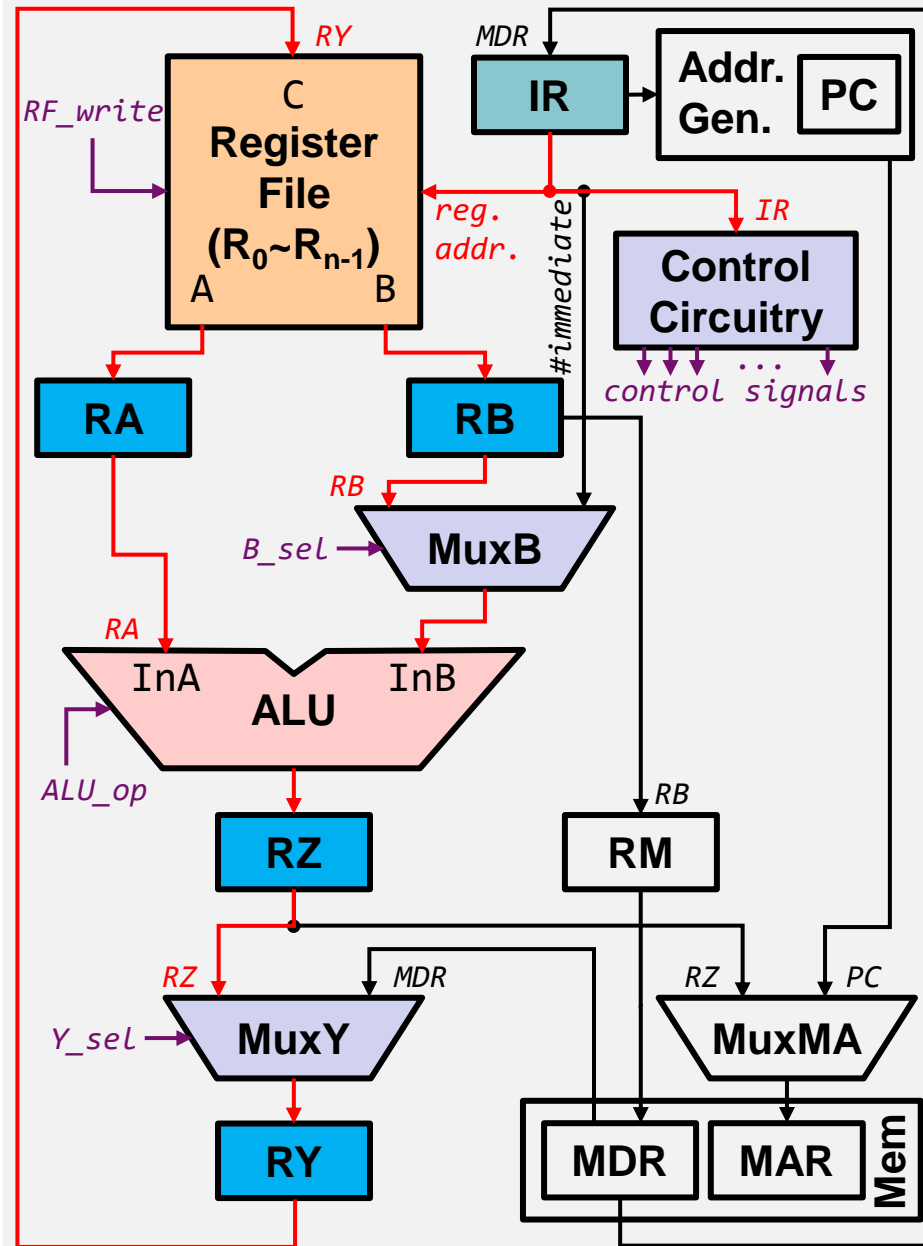- The dest. reg. address is in  $IR_{21-17}$ .
- **RF\_write** is set to allow writing R3.




# Class Exercise 9.1



- Assume **R3**, **R4**, and **R5** originally hold the values **0**, **40**, and **60**, respectively.
- Considering **Add R3, R4, R5**, show the registers' contents “after” the completion of Stages ② to ⑤:
  - *Note: Fill in “?” for those blanks that cannot be determined.*

	RA	RB	RZ	RY	R3
②					
③					
④					
⑤					

# Ex 2: Load R5, X(R7)

 

①  $MAR \leftarrow [PC]$ , Read memory, Wait\_MFC,  $IR \leftarrow [MDR]$ ,  $PC \leftarrow [PC] + 4$  (shown [here](#))

② Decode instruction,  $RA \leftarrow [R7]$

- The src. reg. address is in  $IR_{31-27}$ .

③  $RZ \leftarrow [RA] + X$


- The immediate value  $X$  is from  $IR$ .
- **MuxB** is set to select input from  $IR$ .
- **ALU** is set to perform an **Add**.

④  $MAR \leftarrow [RZ]$ , Read memory, Wait\_MFC,  $RY \leftarrow [MDR]$

- **MuxMA** is set to select input from **RZ**.
- **MuxY** is set to select input from **MDR**.

⑤  $R5 \leftarrow [RY]$

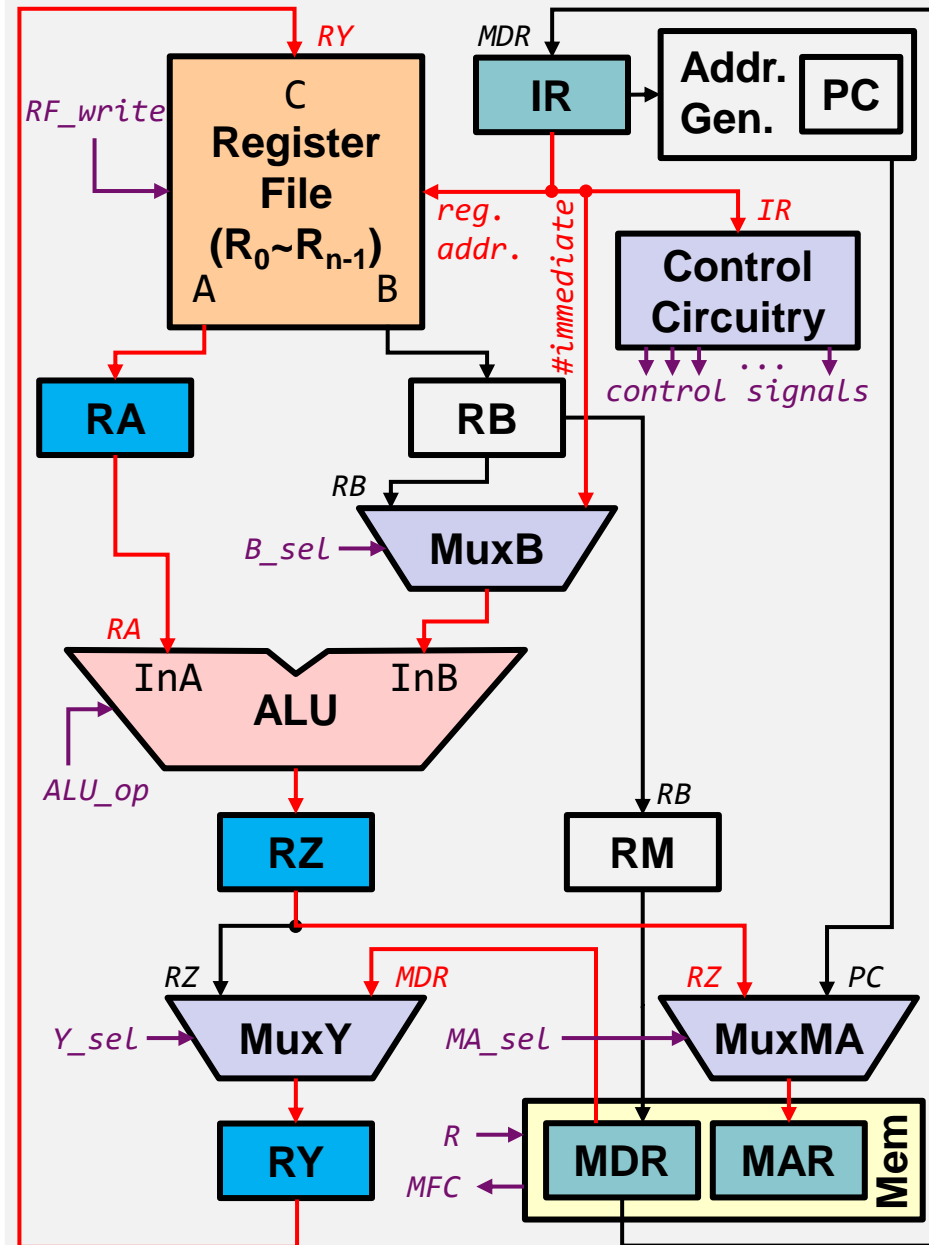- The dest. reg. address is in  $IR_{26-22}$ .
- **RF\_write** is set to allow writing **R5**.



# Class Exercise 9.2



- Assume **R5** and **R7** originally hold the values **0** and **4**, respectively, and the contents of main memory are shown as follows:

0x0	0x1	0x2	0x3	0x4	0x5	0x6	0x7	0x8	0x9	...
9	8	7	6	5	4	3	2	1	0	...


- Considering **Load R5, 4(R7)**, show the registers' contents "after" the completion of Stages ② to ⑤:
  - Note: Fill in "?" for those blanks that cannot be determined.*

	RA	RB	RZ	RY	MAR	MDR	R5	R7
②								
③								
④								
⑤								

# Ex 3: Store R6, X(R8)

31	27	26	22	21	6	5	0
Rsrc	Rdst	Immediate operand			OP code		



- MAR  $\leftarrow$  [PC], Read memory, Wait\_MFC, IR  $\leftarrow$  [MDR], PC  $\leftarrow$  [PC] + 4 (shown [here](#))
- Decode instruction, RA  $\leftarrow$  [R8], RB  $\leftarrow$  [R6]
  - The src. reg. address is in IR<sub>31-27</sub>.
  - The dest. reg. address is in IR<sub>26-22</sub>.
- RZ  $\leftarrow$  [RA] + X, RM  $\leftarrow$  [RB]
  - The immediate value X is from IR.
  - [R6] is forwarded to ④ via RM.
- MAR  $\leftarrow$  [RZ], MDR  $\leftarrow$  [RM], Write memory, Wait\_MFC
  - MuxMA is set to select input from RZ.
  - The written data are forwarded from RM to MDR.
- No action

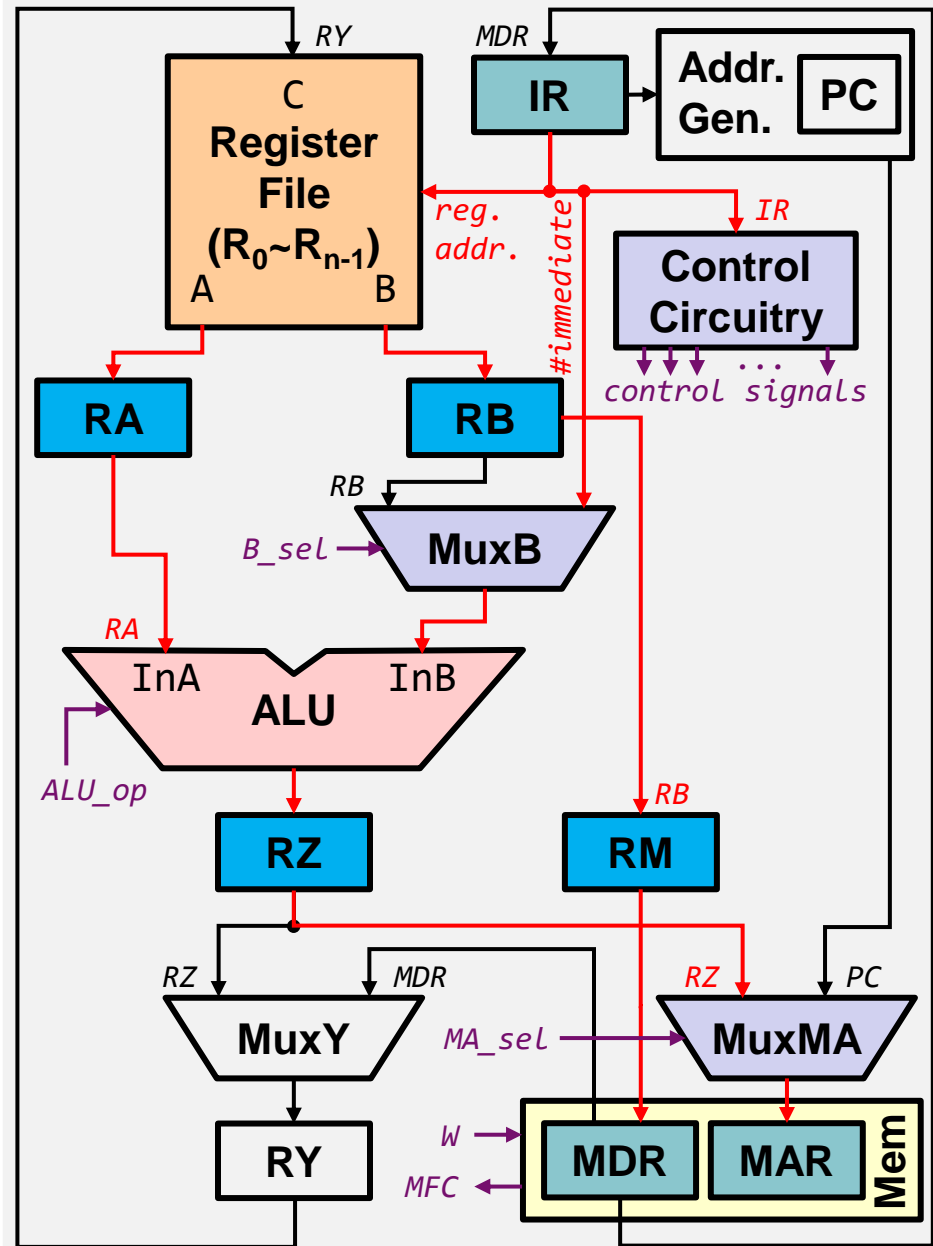


 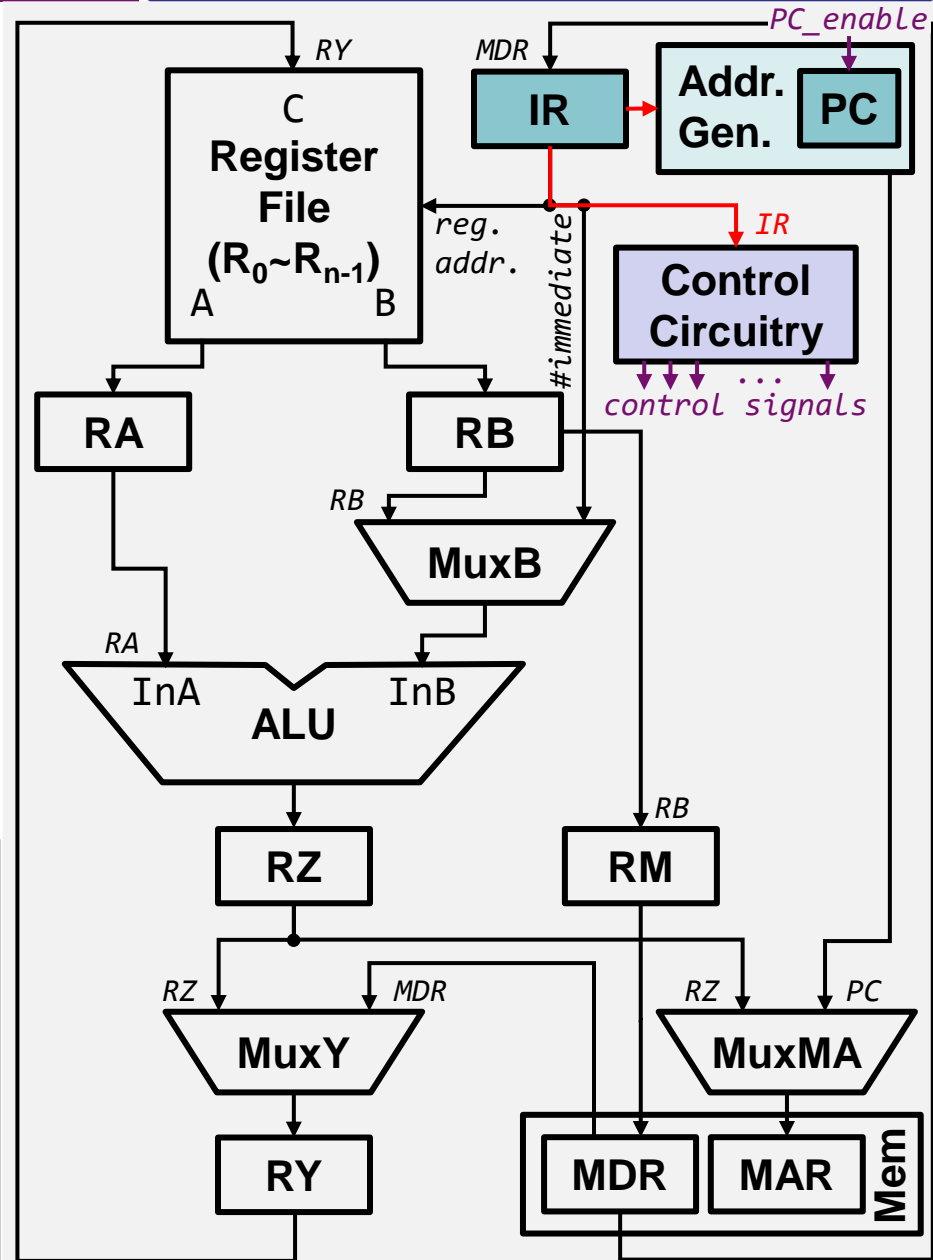
# Ex 4: Branch

- ①  $MAR \leftarrow [PC]$ , Read memory, Wait\_MFC,  $IR \leftarrow [MDR]$ ,  $PC \leftarrow [PC] + 4$  (shown [here](#))
- ② Decode instruction
- ③  $PC \leftarrow [PC] + \text{branch offset}$ 
  - The **branch offset** is from **IR**.
  - **MuxINC** (in **Instruction Address Generator**) is set to select **offset**.
- ④ No action
- ⑤ No action



# Class Exercise 9.3



- Branch instructions typically use the **address field** to specify an **offset** from the current instruction to the branch target.

- Given the program, what is the required **offset** for **Branch LOOP** at the memory address **140**?


– *Note: This program finds out the smallest number in a list.*

LABEL	ADDR.	OPCODE	OPERAND
	100	Move	<u>R2</u> , addr LIST
	104	Clear	R3
	108	Load	<u>R4</u> , N
	112	Load	<u>R5</u> , (R2)
LOOP:	116	Subtract	<u>R4</u> , R4, #1
	120	Branch_if_[R4]=0	DONE
	124	Add	<u>R3</u> , R3, #4
	128	Load	<u>R6</u> , (R2,R3)
	132	Branch_if_[R6]≥[R5]	LOOP
	136	Move	<u>R5</u> , R6
	<b>140</b>	<b>Branch</b>	<b>LOOP</b>
DONE:	144	Store	R5, <u>RESULT</u>
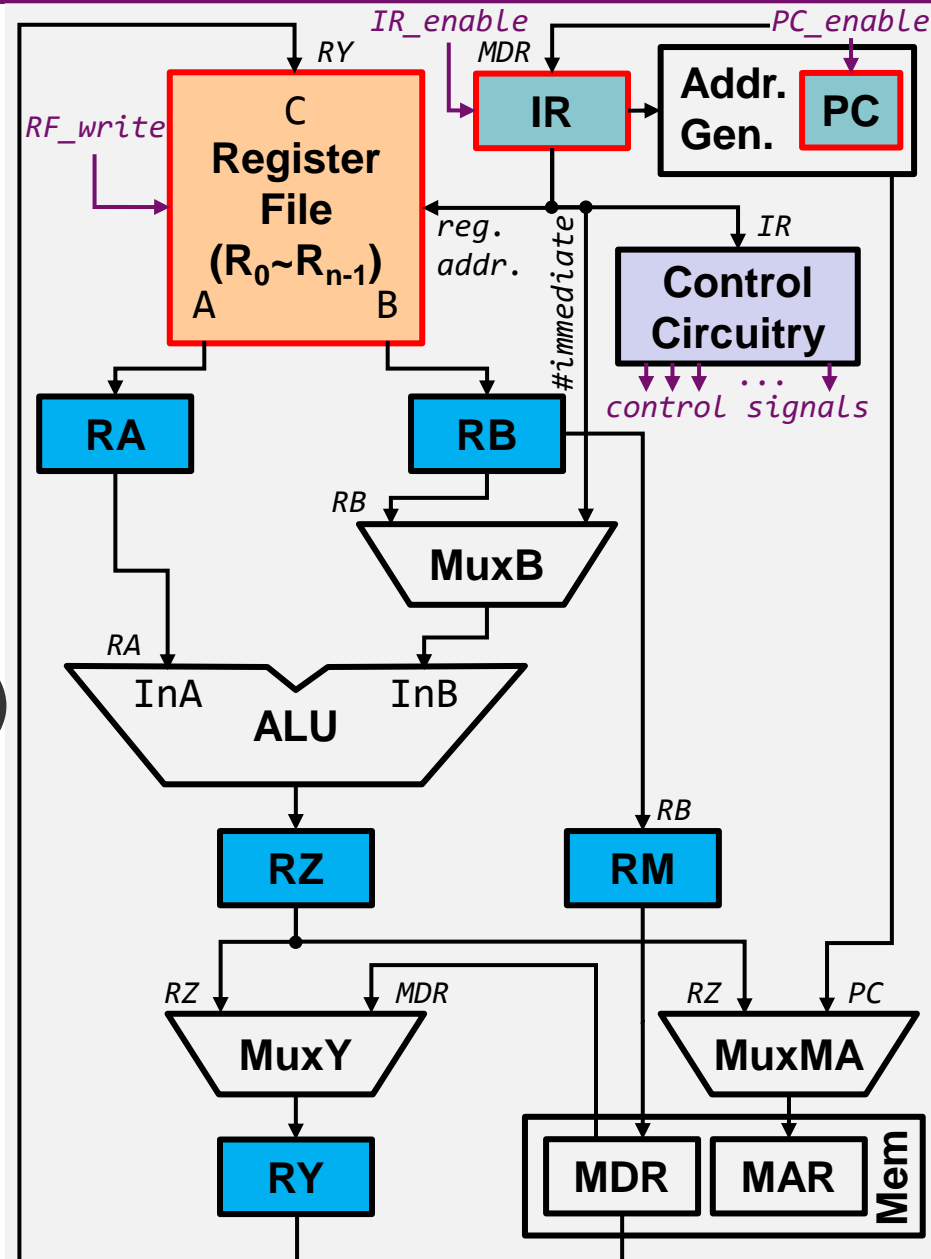
# Remark 1: Register Enabling




- **Inter-stage registers** (i.e., **RA**, **RB**, **RZ**, **RM**, & **RY**) are always enabled.
  - The results from one stage are always transferred to the next for **simplicity**.
- The other registers (e.g., **PC**, **IR**, and **Register File**) must **not** be changed in every stage.
  - They must be enabled only at certain times.
    - How? By setting **PC\_enable**, **IR\_enable** and **RF\_write**.


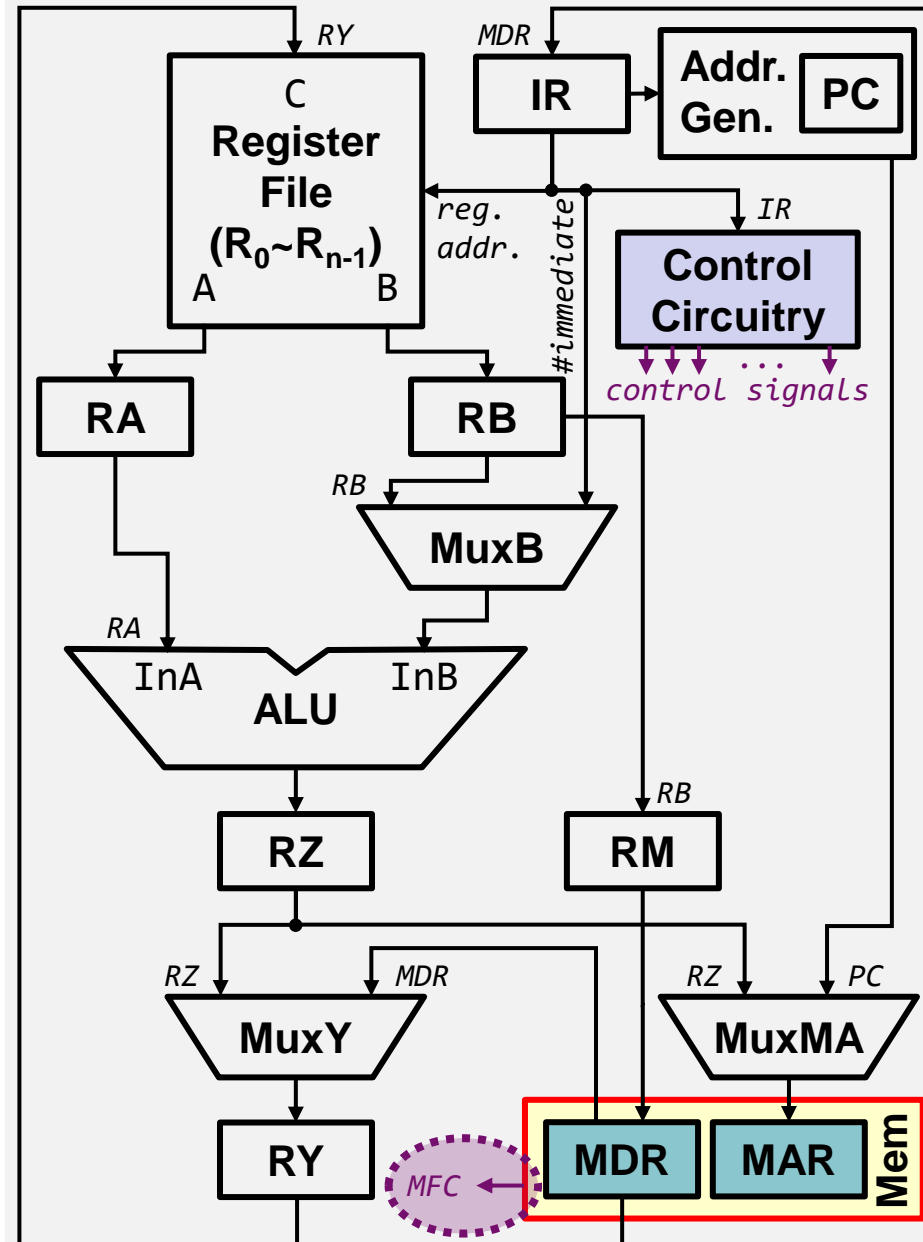
# Remark 2: Memory Function Completed

- If data are **in cache**, the stage can be completed in **one clock cycle**.
- If data are **not in cache**, the stage may take **several clock cycles**.
  - To handle such uncertainty:
    - **Processor-Memory Interface** generates the **MFC signal** upon the completion of a memory operation.
    - **Control Circuitry** checks the **MFC signal** during any stage involving memory to delay subsequent stage(s).






- Main Components of a Processor
- RISC-Style Processor Design
  - Five-Stage Organization
  - Instruction Execution
- **CISC-Style Processor Design**
  - Multi-Bus Interconnect
  - Instruction Execution
- Control Signal Generation
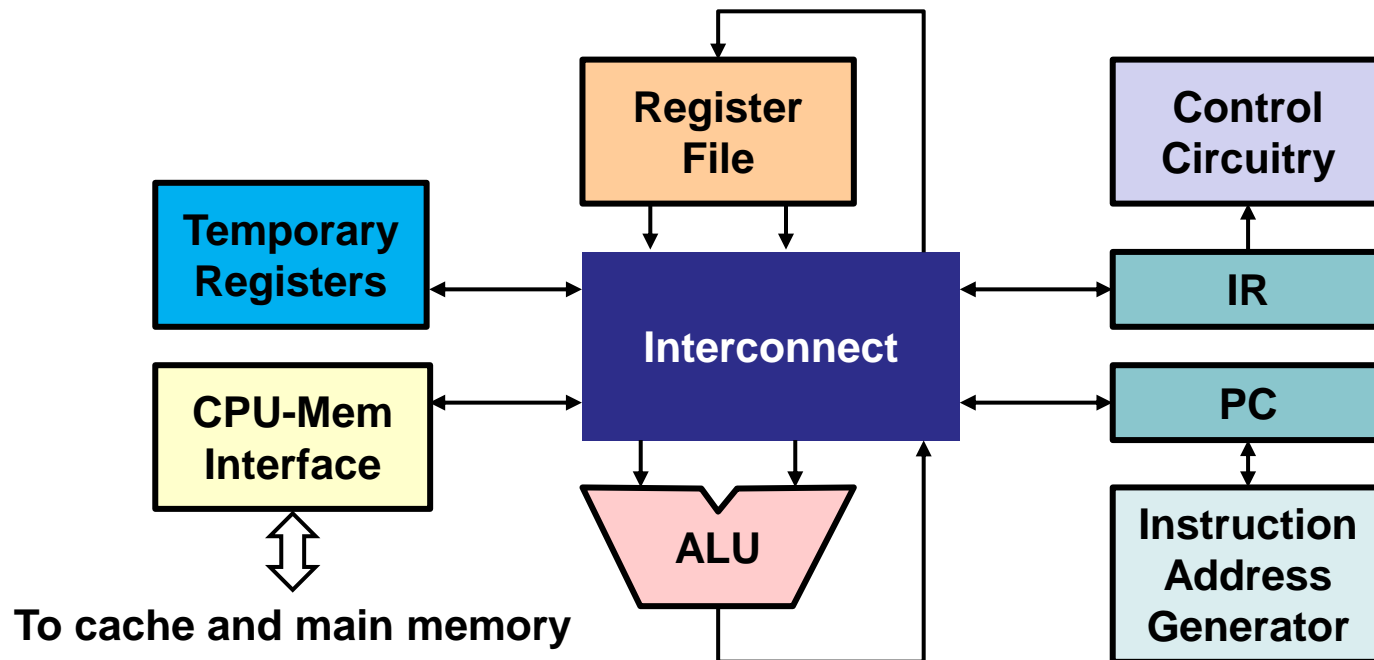
# Interconnect (CISC CPU)




- CISC-style instructions require a different and more flexible organization of the processor hardware:
  - **Interconnect** provides interconnections among other units but does **not** prescribe any pattern of data flow.
  - Inter-stage registers are **not** needed, but it is still necessary to have some **Temporary Registers**.


 
# Buses: Key to Transferring Data




- It is typical to use **buses** to implement **Interconnect**.
  - A bus consists of a set of lines that enable **data transferring** from any one device to any other (connected to the bus).
- There may be multiple devices connected to the bus:
  - **Only one** can drive the bus at any given time.
  - **More than one** can receive data from the bus at the same t.
  - For this reason, **switches** ( $\rightarrow \text{switch} \rightarrow$ ) are often needed to allow data to be transferred into or transferred out from a device.


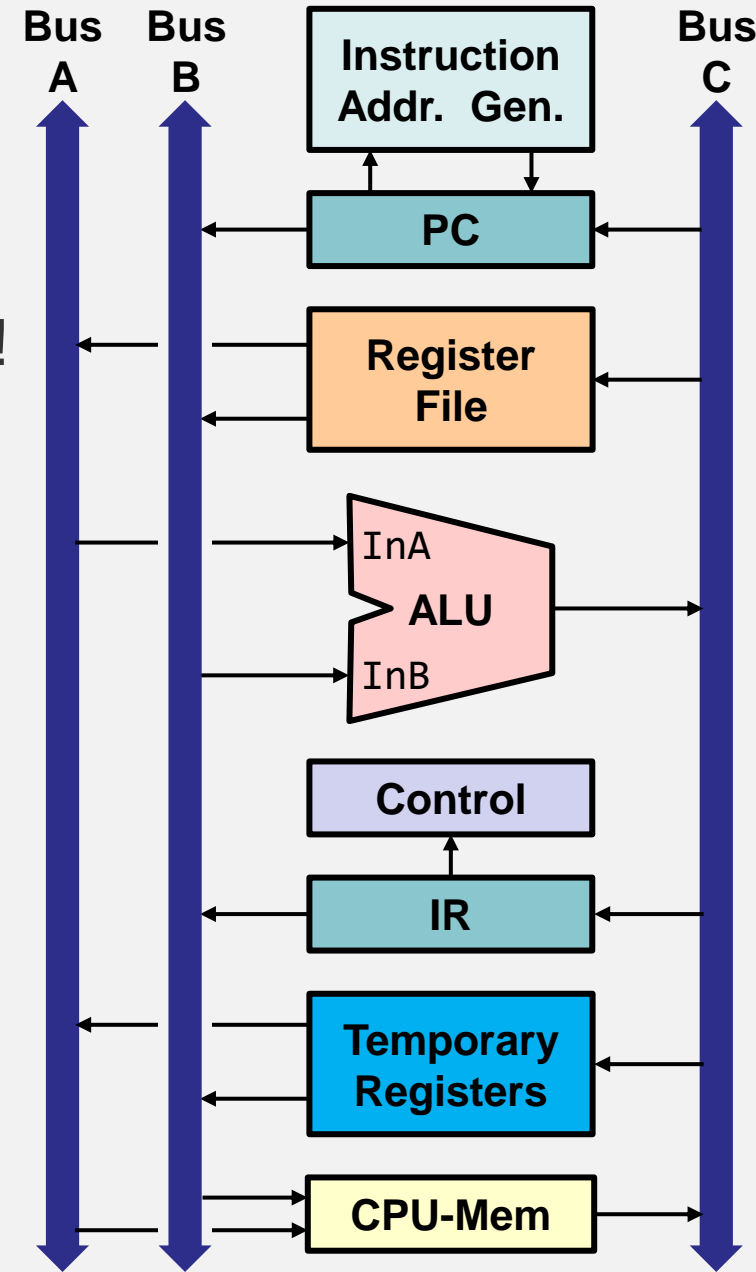
# Three-Bus Implementation



- It is common to interconnect the processor hardware via **three buses**:
  - Why 3? Typical instruction format!
  - **Bus A** and **Bus B** allow the **data transfer of two source operands** to **ALU** simultaneously.
  - **Bus C** allows **transferring the result** (computed by **ALU**) to the destination operand.
  - *Note: **Addresses** for the three ports of **Register File** are generated by **Control Circuitry** (not shown in the figure).*







- Main Components of a Processor
- RISC-Style Processor Design
  - Five-Stage Organization
  - Instruction Execution
- **CISC-Style Processor Design**
  - Multi-Bus Interconnect
  - **Instruction Execution**
- Control Signal Generation

# Instruction Fetching and Decoding




- All the instructions **share the same actions of fetching and decoding:**

①  $MAR \leftarrow [PC]$ , Read memory,  
 $Wait\_MFC$ ,  $IR \leftarrow [MDR]$ ,  
 $PC \leftarrow [PC] + 4$

- Bus B** is used to send  $[PC]$  to **CPU-Memory Interface** to fetch the instruction.
- The data read from the memory are sent to **IR** over **Bus C**.
- Note: **Wait\_MFC** is needed since the data may be read from the main memory.

② Decode instruction

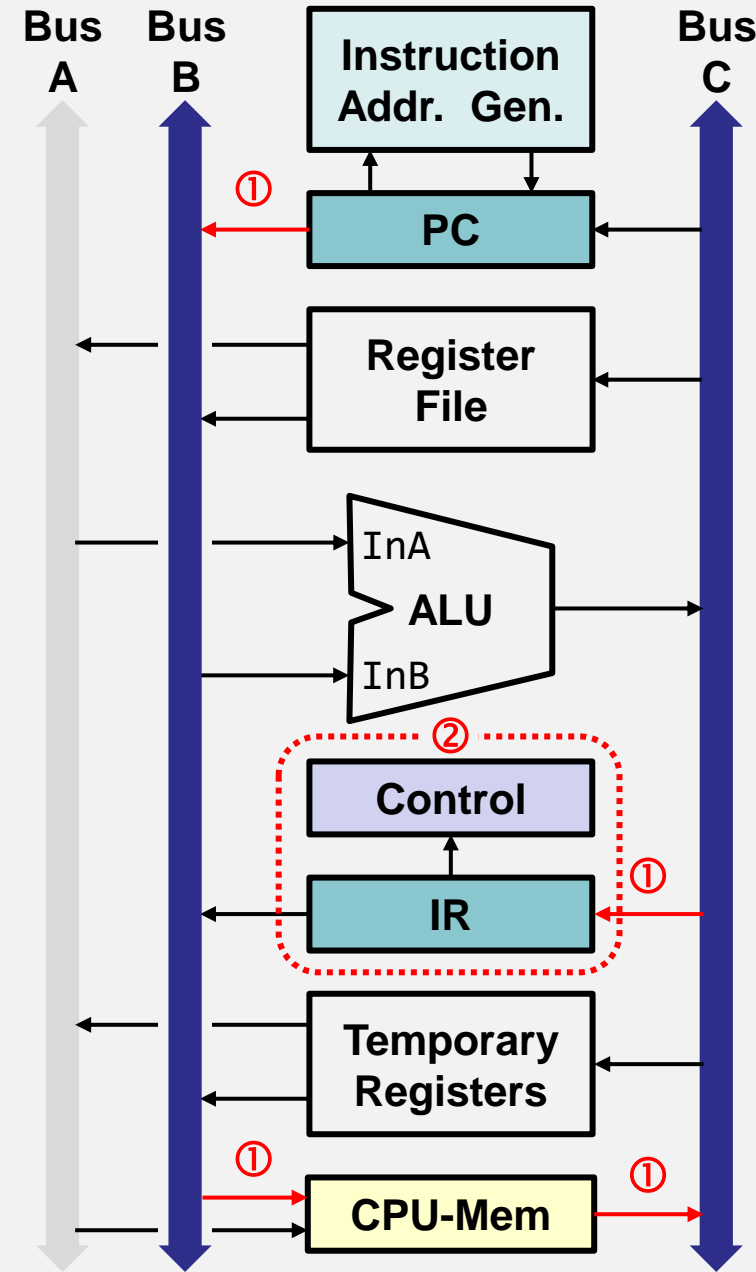- $[IR]$  is decoded by **Control Circuitry** to generate control signals (not shown).




# Ex 1: Add R5, R6



- ①  $MAR \leftarrow [PC]$ , Read memory, Wait\_MFC,  $IR \leftarrow [MDR]$ ,  $PC \leftarrow [PC] + 4$  (shown [here](#))
- ② Decode instruction (shown [here](#))
- ③  $R5 \leftarrow [R5] + [R6]$

- [R5] is read from Register File and transferred to InA of ALU via Bus A.
- [R6] is read from Register File and transferred to InB of ALU via Bus B.
- ALU is set to perform an Add.
- The sum is stored back into R5 via Bus C.

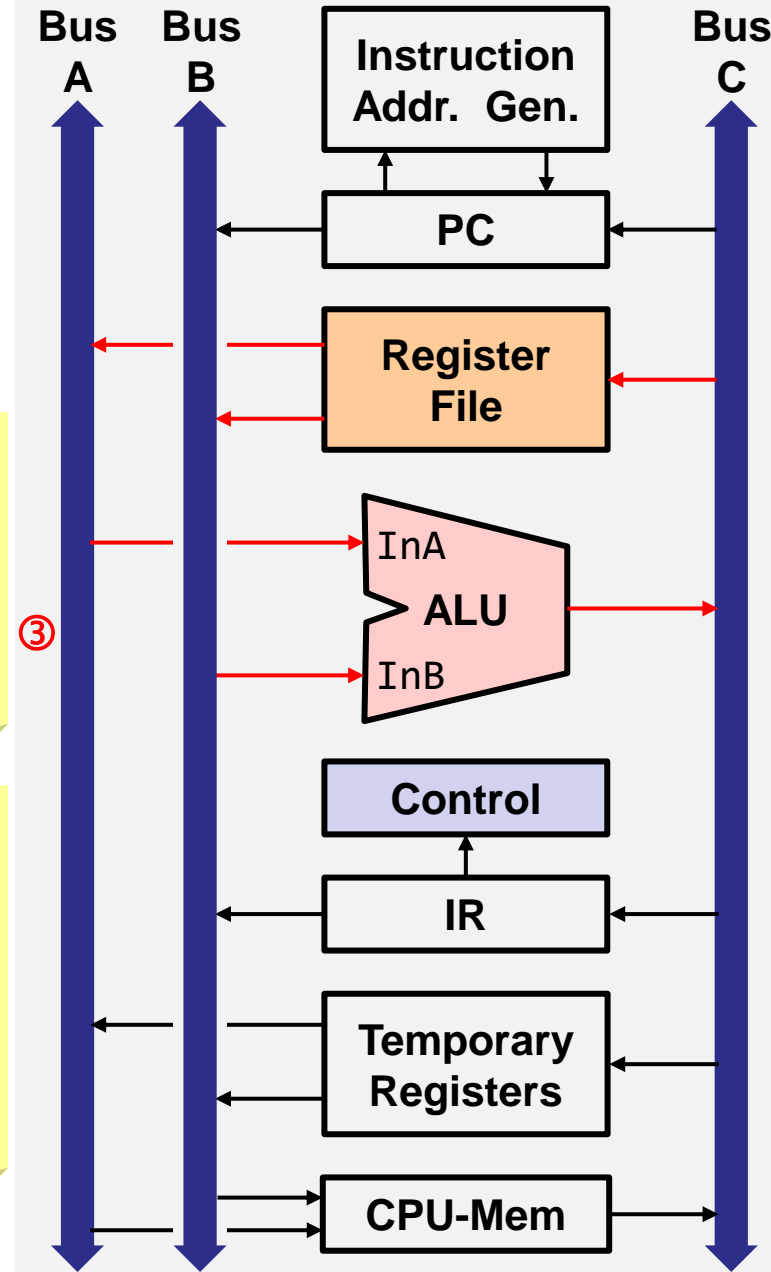
- Note 1: Reading source registers *cannot* proceed in parallel with the decoding, since CISC-style instructions do *not* always use the same fields to specify reg. addresses.
- Note 2: Control Circuitry must *carefully coordinate* how to read and write Register File within the same step.


 
# Ex 2: And X(R7), R9




- Assume the index offset is a 32-bit value given as the **second word** of the instruction.



- MAR  $\leftarrow$  [PC], Read memory, Wait\_MFC, IR  $\leftarrow$  [MDR], PC  $\leftarrow$  [PC] + 4 (shown [here](#))
- Decode instruction (shown [here](#))
- MAR  $\leftarrow$  [PC], Read memory, Wait\_MFC, Tmp1  $\leftarrow$  [MDR], PC  $\leftarrow$  [PC] + 4

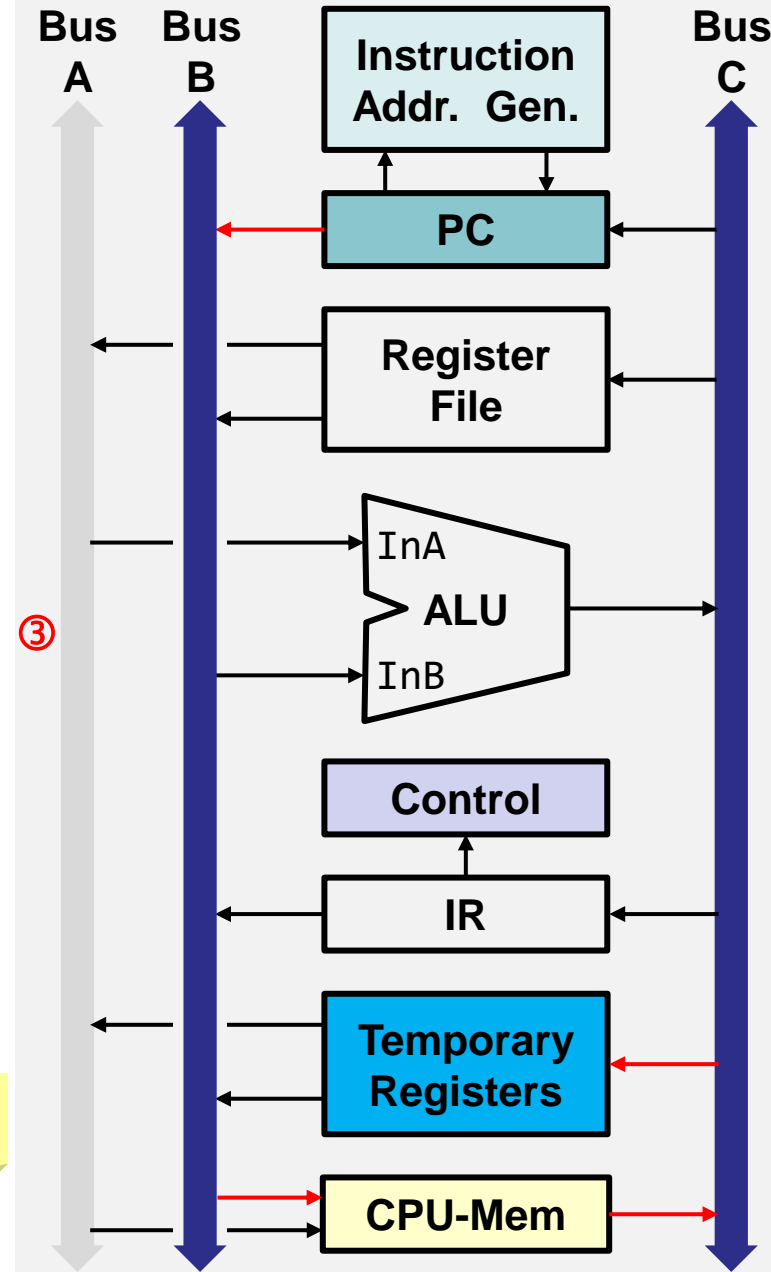
- The second word (i.e., X) is fetched from memory into the temporary register **Tmp1**.


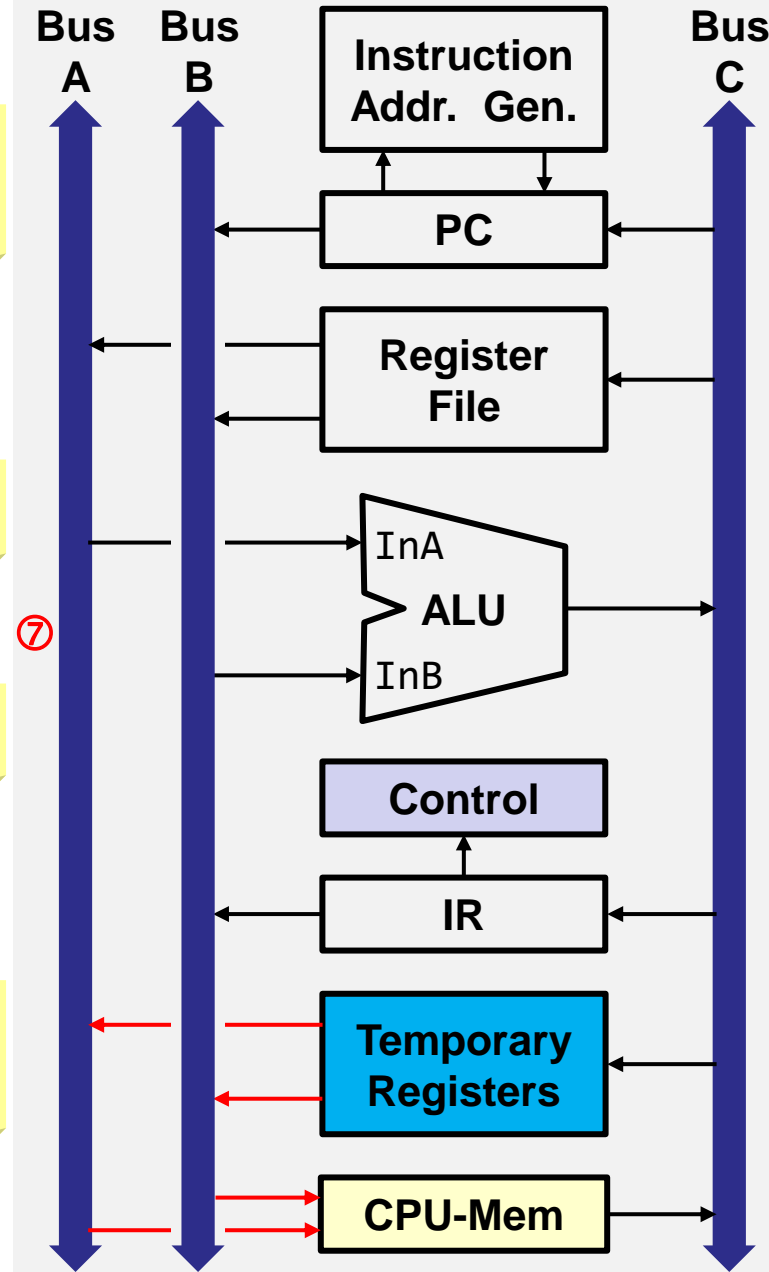
# Ex 2: And X(R7), R9 (Cont'd)



- ④  $\text{Tmp2} \leftarrow [\text{Tmp1}] + [\text{R7}]$ 
  - $[\text{Tmp1}]$  and  $[\text{R7}]$  are sent to ALU over Buses A and B, and the effective address is placed into the temporary register **Tmp2**.
- ⑤  $\text{MAR} \leftarrow [\text{Tmp2}]$ , Read memory, Wait\_MFC,  $\text{Tmp1} \leftarrow [\text{MDR}]$ 
  - The contents of memory address  $X(\text{R7})$  are read and placed into **Tmp1**.
- ⑥  $\text{Tmp1} \leftarrow [\text{Tmp1}] \text{ AND } [\text{R9}]$ 
  - The **AND** computation is performed, and the result is placed into **Tmp1**.
- ⑦  $\text{MAR} \leftarrow [\text{Tmp2}]$ ,  $\text{MDR} \leftarrow [\text{Tmp1}]$ , Write memory, Wait\_MFC
  - The result is stored into the memory at the address  $X(\text{R7})$ , which is “still” available in **Tmp2** since the completion of ④.



# Class Exercise 9.4



- Consider the three-bus implementation of a CISC-style processor design.
- How many times of memory accesses are involved in **Add R5, R6** and **And X(R7), R9**, respectively?





- Main Components of a Processor
- RISC-Style Processor Design
  - Five-Stage Organization
  - Instruction Execution
- CISC-Style Processor Design
  - Multi-Bus Interconnect
  - Instruction Execution
- **Control Signal Generation**
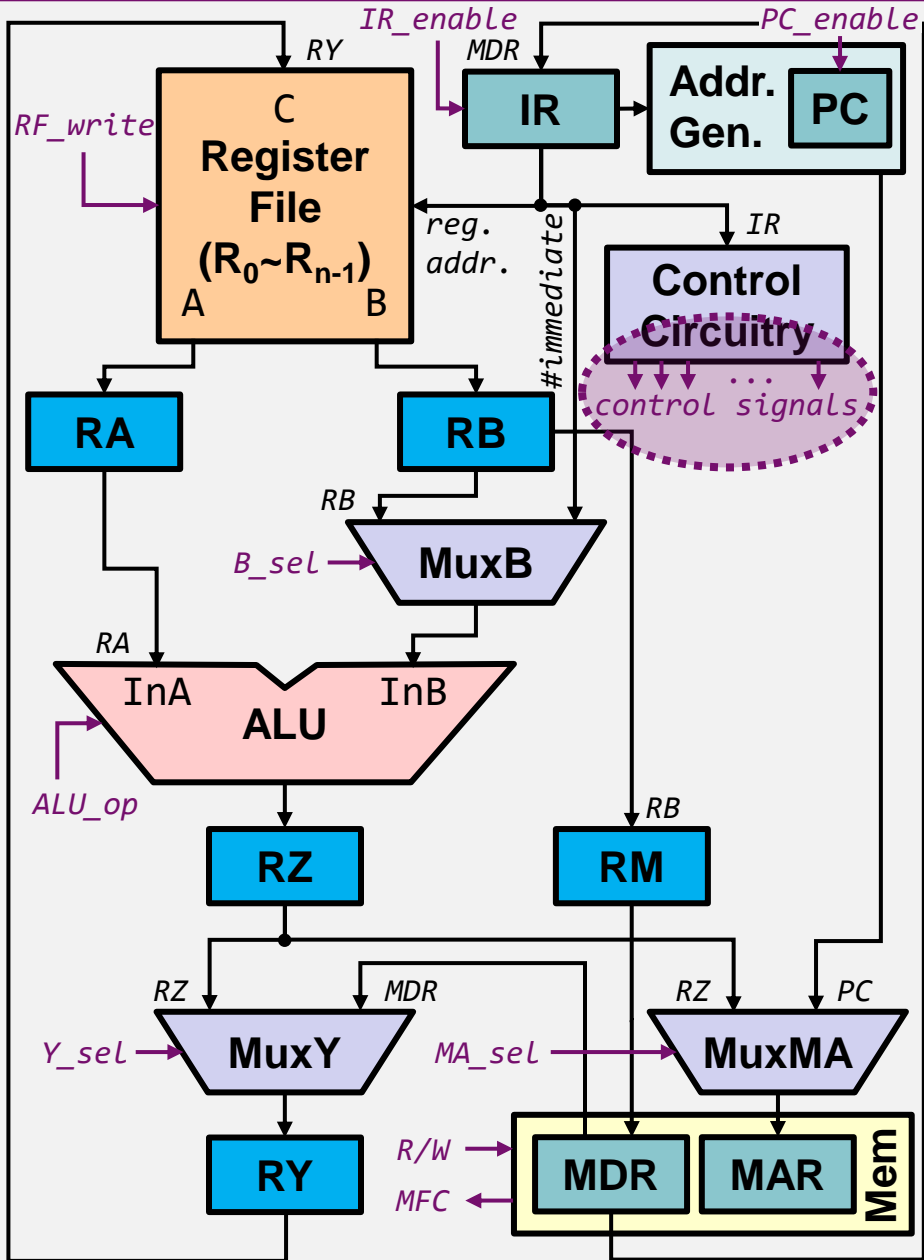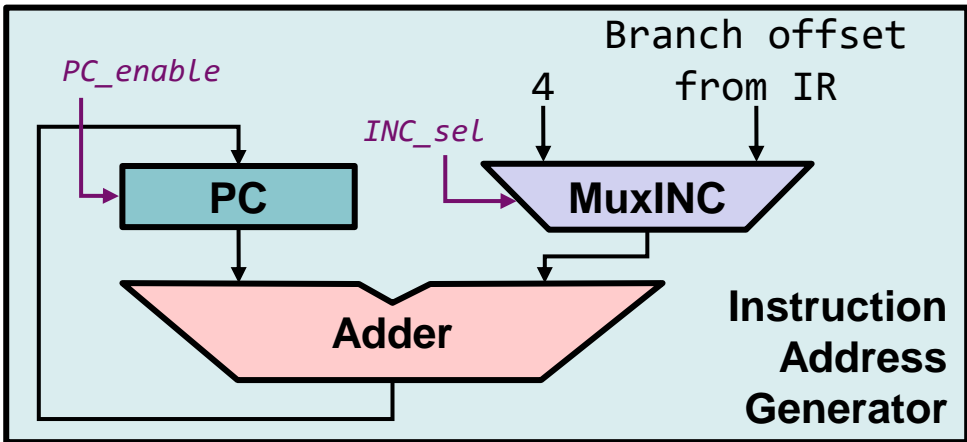
# Recall: Control Signals



- The processor's hardware is governed by **control signals** that determine:
  - What is the input data appearing at a **Multiplexer's** output?
  - What will be the operation performed by **ALU**?
  - Will the data be loaded into the selected **register**?
  - Etc.






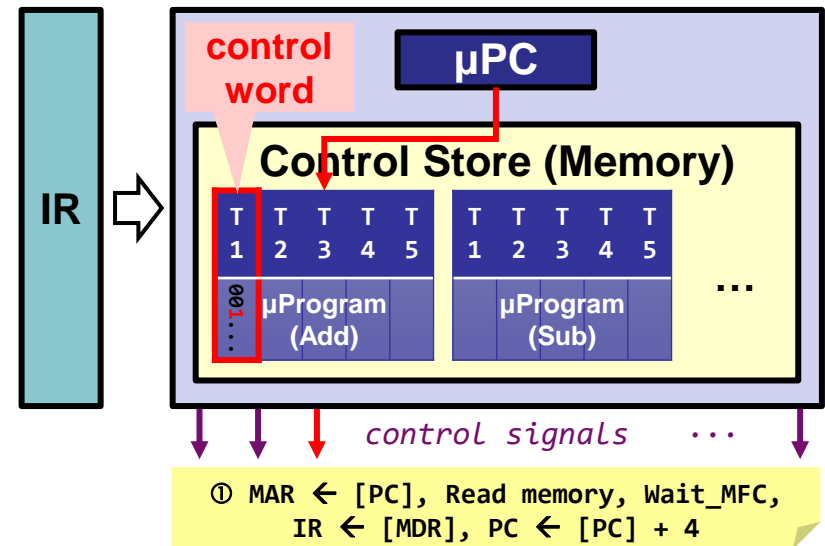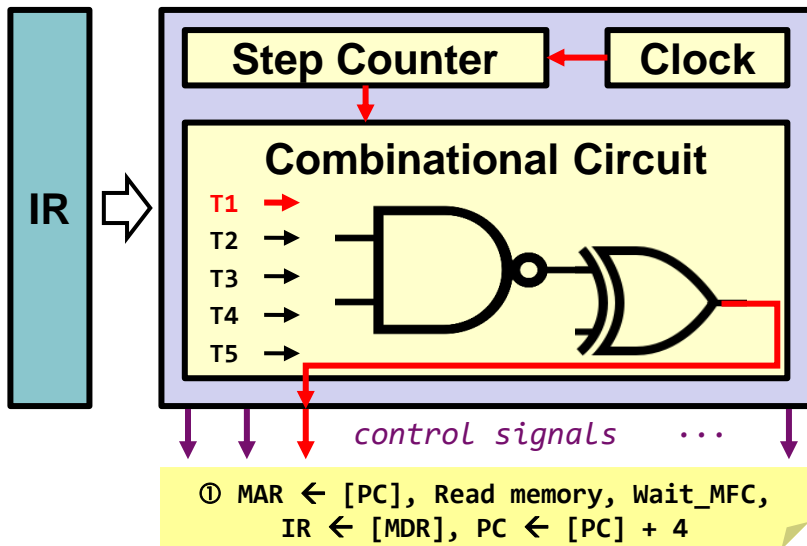
# Control Signal Generation



- There're two typical ways to generate control signals:
  - 1) Hardwired Control:**
    - The **combinational circuit** is used to “**hard code**” the generation of control signals with **logic gates**.
      - The **clock** and **counter** specify the current step (e.g., **T1**).
    - It is a “hardware approach” and can operate at **high speed**.
  - 2) Microprogrammed Control:**
    - Control signals are specified by “**micro-programs**” in **Control Store**.
      - The **micro-Program Counter** ( $\mu$ PC) always points to the next **control word** (or  **$\mu$ -instruction**).
    - It is a “software approach” and can support a **complex instruction set**.



- Main Components of a Processor
- RISC-Style Processor Design
  - Five-Stage Organization
  - Instruction Execution
- CISC-Style Processor Design
  - Multi-Bus Interconnect
  - Instruction Execution
- Control Signal Generation

