



香港中文大學

The Chinese University of Hong Kong

CENG3430 Rapid Prototyping of Digital Systems

Lecture 10:

VHDL versus Verilog

Ming-Chang YANG

mcyang@cse.cuhk.edu.hk




- VHDL & Verilog: Background & Design Concept
- VHDL vs. Verilog
 - Modeling Capacity
 - Syntax & Popularity
 - Overall Structure
 - I/O Declaration
 - Concurrent Statements
 - Sequential Statements
 - Non-blocking Assignment: Combinational Logic
 - Blocking Assignment: Sequential Logic
 - Structural Design
 - Design Constructions
 - Example: Flip-flop with Synchronous Reset

What are VHDL and Verilog?



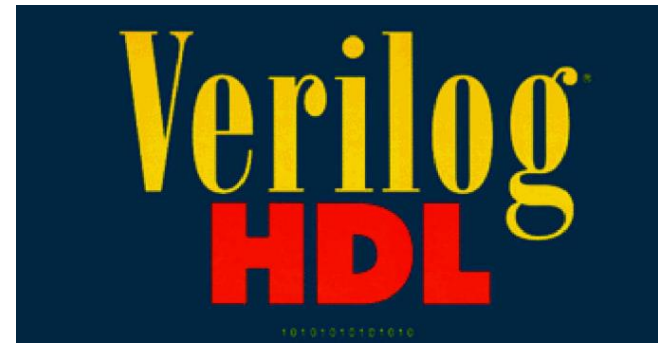VHDL
Very High Speed Integrated Circuit
Hardware Description Language



- They are both **hardware description languages** for **modeling hardware**.
- They are each a **notation** to describe the **behavioral** and **structural** aspects of an electronic digital circuit.

VHDL: Background



- **V**HSIC **H**ardware **D**escription **L**anguage
 - VHSIC: Very High Speed Integrated Circuit.
- Developed by the department of defense (1981)
 - In 1986 rights were given to IEEE.
 - Became a standard and published in 1987.
 - Revised standard we know now published in 1993 (VHDL 1076-1993) regulated by VHDL international (VI).

VHDL
Very High Speed Integrated Circuit
Hardware Description Language

VHDL: Design Concept



- VHDL uses **top-down approach** to partition design into small blocks (i.e., “**components**”)
 - **Entity**: Describe interface signals & basic building blocks
 - **Architecture**: Describe behavior, each entity can have multiple Architectures
 - ***Configuration**: Specify different architectures for a single entity
 - The internals can change while the interface remains the same.
 - It is not required to get a basic VHDL design running.
 - ***Package**: Contain user-defined subprograms, constant definitions, and/or type definitions to be used throughout one or more design units

**: optional*

Verilog: Background



- Developed by Gateway Design Automation (1980)
 - Later acquired by Cadence Design(1989) who made it public in 1990
 - Became a standardized in 1995 by IEEE (Std 1364) regulated by Open Verilog International (OVI)




Verilog: Design Concept




- Verilog only has one building block: **module**
 - There is only one module per file (.v) usually.
 - Modules connect through their **ports** (similarly as in VHDL).
 - A **top level module** invokes instances of other modules.
- Modules can be specified **behaviorally** or **structurally**.
 - **Behavioral**: Define behavior of digital system.
 - Similarly as the behavioral design (“**process**”) in VHDL
 - **Structural**: Define hierarchical interconnection of modules.
 - Similarly as the structural design (“**port map**”) in VHDL

Modeling Capacity

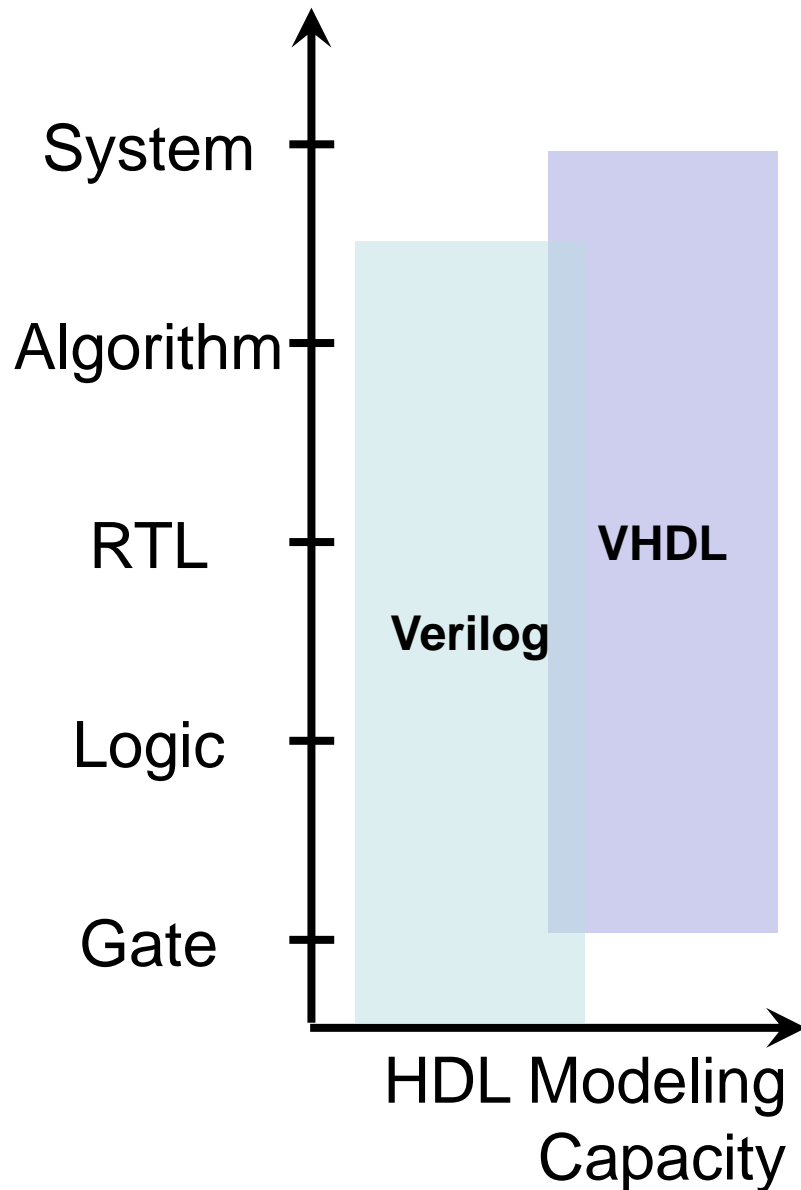

- High-Level: **VHDL** is better.
 - VHDL has more features for **high-level hardware modeling**.
 - Such as user-defined data types, package, configuration, library management.
- Low-Level: **Verilog** is better.
 - Verilog is originally created for modeling **logic gates**.
 - Verilog has built-in **primitives** or **low-level logic gates**.
 - Verilog supports **user-defined primitives (UDP)**.

IC Design Flow

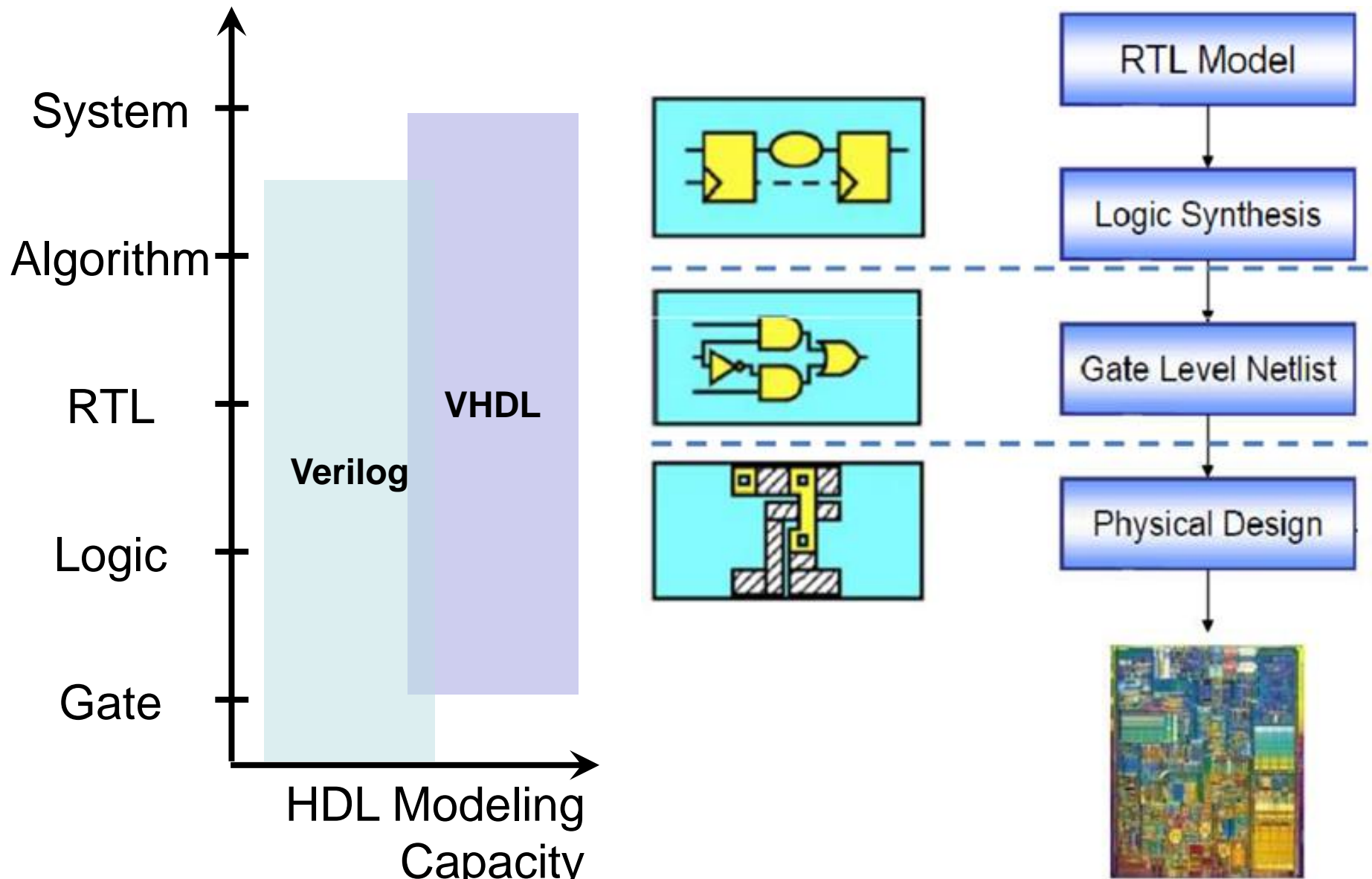



VHDL
Very High Speed Integrated Circuit
Hardware Description Language



Programming Style (Syntax)

VHDL is similar to **Ada** programming language.

Verilog is similar to **C/Pascal** programming language.

VHDL is **NOT** case-sensitive.

Verilog is **case-sensitive**.

VHDL is more “**verbose**” than **Verilog**.

Popularity

VHDL is more popular with **European** companies.

Verilog is more popular with **US** companies.

Overall Structure



VHDL

-- Library Declaration

```
library IEEE;
```

...

-- Entity Declaration

```
entity mux is
```

...

```
end mux
```

-- Architecture Body

```
architecture arch of mux is
```

```
begin
```

...

```
end arch;
```

Verilog

// One Module

```
module mux (a, b, s, y);
```

...

```
endmodule
```



VHDL

-- Library Declaration

...

-- Entity Declaration

entity mux is

```
port(a,b,s: in std_logic;  
      y: out std_logic);
```

end mux

-- Architecture Body

architecture arch of mux is

begin

...

end arch;

Verilog

// One Module

```
module mux (a, b, s, y);
```

```
input a,b,s;
```

```
output y;
```

...

```
endmodule
```

Concurrent Statement: **assign**



VHDL: *inside architecture body, outside the process*

```
signal a, b: std_logic_vector(7 downto 0);
```

```
signal c, d, e: std_logic;
```

```
a(3 downto 0) <= b(7 downto 4);
```

```
b <= "00001010";
```

```
c <= d and e;
```

Verilog: *outside the always block*

```
wire [7:0] a, b;
```

```
wire c, d, e;
```

```
assign a[3:0] = c[7:4];
```

```
assign a[7:4] = 'b0000; // binary
```

```
assign a = b & c; // logical AND
```

assign:

- Assignments outside an **always** block are concurrent.
- LHS must be **wire**.
- The LHS will be updated whenever RHS changes.


Class Exercise 10.1

Student ID: _____ Date: _____

Name: _____

- Translate the following VHDL program to Verilog:
 
```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity abc is
    port (a,b,c: in std_logic;
          y: out std_logic);
end abc;
architecture abc_arch of
abc is
signal x : std_logic;
begin
    x <= a nor b;
    y <= x and c;
end abc_arch;
```



Sequential Statement: = or <=



VHDL

```
architecture arch of ex is
begin
process (...)
begin
    -- LHS could be signals or
    variables
    -- signal assignment (<=)
    --          or
    -- variable assignment (:=)
end;
end arch;
```

Verilog

```
module ex (...);
reg a, b, c;
always @ (...)
begin
    // LHS must be reg (not wire)
    // blocking assignment (=)
    //   for combinational logic
    //          or
    // non-blocking assignment
    //   (<=) for sequential logic
end
endmodule
```

Blocking Assignment: Combinational Logic

- **Blocking Assignment (=):** *Executed before the execution of the statements in a sequential block (e.g., always block).*
 - A **blocking assignment (=)** will evaluate the RHS and perform the LHS assignment immediately.
 - The second assignment is performed, once the first one is complete.
 - The assignments are executed in a **sequential** way.
- **Usage:** Use **blocking assignment (=)** for always blocks that are purely **combinational logic**.

```
reg t1, t2, t3;
always @ (a or b) begin
    t1 = a & b; // logical AND
    t2 = c | d; // logical OR
    t3 = t1 | t2;
end
```


Non-blocking Assignment: Sequential Logic

- **Non-blocking Assignment (\leftarrow):** *Schedule assignments without blocking the procedural flow.*
 - A **non-blocking assignment (\leftarrow)** samples RHS at the beginning of a clock edge; with the actual LHS assignment taking place at the end of that clock edge.
- **Usage:** Use **non-blocking assignments (\leftarrow)** in always blocks to synthesize/simulate **sequential logic**.

```
reg y1, y2;
```


```
always @(posedge clk)
```

```
begin
```

```
    y1  $\leftarrow$  a;
```

```
    y2  $\leftarrow$  y1;
```

```
end
```

 

“wire” vs. “reg” in Verilog




- **Wire:** Has no memory
 - Physical wire in the circuit
 - A wire does not store its value, it must be driven by
 - Connecting the wire to the output of a gate or module, or
 - Assigning a value to the wire in a concurrent assignment
 - **Usage:** Cannot use “**wire**” in left-hand-side of assignments in always blocks.
- **Register:** Has memory
 - Not “register” of CPU
 - Could be a flip-flop (DFF) or a physical wire
 - Holding value until a new value is assigned
 - **Usage:** Cannot use “**reg**” in left-hand side of assignments outside always blocks (i.e., concurrent assignment)

Structural Design in VHDL (1/2)



 - **Structural Design in VHDL:** Like a circuit but describe it by text.



Connected by **port map** in architecture body

- **Design Steps:**
 - Step 1: Create **entities**
 - Step 2: Create **components** from **entities**
 - Step 3: Use “**port map**” to relate the components

Structural Design in VHDL (2/2)



```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity and2 is Step 1
4 port (a,b: in STD_LOGIC;
5       c: out STD_LOGIC );
6 end and2;
7 architecture and2_arch of and2 is
8 begin
9     c <= a and b;
10 end and2_arch;
```

```
11 -----
12 library IEEE;
13 use IEEE.STD_LOGIC_1164.ALL;
14 entity or2 is Step 1
15 port (a,b: in STD_LOGIC;
16       c: out STD_LOGIC );
17 end or2;
18 architecture or2_arch of or2 is
19 begin
20     c <= a or b;
21 end or2_arch;
```

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 -----
4 entity test is
5 port ( in1: in STD_LOGIC; in2: in STD_LOGIC;
6       in3: in STD_LOGIC;
7       out1: out STD_LOGIC );
8 end test;
9 architecture test_arch of test is
```

```
10 component and2 --create component Step 2
11   port (a,b: in std_logic; c: out std_logic);
12 end component ;
13 component or2 --create component
14   port (a,b: in std_logic; c: out std_logic);
15 end component ;
```


```
16 signal inter_sig: std_logic;
17 begin Step 3
18     label1: and2 port map (in1, in2, inter_sig);
19     label2: or2 port map (inter_sig, in3, out1);
20 end test_arch;
```



Structural Design in Verilog (1/2)



 - **Structural Design in Verilog:** One top module, several (sub) modules.



Connected by relating **I/O** and **internal** wires

- **Design Steps:**
 - Step 1: Create (sub) **module (s)** (usually in separate **.v** files)
 - Step 2: Define a **top-module** to interconnect **module (s)**

Structural Design in Verilog (2/2)



and2.v

```
module and2( Step 1
  input a,
  input b,
  output c
);
assign c = a && b;
endmodule
```

or2.v

```
module or2( Step 1
  input a,
  input b,
  output c
);
assign c = a || b;
endmodule
```

top_module.v

```
module top_module( Step 2
  input in1, input in2, input in3,
  output out1 );
  wire inter_sig;
  and2 and2_ins(
    .a(in1),
    .b(in2),
    .c(inter_sig)
  );
  or2 or2_ins(
    .a(inter_sig),
    .b(in3),
    .c(out1)
  );
endmodule
```




Class Exercise 10.2

Student ID: _____ Date: _____

Name: _____

 - Implement the following circuit in Verilog:



Design Constructions (1/4)



VHDL: when-else (*concurrent, outside process*)

```
architecture arch of ex is
```

```
begin
```

```
    out1 <= '1' when in1 = '1' and in2 = '1' else '0';
```

```
end arch ex_arch;
```

Verilog: assign ? : (*concurrent, outside always @ block*)

```
module ex (...);
```

```
    assign out1 = (in1=='b1 && in2=='b1) ? 'b1 : 'b0;
```

```
    // 'b: binary; 'o: octal; 'd: decimal; 'h: hexadecimal
```

```
endmodule
```


Design Constructions (2/4)



VHDL: **if-then-else**

(sequential, inside process)

```
process(in1, in2)
begin
    if in1='1' and in2='1'
    then
        out1 <= '1';
    else
        out1 <= '0';
    end if;
end process;
```

Verilog: **if-else**

(sequential, inside always@)

```
always @(in1, in2)
begin
    if (in1=='b1 && in2=='b1)
    begin
        out1 = 'b1;
    end
    else
    begin
        out1 = 'b0;
    end
end
```

Design Constructions (3/4)



VHDL: **case-when**

(sequential, inside process)

```
process (b)
```

```
begin
```

```
  case b is
```

```
    when "00"|"11" =>
```

```
      out1 <= '0';
```

```
      out2 <= '1';
```

```
    when others      =>
```

```
      out1 <= '1';
```

```
      out2 <= '0';
```

```
  end case;
```

```
end process;
```

CENG3430 Lec10: VHDL versus Verilog

Verilog: **case**

(sequential, inside always @)

```
always @ (b)
```

```
begin
```

```
  case (b)
```

```
    'b00 || 'b11:
```

```
      out1 = 'b0;
```

```
      out2 = 'b1;
```

```
  default:
```


```
    out1 = 'b1;
```

```
    out2 = 'b0;
```

```
  endcase
```

```
end
```

Design Constructions (4/4)

 

VHDL: **for-in-to-loop**

(sequential, inside process)

```
process (in1)
begin
    for i in 0 to 3 loop
        out1(i) <= not in1(i);
    end loop;
end process;
```

Verilog: **for-loop**

(sequential, inside always @)

```
always @(in1)
begin
    for(idx=0; idx<4; idx+=1)
        begin
            out1[idx] = ~in1[idx];
        end
end
```

Example: Flip-flop with Sync. Reset



VHDL

```
entity dff is
port (D,CLK,RESET:
      in std_logic;
      Q: out std_logic);
end dff;
architecture dff_arch of
dff is begin
  process(CLK) begin
    if rising_edge(CLK) then
      if (RESET = '1') then
        Q <= '0';
      else
        Q <= D;
      end if;
    end if;
  end process;
end dff_arch;
```

Verilog

```
module dff(
  input D,
  input CLK,
  input RESET,
  output reg Q); // why?
always @(posedge CLK)
begin
  if (RESET) begin
    Q <= 1'b0; // non-blocking
  end
  else begin
    Q <= D; // non-blocking
  end
end
end
endmodule
```

```
always @(...)
begin
  // LHS must be reg (not wire)
```

Example: Flip-flop with Async. Reset



VHDL

```
entity dff is
port (D,CLK,RESET:
      in std_logic;
      Q: out std_logic);
end dff;
architecture dff_arch of
dff is begin
  process (CLK) begin
    if rising_edge(CLK) then
      if (RESET = '1') then
        Q <= '0';
      else
        Q <= D;
      end if;
    end if;
  end process;
end dff_arch;
```

Verilog

```
module dff(
  input D,
  input CLK,
  input RESET,
  output reg Q); // why?
  always @(posedge CLK or
          posedge RESET)
  begin
    if (RESET) begin
      Q <= 1'b0; // non-blocking
    end
    else begin
      Q <= D; // non-blocking
    end
  end
end
endmodule
```

```
always @(...)
begin
  // LHS must be reg (not wire)
```



- VHDL & Verilog: Background & Design Concept
- VHDL vs. Verilog
 - Modeling Capacity
 - Syntax & Popularity
 - Overall Structure
 - I/O Declaration
 - Concurrent Statements
 - Sequential Statements
 - Non-blocking Assignment: Combinational Logic
 - Blocking Assignment: Sequential Logic
 - Structural Design
 - Design Constructions
 - Example: Flip-flop with Synchronous Reset