

# CENG4480 Homework 1

**Due:** Oct. 25, 2017

- **Small-Signal Gain:** For given amp circuits, small changes of input  $\Delta V_{in}$  will cause output change of  $\Delta V_{out}$ . Small-signal gain is defined by  $\frac{\Delta V_{out}}{\Delta V_{in}}$ .

**Q1** (10%) Show that the circuit of Fig. 1 is a non-inverting summer. Assume the op-amp is ideal.

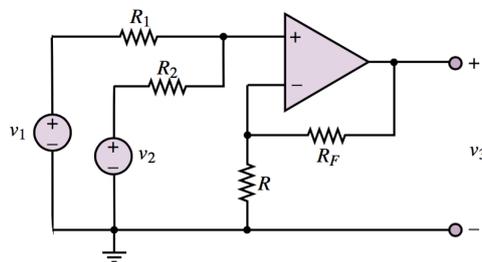


Figure 1: Non-inverting Summer

**Q2** (10%) In the circuit of Fig. 2,  $R_1 = R_2 = R' = R_f = R = 100\text{k}\Omega$  and  $C = 1\mu\text{F}$ . Assume the op-amps are ideal.

- The relationship between  $U_i$  and  $U_o$  ( $U_{o1}$  is unknown).
- Assume that when the time  $t = 0$ ,  $U_o = 0\text{V}$  and  $U_i$  jumps from  $0\text{V}$  to  $-1\text{V}$ . How long will the  $U_o$  take to change from  $0\text{V}$  to  $6\text{V}$ ?

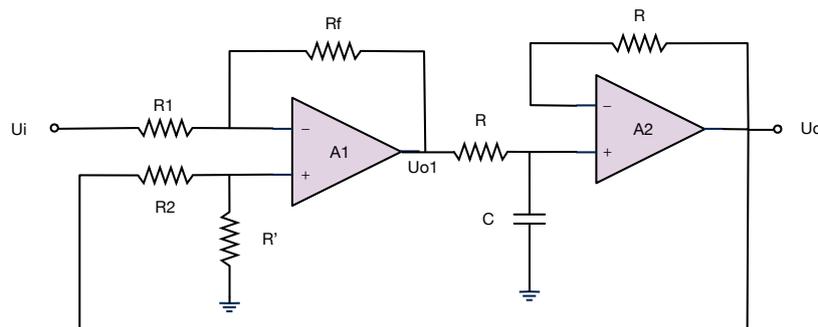


Figure 2: Voltage Follower

**Q3** (10%) Try to analyze the relationship between  $U_i$  and  $U_o$  in the circuit of Fig. 3.  $R_1 = R_2 = R_3 = R_5 = 50\text{k}\Omega$ ,  $R_4 = 25\text{k}\Omega$  and  $C = 10\mu\text{F}$ . Assume the op-amps are ideal.

**Q4** (15%) In the circuit of Fig. 4, assume that  $U_{i1} = 4U_{i2} = 4\text{V}$ ,  $R_1 = 50\text{k}\Omega$  and  $C = 1\mu\text{F}$ . The op-amps are ideal.

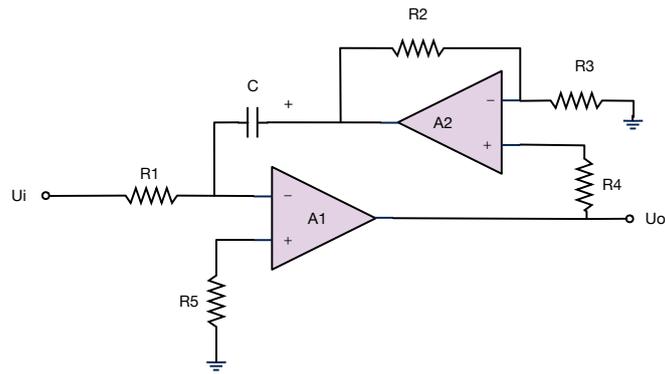


Figure 3

- Calculate  $U_A, U_B, U_C, U_D$  and  $U_o$ , when the switch  $S$  is closed.
- Assume that when the time  $t = 0$ , switch  $S$  is open. How long will the  $U_o$  take to become  $0V$ ?

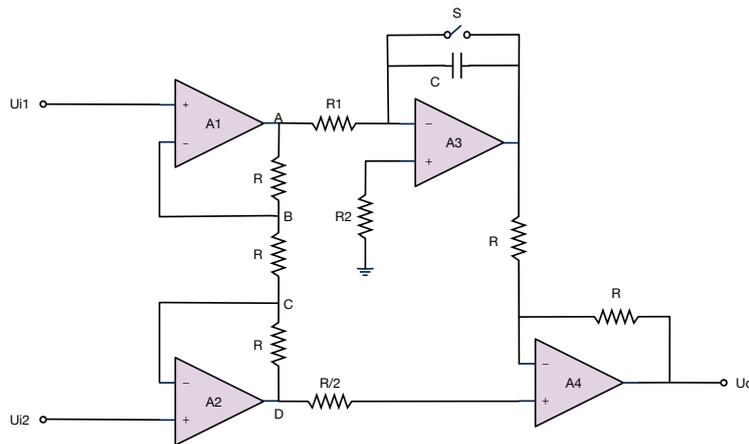


Figure 4

**Q5** (10%) Let us consider the Schmitt Trigger shown in Fig. 5

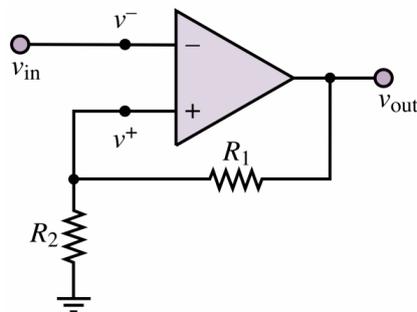


Figure 5: Schmitt Trigger

- (5%) Due to the manufacturing defects, a parasitic resistor  $R_3$  occurs between the output node and ground, calculate the reference voltages.

2. (5%) If the parasitic device is a capacitor  $C$ , sketch  $v_{out}$  versus  $v_{in}$ . Label the key coordinates on the curve.

**Q6** (10%) Prove that current is split into two equal parts for  $R - 2R$  DAC.

**Q7** (10%) Compute and sketch the output voltage of the op. amp in Fig. 6. Given  $R_S = 1\text{k}\Omega$ ,  $R_F = 10\text{k}\Omega$ ,  $R_L = 1\text{k}\Omega$ ,  $V_S^+ = 15\text{V}$ ,  $V_S^- = -15\text{V}$ ,  $v_s(t) = 2\sin(1000t)$ . Repeat the problem if  $V_S^+ = 20\text{V}$  and  $V_S^- = -20\text{V}$ .

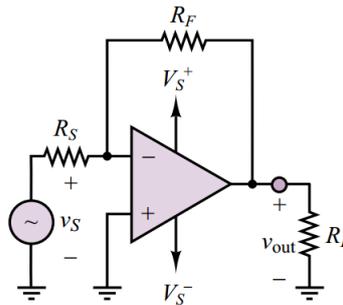


Figure 6: Inverting Amplifier

- Q8** (10%) What is the minimum number of bits required to digitize an analog signal with a resolution of 1%, 10%, 20%, respectively. (**Resolution:** Ratio between minimum voltage that can be sensed and the input voltage range.)
- Q9** (15%) Metal-Oxide-Semiconductor-Field-Effect-Transistor (MOSFET) is the core component of a variety of amplifiers. Fig. 7 shows a common source amplifier circuit with N-type MOS (M1). Typically, when M1 works as amplifier, drain current  $I_D$  has the following relationship with bias voltage  $V_{in}$ :

$$I_D = k(V_{in} - V_{th})^2, \quad (1)$$

where  $k$  is positive and related to material properties of MOSFET and  $V_{th}$  is threshold voltage to turn the device on. Calculate small-signal gain of common source amplifier and show that this amplifier is an inverting amplifier.

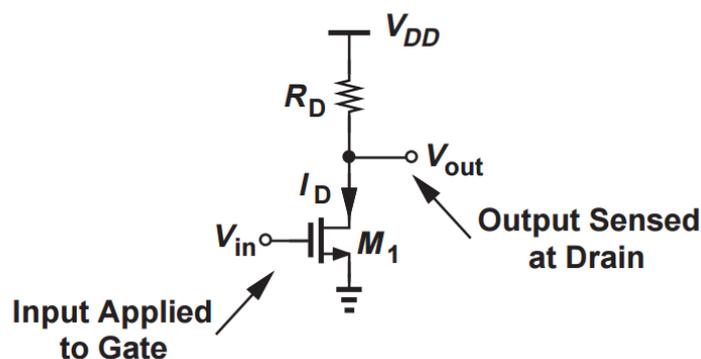


Figure 7: Common Source Amplifier