
CENG 3420

Lecture 05: Arithmetic and Logic Unit

Bei Yu

byu@cse.cuhk.edu.hk



香港中文大學

The Chinese University of Hong Kong


Outline

- ❑ 1. Overview
- ❑ 2. Addition
- ❑ 3. Multiplication & Division
- ❑ 4. Shift
- ❑ 5. Floating Point Number

Outline


- 1. Overview
- 2. Addition
- 3. Multiplication & Division
- 4. Shift
- 5. Floating Point Number

Abstract Implementation View

 


Arithmetic

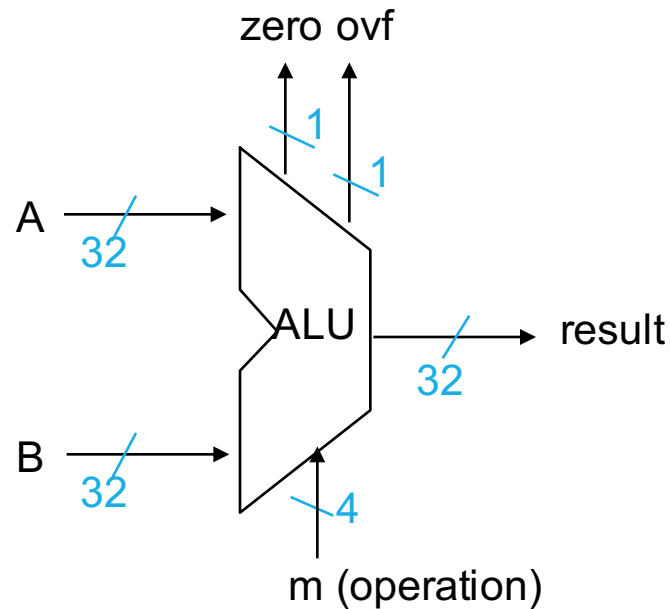- ❑ Where we've been
 - Abstractions
 - Instruction Set Architecture (ISA)
 - Assembly and machine language
- ❑ What's up ahead
 - Implementing the ALU architecture



Review: VHDL

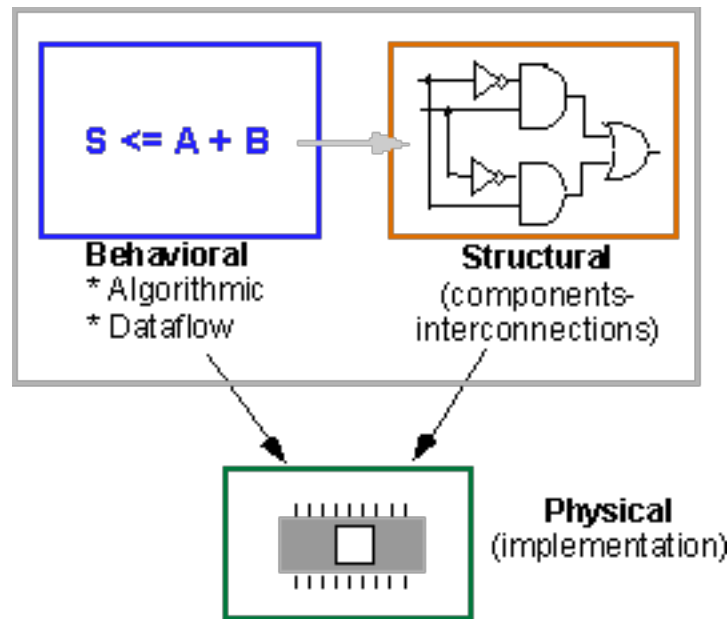
- ❑ Supports design, documentation, simulation & verification, and synthesis of hardware
- ❑ Allows integrated design at **behavioral** & **structural** levels



Review: VHDL

□ Basic structure

 - Design **entity-architecture** descriptions
- Time-based execution (discrete event simulation) model



Review: Entity-Architecture Features

- **Entity** defines externally visible characteristics
 - Ports: channels of communication
 - **signal** names for inputs, outputs, clocks, control
 - Generic parameters: define class of components
 - timing characteristics, size (fan-in), fan-out
- **Architecture** defines the internal behavior or structure of the circuit
 - Declaration of internal **signals**
 - Description of behavior
 - collection of **Concurrent Signal Assignment** (CSA) statements (indicated by `<=`); can also model temporal behavior with the **delay** annotation
 - one or more processes containing CSAs and (sequential) variable assignment statements (indicated by `:=`)
 - Description of structure
 - interconnections of components; underlying behavioral models of each component must be specified

ALU VHDL Representation

```
entity ALU is
  port(A, B:  in std_logic_vector (31 downto 0);
        m:  in std_logic_vector (3 downto 0);
        result: out std_logic_vector (31 downto 0);
        zero: out std_logic;
        ovf: out std_logic)
end ALU;

architecture process_behavior of ALU is
  . . .
begin
  ALU: process (A, B, m)
  begin
    . . .
    result := A + B;
    . . .
  end process ALU;
end process_behavior;
```

Machine Number Representation

- ❑ Bits are just bits (have no inherent meaning)
 - conventions define the relationships between bits and numbers
- ❑ Binary numbers (base 2) - integers
 - 0000 -> 0001 -> 0010 -> 0011 -> 0100 -> 0101 -> ...
 - in decimal from 0 to 2^n-1 for n bits
- ❑ Of course, it gets more complicated
 - storage locations (e.g., register file words) are **finite**, so have to worry about **overflow** (i.e., when the number is too big to fit into 32 bits)
 - have to be able to represent **negative** numbers, e.g., how do we specify -8 in
 - `addi $sp, $sp, -8` `#$sp = $sp - 8`
 - in real systems have to provide for more than just integers, e.g., fractions and real numbers (and **floating point**) and alphanumeric (characters)

MIPS Representations

□ 32-bit signed numbers (2's complement):

0000	0000	0000	0000	0000	0000	0000	0000	$_{two} = 0_{ten}$
0000	0000	0000	0000	0000	0000	0000	0001	$_{two} = + 1_{ten}$
0000	0000	0000	0000	0000	0000	0000	0010	$_{two} = + 2_{ten}$
...								
0111	1111	1111	1111	1111	1111	1111	1110	$_{two} = + 2,147,483,646_{ten}$
0111	1111	1111	1111	1111	1111	1111	1111	$_{two} = + 2,147,483,647_{ten}$
1000	0000	0000	0000	0000	0000	0000	0000	$_{two} = - 2,147,483,648_{ten}$
1000	0000	0000	0000	0000	0000	0000	0001	$_{two} = - 2,147,483,647_{ten}$
1000	0000	0000	0000	0000	0000	0000	0010	$_{two} = - 2,147,483,646_{ten}$
...								
1111	1111	1111	1111	1111	1111	1111	1101	$_{two} = - 3_{ten}$
1111	1111	1111	1111	1111	1111	1111	1110	$_{two} = - 2_{ten}$
1111	1111	1111	1111	1111	1111	1111	1111	$_{two} = - 1_{ten}$

maxint

minint

□ What if the bit string represented addresses?

- need operations that also deal with only positive (unsigned) integers

Two's Complement Operations

- ❑ Negating a two's complement number –
complement all the bits and then **add** a 1
 - remember: “negate” and “invert” are quite different!

- ❑ Converting n-bit numbers into numbers with more than n bits:
 - MIPS 16-bit immediate gets converted to 32 bits for arithmetic
 - **sign extend** - copy the most significant bit (the sign bit) into the other bits
 - 0010 -> 0000 0010
 - 1010 -> 1111 1010

 - sign extension versus zero extend (lb vs. lbu)

Design the MIPS Arithmetic Logic Unit (ALU)

- Must support the Arithmetic/Logic operations of the ISA

add, addi, addiu, addu


sub, subu

mult, multu, div, divu

sqrt

and, andi, nor, or, ori, xor, xori


beq, bne, slt, slti, sltiu, sltu

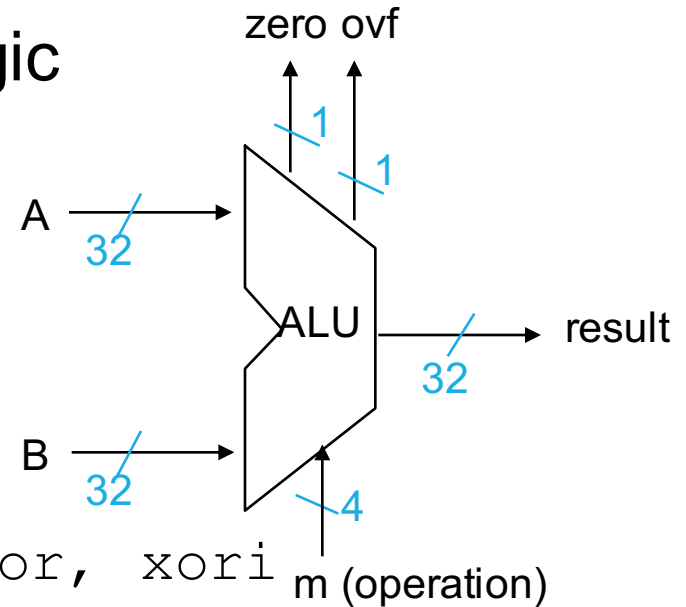

- With special handling for

- sign extend – addi, addiu, slti, sltiu
- zero extend – andi, ori, xori
- Overflow detected – add, addi, sub

MIPS Arithmetic and Logic Instructions

 


Type	op	funct
ADDI	001000	xx
ADDIU	001001	xx
SLTI	001010	xx
SLTIU	001011	xx
ANDI	001100	xx
ORI	001101	xx
XORI	001110	xx
LUI	001111	xx

Type	op	funct
ADD	000000	100000
ADDU	000000	100001
SUB	000000	100010
SUBU	000000	100011
AND	000000	100100
OR	000000	100101
XOR	000000	100110
NOR	000000	100111

Type	op	funct
	000000	101000
	000000	101001
SLT	000000	101010
SLTU	000000	101011
	000000	101100

Design Trick: Divide & Conquer

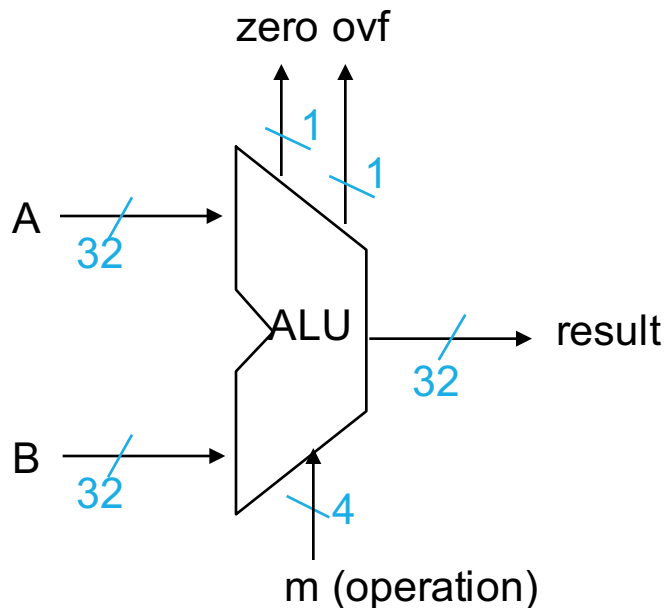- Break the problem into simpler problems, solve them and glue together the solution
- Example: assume the immediates have been taken care of before the ALU
 - now down to 10 operations
 - can encode in 4 bits



0	add
1	addu
2	sub
3	subu
4	and
5	or
6	xor
7	nor
a	slt
b	sltu

Outline

- 1. Overview
- 2. Addition
- 3. Multiplication & Division
- 4. Shift
- 5. Floating Point Number

Addition & Subtraction

- Just like in grade school (carry/borrow 1s)

$$\begin{array}{r} 0111 \\ + 0110 \\ \hline 1101 \end{array}$$

$$\begin{array}{r} 0111 \\ - 0110 \\ \hline 0001 \end{array}$$

$$\begin{array}{r} 0110 \\ - 0101 \\ \hline 0001 \end{array}$$

- Two's complement operations are easy
 - do subtraction by negating and then adding


$$\begin{array}{r} 0111 \\ - 0110 \\ \hline 0001 \end{array} \quad \rightarrow \quad \begin{array}{r} 0111 \\ + 1010 \\ \hline 1\ 0001 \end{array}$$

- Overflow (result too large for **finite** computer word)

- e.g., adding two n-bit numbers does not yield an n-bit number

$$\begin{array}{r} 0111 \\ + 0001 \\ \hline 1000 \end{array}$$

Building a 1-bit Binary Adder

 

A	B	carry_in	carry_out	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \text{ xor } B \text{ xor } \text{carry_in}$$

$$\text{carry_out} = A \& B \mid A \& \text{carry_in} \mid B \& \text{carry_in}$$

(majority function)

- ❑ How can we use it to build a 32-bit adder?
- ❑ How can we modify it easily to build an adder/subtractor?

Building 32-bit Adder

 


- Just connect the carry-out of the least significant bit FA to the carry-in of the next least significant bit and connect . . .

- Ripple Carry Adder (RCA)


- advantage: simple logic, so small (low cost)
- disadvantage: slow and lots of **glitching** (so lots of energy consumption)

Glitch

 - ❑ Glitch: **invalid** and **unpredicted** output that can be read by the next stage and result in a wrong action
- ❑ **Example:** Draw the propagation delay




Glitch in RCA

 

A	B	carry_in	carry_out	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

But What about Performance?

 - ❑ Critical path of n-bit ripple-carry adder is $n \cdot CP$




- ❑ Design trick – throw hardware at it (Carry Lookahead)



A 32-bit Ripple Carry Adder/Subtractor

Remember 2's complement is just

- complement all the bits

 

- add a 1 in the least significant bit

  

Minimal Implementation of a Full Adder

- Gate library: inverters, 2-input nands, or-and-inverters

architecture `concurrent_behavior` of `full_adder` is

```
    signal t1, t2, t3, t4, t5: std_logic;
```

```
begin
```

```
    t1 <= not A after 1 ns;
```

```
    t2 <= not cin after 1 ns;
```

```
    t4 <= not((A or cin) and B) after 2 ns;
```

```
    t3 <= not((t1 or t2) and (A or cin)) after 2 ns;
```

```
    t5 <= t3 nand B after 2 ns;
```

```
    S <= not((B or t3) and t5) after 2 ns;
```

```
    cout <= not((t1 or t2) and t4) after 2 ns;
```


```
end concurrent_behavior;
```

- [Optional] Can you create the equivalent schematic?
Can you determine worst case delay (the worst case timing path through the circuit)?


Tailoring the ALU to the MIPS ISA

- ❑ Also need to support the logic operations (`and`, `nor`, `or`, `xor`)
 - Bit wise operations (no carry operation involved)
 - Need a logic gate for each function and a mux to choose the output
- ❑ Also need to support the set-on-less-than instruction (`slt`)
 - Uses subtraction to determine if $(a - b) < 0$ (implies $a < b$)
- ❑ Also need to support test for equality (`bne`, `beq`)
 - Again use subtraction: $(a - b) = 0$ implies $a = b$
- ❑ Also need to add overflow detection hardware
 - overflow detection enabled only for `add`, `addi`, `sub`
- ❑ immediates are sign extended outside the ALU with wiring (i.e., no logic needed)

A Simple ALU Cell with Logic Op Support

 


Modifying the ALU Cell for s1t

 



Modifying the ALU for slt

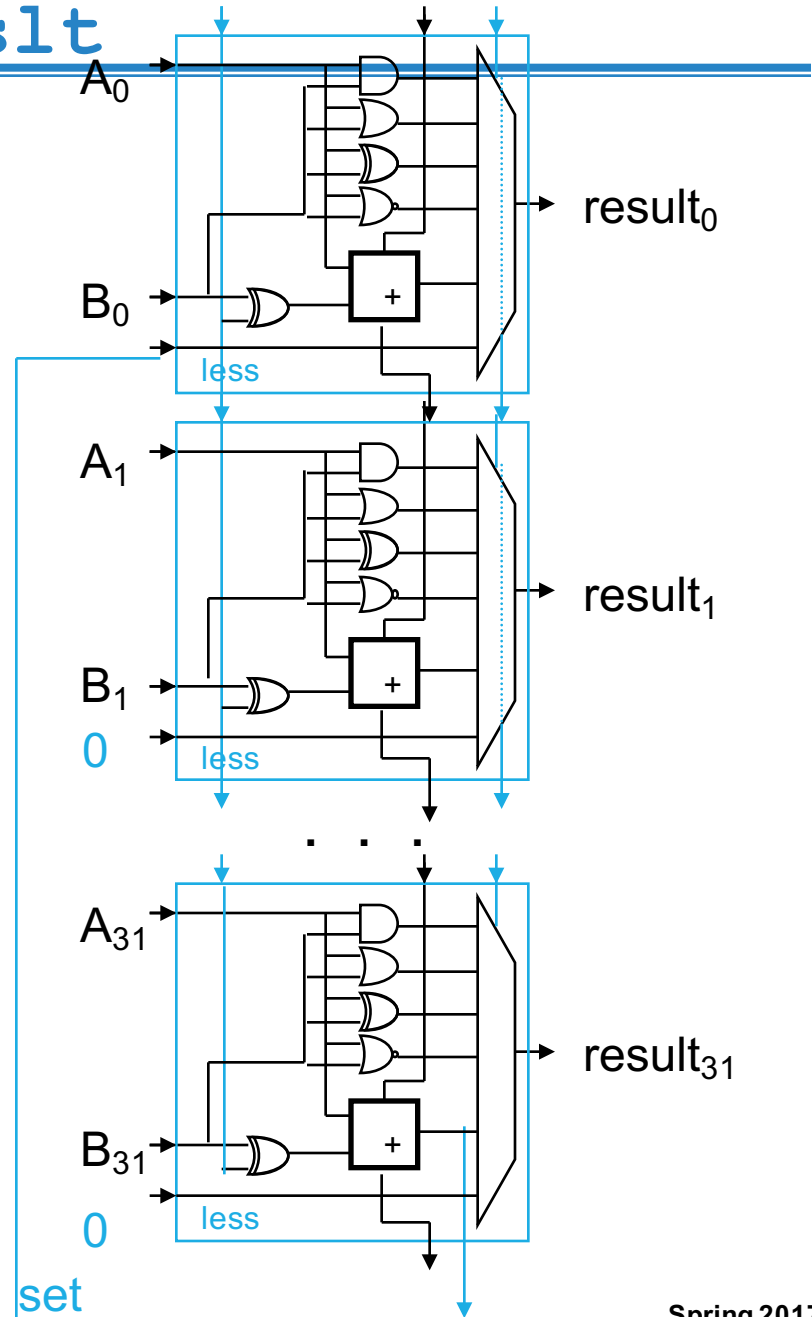- ❑ First perform a subtraction
- ❑ Make the result 1 if the subtraction yields a negative result
- ❑ Make the result 0 if the subtraction yields a positive result
 - tie the most significant sum bit (sign bit) to the low order **less** input




Overflow Detection

  - Overflow occurs when the result is too large to represent in the number of bits allocated
 - adding two positives yields a negative
 - or, adding two negatives gives a positive
 - or, subtract a negative from a positive gives a negative
 - or, subtract a positive from a negative gives a positive
- On your own: **Prove** you can detect overflow by:
 - Carry into MSB xor Carry out of MSB



Modifying the ALU for Overflow

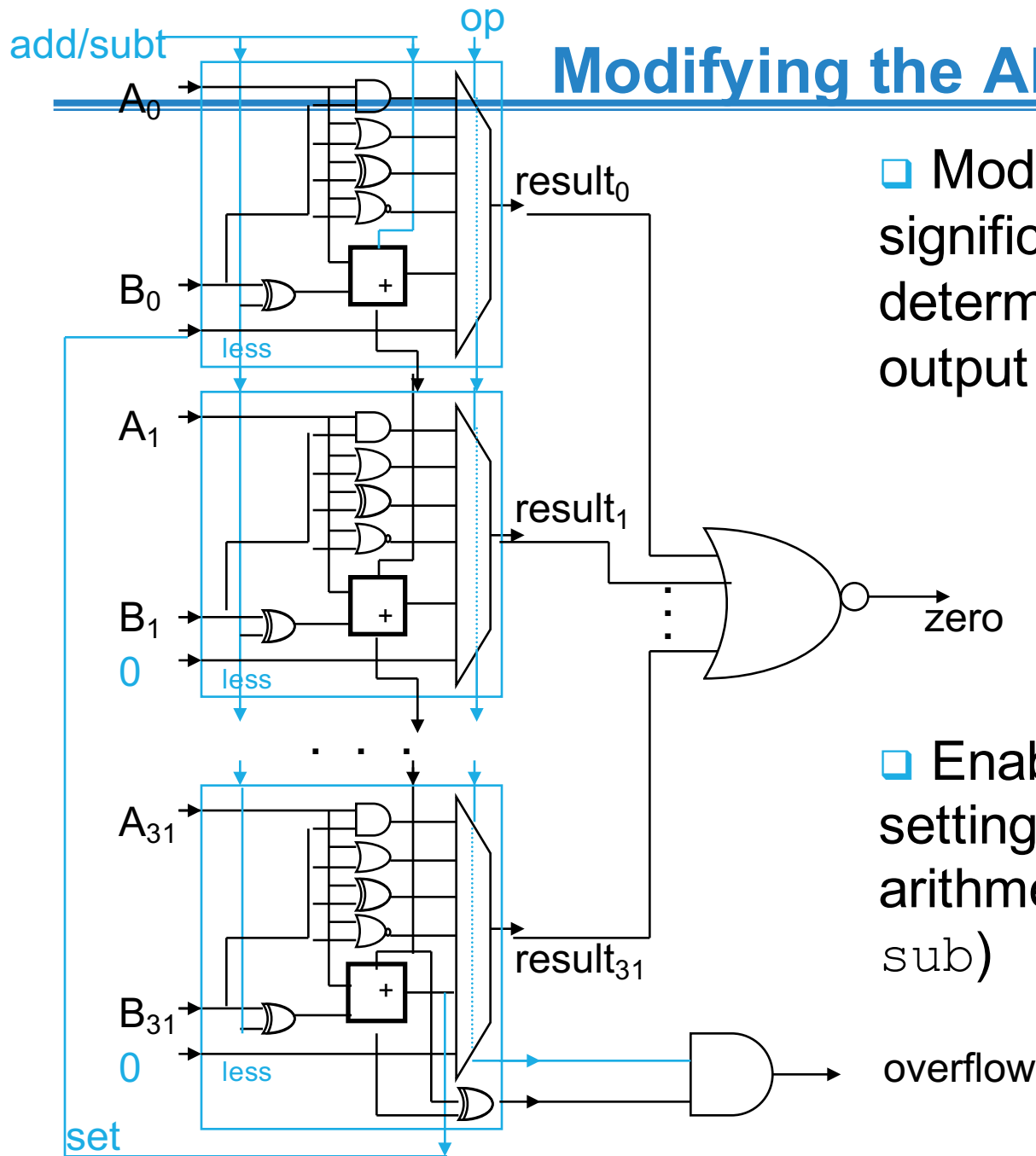

- Modify the most significant cell to determine overflow output setting

- Enable overflow bit setting for signed arithmetic (add, addi, sub)

Overflow Detection and Effects

- ❑ On overflow, an exception (interrupt) occurs
 - Control jumps to predefined address for exception
 - Interrupted address (address of instruction causing the overflow) is saved for possible resumption
- ❑ Don't always want to detect (interrupt on) overflow

New MIPS Instructions

Category	Instr	Op Code	Example	Meaning
Arithmetic (R & I format)	add unsigned	0 and 21	addu \$s1, \$s2, \$s3	$\$s1 = \$s2 + \$s3$
	sub unsigned	0 and 23	subu \$s1, \$s2, \$s3	$\$s1 = \$s2 - \$s3$
	add imm.unsigned	9	addiu \$s1, \$s2, 6	$\$s1 = \$s2 + 6$
Data Transfer	ld byte unsigned	24	lbu \$s1, 20(\$s2)	$\$s1 = \text{Mem}(\$s2+20)$
	ld half unsigned	25	lhu \$s1, 20(\$s2)	$\$s1 = \text{Mem}(\$s2+20)$
Cond. Branch (I & R format)	set on less than unsigned	0 and 2b	sltu \$s1, \$s2, \$s3	if ($\$s2 < \$s3$) $\$s1=1$ else $\$s1=0$
	set on less than imm unsigned	b	sltiu \$s1, \$s2, 6	if ($\$s2 < 6$) $\$s1=1$ else $\$s1=0$

- ❑ Sign extend – addi, addiu, slti
- ❑ Zero extend – andi, ori, xori
- ❑ Overflow detected – add, addi, sub

Outline

- 1. Overview
- 2. Addition
- 3. Multiplication & Division
- 4. Shift
- 5. Floating Point Number

Multiplication


- ❑ More complicated than addition
 - Can be accomplished via shifting and adding

$$\begin{array}{r} 0010 \quad (\text{multiplicand}) \\ \times 1011 \quad (\text{multiplier}) \\ \hline 0010 \\ 0010 \\ 0000 \\ 0010 \\ \hline 00010110 \quad (\text{product}) \end{array}$$


The partial products (0010, 0010, 0000, 0010) are grouped by a bracket and labeled "(partial product array)". The final product (00010110) is highlighted with a blue box.

- ❑ Double precision product produced
- ❑ More time and more area to compute


First Version of Multiplication Hardware

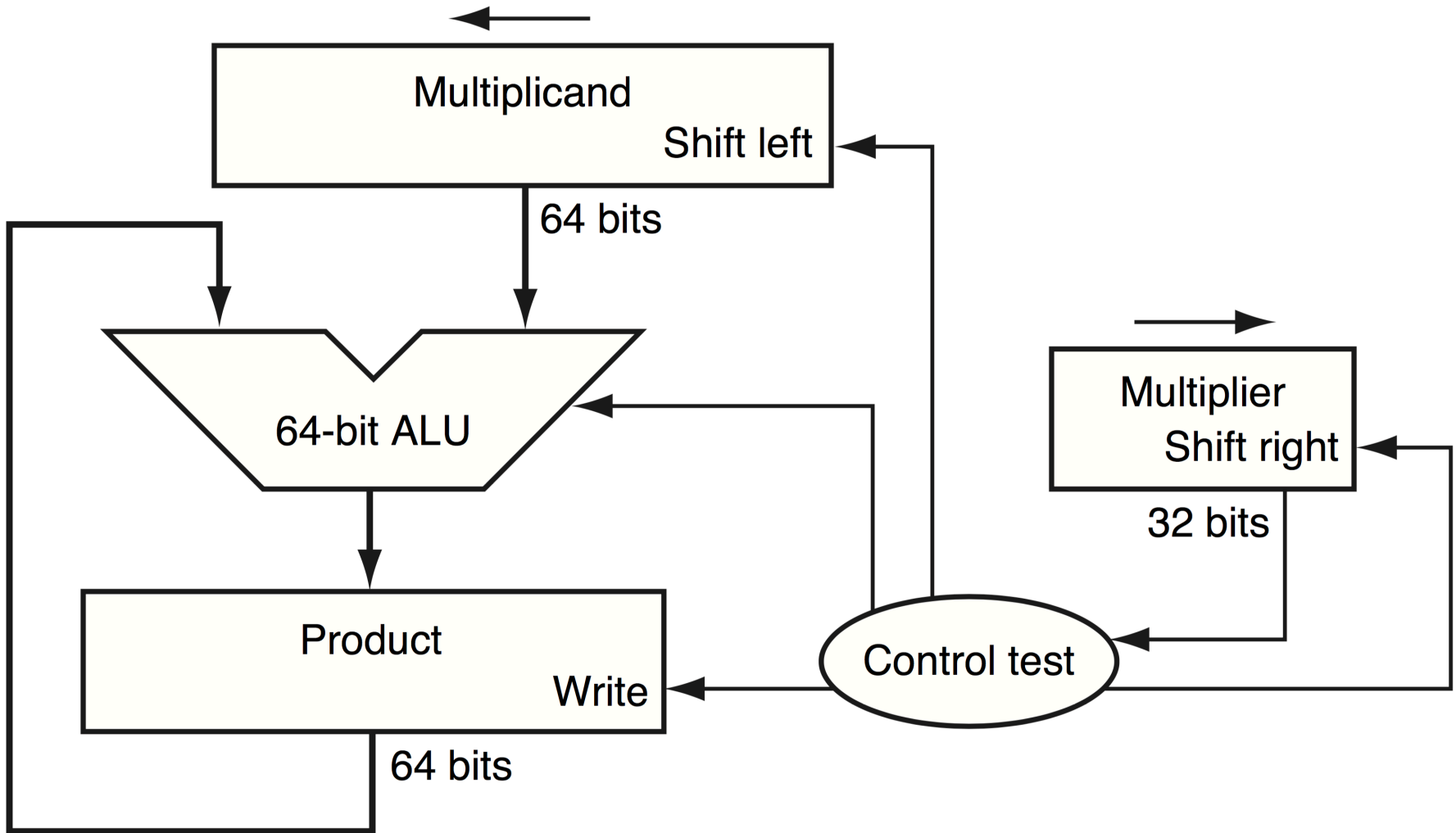

Add and Right Shift Multiplier Hardware

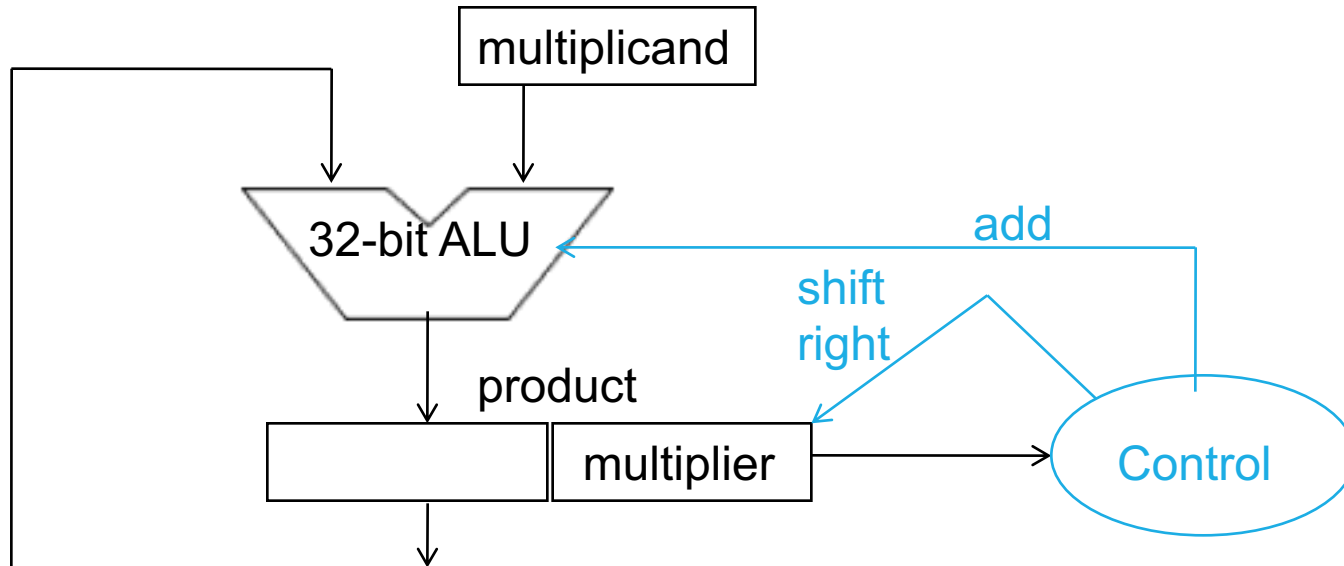

Add and Right Shift Multiplier Hardware

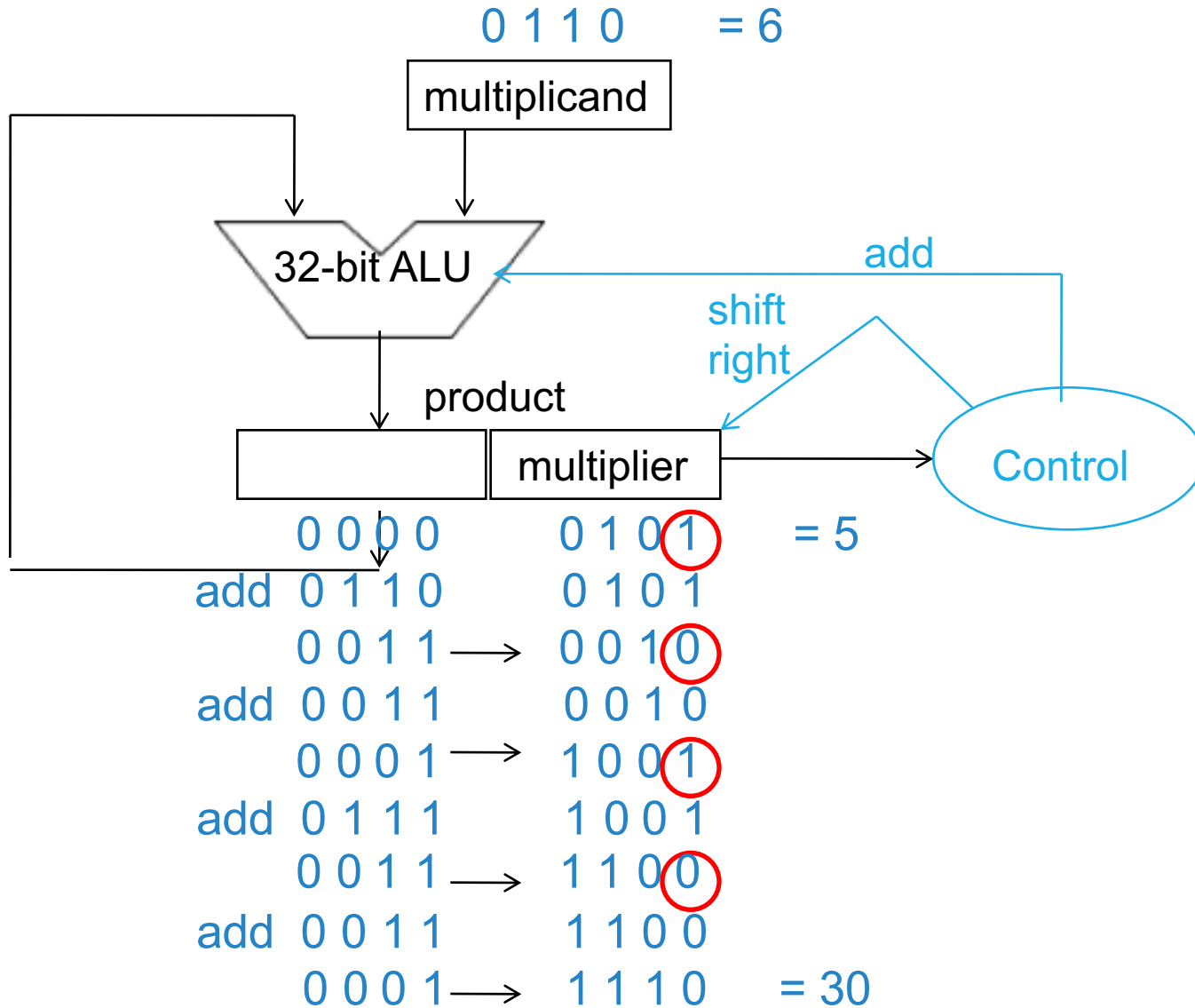

MIPS Multiply Instruction

- ❑ Multiply (`mult` and `multu`) produces a double precision product


```
mult    $s0, $s1    # hi||lo = $s0 * $s1
```

0	16	17	0	0	0x18
---	----	----	---	---	------

- Low-order word of the product is left in processor register `lo` and the high-order word is left in register `hi`
 - Instructions `mfhi rd` and `mflo rd` are provided to move the product to (user accessible) registers in the register file
- ❑ Multiplies are usually done by fast, dedicated hardware and are much more complex (and slower) than adders

Division

 - Division is just a *bunch* of quotient digit guesses and left shifts and subtracts



Example: Division

- Dividing 1001010 by 1000

MIPS Divide Instruction

- Divide generates the remainder in `hi` and the quotient in `lo`

```
div    $s0, $s1           # lo = $s0 / $s1
                               # hi = $s0 mod $s1
```



- Instructions `mflo rd` and `mfhi rd` are provided to move the quotient and remainder to (user accessible) registers in the register file
- As with multiply, divide ignores overflow so software must determine if the quotient is too large. Software must also check the divisor to avoid division by 0.

Outline

- 1. Overview
- 2. Addition
- 3. Multiplication & Division
- 4. **Shift**
- 5. Floating Point Number

Shift Operations

- Shifts move all the bits in a word left or right

`sll $t2, $s0, 8` #`$t2 = $s0 << 8 bits`


`srl $t2, $s0, 8` #`$t2 = $s0 >> 8 bits`

`sra $t2, $s0, 8` #`$t2 = $s0 >> 8 bits`


op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------

- Notice that a 5-bit shamt field is enough to shift a 32-bit value $2^5 - 1$ or **31 bit positions**
- Logical** shifts fill with **zeros**, **arithmetic** left shifts fill with the **sign bit**
- The shift operation is implemented by hardware separate from the ALU
 - using a **barrel shifter** (which would takes lots of gates in discrete logic, but is pretty easy to implement in VLSI)


A Simple Shifter

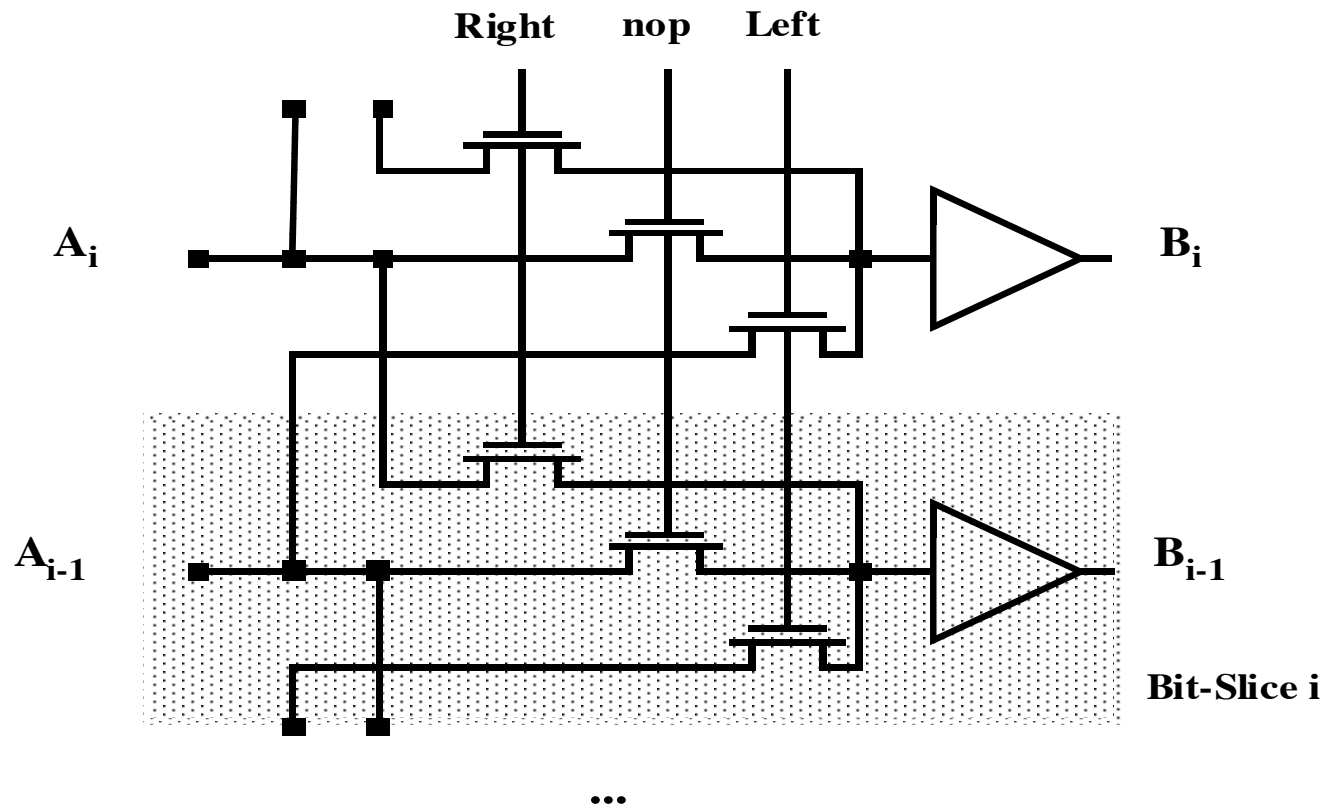


Parallel Programmable Shifters

 

Logarithmic Shifter Structure

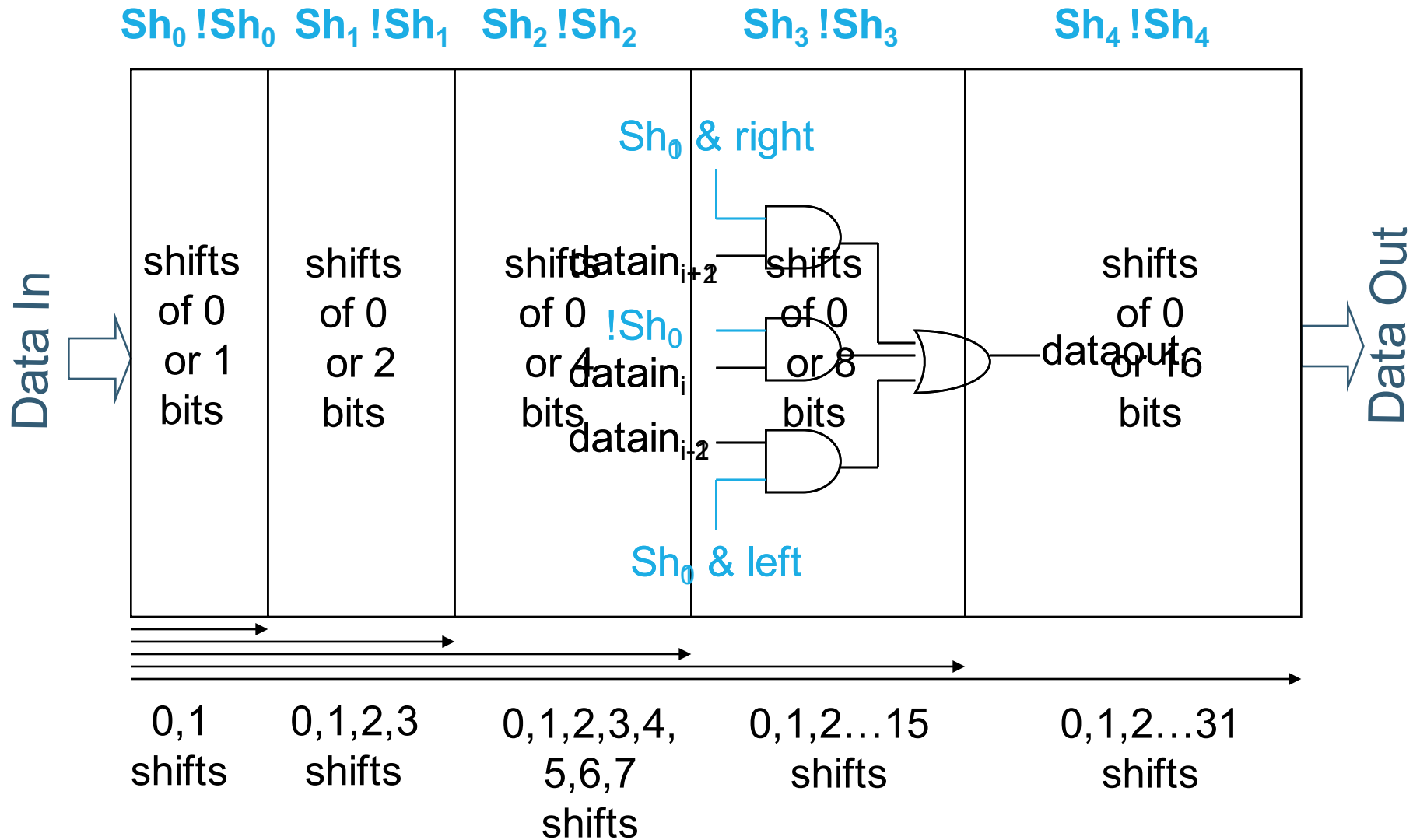

Logarithmic Shifter Structure

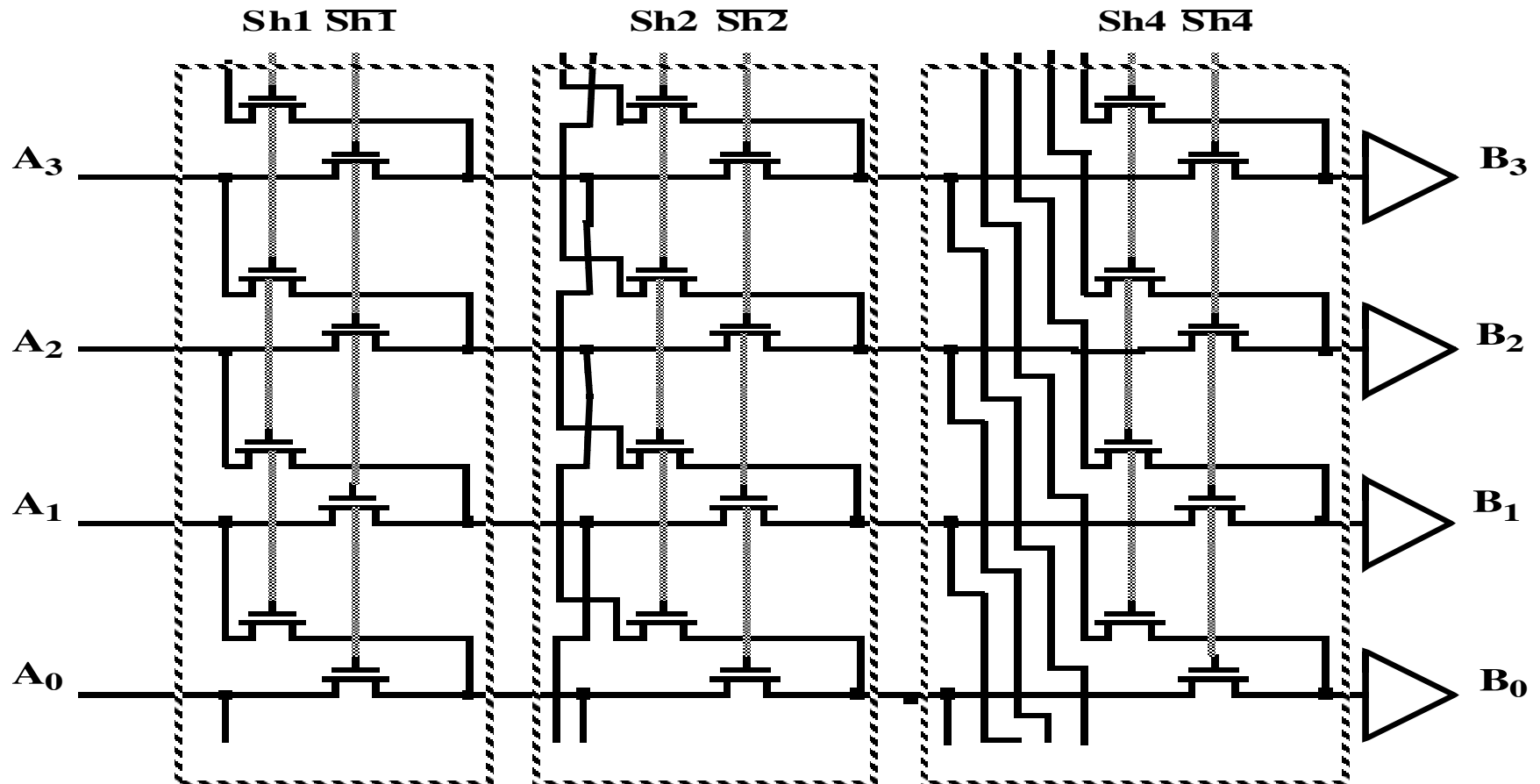

Outline

- 1. Overview
- 2. Addition
- 3. Multiplication & Division
- 4. Shift
- 5. Floating Point Number

Floating Point Number

- Scientific notation: 6.6254×10^{-27}
 - A *normalized* number of certain accuracy
e.g. 6.6254 is called the **mantissa**

 - Scale factors to determine the position of the decimal point
e.g. 10^{-27} indicates position of decimal point and is called the **exponent** (the **base** is implied)

 - **Sign** bit

Normalized Form

- Floating Point Numbers can have multiple forms, e.g.


$$\begin{aligned} 0.232 \times 10^4 &= 2.32 \times 10^3 \\ &= 23.2 \times 10^2 \\ &= 2320. \times 10^0 \\ &= 232000. \times 10^{-2} \end{aligned}$$

- It is desirable for each number to have a **unique** representation => **Normalized Form**
- We normalize Mantissa's in the **Range [1 .. R)** where R is the Base, e.g.:

[1 .. 2) for BINARY

 
[1 .. 10) for DECIMAL

IEEE Standard 754 Single Precision (32-bit, float in C/ C++/ Java)



$$\text{Value represented} = \pm 1. M \times 2^{E' - 127}$$

(a) Single precision

 


$$\text{Value represented} = +1.001010 \dots 0 \times 2^{-87}$$

(b) Example of a single-precision number

00101000 → 40

40 - 127 = -87

 IEEE Standard 754 Double Precision (64-bit, double in C/ C++/ Java)



$$\text{Value represented} = \pm 1. M \times 2^{E' - 1023}$$

(c) Double precision

Example

□ What is the IEEE single precision number $40C0\ 0000_{16}$ in decimal?

● Binary:

0100 0000 1100 0000 0000 0000 0000 0000

● Sign: +

● Exponent: $129 - 127 = +2$

● Mantissa: $1.100\ 0000\ \dots_2 \rightarrow 1.5_{10} \times 2^{+2}$
 $\rightarrow +110.0000\ \dots_2$

● Decimal Answer = $+6.0_{10}$

Class Exercise

□ What is -0.5_{10} in IEEE single precision binary floating point format?

● $0.5 = 1.0... * 2^{-1}$ (in binary)

● Exponent bit = $127 + (-1) = 01111110$

Sign bit = 1

Mantissa = 1.000 0000 0000 0000 0000 0000

● binary representation =

1 01111110 000 0000 0000 0000 0000 0000


Ref: IEEE Standard 754 Numbers

- Normalized $\pm 1.d\dots d \times 2^{\text{exp}}$
- **Denormalized** $\pm 0.d\dots d \times 2^{\text{min_exp}}$ → to represent near-zero numbers
e.g. $+ 0.0000\dots 0000001 \times 2^{-126}$ for Single Precision

Format	# bits	# significant bits	macheps	# exponent bits	exponent range
Single	32	1+23	2^{-24} ($\sim 10^{-7}$)	8	$2^{-126} - 2^{+127}$ ($\sim 10^{\pm 38}$)
Double	64	1+52	2^{-53} ($\sim 10^{-16}$)	11	$2^{-1022} - 2^{+1023}$ ($\sim 10^{\pm 308}$)
Double Extended	≥ 80	≥ 64	$\leq 2^{-64}$ ($\sim 10^{-19}$)	≥ 15	$2^{-16382} - 2^{+16383}$ ($\sim 10^{\pm 4932}$)

(Double Extended is 80 bits on all Intel machines)

 macheps = Machine Epsilon = $_{mach} = 2^{-\text{(# significant bits)}}$



Other Features

- ❑ +, −, x, /, sqrt, remainder, as well as conversion to and from integer are correctly rounded
 - As if computed with infinite precision and then rounded
 - Transcendental functions (that cannot be computed in a finite number of steps e.g., sine, cosine, logarithmic, π , e, etc.) may not be correctly rounded

- ❑ Exceptions and Status Flags
 - Invalid Operation, Overflow, Division by zero, Underflow, Inexact

- ❑ Floating point numbers can be treated as "integer bit-patterns" for comparisons
 - If Exponent is all zeroes, it represents a denormalized, very small and near (or equal to) zero number

 - If Exponent is all ones, it represents a very large number and is considered infinity (see next slide.)

Special Values

- Exponents of all 0's and all 1's have special meaning
 - $E=0, M=0$ represents 0 (sign bit still used so there is +/- 0)
 - $E=0, M \neq 0$ is a denormalized number $\pm 0.M \times 2^{-127}$ (smaller than the smallest normalized number)
 - $E=\text{All } 1\text{'s}, M=0$ represents $\pm\text{Infinity}$, depending on Sign
 - $E=\text{All } 1\text{'s}, M \neq 0$ represents NaN

Other Features

- ❑ Dual Zeroes: +0 (0x00000000) and -0 (0x80000000) (they are treated as the same)

- ❑ **Infinity** is like the mathematical one
 - Finite / Infinity → 0
 - Infinity x Infinity → Infinity
 - Non-zero / 0 → Infinity
 - Infinity ^ (Finite or Infinity) → Infinity

- ❑ **NaN** (Not-a-Number) is produced whenever a *limiting value* cannot be determined:
 - Infinity – Infinity → NaN
 - Infinity / Infinity → NaN
 - 0 / 0 → NaN
 - Infinity x 0 → NaN
 - Many systems just store the result quietly as a NaN (all 1's in exponent) some systems will signal or raise an exception

- ❑ If x is a NaN, x != x

Inaccurate Floating Point Operations

- E.g. Find 1st root of a quadratic equation

- $r = (-b + \sqrt{b*b - 4*a*c}) / (2*a)$

Sparc processor, Solaris, gcc 3.3 (ANSI C),

Expected Answer	0.00023025562642476431
double	0.00023025562638524986
float	0.00024670246057212353

- Problem is that if c is near zero,

$$\sqrt{b*b - 4*a*c} \approx b$$

- Rule of thumb: use the highest precision which does not give up too much speed

Catastrophic Cancellation

- $(a - b)$ is inaccurate when $a \approx b$
- Decimal Examples
 - Using 2 significant digits to compute mean of 5.1 and 5.2 using the formula $(a+b) / 2$:
 $a + b = 10$ (with 2 sig. digits, 10.3 can only be stored as 10)
 $10 / 2 = 5.0$ (the computed mean is less than both numbers!!!)
 - Using 8 significant digits to compute sum of three numbers:
 $(11111113 + (-11111111)) + 7.5111111 = 9.5111111$
 $11111113 + ((-11111111) + 7.5111111) = 10.000000$
- Catastrophic cancellation occurs when

$$\left| \frac{[\text{round}(x) \bullet \text{round}(y)] - \text{round}(x \bullet y)}{\text{round}(x \bullet y)} \right| \gg \epsilon_{mach}$$