



香港中文大學

The Chinese University of Hong Kong

CENG3430 Rapid Prototyping of Digital Systems

Lecture 05:

Finite State Machine

Ming-Chang YANG

mcyang@cse.cuhk.edu.hk





- Finite State Machine (FSM)
 - Clock Edge Detection
 - Feedback
- Use of Signals and Variables
 - Outside Process: Concurrent Statement
 - Inside Process: Sequential Statement
 - Combinational Process
 - Clocked Process
- Types of FSMs: Moore vs. Mealy
- Practical Examples
 - Up/Down Counter
 - Pattern Generator

Finite State Machine (FSM)



  - **Finite State Machine (FSM):** A system jumps from one state to another:
 - Within a pool of finite states, and
 - Upon clock edges and/or input transitions.
- Example of FSM: traffic light, digital watch, CPU, etc.



- Two crucial factors: *time (clock edge)* and *state (feedback)*



- Finite State Machine (FSM)
 - Clock Edge Detection
 - Feedback
- Use of Signals and Variables
 - Outside Process: Concurrent Statement
 - Inside Process: Sequential Statement
 - Combinational Process
 - Clocked Process
- Types of FSMs: Moore vs. Mealy
- Practical Examples
 - Up/Down Counter
 - Pattern Generator


Clock Edge Detection



- “**if**” or “**wait until**” statements can be used to detect the clock edge of a clock signal (e.g., **CLK**):


- “**if**” statement:

 - **if** CLK'event and CLK = '1' -- rising edge
- **if** CLK'event and CLK = '0' -- falling edge




OR

 - **if**(rising_edge(CLK)) -- rising edge
- **if**(falling_edge(CLK)) -- falling edge



- “**wait until**” statement:

 - **wait until** CLK = '1'; -- rising edge
- **wait until** CLK = '0'; --falling edge



rising_edge (CLK) vs. CLK'event



- **rising_edge ()** function in std_logic_1164 library

```
FUNCTION rising_edge (SIGNAL s : std_ulogic) RETURN BOOLEAN IS
BEGIN
    RETURN (s'EVENT AND (To_X01(s) = '1') AND
            (To_X01(s'LAST_VALUE) = '0'));
END;
```

- This function returns a value **TRUE** only when the present value is '1' and the last value is '0'.
 - If the past value is something like 'z','u' etc. then it will return a **FALSE** value.
- The statement (**clk'event and clk='1'**)
 - It results **TRUE** when the present value is '1' and there is an edge transition in the clk.
 - *It does not see whether the previous value is '0' or not.*

Just use rising_edge () and falling_edge () functions!

How to use “if” or “wait until”? (1/2)

- **Synchronous Process:** Computes values only on clock edges (i.e., only sensitive/sync. to clock signal).
 - Both “**wait-until**” or “**if**” statements can be used:

```
process ← NO sensitivity list implies that there is one clock signal.  
begin
```

Usage
of
“wait
until”

```
    wait until clk='1' ; ← The first statement must be wait until.  
    ...  
end process
```

*Note: IEEE VHDL requires that a process with a wait statement must not have a sensitivity list, and the first statement must be **wait until**.*

```
process (clk) ← The clock signal must be in the sensitivity list.  
begin
```

Usage
of
“if”

```
    ...  
    if ( rising_edge (clk) ) ← NOT necessary to be the first.  
    ...  
end process
```

How to use “if” or “wait until”? (2/2)

- **Asynchronous Process:** Computes values on clock edges or when asynchronous conditions are TRUE.
 - That is, it must be sensitive to the clock signal (if any), and to all inputs that may affect the asynchronous behavior.
 - For async. processes, only “**if**” statements can be used:

```
process (clk, input_a, input_b, ...) ← The sensitivity list
begin
  ...
  if ( rising_edge (clk) )
  ...
end process
```

← The sensitivity list should include the clock signal, and all inputs that may affect asynchronous behavior.

Usage
of
“if”




- **Finite State Machine (FSM)**
 - Clock Edge Detection
 - **Feedback**
- Use of Signals and Variables
 - Outside Process: Concurrent Statement
 - Inside Process: Sequential Statement
 - Combinational Process
 - Clocked Process
- Types of FSMs: Moore vs. Mealy
- Practical Examples
 - Up/Down Counter
 - Pattern Generator

Feed-forward and Feedback Paths



 - So far, we only learned logic with **feed-forward (or open-loop) paths**.



- Now, we are going to learn **feedback (or closed-loop) paths**—*the key step of making a finite state machine*.
- There are three types of feedback paths:
 - 1) **Direct Feedback**
 - 2) **Feedback using Signals**
 - 3) **Feedback using Variables**

1) Direct Feedback



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity feedback_1 is
port (a, clk, reset: in std_logic;
      c: buffer std_logic);
end feedback_1;
```

```
architecture feedback_1_arch of feedback_1 is
begin
```

```
    process (clk, reset) -- async.
```

```
    begin
```

```
        if reset = '1' then c <= '0';
```


```
        elsif rising_edge(clk) then
```

```
            c <= not (a and c);
```

```
        end if;
```

```
    end process;
```

```
end feedback_1_arch ;
```

 


c <= not (a and c); ← not(a and c) will take effect and be assigned to **c** at the next rising clock edge.

Internal Feedback: inout or buffer



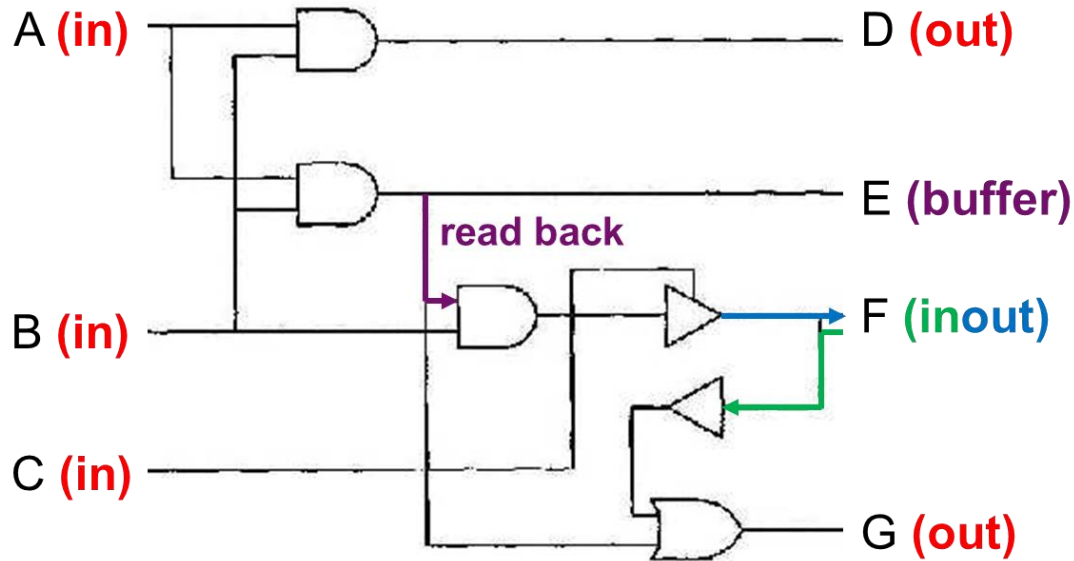- Recall (*Lec01*): There are 4 modes of I/O pins:
 - 1) **in**: Data flows **in** only
 - 2) **out**: Data flows **out** only (cannot be read back by the entity)
 - 3) **inout**: Data flows **bi-directionally** (i.e., in or out)
 - 4) **buffer**: Similar to **out** but it can be **read back** by the entity





- Both **buffer** and **inout** can be **read back** internally.
 - **inout** can also read external input signals.

Class Exercise 5.1

Student ID: _____ Date: _____

Name: _____

  - Draw the signal **c**
 - Assume initially $c = 0$
- ```
elsif rising_edge(clk) then
 c <= not(a and c);
```



## 2) Feedback using Signals



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity feedback_2 is
port (a, clk, reset: in std_logic;
 c: buffer std_logic);
end feedback_2;
```

```
architecture feedback_2_arch of feedback_2 is
```

```
signal b: std_logic; -- internal signal b
```

```
begin
```

```
 process (clk, reset)
```

```
 begin
```

```
 if reset = '1' then c <= '0';
```

```
 elsif rising_edge(clk) then
```


```
 b <= not (a and c); ← not (a and c) will take effect and
 be assigned to b at the next rising clock edge.
```

```
 c <= b; ← b will be assigned to c at the next rising
clock edge.
```

```
 end if;
```

```
 end process;
```

```
end feedback_2_arch ;
```

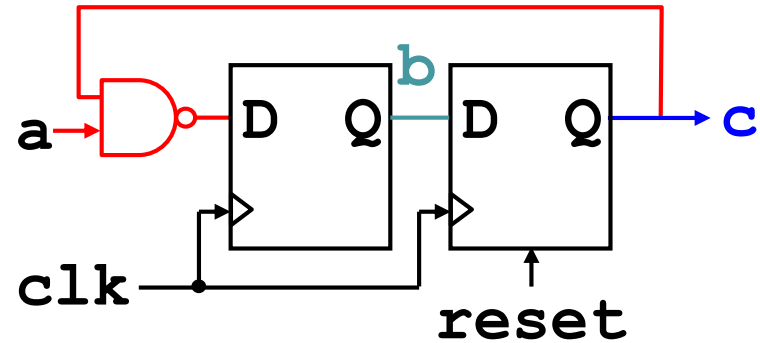



Why? Combinational logic

# Class Exercise 5.2

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

  
- Draw signals **b**, and **c**
  - Assume initially **b=1** and **c=0**
  - elseif **rising\_edge (clk)** then
  - b** <= **not (a and c)** ;
  - c** <= **b** ;


 
# 3) Feedback using Variables



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity feedback_3 is
Port(a,clk,reset: in std_logic;
 c: buffer std_logic);
End feedback_3;
```



```
architecture feedback_3_arch of feedback_3 is
begin
```

```
process -- no sensitivity list
variable v: std_logic; -- local variable v
begin
```

```
wait until clk = '1';
```

```
if reset = '1' then v := '0';
```

```
else
```

```
v := not(a and c); ← not(a and c) affects v immediately at the
next rising clock edge.
```

```
c <= v; ← The previous new v will be assigned to c at
the same rising clock edge.
```

```
end if;
```

```
end process;
```

```
end feedback_3_arch ;
```



# Class Exercise 5.3

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_



- Draw variable  $v$  and signal  $c$

– Assume initially  $c = 0$


`wait until clk = '1';`

`v := not(a and c);`

`c <= v;`

  
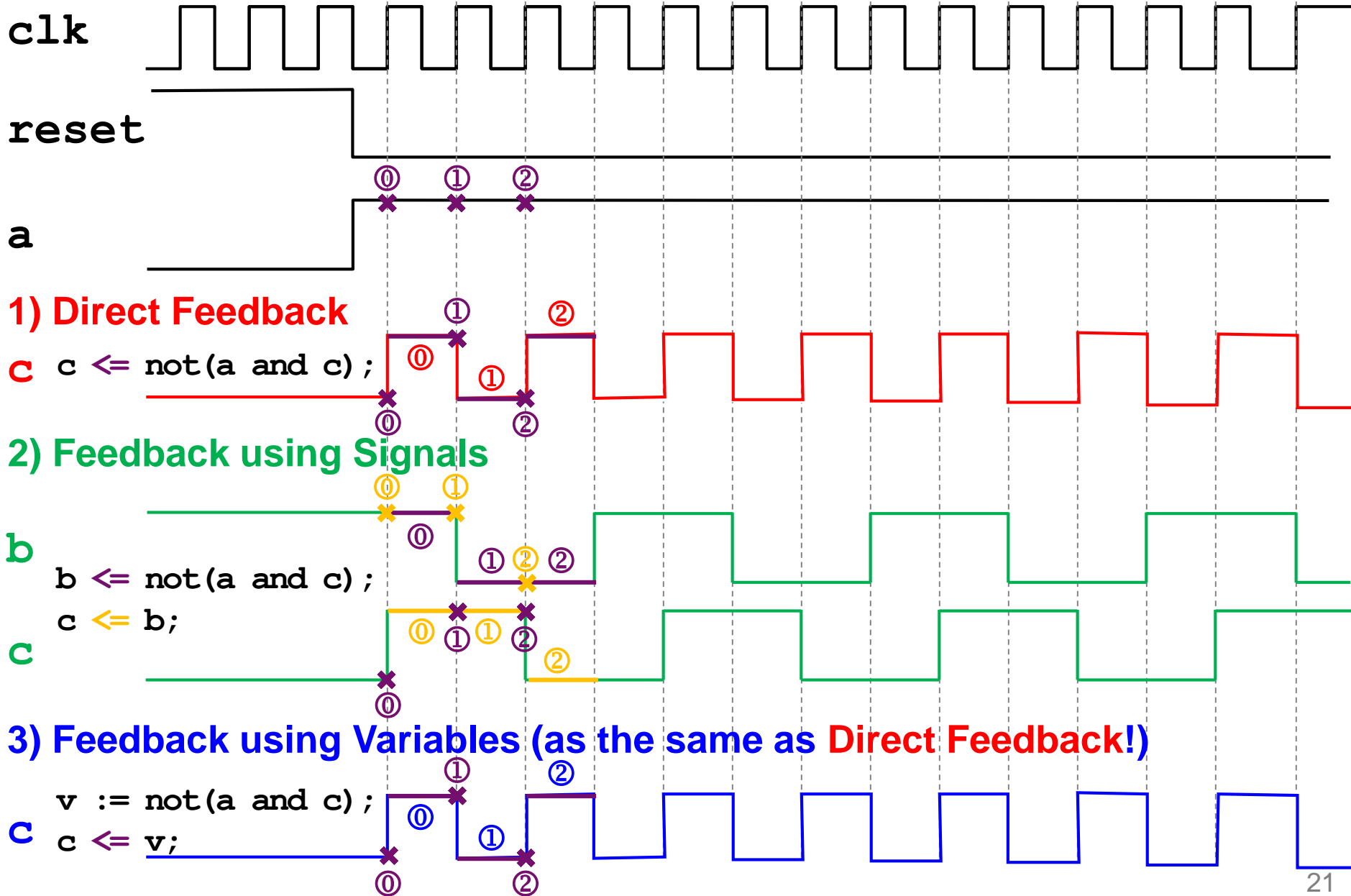
# Direct vs. Signal vs. Variable Feedback



# Signal Feedback vs. Variable Feedback

- Feedback using signals or variables will have **different results**.
- **Signals**
  - Signal assignment “ $\leq$ ” can be treated as a **flip-flop**.
    - Left-hand-side of “ $\leq$ ” is output
    - Right-hand-side of “ $\leq$ ” is input
  - A signal can be **only updated once**, when the process is performed at the **triggering clock edge**.
    - When a signal is assigned to different values by different statements in a process, only **the last statement is effective**.
- **Variables**
  - Variable assignment “ $:=$ ” will **take effect immediately**.
  - A variable in a process can be **updated many times**.



- Finite State Machine (FSM)
  - Clock Edge Detection
  - Feedback
- Use of Signals and Variables
  - Outside Process: Concurrent Statement
  - Inside Process: Sequential Statement
    - Combinational Process
    - Clocked Process
- Types of FSMs: Moore vs. Mealy
- Practical Examples
  - Up/Down Counter
  - Pattern Generator

# Overview: Use of Signals and Variables

architecture body

**Outside Process**

**process (sensitivity list)**

**Combinational Process**

*NO Clock Triggering*

**if/wait until CLK;**

**Clocked Process**

*Clock Triggering Exists*

**1) Synchronous Inputs**

*NOT in sensitivity list*

**2) Asynchronous Inputs**

*IN sensitivity list*

- **Outside Process**
  - Concurrent Statements
- **Inside Process**
  - Sequential Statements
    - 1) Combinational Process:**  
NO **CLK** triggering
      - “<=” is a combinational logic
      - All involved inputs should be in the sensitivity list
    - 2) Clocked Process:**  
Has **CLK** triggering
      - “<=” is a flip-flop
      - **Synchronous Inputs:** should NOT be in the sensitivity list
      - **Asynchronous Inputs:** should be in sensitivity list

# Overview: Use of Signals and Variables

architecture body

## Outside Process

process (sensitivity list)

### Combinational Process

*NO Clock Triggering*

**if/wait until CLK;**

### Clocked Process

*Clock Triggering Exists*

#### 1) Synchronous Inputs

*NOT in sensitivity list*

#### 2) Asynchronous Inputs

*IN sensitivity list*

- **Outside Process**

- Concurrent Statements

- **Inside Process**

- Sequential Statements

- 1) **Combinational Process:**  
NO CLK triggering

- “<=” is a combinational logic
- All involved inputs should be in the sensitivity list

- 2) **Clocked Process:**  
Has CLK triggering

- “<=” is a flip-flop
- **Synchronous Inputs:** should NOT be in the sensitivity list
- **Asynchronous Inputs:** should be in sensitivity list

# Outside Process: Concurrent Statement

- **Signal Assignments** **outside a Process**

- All the statements outside processes are “concurrent”.
  - All concurrent statements can be *interchanged* freely.
  - Each statement will be *executed once* when any signal in it changes.
- Signals can be assigned with *multiple values* if “**resolved logic**” (i.e., `std_logic` rather than `std_u`logic) is allowed.

**Ex:** architecture `test_arch` of `test` is

```
 out1 <= in1 and in2; -- concurrent statement
 out2 <= in1 or in2; -- concurrent statement
 out2 <= in2; -- multi-value assignment
end test_arch;
```

- **Variable Assignments** **outside a Process**

- Variables can only live *inside* processes!



# Overview: Use of Signals and Variables

architecture body

**Outside Process**

**process (sensitivity list)**

**Combinational Process**

*NO Clock Triggering*

**if/wait until CLK;**

**Clocked Process**

*Clock Triggering Exists*

**1) Synchronous Inputs**

*NOT in sensitivity list*

**2) Asynchronous Inputs**

*IN sensitivity list*

- **Outside Process**
  - Concurrent Statements
- **Inside Process**
  - Sequential Statements
    - 1) **Combinational Process:**  
NO CLK triggering
      - “<=” is a combinational logic
      - All involved inputs should be in the sensitivity list
    - 2) **Clocked Process:**  
Has CLK triggering
      - “<=” is a flip-flop
      - **Synchronous Inputs:** should NOT be in the sensitivity list
      - **Asynchronous Inputs:** should be in sensitivity list



# Inside Process: Sequential Statement



- Statements inside **process** are executed **sequentially**.
  - The process will be **executed once** when one or more signals in the **sensitivity list** changes.

Ex: `process (in1, in2) -- sensitivity list`  
`variable v1, v2: std_logic;`  
`begin`  
`s1 <= in1 and in2;`  
`s1 <= in1 or in2;`  
`v1 := in1 and in2;`  
`v1 := in1 or in2;`  
`end process`

- **Signals Assignments (<=)** inside a Process:  
Only the last assignment for a particular signal takes effect.
- **Variables Assignments (:=)** inside a Process:  
All assignments take effect **immediately** and **sequentially**.

- A process can be: “**combinational**” or “**clocked**”.

# Overview: Use of Signals and Variables

**architecture body**

**Outside Process**

**process (sensitivity list)**

**Combinational Process**

*NO Clock Triggering*

**if/wait until CLK;**

**Clocked Process**

*Clock Triggering Exists*

**1) Synchronous Inputs**

*NOT in sensitivity list*

**2) Asynchronous Inputs**

*IN sensitivity list*

- **Outside Process**
  - Concurrent Statements
- **Inside Process**
  - Sequential Statements
  - 1) **Combinational Process:**  
NO **CLK** triggering
    - “<=” is a combinational logic
    - All involved inputs should be in the sensitivity list
  - 2) **Clocked Process:**  
Has **CLK** triggering
    - “<=” is a flip-flop
    - **Synchronous Inputs:** should NOT be in the sensitivity list
    - **Asynchronous Inputs:** should be in sensitivity list

# 1) Combinational Process



- **Combinational Process**

- NO clock triggering condition can be found inside.
  - **Clock Triggering Condition:** `if (clk='1' and clk'event), (wait until clk='1'), etc.`
- Each “<=” is a **combinational logic**.
- All involved inputs should be in the **sensitivity list**.
  - Otherwise the results will be unpredictable.

**Ex:** `combinational_process: process (in1, in2)`  
`begin`  
`out3 <= in1 xor in2;`  
`out3 <= '1';`  
`end process;`

# Class Exercise 5.4

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_  
Name: \_\_\_\_\_

```
1 signal S1, S2: bit;
2 signal S_OUT: bit_vector(1 to 8);
3 process (S1, S2)
4 variable V1, V2: bit;
5 begin
6 V1 := '1';
7 V2 := '1';
8 S1 <= '1';
9 S2 <= '1';
10 S_OUT(1) <= V1;
11 S_OUT(2) <= V2;
12 S_OUT(3) <= S1;
13 S_OUT(4) <= S2;
14 V1 := '0';
15 V2 := '0';
16 S2 <= '0';
17 S_OUT(5) <= V1;
18 S_OUT(6) <= V2;
19 S_OUT(7) <= S1;
20 S_OUT(8) <= S2;
21 end process;
```

- Which line(s) will NOT take effect?

Answer: \_\_\_\_\_

- When will the process be executed?

Answer: \_\_\_\_\_

- What are the values of **S\_OUT** after execution?

Answer:

|            |            |
|------------|------------|
| S_OUT(1) : | S_OUT(5) : |
| S_OUT(2) : | S_OUT(6) : |
| S_OUT(3) : | S_OUT(7) : |
| S_OUT(4) : | S_OUT(8) : |

# Overview: Use of Signals and Variables

architecture body

**Outside Process**

process (sensitivity list)

**Combinational Process**

*NO Clock Triggering*

**if/wait until CLK;**

**Clocked Process**

*Clock Triggering Exists*

- **Outside Process**
  - Concurrent Statements
- **Inside Process**
  - Sequential Statements
  - 1) **Combinational Process:**  
NO CLK triggering
    - “<=” is a combinational logic
    - All involved inputs should be in the sensitivity list
  - 2) **Clocked Process:**  
Has CLK triggering
    - “<=” is a flip-flop
    - **Synchronous Inputs:** should NOT be in the sensitivity list
    - **Asynchronous Inputs:** should be in sensitivity list

# 2) Clocked Process



- **Clocked Process**

- A **clock edge expression** can be found inside:

- **“if” statement:**

```
clocked_process: process (sensitivity list)
```

```
begin
```

```
... -- same as combinational process
```

```
if (clk='1' and clk'event) then
```

```
 out1 <= in1 and in2;
```

```
end if;
```

```
... -- same as combinational process
```

```
end process;
```

- **“wait until” statement:**

```
clocked_process: process -- no sensitivity list
```

```
begin
```

```
wait until clk='1';
```

```
 out1 <= in1 and in2;
```

```
end process;
```

1) Each “<=” is a flip-flop.

2) The assignment takes effect on next clock edge.

1) Each “<=” is a flip-flop.

2) The assignment takes effect on next clock edge.


# Class Exercise 5.5

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

- Find the signal results after clock edges  $t_1 \sim t_4$ :
 
```
process
signal s1: integer:=1;
signal s2: integer:=2;
signal s3: integer:=3;
begin
wait until rising_edge (clk);
 s1 <= s2 + s3;
 s2 <= s1;
 s3 <= s2;
 sum <= s1 + s2 + s3;
end process
end
```



|            | $t_1$ | $t_2$ | $t_3$ | $t_4$ |
|------------|-------|-------|-------|-------|
| <b>s1</b>  |       |       |       |       |
| <b>s2</b>  |       |       |       |       |
| <b>s3</b>  |       |       |       |       |
| <b>sum</b> |       |       |       |       |

**Signals Assignments ( $\leftarrow$ ) inside a Process:**

Only *the last* assignment for a particular signal takes effect.

**Variables Assignments ( $:=$ ) inside a Process:**

All assignments take effect **immediately** and **sequentially**.


# Class Exercise 5.6

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

- Find the signal results after clock edges  $t_1 \sim t_4$ :
 
```
process
variable v1: integer:=1;
variable v2: integer:=2;
variable v3: integer:=3;
begin
wait until rising_edge(clk);
 v1 := v2 + v3;
 v2 := v1;
 v3 := v2;
 sum <= v1 + v2 + v3;
end process
end
```



|     | t1 | t2 | t3 | t4 |
|-----|----|----|----|----|
| v1  |    |    |    |    |
| v2  |    |    |    |    |
| v3  |    |    |    |    |
| sum |    |    |    |    |

**Signals Assignments ( $\leftarrow$ ) inside a Process:**

Only *the last* assignment for a particular signal takes effect.

**Variables Assignments ( $:=$ ) inside a Process:**

All assignments take effect **immediately** and **sequentially**.



 
# Do Variables Have Memory?



- **Yes.** After a process is called, the state of a variable will be kept for being used again next time.

```
library IEEE;
use IEEE.std_logic_1164.all;
entity test is port (a, reset_v1: in std_logic;
 b, c: out std_logic); end test;
architecture test_arch of test is
begin
label_procl: process (a, reset_v1)
variable v1 : std_logic;
begin
 if reset_v1 = '1' then
 v1 := not a;
 end if;
 b <= a;
 c <= v1;
end process label_procl;
end test_arch;
```



**v1 stays at two different levels depending on previous result.**

# Overview: Use of Signals and Variables

architecture body

**Outside Process**

**process (sensitivity list)**

**Combinational Process**

*NO Clock Triggering*

**if/wait until CLK;**

**Clocked Process**

*Clock Triggering Exists*

**1) Synchronous Inputs**

*NOT in sensitivity list*

**2) Asynchronous Inputs**

*IN sensitivity list*


- **Outside Process**
  - Concurrent Statements
- **Inside Process**
  - Sequential Statements
  - 1) **Combinational Process:**  
NO CLK triggering
    - “<=” is a combinational logic
    - All involved inputs should be in the sensitivity list
  - 2) **Clocked Process:**  
Has CLK triggering
    - “<=” is a flip-flop
    - **Synchronous Inputs:** should NOT be in the sensitivity list
    - **Asynchronous Inputs:** should be in sensitivity list
 
# Synchronous & Asynchronous Inputs



- Besides of the clock signal (**CLK**), other signals in a **clocked process** can be classified into two types:
  - Synchronous Inputs** (e.g., **D** input of flip-flops)
    - Inputs that should be **checked** only at the next clock edge.
    - NO need to put synchronous input signals in the **sensitivity list**.
  - Asynchronous Inputs** (e.g., **RESET** input of flip-flops)
    - Inputs that should be **checked** either at the next clock edge or when any asynchronous input in the sensitivity list changes.
    - Asynchronous inputs **NEVER** exist in **wait-until** clocked processes.

```
process (CLK, RESET) -- no need to put D, why?
begin
 if (RESET = '1') then
 Q <= '0'; -- Reset Q immediately
 elsif CLK = '1' and CLK'event then
 Q <= D; -- Q follows input D
 end if;
end process;
```



# Class Exercise 5.7

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_  
Name: \_\_\_\_\_

- What are processes p1 and p2 (combinational or clocked)?
- Which signals are sync., async., or combinational inputs?

...

```
port (clock, reset: in std_logic;
 t_light: out std_logic_vector (2 downto 0));
```

...

```
type traffic_state_type is (s0, s1, s2, s3);
signal t_state: traffic_state_type; -- internal signal
p1: process(t_state) p2: process
begin begin
 case (t_state) is wait until clock='1';
 when s0 => t_light <= "100"; if reset = '1' then
 when s1 => t_light <= "110"; t_state <= s0;
 when s2 => t_light <= "001"; else
 when s3 => t_light <= "010"; case t_state is
 end case; when s0 => t_state <= s1;
end process; when s1 => t_state <= s2;
 when s2 => t_state <= s3;
 when s3 => t_state <= s0;
 end case;
 end if;
end process;
```

# Class Exercise 5.8

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_  
Name: \_\_\_\_\_

- Based on Class Exercise 5.7, rewrite process p2 using asynchronous reset.

```
sync_p2: process
begin
 wait until clock='1';
 if reset = '1' then
 t_state <= s0;
 else
 case t_state is
 when s0 => t_state <= s1;
 when s1 => t_state <= s2;
 when s2 => t_state <= s3;
 when s3 => t_state <= s0;
 end case;
 end if;
end process;
```

```
async_p2: process
begin
```

```
end process;
```

# Recall: How to use “if” or “wait until”?

- **Asynchronous Process:** Computes values on clock edges and when asynchronous conditions are TRUE.
  - That is, it must be sensitive to the clock signal (if any), and to all inputs that may affect the asynchronous behavior.
  - Only “if” statements can be used: ②

```
process (clk, input_a, input_b, ...)
begin
 ...
 if (rising_edge (clk))
 ...
end process
```

①  
← The sensitivity list should include the clock signal, and all inputs that may affect asynchronous behavior.

Usage  
of  
“if”

# Summary: Inside Process



- **Signals Assignments ( $\leq$ ) inside a Process**
  - Only the *last* assignment for a particular signal takes effect.
  - **Combinational Process:** No clock (CLK) triggering
    - Each “ $\leq$ ” is a **combinational logic**.
    - All involved inputs should be in the **sensitivity list**.
  - **Clocked Process:** Has clock (CLK) triggering
    - Signal assignments *before* or *outside* the clock edge detection:
      - As the same as **combinational process**.
    - Signal assignments *after* or *inside* the clock edge detection:
      - Each “ $\leq$ ” can be treated as a **flip-flop**: The signal assignment will take effect at the next clock edge.
      - **Synchronous inputs** should NOT be in the **sensitivity list**.
      - **Asynchronous inputs** should be in the **sensitivity list**.
- **Variables Assignments ( $:=$ ) inside a Process**
  - All assignments take effect **immediately** and **sequentially**.

# Summary: Use of Signals and Variables

architecture body

**Outside Process**

**process (sensitivity list)**

**Combinational Process**

*NO Clock Triggering*

**if/wait until CLK;**

**Clocked Process**

*Clock Triggering Exists*

**1) Synchronous Inputs**

*NOT in sensitivity list*

**2) Asynchronous Inputs**


*IN sensitivity list*

- **Outside Process**
  - Concurrent Statements
- **Inside Process**
  - Sequential Statements
  - 1) **Combinational Process:**  
NO **CLK** triggering
    - “<=” is a combinational logic
    - All involved inputs should be in the sensitivity list
  - 2) **Clocked Process:**  
Has **CLK** triggering
    - “<=” is a flip-flop
    - **Synchronous Inputs:** should NOT be in the sensitivity list
    - **Asynchronous Inputs:** should be in sensitivity list



# Summary: Multiple Assignments



- **Signals**
  - **Outside Process**
    - Signals can be assigned with multiple values if “resolved logic” is allowed.
  - **Inside Process**
    - Only the last assignment for that particular signal will take effect.
- **Variables**
  - **Outside Process**
    - Variables can only live inside processes! 
  - **Inside Process**
    - ALL variable assignments will take effect immediately and sequentially.




- Finite State Machine (FSM)
  - Clock Edge Detection
  - Feedback
- Use of Signals and Variables
  - Outside Process: Concurrent Statement
  - Inside Process: Sequential Statement
    - Combinational Process
    - Clocked Process
- **Types of FSMs: Moore vs. Mealy**
- Practical Examples
  - Up/Down Counter
  - Pattern Generator
 
# Types of Finite State Machines





- **Moore Machine:**

- **Outputs** are a function of the present **state** only.



- **Mealy Machine:**

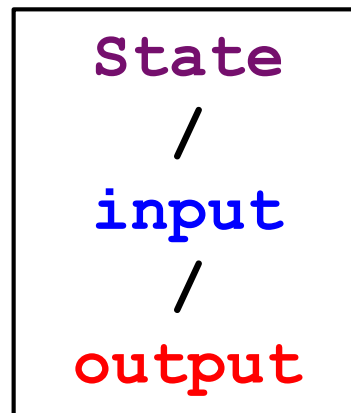 - **Outputs** are a function of the present **state** and the present **inputs**.



# Moore Machine (1/3)




- **Moore Machine:**

- **Outputs** are a function of the present **state** only.

- An Example of Moore Machine:

**F1:**  $C \leftarrow \text{not } (A \text{ and } C)$ ; -- " $\leftarrow$ " is a **flip-flop**

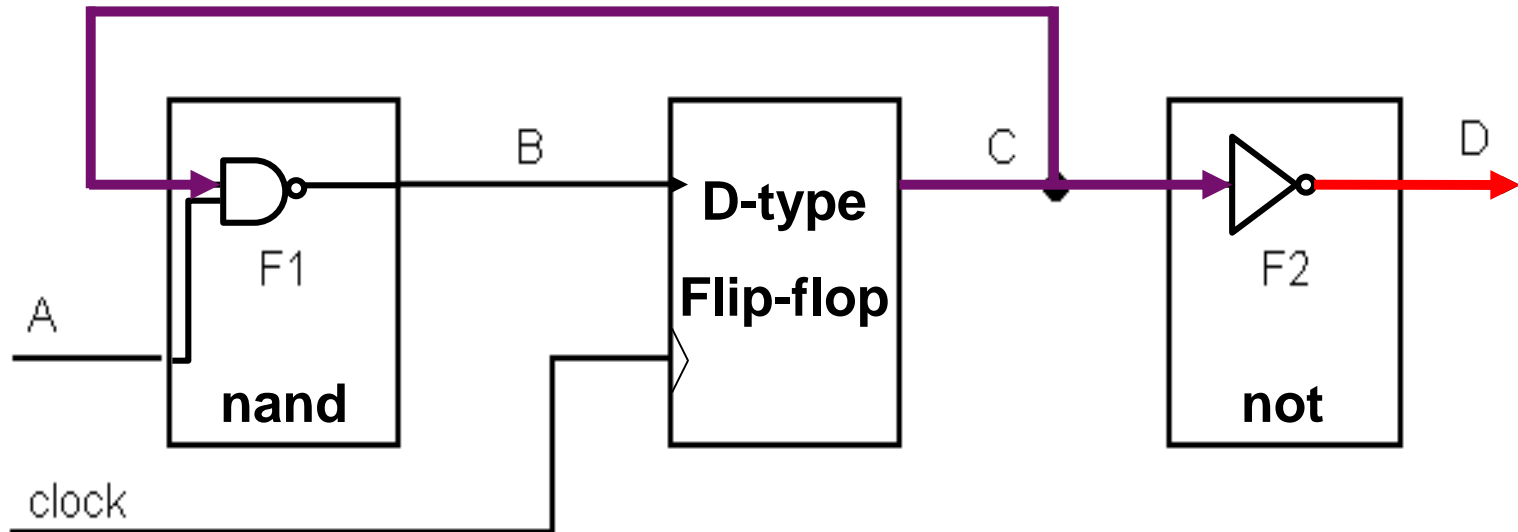**F2:**  $D \leftarrow \text{not } C$ ; -- **Moore Machine**



*B is the current output of  $\text{not}(A \text{ and } C)$ , but B does not need to exist.*

*Writing  $C \leftarrow \text{not } (A \text{ and } C)$  is enough.*

# Moore Machine (2/3)



- The simplest Moore machine uses only one process:

```
1 architecture moore_arch of system is
```

```
2 signal C: bit; -- state
```

```
3 begin
```

```
4 D <= not C; -- combinational logic ← F2
```

```
5 process - sequential logic
```

```
6 begin
```

```
7 wait until rising_edge(clock); ← F1
```

```
8 C <= not (A and C); -- flip-flop
```

```
9 end process;
```

```
10 end moore_arch;
```

# Moore Machine (3/3)



- Using two processes is flexible and easier to design.

```
process (C) -- combinational
begin
 D <= not C; -- Moore Machine
end process;
```

← F2

```
process (clock, reset) -- sequential
begin
 if reset = '1' then c <= '0';
 elsif rising_edge(clock) then
 C <= not (A and C); -- flip-flop
 end if;
end process;
```


← F1

# Class Exercise 5.9

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_


- Draw the waveform of C (initially C=0)

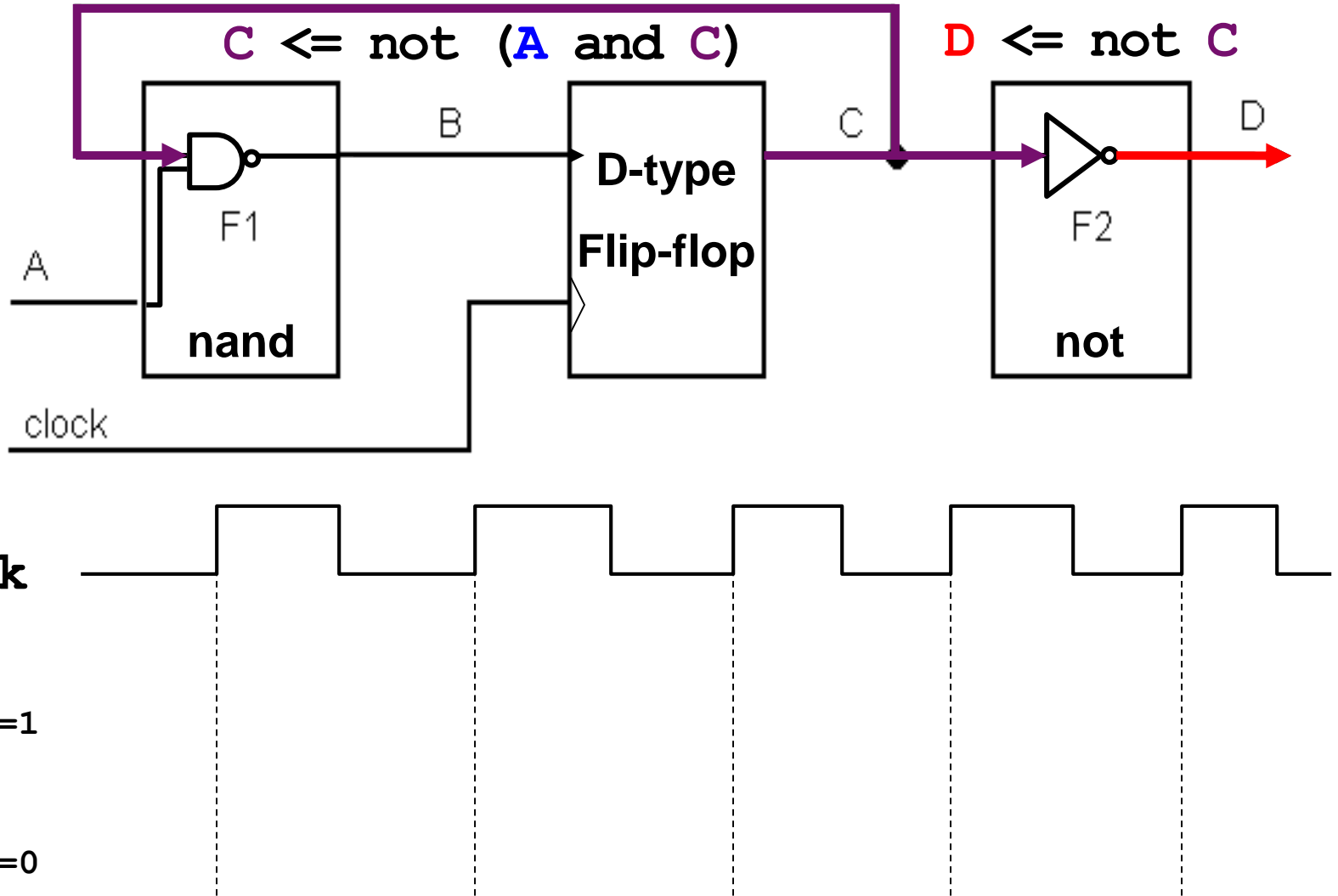
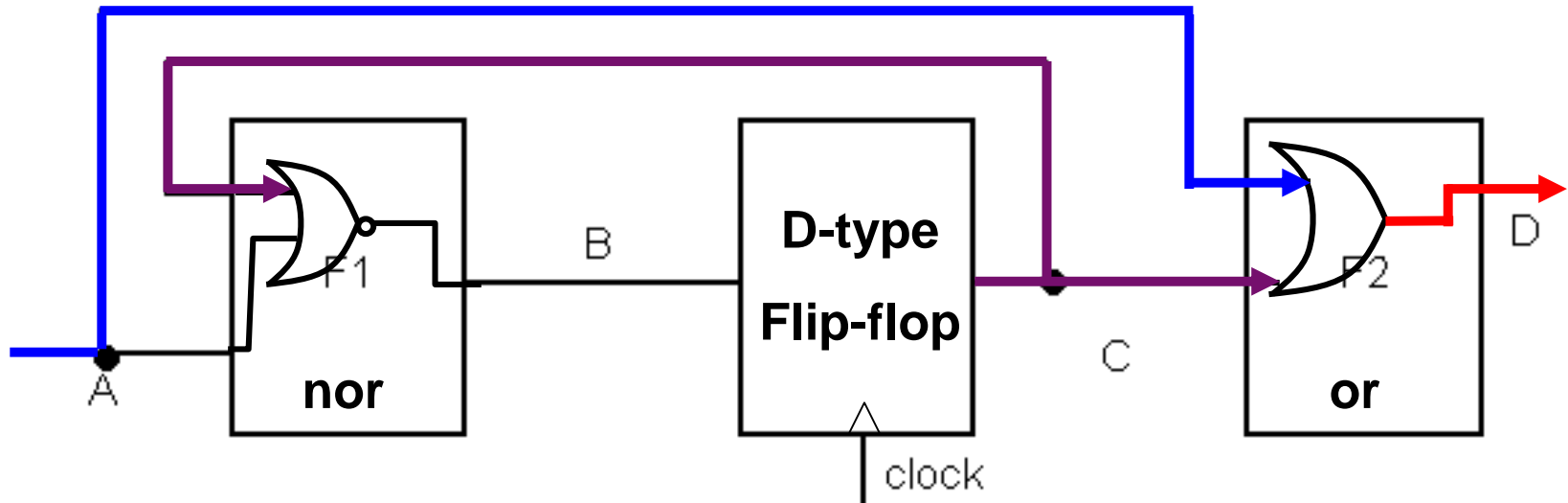
# Mealy Machine (1/2)



- **Mealy Machine:**
  - **Outputs** are a function of the present **state** and **inputs**.
- An Example of Mealy Machine:  
**F1:  $C \leftarrow \text{not}(A \text{ or } C)$  ; -- " $\leftarrow$ " is a **flip-flop****  
**F2:  $D \leftarrow (A \text{ or } C)$  ; -- **Mealy Machine****



*B is the current output of  $\text{not}(A \text{ or } C)$ , but B does not need to exist.  
Writing  $C \leftarrow \text{not}(A \text{ or } C)$  is enough.*



# Mealy Machine (2/2)



architecture mealy\_arch of some\_entity is

```
signal C: std_logic;
```

```
begin
```

```
process (A,C) -- combinational logic
```

```
begin
```

```
 D <= (A or C); -- Mealy Machine
```

```
end process;
```

```
process (clock, reset) -- sequential logic
```

```
begin
```

```
 if reset = '1' then c <= '0';
```

```
 elsif rising_edge(clock) then
```

```
 C <= not (A or C); -- flip-flop
```

```
 end if;
```

```
end process;
```

```
end mealy_arch;
```

← F2



← F1

# Class Exercise 5.10

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

 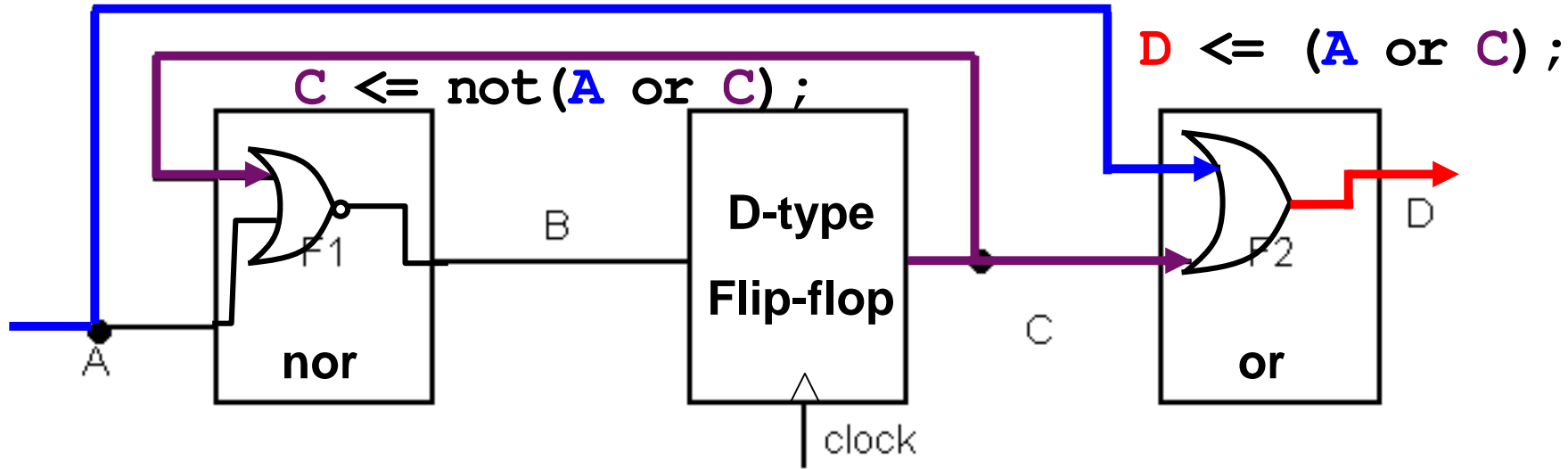- Draw the waveforms of C and D (initially C=0)




# VHDL Coding Tips and Styles



- Separating the combinational and sequential logics.
  - Try to use at least two processes: one contains all combinational logic & the other contains all sequential logic.
- Keeping each process as simple (small) as possible.
  - Try to partition a large process into multiple small ones based on the signals in the sensitivity list.
- Putting every signal that your process needs to know about changes to be in the sensitivity list.
- Avoiding assigning a signal from multiple processes.
  - It may cause the “multi-driven” issue.

# Recall: What we have done in Lab06

 

entity sevenseg is

```
port (
 clk : in STD_LOGIC;
 switch : in STD_LOGIC_VECTOR (7 downto 0);
 btn : in STD_LOGIC;
 ssd : out STD_LOGIC_VECTOR (6 downto 0);
 ssdcats : out STD_LOGIC);
```

end sevenseg; underline: external I/O pins

- *Task1: Display the input number (XY) in hexadecimal*
- *Task2: Count down from the input number (XY) to (00)*

# Example: Lab06 (1/2)



```
-- generate 1ms and 1s clocks
process (clk)
begin
 if rising_edge(clk) then
 if (s_count = 49999999) then
 s_pulse <= not s_pulse;
 s_count <= 0;
 else
 s_count <= s_count + 1;
 end if;
 if (ms_count = 49999) then
 ms_pulse <= not ms_pulse;
 ms_count <= 0;
 else
 ms_count <= ms_count + 1;
 end if;
 end if;
end process;

-- read button (combinational)
process (btn)
begin
 if rising_edge(btn) then
 counter_en <= not counter_en;
 end if;
end process;
```

```
-- count down
process (s_pulse)
begin
 if rising_edge(s_pulse) then
 if (counter_en = '1') then
 if (counter = 0) then
 counter <= to_integer(
 unsigned(switch));
 else
 counter <= counter - 1;
 end if;
 end if;

 counter_vec <= std_logic_vector(
 to_unsigned(counter, 8));
 end if;
end process;
```

```
-- update the seven segment display
process (ms_pulse)
 ... -- see the next page
end process;
```

```
-- output ssd (combinational)
process (digit)
 ... -- see the next page
end process;
```

# Example: Lab06 (2/2)



```
-- generate 1ms and 1s clocks
process (clk)
begin
 if rising_edge(clk) then
 if (s_count = 49999999) then
 s_pulse <= not s_pulse;
 s_count <= 0;
 else
 s_count <= s_count + 1;
 end if;
 if (ms_count = 49999) then
 ms_pulse <= not ms_pulse;
 ms_count <= 0;
 else
 ms_count <= ms_count + 1;
 end if;
 end if;
end process;

-- read button (combinational)
process (btn)
begin
 if rising_edge(btn) then
 counter_en <= not counter_en;
 end if;
end process;
```

```
-- count down
process (s_pulse)
 .. -- see the previous page
end process;

-- update the seven segment display
process (ms_pulse)
begin
 if ms_pulse='1' then
 if (counter_en = '1') then
 digit <= counter_vec(7 downto 4);
 else
 digit <= switch(7 downto 4);
 end if;
 else
 if (counter_en = '1') then
 digit <= counter_vec(3 downto 0);
 else
 digit <= switch(3 downto 0);
 end if;
 end if;
 ssdcat <= ms_pulse; -- select display
end process;

-- output ssd (combinational)
process (digit)
begin
 case digit is
 when "0000" => ssd <= "1111110";
 ...
 end case;
end process;
```



- Finite State Machine (FSM)
  - Clock Edge Detection
  - Feedback
- Use of Signals and Variables
  - Outside Process: Concurrent Statement
  - Inside Process: Sequential Statement
    - Combinational Process
    - Clocked Process
- Types of FSMs: Moore vs. Mealy
- **Practical Examples**
  - Up/Down Counter
  - Pattern Generator

# Example 1) Up/Down Counter



- **Up/Down Counters:** Generate a sequence of gradually increasing or decreasing **counting patterns** according to the clock and inputs.
  - **Synchronous Clock:** All clock inputs of state registers (i.e., flip-flops) are connected.
    - More complex to design
    - More logic
    - Less time delay at outputs
  - **Asynchronous Clock:** The output of one state register (i.e., flip-flop) is the clock of another state register.
    - Easier to design
    - Less logic
    - More time delay at outputs



# 4-Bit Sync. Clock Down Counter



entity sync\_counter is

```
port(CLK: in std_logic;
```

```
RESET: in std_logic;
```

```
COUNT: inout std_logic_vector(3 downto 0));
```

```
end sync_counter ;
```

architecture sync\_counter\_arch of sync\_counter is

```
begin
```

```
process (CLK, RESET) ← synchronous clock, asynchronous reset
```

```
begin
```

```
if(RESET = '1') then COUNT <= "0000";
```

```
else All clock inputs of state registers (i.e., flip-flops) are connected.
```

```
if(rising_edge(CLK)) then
```


```
 COUNT <= COUNT - 1; ← counting
```

```
end if;
```

```
end if;
```

```
end process;
```

```
end sync_counter_arch;
```

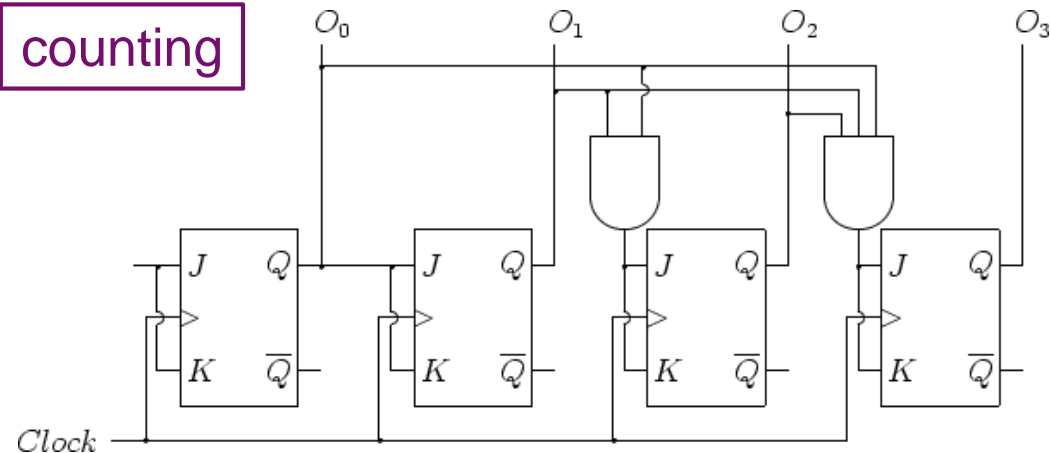

# 4-Bit Async. Clock Down Counter



Asynchronous Clock Counter  
(a.k.a. Ripple Counter)

```
entity async_counter is
 port(CLK: in std_logic;
 RESET: in std_logic;
 COUNT: inout std_logic_vector(3 downto 0));
end async_counter ;
architecture async_counter_arch of async_counter is
begin
 process (RESET, CLK, COUNT (0), COUNT (1), COUNT (2))
 begin
 if RESET = '1' then
 COUNT <= "0000";
 else
 The output of one state register is the clock of another state register.
 if(rising_edge(CLK)) then COUNT (0) <=not COUNT (0); end if;
 if(rising_edge(COUNT (0))) then COUNT (1) <=not COUNT (1); end if;
 if(rising_edge(COUNT (1))) then COUNT (2) <=not COUNT (2); end if;
 if(rising_edge(COUNT (2))) then COUNT (3) <=not COUNT (3); end if;
 end if;
 end process;
end async_counter_arch;
```


Asynchronous clocks

Each assignment is a flip-flop
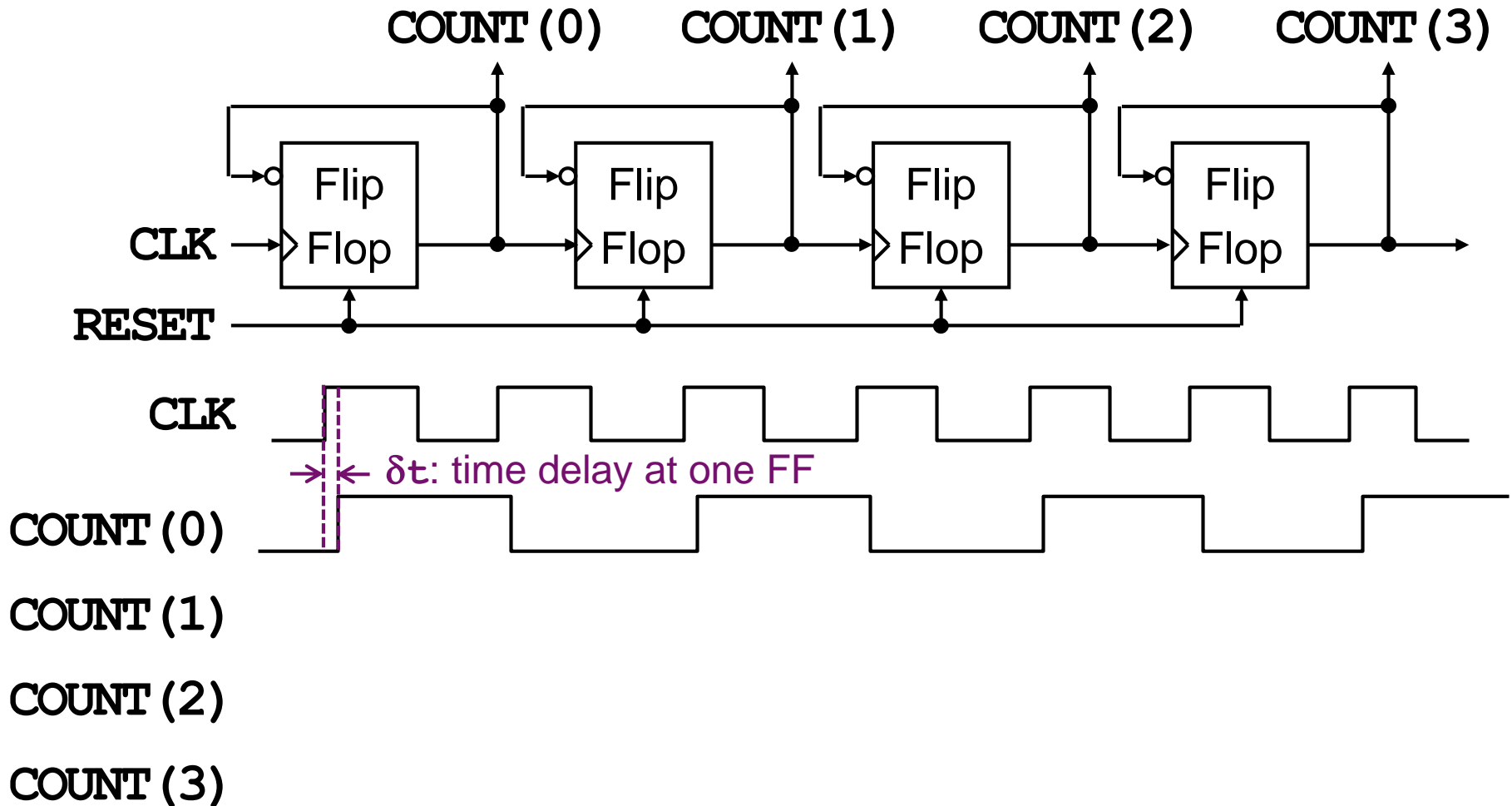
# Class Exercise 5.11

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_  
Name: \_\_\_\_\_

- Draw the waveforms of COUNT (0) ~ COUNT (3) to show the time delays of a 4-bit async. clock counter:



# Example 2) Pattern Generator



- **Pattern Generator:** Generates any pattern we want.
  - Example: the control unit of a CPU, memory controller, traffic light, etc.
- Encoding methods for representing patterns/states:
  - **Binary Encoding:** Using  $N$  flip-flops to represent  $2^N$  states.
    - Less flip-flops but more combinational logics
  - **One-hot Encoding:** Using  $N$  flip-flops for  $N$  states.
    - More flip-flops but less combination logic
  - *Xilinx default setting is one-hot encoding.*
    - *Change at synthesis → options*
    - *<http://www.xilinx.com/itp/xilinx4/data/docs/sim/vtex9.html>*

# Class Exercise 5.12

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

- How many states can a 4-bit counter have?

Answer: \_\_\_\_\_


- Under binary and one-hot encoding schemes, how many bits for the state registers are required, respectively, if you need:

|                  | Binary | One-Hot |
|------------------|--------|---------|
| <b>4 States</b>  |        |         |
| <b>9 States</b>  |        |         |
| <b>21 States</b> |        |         |
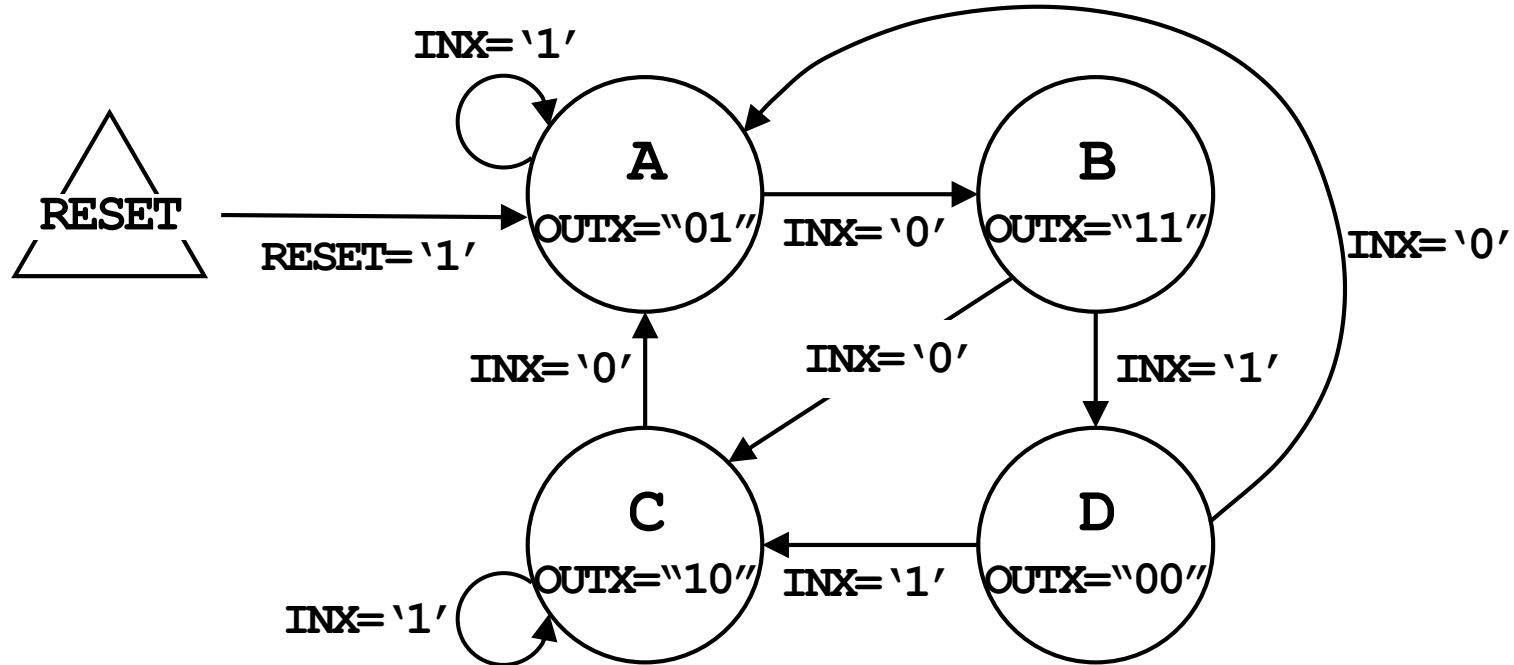
# Class Exercise 5.13

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_  
Name: \_\_\_\_\_

- Given the following machine of 4 states: **A**, **B**, **C** and **D**.



- The machine has an asynchronous **RESET**, a clock signal **CLK** and a 1-bit synchronous input signal **INX**.
- The machine also has a 2-bit output signal **OUTX**.
- Write the complete VHDL program for the design.
- Is this a Moore or Mealy Machine?

# Class Exercise 5.13

Student ID: \_\_\_\_\_ Date: \_\_\_\_\_

Name: \_\_\_\_\_

```
library IEEE;
use IEEE.std_logic_1164.all;
entity ex is port(
 RESET,CLOCK,INX: in STD_LOGIC;
 OUTX: out STD_LOGIC_VECTOR(1 downto 0));
end x7e;
architecture ex_arch of ex is
type state_type is (A,B,C,D);
signal s: state_type;
begin
process(CLOCK, RESET) -- sequential
begin
 if _____ then
 s <= ___;
 OUTX <= "___";
 elsif _____ then
 case s is
 when A =>
 if INX = '___' then s <= ___;
 else s <= ___; end if;

```

```
 when B =>
 if INX = '___' then s <= ___;
 else s <= ___; end if;
 when C =>
 if INX = '___' then s <= ___;
 else s <= ___; end if;
 when D=>
 if INX = '___' then s <= ___;
 else s <= ___; end if;
 end case;
 end if;
end process;
process(s) -- combinational
begin
 case s is
 when A => OUTX <= "___";
 when B => OUTX <= "___";
 when C => OUTX <= "___";
 when D => OUTX <= "___";
 end process;
end ex_arch;
```

Moore or Mealy?



- Finite State Machine (FSM)
  - Clock Edge Detection
  - Feedback
- Use of Signals and Variables
  - Outside Process: Concurrent Statement
  - Inside Process: Sequential Statement
    - Combinational Process
    - Clocked Process
- Types of FSMs: Moore vs. Mealy
- Practical Examples
  - Up/Down Counter
  - Pattern Generator