



香港中文大學
The Chinese University of Hong Kong

CENG3430 Rapid Prototyping of Digital Systems

Lecture 10:

VHDL versus Verilog

Ming-Chang YANG

mcyang@cse.cuhk.edu.hk





Outline

- **VHDL vs. Verilog**
 - Background
 - Popularity and Syntax
 - Operators
 - Overall Structure
 - External I/O Declaration
 - Concurrent Statement
 - Blocking/Non-blocking Statement
 - Wire vs. Reg
 - Structural Design
 - Design Constructions
 - Case Study: Flip-flop

VHDL

Very High Speed Integrated Circuit
Hardware Description Language

Verilog[®]
HDL


The logo features the word "Verilog" in yellow with a registered trademark symbol, and "HDL" in red. Below the text is a row of binary digits: 1 0 1 0 1 0 1 0 1 0 1 0.



What are VHDL and Verilog?

VHDL

 Very High Speed Integrated Circuit
Hardware Description Language



- They are both **hardware description languages** for **modeling hardware**.
- They are each a **notation** to describe the **behavioral** and **structural** aspects of an electronic digital circuit.



Popularity and Syntax

VHDL

Very High Speed Integrated Circuit
Hardware Description Language

Verilog

HDL

Popularity

VHDL is more popular with
European companies.

Verilog is more popular with
US companies.

Programming Style (Syntax)

VHDL is similar to **Ada**
programming language.

Verilog is similar to **C/Pascal**
programming language.

VHDL is **NOT** case-sensitive.

Verilog is **case-sensitive**.

VHDL is more “**verbose**” than **Verilog**.



Outline

- **VHDL vs. Verilog**

- Background
- Popularity and Syntax
- Operators
- Overall Structure
- External I/O Declaration
- Concurrent Statement
- Blocking/Non-blocking Statement
- Wire vs. Reg
- Structural Design
- Design Constructions
- Case Study: Flip-flop

VHDL

Very High Speed Integrated Circuit
Hardware Description Language

Verilog[®]

HDL

101001110110



Operators

	VHDL	Verilog		VHDL	Verilog
Add	+	+	Bitwise Negation	not	~
Subtract	-	-	Bitwise NAND	nand	~&
Multiplication	*	*	Bitwise NOR	nor	~
Division	/	/	Bitwise XNOR	xnor	~^
Modulo	mod	%	Greater (or Equal)	>, >=	>, >=
Absolute	abs	N/A	Less (or Equal)	<, <=	<, <=
Exponentiation	**	**	Logical Equality	=	==
Concatenation	&	{ , }	Logical Inequality	/=	!=
Left Shift	sll	<<	Logical AND	and	&&
Right Shift	srl	>>	Logical OR	or	
Bitwise AND	and	&	Logical Negation	not	!
Bitwise OR	or		Case Equality	N/A	==
Bitwise XOR	xor	^	Case Inequality	N/A	!=



Overall Structure

VHDL (.vhd)

-- *Library Declaration*

```
library IEEE;
```

...

-- *Entity Declaration*

```
entity ex is
```

...

```
end ex
```

-- *Architecture Body*

```
architecture arch of ex is
```

```
begin
```

...

```
end arch;
```

Verilog (.v)

// *One Module*

```
module ex ( ... );
```

...

```
endmodule
```



External I/O Declaration

VHDL

-- Entity Declaration

```
entity ex is
  port(a, b: in std_logic;
       c: in std_logiv_vector(3
       down to 0),
       y: out std_logic);
```

```
end ex
```

-- Architecture Body

```
architecture arch of mux is
```

```
begin
```

```
...
```

```
end ex;
```

Verilog

// One Module

```
// One Module
module ex ( a, b, c, y );
  input a, b;
  input[3:0] c;
  output y;
```

or

```
module ex (
  input a, input b,
  input[3:0] c, output y );
```

```
...
```

```
endmodule
```



Statements

VHDL

-- Entity Declaration

```
entity ex is
```

```
...
```

```
end ex
```

```
architecture arch of ex is
```

```
begin
```

-- concurrent statements

```
process ( sensitivity list )
```

```
begin
```

```
    -- sequential statements
```

```
end process;
```

```
end arch;
```

Verilog

// One Module

```
module ex ( ... );
```

-- concurrent statements

```
always @ ( sen. list or event )  
begin
```

```
    -- blocking/non-blocking  
    statements
```

```
end
```

```
endmodule
```



1) Concurrent Statement

VHDL: inside architecture body, outside the process

```
signal a, b: std_logic_vector(7 downto 0); -- array
signal c, d, e: std_logic;
a(3 downto 0) <= b(7 downto 4);
b(7 downto 4) <= "0000";
c <= d and e; -- bitwise AND
```

LHS <= RHS;

- LHS must be **signal**.
- The **LHS** will be updated whenever **RHS** changes.

Verilog: outside the always@ block

```
wire [7:0] a, b; //array
wire c, d, e;
assign a[3:0] = b[7:4];
assign b[7:4] = 'b0000; //binary
assign c = d & e; //bitwise AND
```

assign LHS = RHS;

- LHS must be **wire**.
- The **LHS** will be updated whenever **RHS** changes.

Class Exercise 10.1

Student ID: _____ Date:
Name: _____

- Translate the following VHDL program to Verilog:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity abc is
    port (a,b,c: in std_logic;
          y: out std_logic);
end abc;
architecture abc_arch of
abc is
signal x : std_logic;
begin
    x <= a nor b;
    y <= x and c;
end abc_arch;
```



2) Blocking/Non-blocking Statement

VHDL

```
architecture arch of ex is module ex (...);  
begin  
process ( sensitivity list )  
variable a, b, c;  
begin  
-- LHS could be signals  
(suggested) or variables  
-- signal assignment (<=)  
-- variable assignment (:=)  
end;  
end arch;
```

Verilog

```
// LHS must be reg (not wire)  
reg a, b, c;  
always @( sen. list or event )  
begin  
// blocking assignment (=)  
// non-blocking assignment (<=)  
end  
endmodule
```

2) Blocking Statement

- **Blocking assignments (=)** in a sequential block (i.e., `always@`) are executed before the execution of the statements that follow it.
 - All blocking assignments are executed in a **sequential** way.
- **Usage:** Use blocking assignments in `always@` blocks to synthesize combinational logic (i.e., **no clock!**).

```

reg r1, r2, r3;
...
always @ (a, b)
begin
    r1 = a & b;
    r2 = a | b;
    r3 = r1 | r2;
end

```

sensitivity list (a, b) OR (a or b)

Class Exercise 10.2

Student ID: _____ Date: _____
Name: _____

- Translate the following Verilog program to VHDL:


```
reg r1, r2, r3;  
...  
always @ (a, b)  
begin  
    r1 = a & b;  
    r2 = a | b;  
    r3 = r1 | r2;  
end
```

2) Non-blocking Statement

- Non-blocking assignments ($<=$) in a sequential block (i.e., `always@`) are executed within the same time step regardless of the order.
 - All non-blocking assignments will take effect at the next clock edge (concurrently, **not sequentially!**).
- Usage:** Use non-blocking assignments in `always@` blocks to synthesize sequential logic (i.e., **has clock!**).


```

 reg r1, r2;
...
always @ (posedge clk)
begin
  → r1 <= a;
  → r2 <= r1;
end
  
```





Edge Detection

 

VHDL

```
process (clk)
begin
...
if rising_edge(CLK)
    or
if falling_edge(CLK)
    ...
end
```

Verilog

```
always @ (posedge clk)
or
always @ (negedge clk)
begin
...
end
```

Class Exercise 10.3

Student ID: _____ Date: _____
Name: _____

- Translate the following Verilog program to VHDL:

```
reg r1, r2;  
...  
always @ (posedge clk)  
begin  
    r1 <= a;  
    r2 <= r1;  
end
```



“wire” vs. “reg” in Verilog

- **Wire:** Has no memory
 - It must be **physical wire** in the circuit.
 - It does not hold the value.
 - **Usage:** Cannot use “**wire**” in the LHS of assignments inside always@ blocks!
- **Reg:** Has memory
 - It could be a **flip-flop** or a **physical wire**.
 - It holds the value until a new value is assigned.
 - **Usage:** Cannot use “**reg**” in the LHS of assignments outside always@ blocks!



Outline

- **VHDL vs. Verilog**


- Background
- Popularity and Syntax
- Operators
- Overall Structure
- External I/O Declaration
- Concurrent Statement
- Blocking/Non-blocking Statement
- Wire vs. Reg
- Structural Design
- Design Constructions
- Case Study: Flip-flop

VHDL
Very High Speed Integrated Circuit
Hardware Description Language

Verilog^{*}
HDL
1010101010101010

Structural Design in VHDL (1/2)

 - Structural Design in VHDL: Like a circuit but describe it by text.



- **Design Steps:**
 - Step 1:** Create **entities**
 - Step 2:** Create **components** from **entities**
 - Step 3:** Use “**port map**” to relate the components

Structural Design in VHDL (2/2)

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity and2 is
4 port (a,b: in STD_LOGIC;
5       c: out STD_LOGIC );
6 end and2;
7 architecture and2_arch of and2 is
8 begin
9   c <= a and b;
10 end and2_arch;
11 -----

```

Step 1

```

12 library IEEE;
13 use IEEE.STD_LOGIC_1164.ALL;
14 entity or2 is
15 port (a,b: in STD_LOGIC;
16       c: out STD_LOGIC );
17 end or2;
18 architecture or2_arch of or2 is
19 begin
20   c <= a or b;
21 end or2_arch;

```

Step 1

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 -----
4 entity test is
5 port ( in1: in STD_LOGIC; in2: in STD_LOGIC;
6        in3: in STD_LOGIC;
7        out1: out STD_LOGIC );
8 end test;
9 architecture test_arch of test is

```

```

10 component and2 --create component
11   port (a,b: in std_logic; c: out std_logic);
12 end component ;
13 component or2 --create component
14   port (a,b: in std_logic; c: out std_logic);
15 end component ;

```

```

16 signal inter_sig: std_logic;
17 begin
18   label1: and2 port map (in1, in2, inter_sig);
19   label2: or2 port map (inter_sig, in3, out1);
20 end test_arch;

```

Step 2

Step 3





Structural Design in Verilog (1/2)

- Structural Design in Verilog: One top module, several (sub) modules.



Connected by relating I/O and internal wires

- **Design Steps:**
 - Step 1:** Create (sub) **module(s)** (usually in separate .v files)
 - Step 2:** Define a **top-module** to interconnect **module(s)**

Structural Design in Verilog (2/2)

and2.v

```
module and2 (           Step 1
    input a,
    input b,
    output c
);
assign c = a & b;
endmodule
```

or2.v

```
module or2 (           Step 1
    input a,
    input b,
    output c
);
assign c = a | b;
endmodule
```

top_module.v


```
module top_module(           Step 2
    input in1, input in2, input in3,
    output out1 );
    wire inter_sig;
    and2 and2_ins(
        .a(in1),
        .b(in2),
        .c(inter_sig)
    );
    or2 or2_ins(
        .a(inter_sig),
        .b(in3),
        .c(out1)
    );
endmodule
```



Class Exercise 10.4

Student ID: _____ Date: _____
Name: _____

 - Implement the following circuit in Verilog:





Outline

- **VHDL vs. Verilog**


- Background
- Popularity and Syntax
- Operators
- Overall Structure
- External I/O Declaration
- Concurrent Statement
- Blocking/Non-blocking Statement
- Wire vs. Reg
- Structural Design
- Design Constructions
- Case Study: Flip-flop

VHDL

**Very High Speed Integrated Circuit
Hardware Description Language**

Verilog[®]
HDL

Design Constructions (1/4)

 

VHDL: when-else (*outside process*)

architecture arch of ex is

begin

```
    out1 <= '1' when in1 = '1' and in2 = '1' else '0';
```

end arch ex_arch;

Verilog: assign ? : (*outside always@ block*)

module ex (...);


```
    assign out1 = (in1=='b1 && in2=='b1) ? 'b1 : 'b0;
```

// 'b: binary; 'o: octal; 'd: decimal; 'h: hexadecimal

endmodule



Design Constructions (2/4)

 

VHDL: if-then-else
(inside process)


```
process(in1, in2)
begin
  if in1='1' and in2='1'
  then
    out1 <= '1';
  else
    out1 <= '0';
  end if;
end process;
```

Verilog: if-else
(inside always@)

```
always @ (in1, in2)
begin
  if (in1=='b1 && in2=='b1)
  begin
    out1 = 'b1;
  end
  else
  begin
    out1 = 'b0;
  end
end
```



Design Constructions (3/4)

 


VHDL: **case**-**when** *(inside process)*

```
process (b)
begin
    case b is
        when "00" | "11" =>
            out1 <= '0';
            out2 <= '1';
        when others      =>
            out1 <= '1';
            out2 <= '0';
    end case;
end process;
```

Verilog: **case** *(inside always@)*

```
always @ (b)
begin
    case (b)
        'b00 || 'b11:
            out1 = 'b0;
            out2 = 'b1;
        default:
            out1 = 'b1;
            out2 = 'b0;
    endcase
end
```

Design Constructions (4/4)

 

VHDL: for-in-to-loop
(inside process)

```

process (in1)
begin
  for i in 0 to 3 loop
    out1(i) <= not in1(i);
  end loop;
end process;
  
```

Verilog: for-loop
(inside always@)

```

always @ (in1)
begin
  for (idx=0; idx<4; idx+=1)
  begin
    out1[idx] = ~in1[idx];
  end
end
  
```



Outline

- **VHDL vs. Verilog**

- Background
- Popularity and Syntax
- Operators
- Overall Structure
- External I/O Declaration
- Concurrent Statement
- Blocking/Non-blocking Statement
- Wire vs. Reg
- Structural Design
- Design Constructions
- Case Study: Flip-flop

VHDL

**Very High Speed Integrated Circuit
Hardware Description Language**

Verilog^{*}
HDL

101010101010

Posedge Flip-flop with Sync Reset (1/2)

VHDL

```
entitydffis
port(D,CLK,RESET:
      in std_logic;
      Q: out std_logic);
enddff;
architecturedff_archof
dffisbegin
process(CLK)begin
  if rising_edge(CLK)then
    if (RESET = '1')then
      Q <= '0';
    else
      Q <= D;
    endif;
  endif;
endprocess;
enddff_arch;
```

Verilog

```
moduledff(
  inputD,
  inputCLK,
  inputRESET,
  output regQ);
  always @ (posedge CLK)
  begin
    if (RESET)
      begin
        Q <= 1'b0;
      end
    else
      begin
        Q <= D;
      end
    end
  endmodule
```

Posedge Flip-flop with Sync Reset (2/2)

VHDL

- Input must be **wire**.
- Output could be either **wire** or **reg**.
 - The default option is **wire**.
 - But you can specify an **output** as **wire** or **reg** depending on how you will assign it a value.

unit is begin

```
process(CLK) begin
    if rising_edge(CLK) then
        if (RESET = '1') then
            Q <= '0';
        else
            Q <= D;
        end if;
    end if;
end process;
end dff_arch;
```

Verilog

```
module dff(
    input D,
    input CLK,
    input RESET,
    output reg Q);
    always @ (posedge CLK)
        begin
            if (RESET)
                begin
                    Q <= 1'b0;
                end
            else
                begin
                    Q <= D;
                end
        end
    end
endmodule
```

Posedge Flip-flop with Async Reset (1/2)

VHDL

```
entitydffis
port(D,CLK,RESET:
      in std_logic;
      Q: out std_logic);
enddff;
architecturedff_archof
dffisbegin
process(CLK,RESET) begin
  if (RESET = '1')
  then
    Q <= '0';
  elsif rising_edge(CLK)
  then
    Q <= D;
  end if;
end process;
enddff_arch;
```

Verilog


```
moduledff(
  input D,
  input CLK,
  input RESET,
  output reg Q);
  always @ (posedge CLK or
            posedge RESET)
    begin
      if (RESET)
        begin
          Q <= 1'b0;
        end
      else
        begin
          Q <= D;
        end
    end
  end
endmodule
```

Posedge Flip-flop with Async Reset (2/2)

VHDL

```
entitydffis  
port(D,CLK,RESET:  
      in std_logic;  
      Q: out std_logic);  
end entity;
```

 
Question: What if we do not specify “**posedge**” for the **RESET** signal?



Verilog

```
moduledff(  
  input D,  
  input CLK,  
  input RESET,  
  output reg Q);  
  always @ (posedge CLK or  
            posedge RESET)  
    begin  
      if (RESET)  
        begin  
          Q <= 1'b0;  
        end  
      else  
        begin  
          Q <= D;  
        end  
    end  
endmodule
```

 ! [Synth 8-434] mixed level sensitive and edge triggered event controls are **not supported** for synthesis!



Summary

- **VHDL vs. Verilog**

- Background
- Popularity and Syntax
- Operators
- Overall Structure
- External I/O Declaration
- Concurrent Statement
- Blocking/Non-blocking Statement
- Wire vs. Reg
- Structural Design
- Design Constructions
- Case Study: Flip-flop

VHDL
Very High Speed Integrated Circuit
Hardware Description Language

