

CENG4480 Homework 1

Due: Oct. 21, 2018

- **Small-Signal Gain:** For given amp circuits, small changes of input ΔV_{in} will cause output change of ΔV_{out} . Small-signal gain is defined by $\frac{\Delta V_{out}}{\Delta V_{in}}$.

Q1 (10%) Given a non-inverting amplifier as shown in Figure 1, $R_1 = 3R_2$ and $A_0 = 1000$, calculate the exact finite gain. Then determine the gain difference if the circuit is expected to have an ideal gain under $A_0 = \infty$.

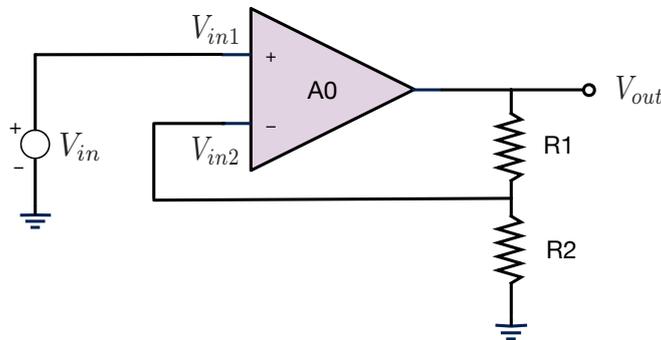


Figure 1: Non-inverting Amplifier.

A1 From the properties of Op Amplifier,

$$V_{out} = A_0(V_{in1} - V_{in2}) \quad (1)$$

Given that,

$$V_{in2} = \frac{R_2}{R_1 + R_2} V_{out} \quad (2)$$

Substituting into (1) we have,

$$G_{real} = \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0} \quad (3)$$

Besides,

$$G_{ideal} = \left(1 + \frac{R_1}{R_2}\right) \quad (4)$$

Substituting data into Eqs. (3) and (4),

$$G_{real} = 3.98, G_{ideal} = 4 \quad (5)$$

Thus, real circuit gain has a 0.5% difference from ideal gain.

Q2 (10%) An op-amp exhibits the following nonlinear characteristic:

$$V_{out} = \alpha \arctan[\beta(V_{in1} - V_{in2})]. \quad (6)$$

Determine the small-signal gain of the op amp in the case $V_{in1} \approx V_{in2}$. (Hint: use Taylor expansion of arctan and definition of aforementioned small-signal gain.)

A2 Taylor expansion of arctan has the following form:

$$\arctan(Z) = Z - \frac{1}{3}Z^3 + \frac{1}{5}Z^5 - \dots \quad (7)$$

When $V_{in1} \approx V_{in2}$,

$$V_{out} \approx \alpha\beta(V_{in1} - V_{in2}) \quad (8)$$

Thus, small-signal gain is,

$$\frac{dV_{out}}{d(V_{in1} - V_{in2})} = \alpha\beta \quad (9)$$

Q3 (10%) In the circuit of Figure 2, $R_1 = R_2 = R' = R_f = R = 100k\Omega$ and $C = 1\mu F$. Assume the op-amps are ideal.

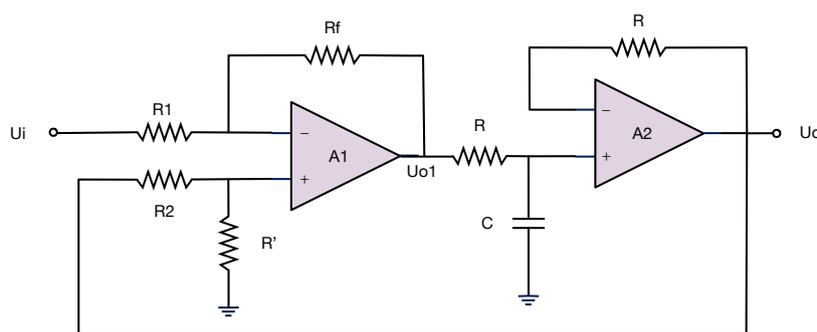


Figure 2: Voltage Follower.

1. (6%) The relationship between U_i and U_o (U_{o1} is unknown).
2. (4%) Assume that when the time $t = 0$, $U_o = 0V$ and U_i jumps from $0V$ to $-1V$. How long will the U_o take to change from $0V$ to $6V$?

A3 1. Because A_2 is a voltage follower (the voltage on the capacitance $U_c = U_o$), so we can obtain U_{o1}

$$U_{o1} = -\frac{R_f}{R_1}U_i + \left(1 + \frac{R_f}{R_1}\right) \frac{R'}{R_2 + R'}U_o = U_o - U_i \quad (10)$$

The voltage on the capacitance $U_c = U_o$, so the current of the capacitance is

$$i_C = \frac{U_{o1} - U_o}{R} = -\frac{U_i}{R} \quad (11)$$

And

$$U_o = \frac{1}{C} \int_{-\infty}^t i_c dt = -\frac{1}{RC} \int_{-\infty}^t U_i dt = -10 \int_{-\infty}^t U_i dt \quad (12)$$

2. We can get $U_o = -10 \int_0^t U_i dt = 10t = 6$. So $t = 0.6 \text{ sec}$

Q4 (15%) Determine the output voltage (i.e. the mathematical expression of $V_{out}(t)$) for the integrator circuit of Figure 3a if the input is a square wave of amplitude $\pm A$ and period T shown in Figure 3b. Assume $T = 10 \text{ ms}$, $C_F = 1 \mu\text{F}$, $R_s = 10 \text{ k}\Omega$ and ideal op-amp. The square wave starts at $t = 0$ and therefore $V_{out}(0) = 0$.

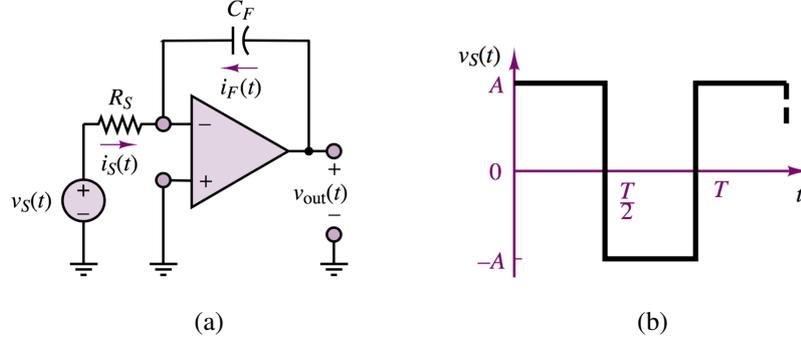


Figure 3: (a) Op-amp integrator; (b) Input of a square wave.

A4 We write the expression for the output of the integrator:

$$\begin{aligned}
 v_{out}(t) &= -\frac{1}{R_s C_F} \int_{-\infty}^t v_s(t') dt' \\
 &= -\frac{1}{R_s C_F} \left(\int_{-\infty}^0 v_s(t') dt' + \int_0^t v_s(t') dt' \right) \\
 &= -\frac{1}{R_s C_F} \int_0^t v_s(t') dt'. \tag{13}
 \end{aligned}$$

Next, we note that we can integrate the square wave in a piecewise fashion by observing that $v_s(t) = A$ for $0 \leq t < T/2$ and $v_s(t) = -A$ for $T/2 \leq t < T$. We consider the first half of the waveform:

$$\begin{aligned}
 v_{out}(t) &= -\frac{1}{R_s C_F} \int_0^t v_s(t') dt' \\
 &= -100At \quad 0 \leq t < T/2, \tag{14}
 \end{aligned}$$

and

$$\begin{aligned}
 v_{out}(t) &= v_{out}\left(\frac{T}{2}\right) - \frac{1}{R_s C_F} \int_{T/2}^t v_s(t') dt' \\
 &= -100A \frac{T}{2} + 100A \left(t - \frac{T}{2}\right) \\
 &= -100A(T - t) \quad T/2 \leq t < T. \tag{15}
 \end{aligned}$$

Since the waveform is periodic, the above result will repeat with period T , as shown in Figure 4.

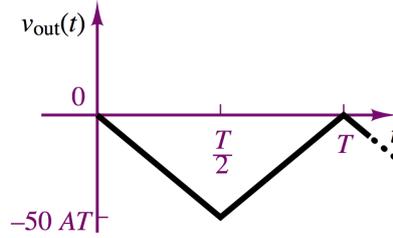


Figure 4: The sketch of output of integrator.

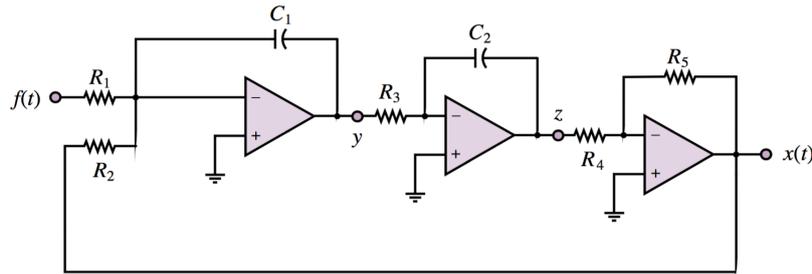


Figure 5: Analog computer simulation of unknown system.

Q5 (20%) Assume op-amps are ideal. Given $R_1 = 0.4\text{M}\Omega$, $R_2 = R_3 = R_5 = 1\text{M}\Omega$, $R_4 = 2.5\text{k}\Omega$ and $C_1 = C_2 = 1\mu\text{F}$, derive the differential equation corresponding to the analog computer simulator of Figure 5, i.e. the mathematical relationship between f and x . Note that $f(t)$ is input signal, y and z are outputs of corresponding op-amps.

A5 We start the analysis from the right-hand side of the circuit, to determine the intermediate variable z as a function of $x(t)$:

$$x = -\frac{R_5}{R_4}z = -400z. \quad (16)$$

Next, we move to the left to determine the relationship between y and z :

$$z = -\frac{1}{R_3 C_2} \int y(t') dt', \quad (17)$$

or

$$y = -\frac{dz}{dt}. \quad (18)$$

Finally, we determine y as a function of x and f :

$$\begin{aligned} y &= -\frac{1}{R_2 C_1} \int x(t') dt' - \frac{1}{R_1 C_1} \int f(t') dt' \\ &= -\int [x(t') + 2.5f(t')] dt', \end{aligned} \quad (19)$$

or

$$\frac{dy}{dt} = -x - 2.5f. \quad (20)$$

Substituting the expressions into one another and eliminating the variables y and z , we obtain the differential equation in x :

$$\begin{aligned} x &= -400z \\ \frac{dx}{dt} &= -400 \frac{dz}{dt} = 400y \\ \frac{d^2x}{dt^2} &= 400 \frac{dy}{dt} = -400(x + 2.5f). \end{aligned} \quad (21)$$

Q6 (10%) Let us consider the Schmitt Trigger shown in Figure 6

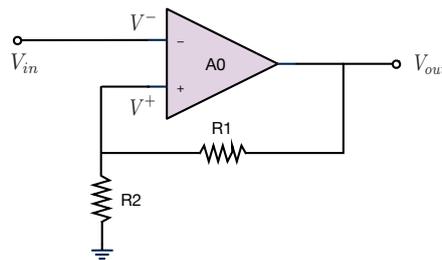


Figure 6: Schmitt Trigger.

1. (5%) Due to the manufacturing defects, a parasitic resistor R_3 occurs between the output node and ground, calculate the reference voltages.
2. (5%) If the parasitic device is a capacitor C , sketch v_{out} versus v_{in} . Label the key coordinates on the curve.

A6 1. According to the properties of comparator, when v_{in} is small, $v_{out} = v_{sat}$ and

$$\frac{v^+}{R_2} = \frac{v_{out} - v^+}{R_1}, \quad (22)$$

i.e.,

$$v^+ = \frac{R_2}{R_1 + R_2} v_{sat}. \quad (23)$$

Similarly, if v_{in} is large, we have

$$v^+ = -\frac{R_2}{R_1 + R_2} v_{sat}. \quad (24)$$

Therefore two reference voltages are given by $\frac{R_2}{R_1+R_2}v_{sat}$ and $-\frac{R_2}{R_1+R_2}v_{sat}$.

2. v_{out} start to change when v_{in} reaches references above. However, due to the existing capacitor, voltage cannot change immediately (Changes fast, then slowly).

Q7 (10%) Compute and sketch the output voltage of the op-amp in Fig. 8. Given $R_S = 1\text{k}\Omega$, $R_F = 10\text{k}\Omega$, $R_L = 1\text{k}\Omega$, $V_S^+ = 15\text{V}$, $V_S^- = -15\text{V}$, $v_s(t) = 2 \sin(1000t)$. Repeat the problem if $V_S^+ = 20\text{V}$ and $V_S^- = -20\text{V}$. Assume the op-amp is supply voltage-limited.

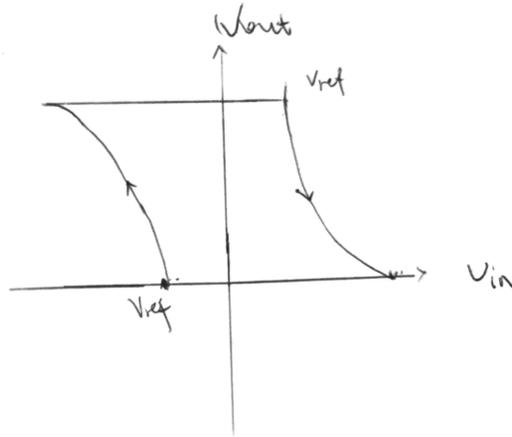


Figure 7: A6(2).

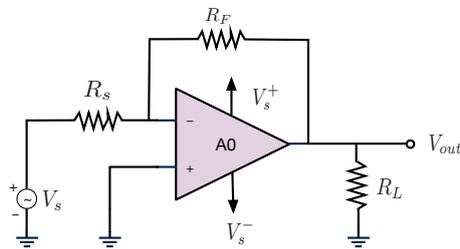


Figure 8: Inverting Amplifier.

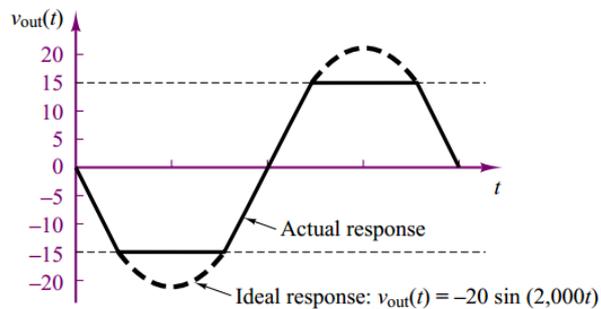


Figure 9: A7. Sketch of output voltage.

A7 The result will be the solid curve with $V_s^+ = 15\text{V}$ and $V_s^- = -15\text{V}$ (actual response); If $V_s^+ = 20\text{V}$ and $V_s^- = -20\text{V}$, the result will be dashed curve (ideal response).

Q8 (15%) Determine the closed-loop voltage gain as a function of frequency (i.e. $A(j\omega) = \frac{V_{out}(j\omega)}{V_s(j\omega)}$) for the op-amp circuit of Fig. 10. Assume the op-amp is ideal. Given only R_1 , R_2 and ω_0 , $R_2C = \frac{L}{R_1} = \omega_0$. (Hint: the impedance of an inductor L equals to $j\omega L$.)

A8 The expression for the gain of the filter of the filter of Fig. 10 can be determined by using

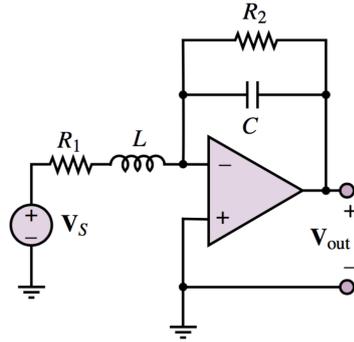


Figure 10: A second-order low-pass filter.

equation:

$$A(j\omega) = \frac{V_{out}(j\omega)}{V_s(j\omega)} = -\frac{Z_F(j\omega)}{Z_s(j\omega)}, \quad (25)$$

where

$$Z_F(j\omega) = R_2 \parallel j\omega C = \frac{R_2}{1 + j\omega C R_2} = \frac{R_2}{1 + j\omega\omega_0}, \quad (26)$$

and

$$Z_s(j\omega) = R_1 + j\omega L = R_1(1 + j\omega\omega_0). \quad (27)$$

Thus, the gain of the filter is:

$$A(j\omega) = -\frac{R_2}{R_1} \frac{1}{(1 + j\omega\omega_0)^2}. \quad (28)$$