

# CENG 3420

# Computer Organization & Design



## Lecture 02: Arithmetic and Logic Unit

**Bei Yu**

(Latest update: January 20, 2021)

Spring 2021

# Overview



Overview

Addition

Multiplication & Division

Shift

Floating Point Number

# Overview



Overview


Addition

Multiplication & Division

Shift

Floating Point Number

# Abstract Implementation View

 

# Arithmetic



Where we've been: **abstractions**


- ▶ Instruction Set Architecture (ISA)
- ▶ Assembly and machine language



Where we've been: **abstractions**


- ▶ Instruction Set Architecture (ISA)
- ▶ Assembly and machine language
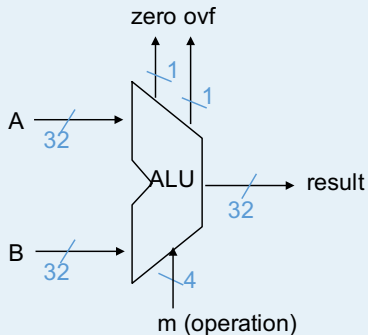
## What's up ahead: Implementing the ALU architecture





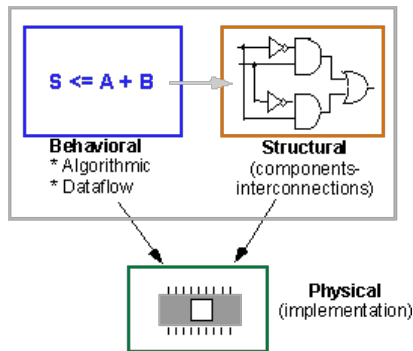
- ▶ Supports design, documentation, simulation & verification, and synthesis of hardware
- ▶ Allows integrated design at **behavioral** & **structural** levels




 
## Basic Structure

- ▶ Design **entity-architecture** descriptions
- ▶ Time-based execution (discrete event simulation) model







## Entity

defines externally visible characteristics

- ▶ Ports: channels of communication
  - ▶ signal names for inputs, outputs, clocks, control
- ▶ Generic parameters: define class of components
  - ▶ timing characteristics, size (fan-in), fan-out



## Architecture

defines the internal behavior or structure of the circuit

- ▶ Declaration of internal signals
- ▶ Description of behavior
  - ▶ collection of Concurrent Signal Assignment (CSA) statements (indicated by  $\leq$ );
  - ▶ can also model temporal behavior with the delay annotation
  - ▶ one or more processes containing CSAs and (sequential) variable assignment statements (indicated by  $:=$ )
- ▶ Description of structure
  - ▶ interconnections of components; underlying behavioral models of each component must be specified

# ALU VHDL Representation



```
entity ALU is
  port(A, B:  in std_logic_vector (31 downto 0);
        m:  in std_logic_vector (3 downto 0);
        result: out std_logic_vector (31 downto 0);
        zero: out std_logic;
        ovf: out std_logic)
end ALU;

architecture process_behavior of ALU is
  . . .
begin
  ALU: process (A, B, m)
  begin
    . . .
    result := A + B;
    . . .
  end process ALU;
end process_behavior;
```

# Machine Number Representation



- ▶ Bits are just bits (have no inherent meaning)\*
- ▶ Binary numbers (base 2) – **integers**

Of course, it gets more complicated:

- ▶ **storage locations** (e.g., register file words) are finite, so have to worry about overflow (i.e., when the number is too big to fit into 32 bits)
- ▶ have to be able to represent **negative numbers**, e.g., how do we specify -8 in

```
addi    $sp, $sp, -8    #$sp = $sp - 8
```

- ▶ in real systems have to provide for more than just integers, e.g., fractions and real numbers (and **floating point**) and alphanumeric (**characters**)

---

\*conventions define the relationships between bits and numbers

# RISC-V Representation



32-bit signed numbers (2's complement):

```
0000 0000 0000 0000 0000 0000 0000 0000two = 0ten
0000 0000 0000 0000 0000 0000 0000 0001two = + 1ten
0000 0000 0000 0000 0000 0000 0000 0010two = + 2ten
...

0111 1111 1111 1111 1111 1111 1111 1110two = + 2,147,483,646ten
0111 1111 1111 1111 1111 1111 1111 1111two = + 2,147,483,647ten
1000 0000 0000 0000 0000 0000 0000 0000two = - 2,147,483,648ten
1000 0000 0000 0000 0000 0000 0000 0001two = - 2,147,483,647ten
1000 0000 0000 0000 0000 0000 0000 0010two = - 2,147,483,646ten
...

1111 1111 1111 1111 1111 1111 1111 1101two = - 3ten
1111 1111 1111 1111 1111 1111 1111 1110two = - 2ten
1111 1111 1111 1111 1111 1111 1111 1111two = - 1ten
```

What if the bit string represented addresses?

- ▶ need operations that also deal with only positive (unsigned) integers

# Two's Complement Operations



- ▶ Negating a two's complement number – complement all the bits and then add a 1
  - ▶ remember: “negate” and “invert” are quite different!
- ▶ Converting n-bit numbers into numbers with more than n bits:
  - ▶ MIPS 16-bit immediate gets converted to 32 bits for arithmetic
  - ▶ **sign extend**: copy the most significant bit (the sign bit) into the other bits

```
0010  -> 0000 0010
1010  -> 1111 1010
```

- ▶ sign extension versus zero extend (1b vs. 1bu)

# Design the RISC-V Arithmetic Logic Unit (ALU)



- ▶ Must support the Arithmetic/Logic operations of the ISA


RV 32I:

add, sub, mul, mulh, mulhu, mulhsu,  
div, divu, rem, li, addi, sll, srl,  
sra, or, xor, not, slt, sltu, slli,  
srli, srai, andi, ori, xori, slti,  
sltiu,



RV 64I:

addw, subw, remu, mulw, divw, divuw,  
remw, remuw, addiw, sllw, srlw, sraw,  
srliw, sraiw,

 - ▶ With special handling for:
  - ▶ sign extend: addi, slti, sltiu
  - ▶ zero extend: andi, xori
  - ▶ Overflow detected: add, addi, sub


  
# RISC-V Arithmetic and Logic Instructions



Type	op	funct
ADDI	001000	xx
ADDIU	001001	xx
SLTI	001010	xx
SLTIU	001011	xx
ANDI	001100	xx
ORI	001101	xx
XORI	001110	xx
LUI	001111	xx

Type	op	funct
ADD	000000	100000
ADDU	000000	100001
SUB	000000	100010
SUBU	000000	100011
AND	000000	100100
OR	000000	100101
XOR	000000	100110
NOR	000000	100111

Type	op	funct
	000000	101000
	000000	101001
SLT	000000	101010
SLTU	000000	101011
	000000	101100



# Overview



Overview

**Addition**

Multiplication & Division

Shift

Floating Point Number

# Addition & Subtraction



- ▶ Just like in grade school (carry/borrow 1s)

$$\begin{array}{r} 0111 \\ + 0110 \\ \hline \end{array} \qquad \begin{array}{r} 0111 \\ - 0110 \\ \hline \end{array} \qquad \begin{array}{r} 0110 \\ - 0101 \\ \hline \end{array}$$


- ▶ Two's complement operations are easy: do subtraction by negating and then adding

$$\begin{array}{r} 0111 \\ - 0110 \\ \hline \end{array} \quad \rightarrow \quad \begin{array}{r} 0111 \\ + 1010 \\ \hline \end{array}$$

- ▶ Overflow (result too large for finite computer word). E.g., adding two n-bit numbers does not yield an n-bit number

$$\begin{array}{r} 0111 \\ + 0001 \\ \hline \end{array}$$

# Building a 1-bit Binary Adder

 

A	B	carry_in	carry_out	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \text{ xor } B \text{ xor } \text{carry\_in}$$

$$\text{carry\_out} = A \& B \mid A \& \text{carry\_in} \mid B \& \text{carry\_in}$$

(majority function)

- ▶ How can we use it to build a 32-bit adder?
- ▶ How can we modify it easily to build an adder/subtractor?

# Building 32-bit Adder

 

- ▶ Just connect the carry-out of the least significant bit FA to the carry-in of the next least significant bit and connect ...
- ▶ Ripple Carry Adder (RCA)
  - ▶ 😊: simple logic, so small (low cost)
  - ▶ ☹️: slow and lots of glitching (so lots of energy consumption)


# Glitch




## Glitch

invalid and unpredicted output that can be read by the next stage and result in a wrong action

**Example:** Draw the propagation delay

 

# Glitch in RCA

 


A	B	carry_in	carry_out	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


 
# But What about Performance?


- ▶ Critical path of n-bit ripple-carry adder is  $n \times CP$
- ▶ Design trick: throw hardware at it (Carry Lookahead)



# A 32-bit Ripple Carry Adder/Subtractor




- complement all the bits

 

- add a 1 in the least significant bit
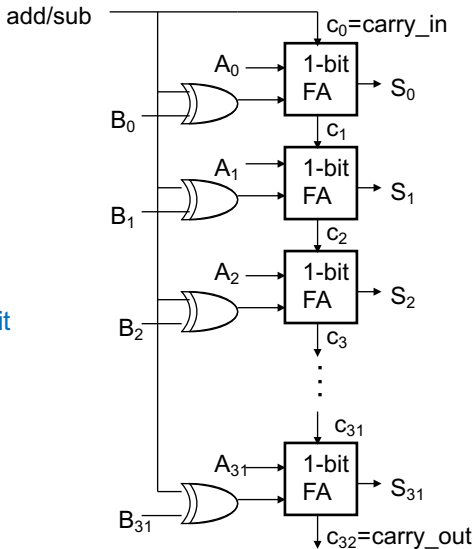
$$\begin{array}{r} A \quad 0111 \quad -> \quad 0111 \\ B \quad - 0110 \quad -> \quad + 1001 \\ \hline \quad 0001 \\ \hline \quad 1 \quad 0001 \end{array}$$





# Minimal Implementation of a Full Adder



Gate library: inverters, 2-input NANDs, or-and-inverters


```
architecture concurrent_behavior of full_adder is
    signal t1, t2, t3, t4, t5: std_logic;
begin
    t1 <= not A after 1 ns;
    t2 <= not cin after 1 ns;
    t4 <= not((A or cin) and B) after 2 ns;
    t3 <= not((t1 or t2) and (A or cin)) after 2 ns;
    t5 <= t3 nand B after 2 ns;
    S <= not((B or t3) and t5) after 2 ns;
    cout <= not((t1 or t2) and t4) after 2 ns;
end concurrent_behavior;
```

# Tailoring the ALU to the MIPS ISA




- ▶ Also need to support the logic operations (`and`, `nor`, `or`, `xor`)
  - ▶ Bit wise operations (no carry operation involved)
  - ▶ Need a logic gate for each function and a mux to choose the output
- ▶ Also need to support the set-on-less-than instruction (`slt`)
  - ▶ Uses subtraction to determine if  $(a - b) < 0$  (implies  $a < b$ )
- ▶ Also need to support test for equality (`bne`, `beq`)
  - ▶ Again use subtraction:  $(a - b) = 0$  implies  $a = b$
- ▶ Also need to add overflow detection hardware
  - ▶ overflow detection enabled only for `add`, `addi`, `sub`
- ▶ **Immediates** are sign extended outside the ALU with wiring (i.e., no logic needed)
 
# A Simple ALU Cell with Logic Op Support


 
# A Simple ALU Cell with Logic Op Support




Modifying the ALU Cell for `slt`
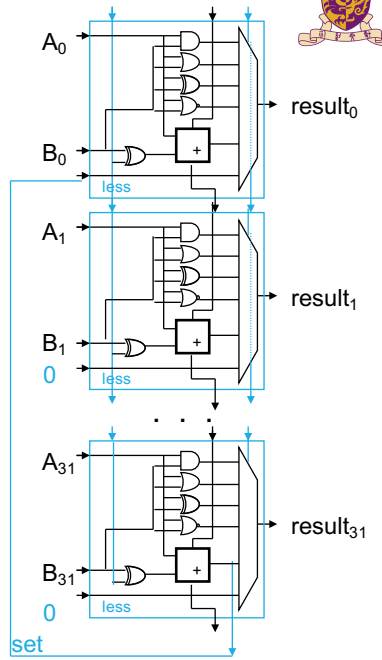
# Modifying the ALU for `slt`



- ▶ First perform a subtraction
- ▶ Make the result 1 if the subtraction yields a negative result
- ▶ Make the result 0 if the subtraction yields a positive result
- ▶ Tie the most significant sum bit (sign bit) to the low order `less` input





# Overflow Detection

Overflow occurs when the result is too large to represent in the number of bits allocated

- ▶ adding two positives yields a negative
- ▶ or, adding two negatives gives a positive
- ▶ or, subtract a negative from a positive gives a negative
- ▶ or, subtract a positive from a negative gives a positive

**Question:** prove you can detect overflow by:

Carry into MSB xor Carry out of MSB


$$\begin{array}{r} \boxed{0} \quad \boxed{1} \quad 1 \quad 1 \quad 1 \quad 7 \\ + \quad 0 \quad 0 \quad 1 \quad 1 \quad 1 \quad 3 \\ \hline 1 \quad 0 \quad 1 \quad 0 \quad -6 \end{array}$$

$$\begin{array}{r} \boxed{1} \quad \boxed{0} \quad 1 \quad 0 \quad 0 \quad -4 \\ + \quad 1 \quad 0 \quad 1 \quad 1 \quad -5 \\ \hline 0 \quad 1 \quad 1 \quad 1 \quad 7 \end{array}$$


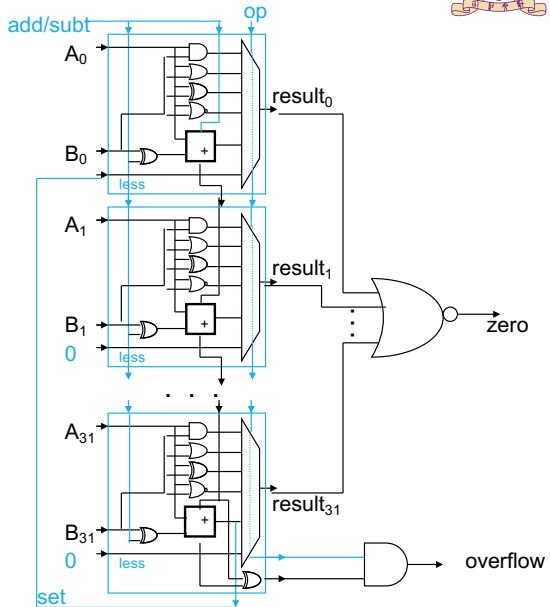
# Modifying the ALU for Overflow

- ▶ Modify the most significant cell to determine overflow output setting
- ▶ Enable overflow bit setting for signed arithmetic (add, addi, sub)



# Overflow Detection and Effects



- ▶ On overflow, an exception (interrupt) occurs
- ▶ Control jumps to predefined address for exception
- ▶ Interrupted address (address of instruction causing the overflow) is saved for possible resumption
- ▶ Don't always want to detect (interrupt on) overflow



# New MIPS Instructions



Category	Instr	Op Code	Example	Meaning
Arithmetic (R & I format)	add unsigned	0 and 21	addu \$s1, \$s2, \$s3	$\$s1 = \$s2 + \$s3$
	sub unsigned	0 and 23	subu \$s1, \$s2, \$s3	$\$s1 = \$s2 - \$s3$
	add imm.unsigned	9	addiu \$s1, \$s2, 6	$\$s1 = \$s2 + 6$
Data Transfer	ld byte unsigned	24	lbu \$s1, 20(\$s2)	$\$s1 = \text{Mem}(\$s2+20)$
	ld half unsigned	25	lhu \$s1, 20(\$s2)	$\$s1 = \text{Mem}(\$s2+20)$
Cond. Branch (I & R format)	set on less than unsigned	0 and 2b	sltu \$s1, \$s2, \$s3	if ( $\$s2 < \$s3$ ) $\$s1=1$ else $\$s1=0$
	set on less than imm unsigned	b	sltiu \$s1, \$s2, 6	if ( $\$s2 < 6$ ) $\$s1=1$ else $\$s1=0$

- ▶ Sign extend: addi, addiu, slti
- ▶ Zero extend: andi, ori, xori
- ▶ Overflow detected: add, addi, sub



# Binary Representations for Integers




Hey guys! How do you negate numbers?



In the early days of computing, designers made computers express numbers using **unsigned binary**.

And they were content...

Until there were negative numbers.

 

What's negation?



To include negative numbers, designers came up with **sign magnitude**.

That took care of the negative numbers...

But the computer had to count backwards for the negative numbers.



00000000?  
10000000?  
00000000?

Get the sign bit!



Plus, this introduced positive and negative zero.

Then designers created **one's complement**.

Now computers only had to count in one direction...

But there were still two zeroes!



00000000?  
11111111?


Flip the bits!



Finally, designers developed **two's complement**.

Now, there was only one zero...

And they were content.

 

Flip the bits and add 1!



# Overview



Overview

Addition

Multiplication & Division

Shift

Floating Point Number

# Multiplication




- ▶ More complicated than addition
- ▶ Can be accomplished via **shifting** and **adding**

$$\begin{array}{r} 0010 \quad \text{(multiplicand)} \\ \times 1011 \quad \text{(multiplier)} \\ \hline 0010 \\ 0010 \\ 0000 \\ 0010 \\ \hline \boxed{0001} \boxed{0110} \quad \text{(product)} \end{array}$$


(partial product array)

- ▶ Double precision product produced
- ▶ More time and more area to compute
 
# First Version of Multiplication Hardware


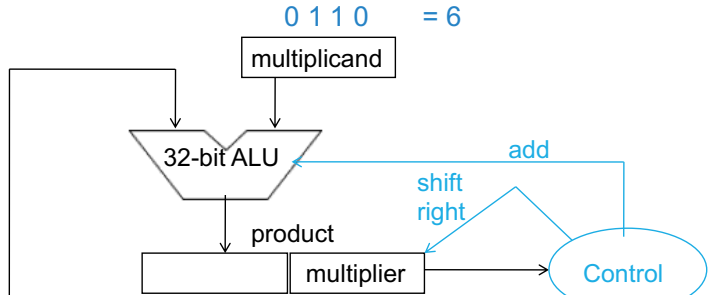
# Add and Right Shift Multiplier Hardware



$0000 \quad 0101 = 5$   
 add  $0110 \quad 0101$   
 $0011 \rightarrow 0010$   
 add  $0011 \quad 0010$   
 $0001 \rightarrow 1001$   
 add  $0111 \quad 1001$   
 $0011 \rightarrow 1100$   
 add  $0011 \quad 1100$   
 $0001 \rightarrow 1110 = 30$

# RISC-V Multiply Instruction



- ▶ Multiply (`mult` and `multu`) produces a double precision product

```
mul $rd, $s0, $s1      # hi||lo = $s0 * $s1
```


0	16	17	0	0	0x18
---	----	----	---	---	------

- ▶ Low-order word of the product is left in processor register `lo` and the high-order word is left in register `hi`
- ▶ Instructions `mfhi rd` and `mflw rd` are provided to move the product to (user accessible) registers in the register file
- ▶ Multiplies are usually done by fast, dedicated hardware and are much more complex (and slower) than adders
 
# Division



- ▶ Division is just a bunch of quotient digit guesses and left shifts and subtracts







## Question: Division

Dividing 1001010 by 1000

# RISC-V Divide Instruction



- ▶ Divide generates the remainder in `hi` and the quotient in `lo`

```
div $rd, $s0, $s1      # lo = $s0 / $s1  
                        # hi = $s0 mod $s1
```

op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------

- ▶ Instructions `mflo rd` and `mfhi rd` are provided to move the quotient and remainder to (user accessible) registers in the register file
- ▶ As with multiply, divide ignores overflow so software must determine if the quotient is too large.
- ▶ Software must also check the divisor to avoid division by 0.

# Overview



Overview

Addition

Multiplication & Division

**Shift**

Floating Point Number

# Shift Operations



- ▶ Shifts move all the bits in a word left or right

```
sll    $t2, $s0, 8 # $t2 = $s0 << 8 bits
srl    $t2, $s0, 8 # $t2 = $s0 >> 8 bits
sra    $t2, $s0, 8 # $t2 = $s0 >> 8 bits
```




- ▶ Notice that a 5-bit `shamt` field is enough to shift a 32-bit value  $2^5 - 1$  or 31 bit positions
- ▶ **Logical** shifts fill with **zeros**, **arithmetic** left shifts fill with the **sign bit**


The shift operation is implemented by hardware separate from the ALU

Using a barrel shifter, which would takes lots of gates in discrete logic, but is pretty easy to implement in VLSI


# A Simple Shifter

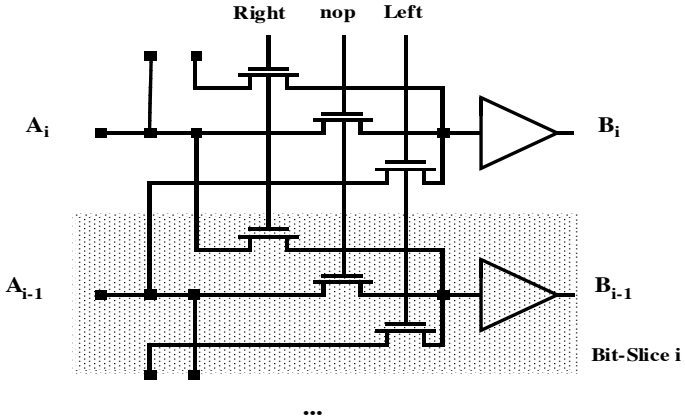


# Parallel Programmable Shifters

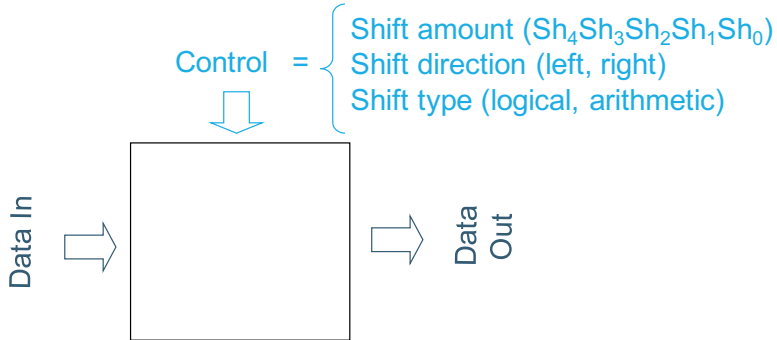

# Logarithmic Shifter Structure

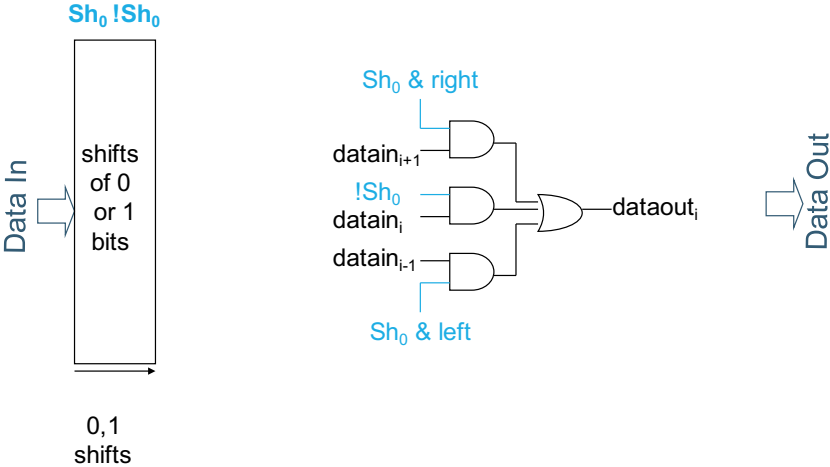


# Logarithmic Shifter Structure

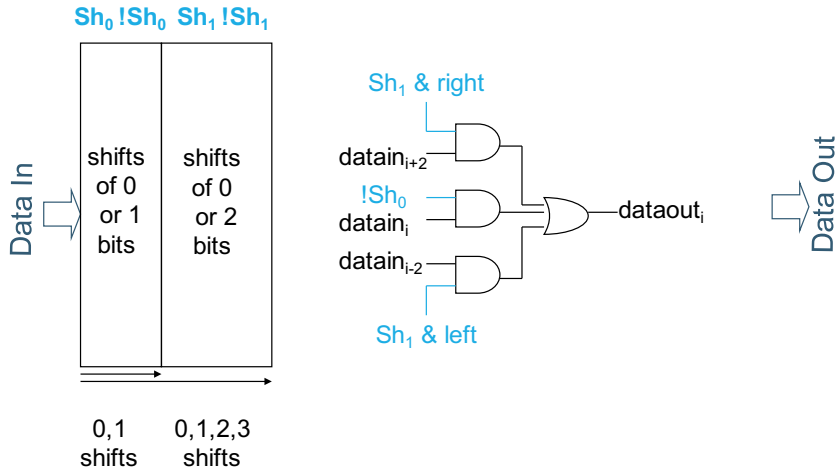





# Logarithmic Shifter Structure

 


# Logarithmic Shifter Structure

 

# Logarithmic Shifter Structure

 

# Logarithmic Shifter Structure

 

# Overview



Overview

Addition

Multiplication & Division

Shift

Floating Point Number

# Floating Point Number



Scientific notation:  $6.6254 \times 10^{-27}$

- ▶ A normalized number of certain accuracy (e.g. 6.6254 is called the **mantissa**)
- ▶ Scale factors to determine the position of the decimal point (e.g.  $10^{-27}$  indicates position of decimal point and is called the exponent; the **base** is implied)
- ▶ **Sign** bit



- ▶ Floating Point Numbers can have multiple forms, e.g.


$$\begin{aligned}0.232 \times 10^4 &= 2.32 \times 10^3 \\ &= 23.2 \times 10^2 \\ &= 2320. \times 10^0 \\ &= 232000. \times 10^{-2}\end{aligned}$$

- ▶ It is desirable for each number to have a unique representation => Normalized Form
- ▶ We normalize Mantissa's in the Range  $[1..R)$ , where R is the Base, e.g.:
  - ▶  $[1..2)$  for BINARY
  - ▶  $[1..10)$  for DECIMAL

# IEEE Standard 754 Single Precision



32-bit, float in C / C++ / Java

 

(a) Single precision



$$\text{Value represented} = +1.001010 \dots 0 \times 2^{-87}$$

(b) Example of a single-precision number


00101000 → 40  
40 - 127 = -87



# IEEE Standard 754 Double Precision



64-bit, float in C / C++ / Java

 

$$\text{Value represented} = \pm 1. M \times 2^{E' - 1023}$$

(c) Double precision



Question:

What is the IEEE single precision number  $40C0\ 0000_{16}$  in decimal?



## Question:

What is  $-0.5_{10}$  in IEEE single precision binary floating point format?

# Ref: IEEE Standard 754 Numbers




- Normalized  $\pm 1.d\dots d \times 2^{\text{exp}}$
- **Denormalized**  $\pm 0.d\dots d \times 2^{\text{min\_exp}}$   $\rightarrow$  to represent near-zero numbers  
e.g.  $+ 0.0000\dots 0000001 \times 2^{-126}$  for Single Precision

Format	# bits	# significant bits	macheps	# exponent bits	exponent range
Single	32	1+23	$2^{-24}$ ( $\sim 10^{-7}$ )	8	$2^{-126} - 2^{+127}$ ( $\sim 10^{\pm 38}$ )
Double	64	1+52	$2^{-53}$ ( $\sim 10^{-16}$ )	11	$2^{-1022} - 2^{+1023}$ ( $\sim 10^{\pm 308}$ )
Double Extended	$\geq 80$	$\geq 64$	$\leq 2^{-64}$ ( $\sim 10^{-19}$ )	$\geq 15$	$2^{-16382} - 2^{+16383}$ ( $\sim 10^{\pm 4932}$ )

(Double Extended is *80 bits on all Intel machines*)  
 macheps = Machine Epsilon =  $2^{-\text{(# significant bits)}}$

$$\mathcal{E}_{mach}$$

 



Exponents of all 0's and all 1's have special meaning

- ▶ E=0, M=0 represents 0 (sign bit still used so there is  $\pm 0$ )
- ▶ E=0, M $\neq$ 0 is a denormalized number  $\pm 0.M \times 2^{-127}$  (smaller than the smallest normalized number)
- ▶ E=All 1's, M=0 represents  $\pm$ Infinity, depending on Sign
- ▶ E=All 1's, M $\neq$ 0 represents NaN



**+, -, x, /, sqrt, remainder, as well as conversion to and from integer are correctly rounded**

- ▶ As if computed with infinite precision and then rounded
- ▶ Transcendental functions (that cannot be computed in a finite number of steps e.g., sine, cosine, logarithmic,  $e$ , etc. ) may not be correctly rounded

## **Exceptions and Status Flags**

- ▶ Invalid Operation, Overflow, Division by zero, Underflow, Inexact

**Floating point numbers can be treated as “integer bit-patterns” for comparisons**

- ▶ If Exponent is all zeroes, it represents a denormalized, very small and near (or equal to) zero number
- ▶ If Exponent is all ones, it represents a very large number and is considered infinity (see next slide.)

**Dual Zeroes:** +0 (0x00000000) and -0 (0x80000000): they are treated as the same



## Infinity is like the mathematical one

- ▶ `Finite / Infinity` → `0`
- ▶ `Infinity × Infinity` → `Infinity`
- ▶ `Non-zero / 0` → `Infinity`
- ▶ `Infinity`  $\{\text{Finite or Infinity}\}$  → `Infinity`

## NaN (Not-a-Number) is produced whenever a limiting value cannot be determined:

- ▶ `Infinity - Infinity` → `NaN`
- ▶ `Infinity / Infinity` → `NaN`
- ▶ `0 / 0` → `NaN`
- ▶ `Infinity × 0` → `NaN`
- ▶ If `x` is a `NaN`, `x ≠ x`
- ▶ Many systems just store the result quietly as a `NaN` (all 1's in exponent), some systems will signal or raise an exception

# Inaccurate Floating Point Operations



- E.g. Find 1<sup>st</sup> root of a quadratic equation
  - $r = (-b + \sqrt{b*b - 4*a*c}) / (2*a)$

Sparc processor, Solaris, gcc 3.3 (ANSI C),

<b>Expected Answer</b>	<b>0.00023025562642476431</b>
<b>double</b>	<b>0.00023025562638524986</b>
<b>float</b>	<b>0.00024670246057212353</b>

- Problem is that if c is near zero,

$$\sqrt{b*b - 4*a*c} \approx b$$

- Rule of thumb: use the highest precision which does not give up too much speed



# Catastrophic Cancellation



- $(a - b)$  is inaccurate when  $a \approx b$
- Decimal Examples
  - Using 2 significant digits to compute mean of 5.1 and 5.2 using the formula  $(a+b) / 2$ :  
 $a + b = 10$  (with 2 sig. digits, 10.3 can only be stored as 10)  
 $10 / 2 = 5.0$  (the computed mean is less than both numbers!!!)
  - Using 8 significant digits to compute sum of three numbers:  
 $(11111113 + (-11111111)) + 7.5111111 = 9.5111111$   
 $11111113 + ((-11111111) + 7.5111111) = 10.000000$
- Catastrophic cancellation occurs when

$$\left| \frac{[\text{round}(x) \bullet \text{round}(y)] - \text{round}(x \bullet y)}{\text{round}(x \bullet y)} \right| \gg \epsilon_{mach}$$