



CENG 4480

Lecture 10: Clock


Bei Yu

Reference:

- Chapter 11 Clock Distribution
- High speed digital design
- by Johnson and Graham


A 2-bit ring counter example

 - 2-bit ring counter
- Initially $A = B = 0$; $A = 0011001100$
- What is B ?



A 2-bit ring counter example

 - The result is Okay when clock is **slow**
- But, when clock is **TOO fast**, get some **problem**




Arduino uno: 16 MHz


Setup Time and Time Margin

- **Setup Time**: The time that the input data must be stable before the clock transition of the system occurs
- **Time Margin**: measures the **slack**, or excess time, remaining in each clock cycle
 - ♦ Protects your circuit against signal cross-talk, miscalculation of logic delays, and later minor changes in the layout
 - ♦ Depends on both time delay of logic paths and clock interval

Notations in Clock Skew Calculation

 
- **T_{ff}**: delay of flip-flop (FF)
- **T_G**: delay of gate G, including track delay
- **T_{setup}**: worst-case setup time required by FF2, data at D2 must arrive at least T_{setup} before CLK₂
- **T_{CLK}**: clock period; interval between clocks



 

EX. B2-1

- CLK1 = CLK2 = 20MHz; $T_{ff} = 8\text{ns}$; $T_{\text{setup}} = 5\text{ns}$; $T_G = 10\text{ns}$.
- **Questions:**
 - ♦ Find time margin
 - ♦ How many delay G gates can you insert between A and B without creating error?

 

CENG4480


7

L10. Clock


20MHz = 50 ns

Clock Skew

 - The clock does NOT reach FF1, FF2 at the same time



Why Care Clock Skew?

 

Why Care Clock Skew?

- $T_{\text{delay}} = T_{c1,\text{max}} + T_{\text{ff}} + T_{\text{G}}$
- $T_{\text{clk}'} = T_{\text{CLK}} + T_{c2,\text{min}} - T_{\text{setup}}$
- Since $T_{\text{delay}} < T_{\text{clk}'} \Rightarrow$

$$T_{\text{CLK}} > T_{\text{ff}} + T_{\text{setup}} + T_{\text{G}} + T_{c1,\text{max}} - T_{c2,\text{min}}$$

Constant Delay Logic Delay Skew Impact

EX. B2-2

Question: Given

- $T_{ff} = 7\text{ns};$
- $T_G = 5\text{ns};$
- $T_{\text{setup}} = 4\text{ns};$
- $T_{\text{CLK}} = 40\text{MHZ};$

What's the biggest time skew allowed?


Answer:

$$40\text{MHz} = 4 \times 10^7 \text{ cycles per second} = 25 \text{ ns}$$

Strategies to reduce clock skew

- Drive them from the **same** source & balance the delays
- **Style 1**: Spider-leg distribution network
 - ♦ use a power driver to drive N outputs.
 - ♦ Use load (R) termination to reduce reflection if the traces are long (distributed circuit). Total load =R/N.
 - ♦ Two or more driver outputs in parallel may be needed.
- **Style 2**: Clock distribution tree

Style 1: Spider-leg Clock

 


Distributes clocks from a single source to N remote destinations.

Reflections are damped by resistive terminations R at the end of each spider leg.


The drive circuit experiences a total load of R/N .

We need a more powerful clock driver.

Style 2: Clock Tree

 


Modern Clock Design — 1

 


[Ho et al, ISPD'2009]

Modern Clock Design — 2

 


[Yeh et al, ISQED'2006]

Modern Clock Design — 3

 

[Seok et al, ISLPED'2010]


Clock Skew Distribution

 

[Pham et al, JSSC'2006]

EX. Skew Optimization

 - Instead of Zero-Skew, take advantage of Skew.
- **Question:** Given $T_G=6\text{ns}$, $T_{ff}=10\text{ns}$, $T_{\text{setup}}=2\text{ns}$, what's the minimal T_{CLK} ? Assume $T_{c3} = 0$.



Thank You